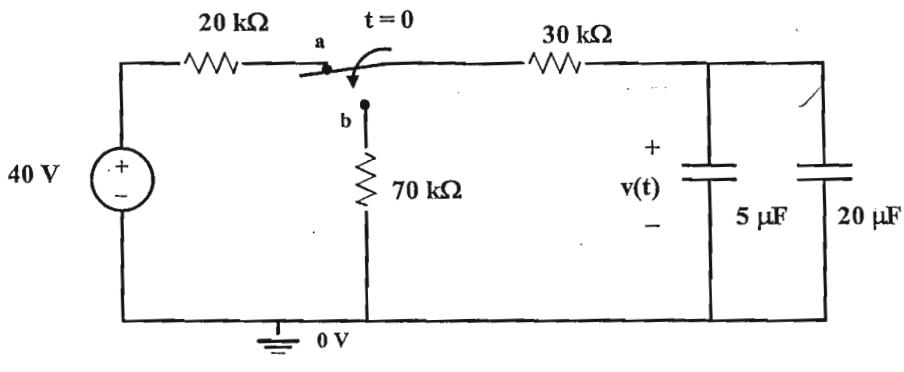


- (1) Consider the circuit shown in Figure 1. The switch has been in position "a" for a very long time and is switched to position "b" at  $t = 0$ .

- (a) Develop and solve the differential equation for  $v(t)$ . Do not use the step-by-step method.  
 (b) Sketch the voltage  $v(t)$  vs  $t$  approximately to scale.




For  $t < 0$

The capacitors charge to the source voltage of 40V.

$$V(0^-) = 40V$$

For  $t > 0$

$$V(0^+) = V(0^-) = 40V$$

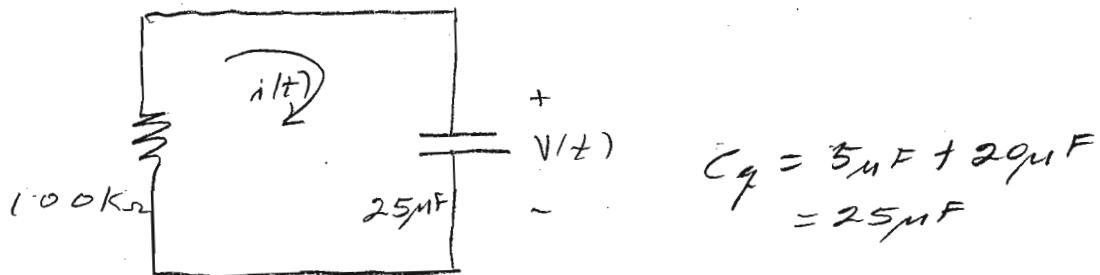

$$Ri(t) + V(t) = 0 \quad \text{but } i = C \frac{dV}{dt}$$

$$RC \frac{dV}{dt} + V(t) = 0$$

$$\frac{dV(t)}{dt} + \frac{V(t)}{RC} = 0$$

The solution to the 1<sup>st</sup> order differential equation is of the form

$$V(t) = V_p(t) + V_c(t)$$

$V_p(t) = 0$  because there is no forcing function. We know that  $V_c(t)$  is of the form

$$V_c(t) = Ke^{st}$$


$$s + \frac{1}{RC} = 0 \quad ; \quad s = -\frac{1}{1 \times 10^4 \times 25 \times 10^{-6}}$$

$$s = -0.4 \quad T = RC = 2.5 \text{ sec}$$

$$V = V_c = Ke^{-0.4t} \quad u(t) \quad V$$


$$\text{We know that } V(0^+) = 40 = Ke^0 = K$$
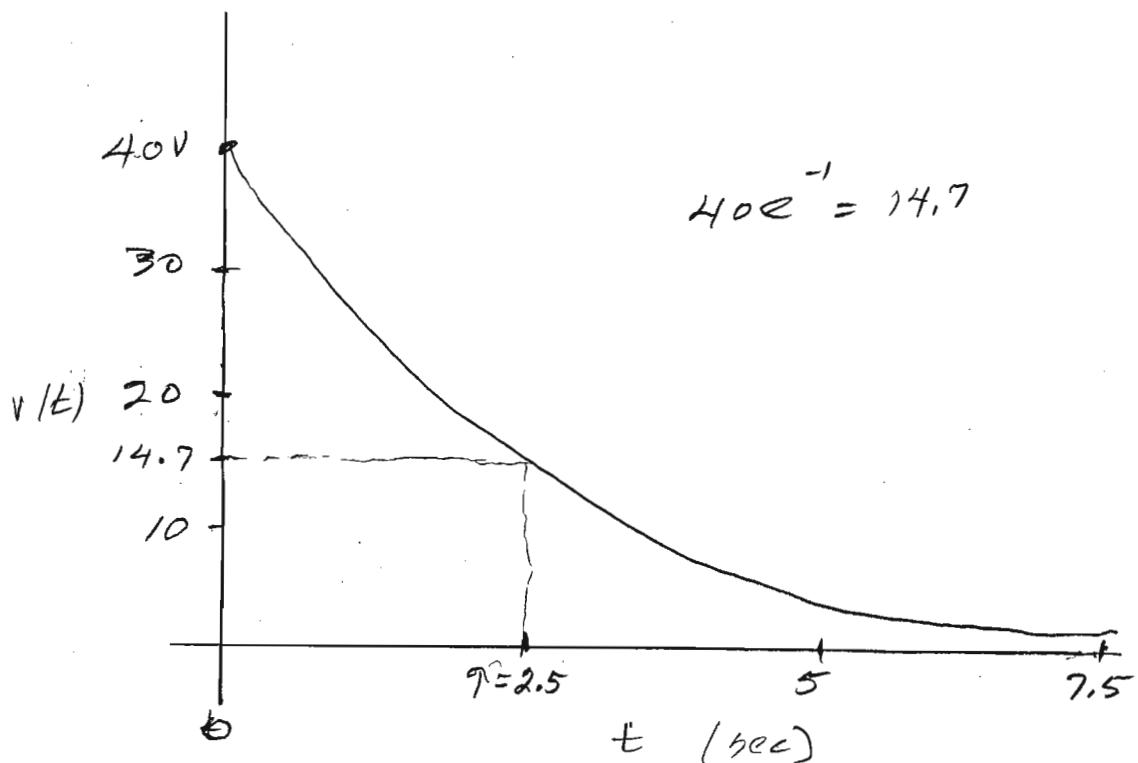
$$\therefore V(t) = 40e^{-0.4t} \quad u(t) \quad V$$



3A

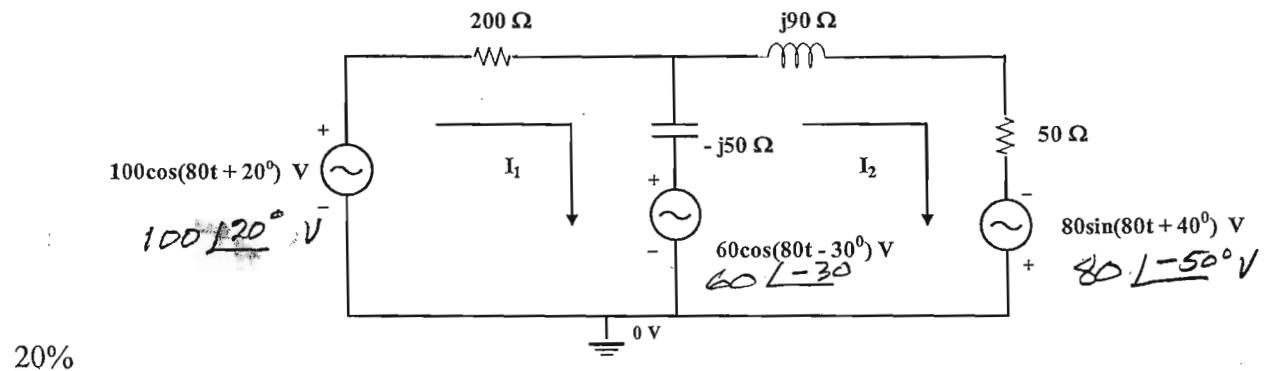- (2) You are given the AC circuit of Figure 2. Use a cosine reference. Use mesh analysis to solve for the phasor currents  $I_1$  and  $I_2$ . Give their values in polar form.



$$80 \sin(80t + 40^\circ) = 80 \cos(80t - 50^\circ)$$

As a phasor  $80 \angle -50^\circ$

Mesh #1

$$-100 \angle 20^\circ + 200 \vec{I}_1 - j50 \vec{I}_1 + j50 \vec{I}_2 + 60 \angle -30^\circ = 0$$

$$(200 - j50) \vec{I}_1 + j50 \vec{I}_2 = 100 \angle 20^\circ - 60 \angle -30^\circ$$

Mesh #2

$$-60 \angle -30^\circ - j50(\vec{I}_2 - \vec{I}_1) + j90 \vec{I}_2 + 50 \vec{I}_2 - 80 \angle -50^\circ$$

$$j50 \vec{I}_1 + (50 + j40) \vec{I}_2 = 60 \angle -30^\circ + 80 \angle -50^\circ$$


$$\begin{bmatrix} (200 - j50) & (0 + j50) \\ (0 + j50) & (50 + j40) \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 100 \angle 20^\circ - 60 \angle -30^\circ \\ 60 \angle -30^\circ + 80 \angle -50^\circ \end{bmatrix}$$

$$\vec{I}_1 = 0.325 \angle 162.4^\circ \text{ A}$$

$$\vec{I}_2 = 2.06 \angle -73.6^\circ \text{ A}$$

3A

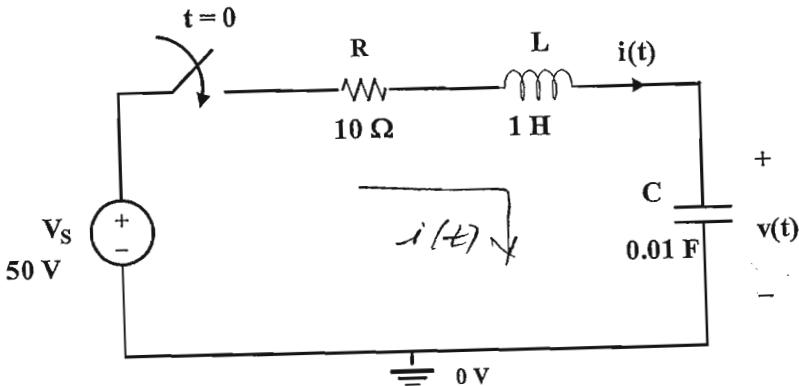(3) You are given the RLC circuit of Figure 3.



- (a) Develop the differential equation that can be used to solve for  $v(t)$ .  
Show your steps.

(b) Give (determine) the values of  $v(0^+)$  and  $\frac{dv(0^+)}{dt}$ .

(c) Determine which form below should be used to solve for  $v(t)$ .  
Do not solve the equation. Explain your answer.

- $v(t) = 50 + (A_1 + A_2 t)e^{-5t} u(t), V$
- $v(t) = 50 + e^{-5t} [A_1 \cos(8.66t) + A_2 \sin(8.66t)] u(t), V$
- $v(t) = 50 + A_1 e^{-4t} + A_2 e^{-8t} u(t), V$

For  $t > 0$

$$Ri(t) + L \frac{di}{dt} + v(t) = V_s$$

but  $i = C \frac{dv}{dt}$

$$RC \frac{dv}{dt} + LC \frac{d^2v}{dt^2} + v = V_s$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{V_s}{LC} = \frac{V_s}{LC}$$

with numbers

$$\frac{d^2v}{dt^2} + 10 \frac{dv}{dt} + 100 v(t) = 50$$

Characteristic equation

$$s^2 + 10s + 100 = 0$$

$$(s + 5 + j8.66)(s + 5 - j8.66) = 0$$

So

$$V(t) = 50 + e^{-5t} [A_1 \cos 8.66t + A_2 \sin 8.66t]$$

Initial conditions

$$i(0^-) = 0 = i(0^+) = 0$$

$$V(0^-) = 0 = V(0^+) = 0$$

$$\boxed{V(0^+) = 0}$$


$$i(t) = C \frac{dV}{dt}$$

$$\frac{dV(0^+)}{dt} = \frac{i(0^+)}{C} = 0$$

$$\boxed{\frac{dV(0^+)}{dt} = 0}$$


3A

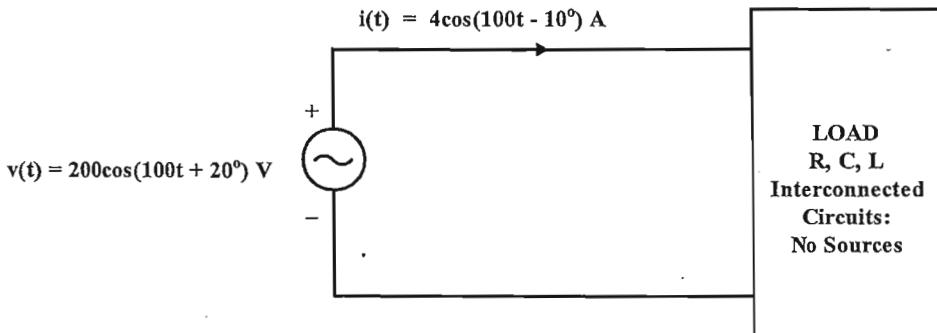- (4) You are given the circuit configuration of Figure 4. Assume  $\mathbf{V}$  is the phasor voltage for  $200\cos(100t + 20^\circ)$  V and  $\mathbf{I}$  is the phasor current for  $4\cos(100t - 10^\circ)$  A
- Prepare the phasor diagram showing phasors  $\mathbf{V}$  and  $\mathbf{I}$ .
  - Use inspection to determine if the load is inductive or capacitive. Explain your answer.



10%
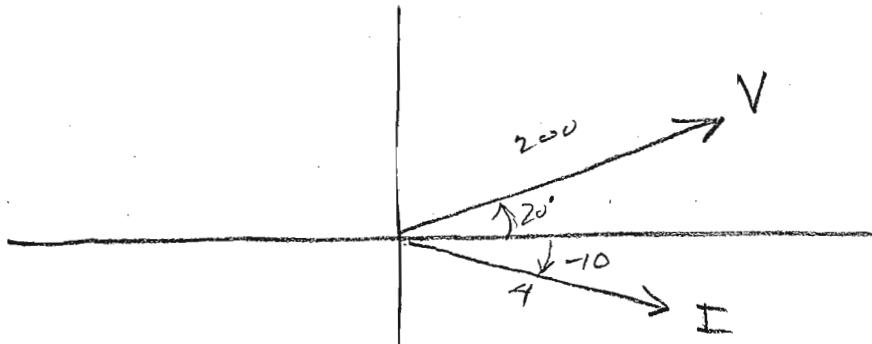
$$(a) \quad \mathbf{V} = 200 \angle 20^\circ \text{ V} \quad \mathbf{I} = 4 \angle -10^\circ \text{ A}$$



(b) Since  $\mathbf{V}$  leads  $\mathbf{I}$  the load  
is inductive.  $\frac{\mathbf{V}}{\mathbf{I}}$

Another View


$$Z = \frac{\mathbf{V}}{\mathbf{I}} = \frac{200 \angle 20^\circ}{4 \angle -10^\circ} = 50 \angle 30^\circ$$

Since  $Z$  has a positive  $j$  part  
the load is inductive

3A

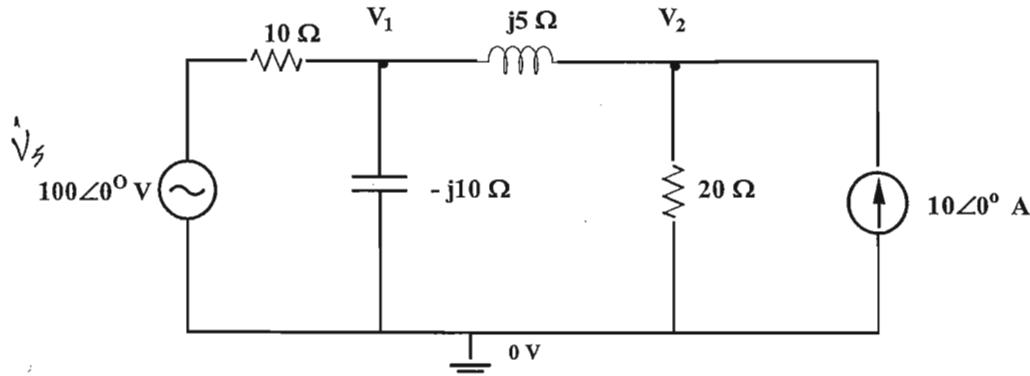(5) You are given the circuit shown in Figure 5. Assume a cosine reference.

- Use nodal analysis to find the phasor voltages  $V_1$  and  $V_2$  and express these voltages in polar form.
- Give the expression for  $v_1(t)$ .
- Prepare a phasor diagram for phasor  $V_s$ ,  $V_1$  and  $V_2$ .
- For the phasors  $V_s$  and  $V_2$  which is leading and by how much angle?



20%

(a) At  $V_1$

$$\frac{V_1 - 100}{10} + \frac{V_1}{-j10} + \frac{V_1 - V_2}{j5} = 0$$

$$0.1V_1 - 10 + j0.1V_1 - j0.2V_1 + j0.2V_2 = 0$$

$$(0.1 - j0.1)V_1 + (0 + j0.2)V_2 = 10$$

At  $V_2$

$$\frac{V_2}{20} + \frac{V_2 - V_1}{j5} = 10$$

$$0.05V_2 - j0.2V_2 + j0.2V_1 = 10$$

$$(0 + j0.2)V_1 + (0.05 - j0.2)V_2 = 10$$

$$\begin{bmatrix} (0.1 - j0.1), (0 + j0.2) \\ j0.2, 0.05 - j0.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$


$$V_1 = 11.4 \angle -37.8^\circ \quad V_2 = 8.9 \angle -26.6^\circ$$

(5)

(b)


$$V_1(t) = 64.7 \cos(\omega t + 6.3^\circ) V$$

(c)

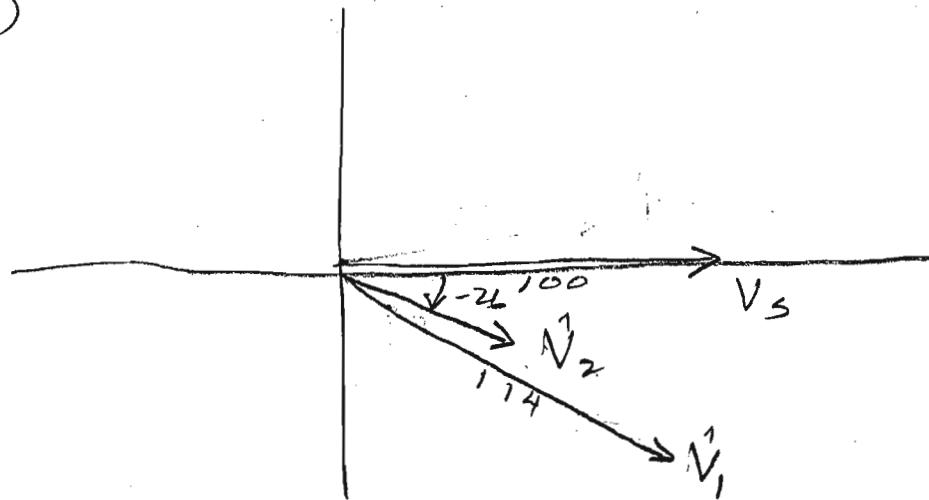(d)  $\vec{V}_s$  leads  $\vec{V}_2$  by  $26.6^\circ$

3A

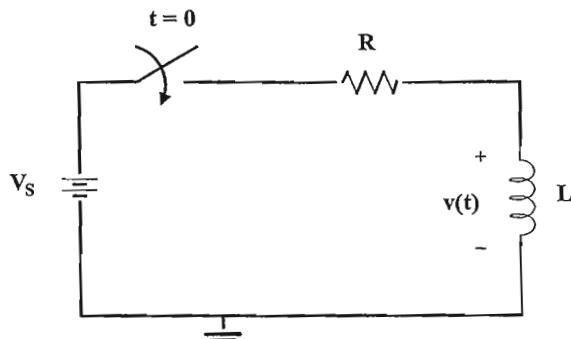- (6) You are given the circuit of Figure 6A. The switch has been open for a very long time. The switch is closed at  $t = 0$  and the resulting voltage,  $v(t)$ , is shown in Figure 6B.
- Determine the time constant for the circuit.
  - If  $R = 10$  ohms, what is the value of  $L$ ?



10%

Figure 6A: Circuit for problem 6.

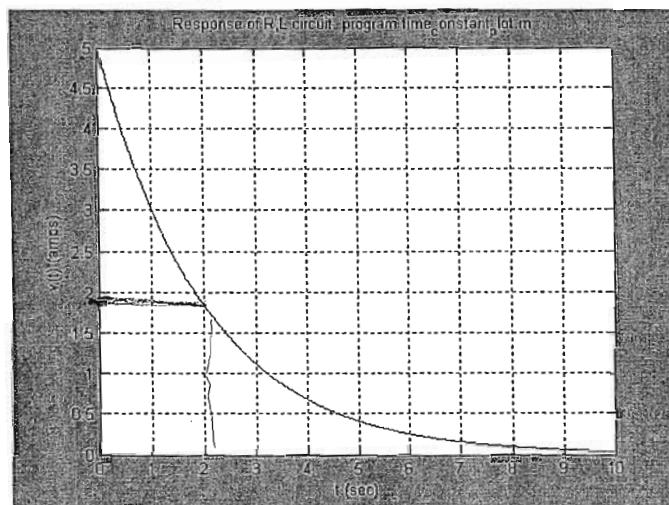


Figure 6B: Response from circuit of Figure 6A.

$$(a) \quad i = 5 e^{-\frac{t}{\tau}} \text{ A} \quad \tau = \frac{L}{R}$$

$$\text{At } t = \tau, \quad i(\tau) = 5 e^{-1} = 1.84 \text{ A}$$

$$\text{At } 1.84, \quad t = \tau = 2$$

$$(b) \quad \frac{L}{R} = 2 \quad \therefore L = 20 \text{ H}$$