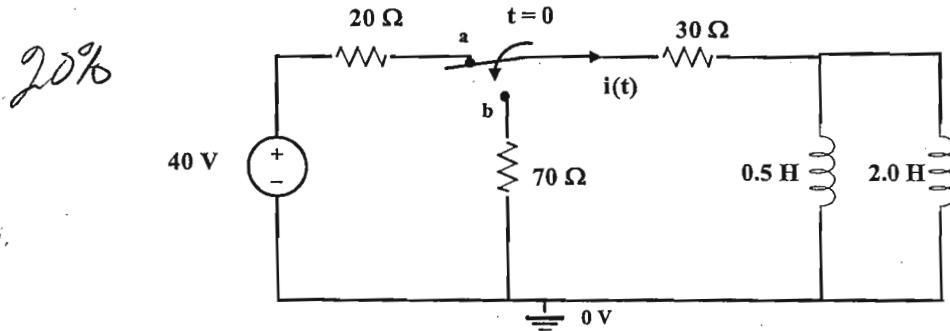


wlg

- (1) Consider the circuit shown in Figure 1. The switch has been in position "a" for a very long time and is switched to position "b" at $t = 0$.

- (a) Develop and solve the differential equation for $i(t)$. Do not use the step-by-step method.
 (b) Sketch the current $i(t)$ vs t approximately to scale.


For $t < 0$

The coils look like a short.

$$i(0^-) = \frac{40}{50} = 0.8 \text{ A}$$

For $t > 0$

$$i(0^+) = i(0^-) = 0.8 \text{ A}$$

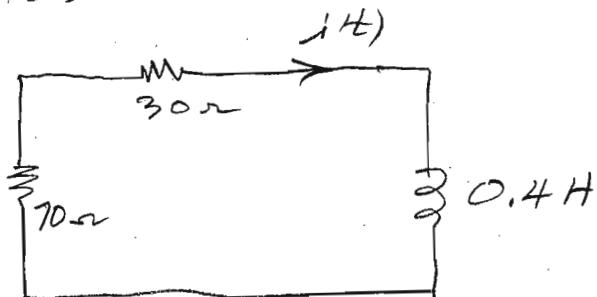

$$100i + 0.4 \frac{di}{dt} = 0$$

$$\frac{di}{dt} + 250i(t) = 0 \quad \text{basic diff. eq.}$$

The solution of the diff. eq. is
of the form

$$i(t) = i_p(t) + i_c(t)$$

$i_p(t) = 0$ because the forcing function = 0

The characteristic equation is

$$s + 250 = 0$$


$$i(t) = i_c(t) = k e^{-250t} u(t) A$$

We know

$$i(0^+) = 0.8 = k e^0 = k$$


$$\therefore i(t) = 0.8 e^{-250t} u(t) A$$

1b)

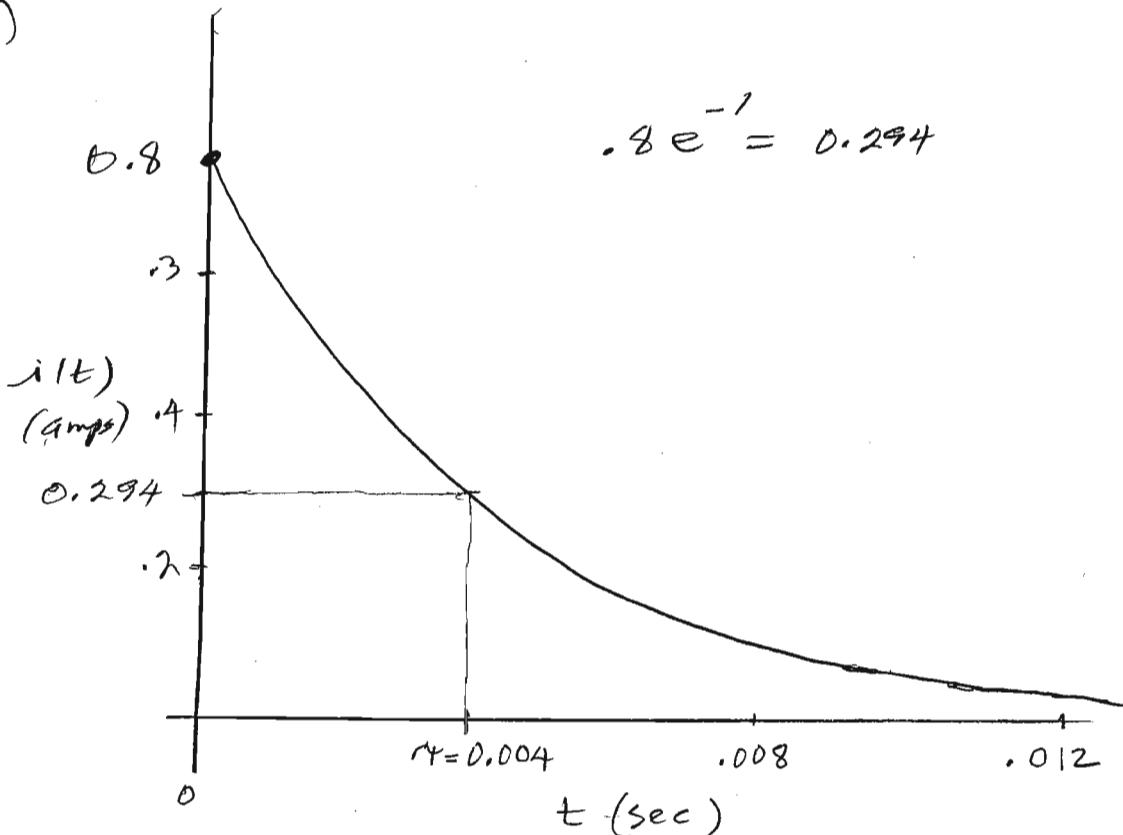

3B

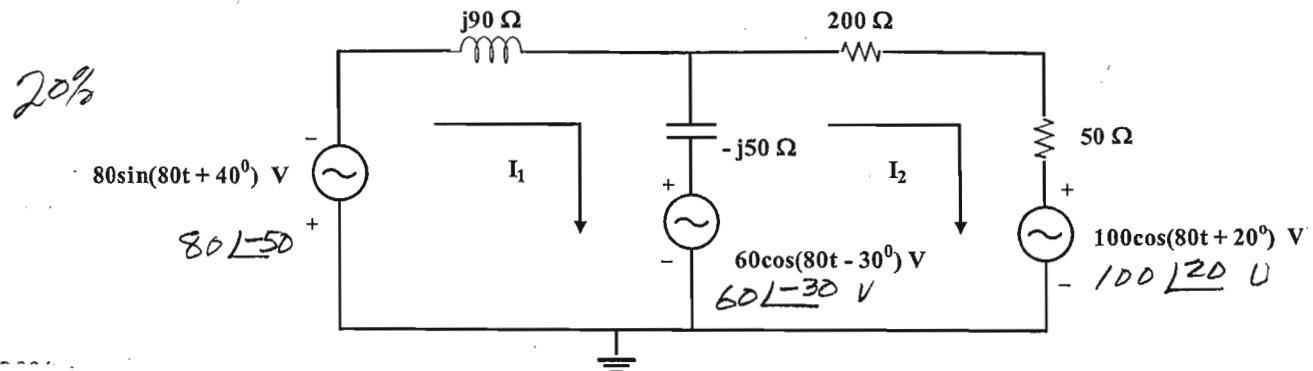- (2) You are given the AC circuit of Figure 2. Use a cosine reference. Use mesh analysis to solve for the phasor currents \mathbf{I}_1 and \mathbf{I}_2 . Give their values in polar form.



$$80 \sin(80t + 40^\circ) = 80 \cos(80t - 50^\circ)$$

As a phasor $80 \angle -50^\circ$

For mesh #1

$$80 \angle -50^\circ + j90 \vec{I}_1 - j50 \vec{I}_1 + j50 \vec{I}_2 + 60 \angle -30^\circ = 0$$

$$\begin{aligned} (j40) \vec{I}_1 + j50 \vec{I}_2 &= -80 \angle -50^\circ - 60 \angle -30^\circ \\ &= 80 \angle 130^\circ + 60 \angle 150^\circ \end{aligned}$$

mesh #2

$$-60 \angle -30^\circ - j50 \vec{I}_2 + j50 \vec{I}_1 + 250 \vec{I}_2 + 100 \angle 20^\circ = 0$$

$$\begin{aligned} j50 \vec{I}_1 + (250 - j50) \vec{I}_2 &= 60 \angle -30^\circ - 100 \angle 20^\circ \end{aligned}$$


$$\begin{bmatrix} (0+j40) (0+j50) \\ (0+j50) (250-j50) \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 80 \angle 130^\circ + 60 \angle 150^\circ \\ 60 \angle -30^\circ - 100 \angle 20^\circ \end{bmatrix}$$

$$\vec{I}_1 = 3.54 \angle 63.37^\circ \text{ A}$$

$$\vec{I}_2 = 6.72 \angle -39.7^\circ \text{ A}$$

3B

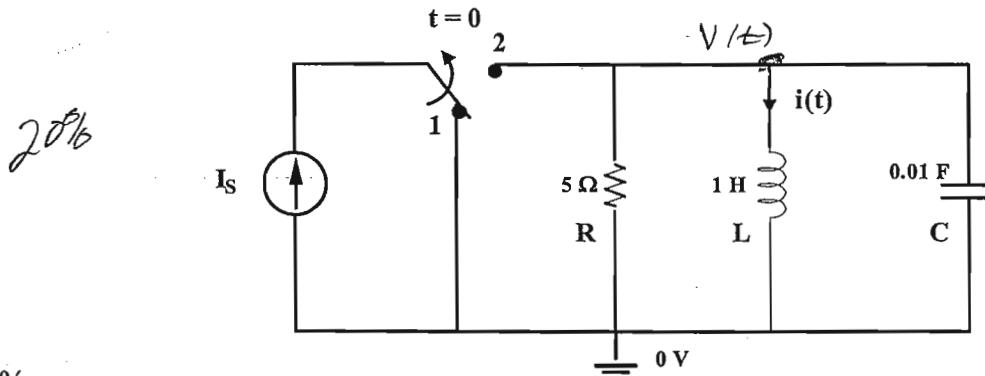- (3) You are given the parallel RLC circuit of Figure 3. The switch has been in position 1 for a very long time. All initial conditions on the circuit elements are zero for $t = 0^-$. At $t = 0$ the switch is moved from position 1 to position 2.



(a) Develop the differential equation that can be used to solve for $i(t)$.

(b) Give (determine) $i(0^+)$, and $\frac{di(0^+)}{dt}$.

(c) Which of the following forms would be used to find $i(t)$ for this circuit?
Explain your answer. You are not required to solve for A_1 and A_2 .

- $i(t) = 10 + (A_1 + A_2 t)e^{-10t} u(t)$, A
- $i(t) = 10 + A_1 e^{-2t} + A_2 e^{-5t} u(t)$, A
- $i(t) = 10 + e^{-10t} [A_1 \cos(100t) + A_2 \sin(100t)] u(t)$, A

For $t < 0$

$$i(0^-) = 0 \quad \therefore i(0^+) = 0 \quad \text{inductor}$$

$$V(0^-) = 0 \quad \therefore V(0^+) = 0 \quad \text{capacitor}$$

For $t > 0$

No δ analysis

$$\frac{V}{R} + C \frac{dV}{dt} + i(t) = I_s$$

$$\text{but } V(t) = L \frac{di}{dt}$$

$$\frac{L}{R} \frac{di}{dt} + LC \frac{d^2i}{dt^2} + i(t) = I_s$$

$$\frac{d^2i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{1}{LC} i = \frac{I_s}{LC}$$

with numbers

$$\frac{d^2i}{dt^2} + 20\frac{di}{dt} + 100i(t) = 100I_s$$

Characteristic Equation:

$$s^2 + 20s + 100 = 0$$

$$(s+10)(s+10) = 0$$

Form:


$$i(t) = 10 + [A_1 + A_2 t] e^{-10t}$$

$$i(0^+) = 0$$


$$V(0^+) = 0 = L \frac{di(0^+)}{dt}$$

$$\frac{d(i(0^+))}{dt} = 0$$

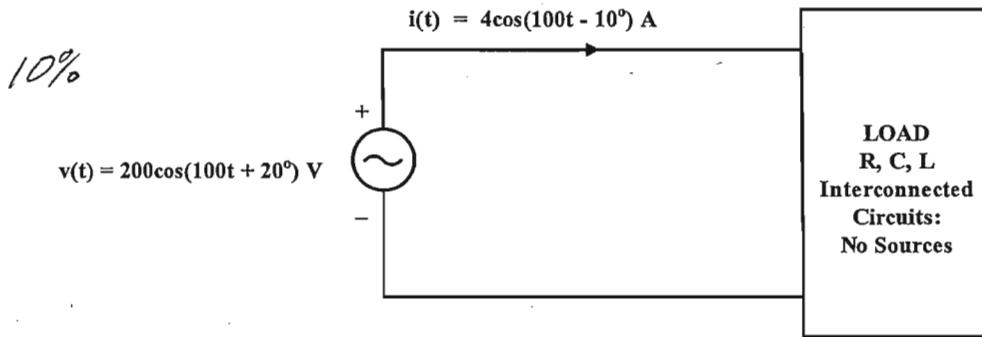- (4) You are given the circuit configuration of Figure 4. Assume V is the phasor voltage for $200\cos(100t + 20^\circ)$ V and I is the phasor current for $4\cos(100t - 10^\circ)$ A.
- Prepare the phasor diagram showing phasors V and I .
 - Use inspection to determine if the load is inductive or capacitive. Explain your answer.



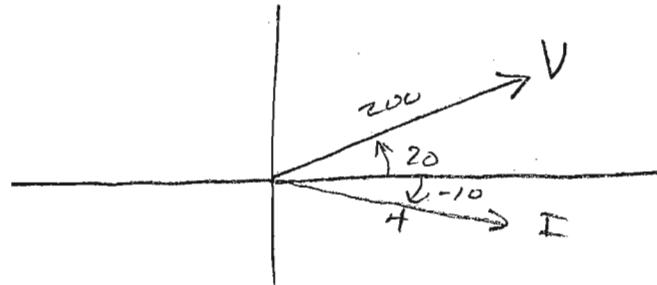(a) $\vec{V} = 200 \angle 20^\circ$ $\vec{I} = 4 \angle -10^\circ$



(b) Since \vec{V} leads \vec{I} the load is inductive.

Another view:


$$\vec{Z} = \frac{\vec{V}}{\vec{I}} = \frac{200 \angle 20^\circ}{4 \angle -10^\circ} = 50 \angle 30^\circ$$

Since Z has a positive \Im part the load is inductive.

3B

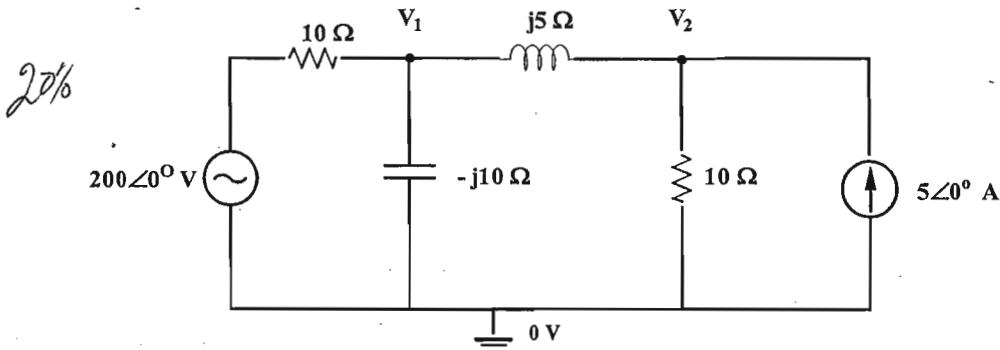(5) You are given the circuit shown in Figure 5. Assume a cosine reference.

- Use nodal analysis to find the phasor voltages V_1 and V_2 . Express these voltages in polar form.
- Give the expression for $v_2(t)$.
- Prepare a phasor diagram for phasor V_s , V_1 and V_2 .
- For the phasors V_s and V_1 which is leading and by how much angle?



At V_1

$$\frac{V_1 - 200}{10} + \frac{V_1}{-j10} + \frac{V_1 - V_2}{j5} = 0$$

$$0.1V_1 - 20 + j0.1V_1 - j0.2V_2 + j0.2V_2 = 0$$

$$(0.1 - j0.1)V_1 + (0 + j0.2)V_2 = 20$$

At V_2

$$\frac{V_2}{10} + \frac{V_2 - V_1}{j5} = 5\angle 0^\circ$$

$$0.1V_2 - j0.2V_2 + j0.2V_1 = 5\angle 0^\circ$$

$$(0.2V_1 + (0.1 - j0.2)V_2 = 5\angle 0^\circ)$$

$$\begin{bmatrix} 0.1 - j0.1 & j0.2 \\ j0.2 & 0.1 - j0.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 5 \end{bmatrix}$$


$$V_1 = 126.9 \angle -23.1^\circ \text{ V} \quad V_2 = 106.7 \angle -38.6^\circ \text{ V}$$

(15)

(16)


$$V_2(t) = 106.7 \cos(\omega t - 38.6^\circ) V$$

(1c)

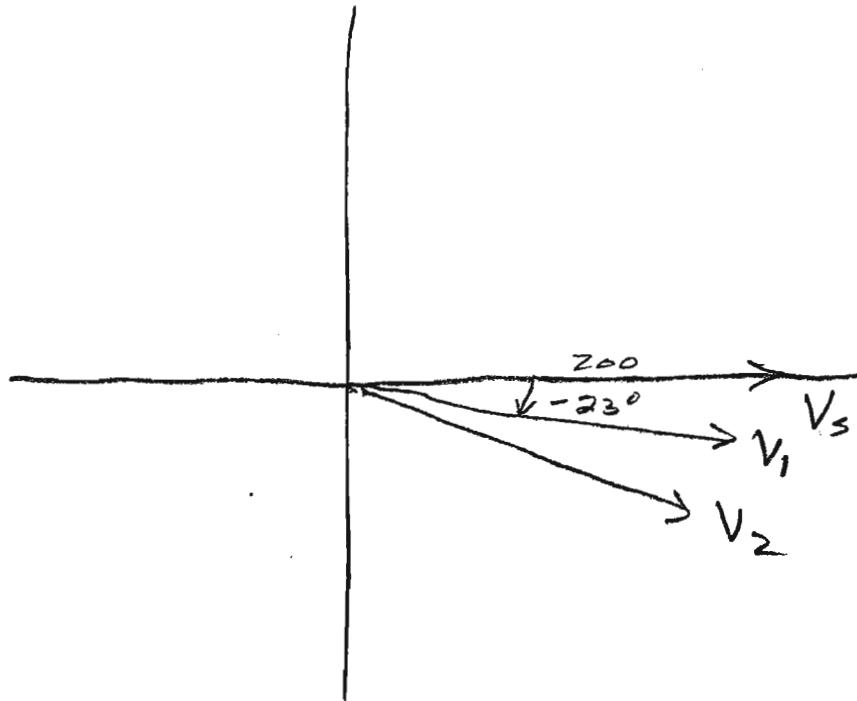(d) V_s leads V_1 by 23°

3B

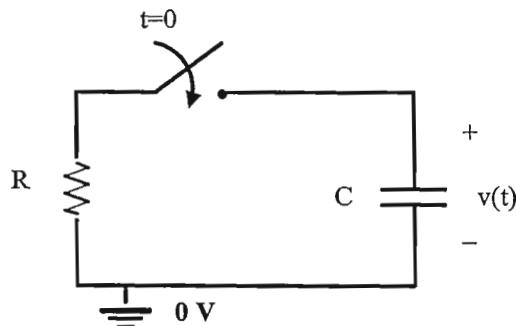- (6) Consider the circuit shown in Figure 6A. The switch has been open for a very long time and is closed at $t = 0$. Prior to $t = 0$, the capacitor is initially charged to 20 volts. The capacitor voltage for $t \geq 0$ is shown in Figure 6B.
- Determine the time constant for the circuit.
 - If $R = 20 \Omega$, what is the value of C ?



10%

Figure 6B: Circuit for problem 6.

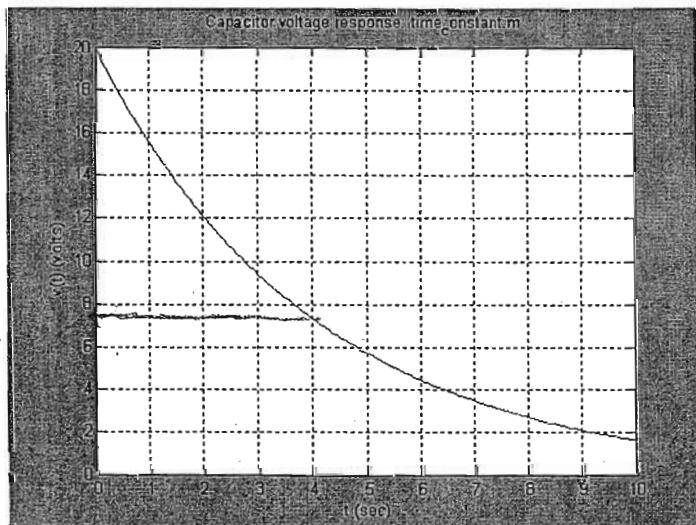


Figure 6B: Voltage response for the circuit of Figure 6B.

$$(a) V(t) = 20 e^{-\frac{t}{T}} \quad |_{t=\tau} = 20 e^{-1} = 7.36$$

$\boxed{\text{At } V = 7.36, \quad t = \tau = 4}$

$$(b) \tau = 4 = RC = 20 \text{ sec}$$

$$C = \frac{4}{20} = \frac{1}{5} = 0.2 \text{ F}$$