

*Jeak copy*

**ECE 300  
Spring Semester, 2005  
HW Set #2**

**January 25, 2005**

wlg

AM

PM

Name GREEN

Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 4 points.

Study and work the Review Questions at the end of Chapter 2: You are not required to submit your solutions to these review questions.

2.10  $i_1 = 7 \text{ A}, i_2 = -5 \text{ A}$

2.16  $v_1 = 14 \text{ V}, v_2 = 22 \text{ V}$

2.18 On your own

2.22  $v_o = -4.44 \text{ V}, P_{\text{disp}} = 99 \text{ W}$

2.31  $v = 10 \text{ V}, I = 1 \text{ A}, P_{\text{abs } 4 \text{ ohm}} = 4 \text{ W}$

2.33  $v = 3 \text{ V}, I = 6 \text{ A}$

2.34  $i_1 = 2 \text{ A}, i_2 = 0.24 \text{ A}, v_1 = 12 \text{ V}, v_2 = 3.12 \text{ V}$

2.40  $R_{\text{eq}} = 5 \text{ ohms}, I = 2 \text{ A}$

2.43 (a)  $R_{\text{ab}} = 12 \text{ ohms},$  (b)  $R_{\text{ab}} = 16 \text{ ohms}$

2.56  $v = 42.18 \text{ V}$

2.58  $V_s = 210 \text{ V}$

2.64  $R = 11 \text{ ohms}, R_x = 99 \text{ ohms}$

2.77 (a) 4 @ 20 in parallel


(b) 300 ohms in series with 1.8 ohms and a parallel combination of two 20 ohms resistors

(c) two 29 k ohms in parallel, connected in series with 2, 50 k ohms in parallel

wlg

# Homework Set #2 ECE 300

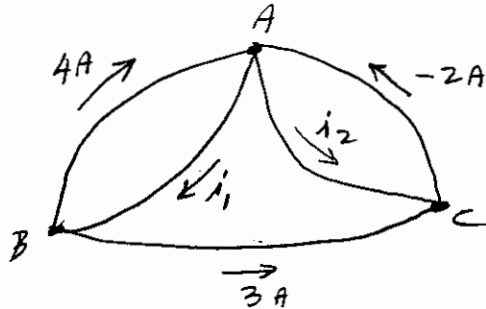2.10 Find  $i_1$  &  $i_2$  in the following circuit



At C:

$$i_2 + 3 = -2$$

$$i_2 = -5A$$


At B:

$$i_1 = 3 + 4 = 7$$

$$i_1 = 7A$$

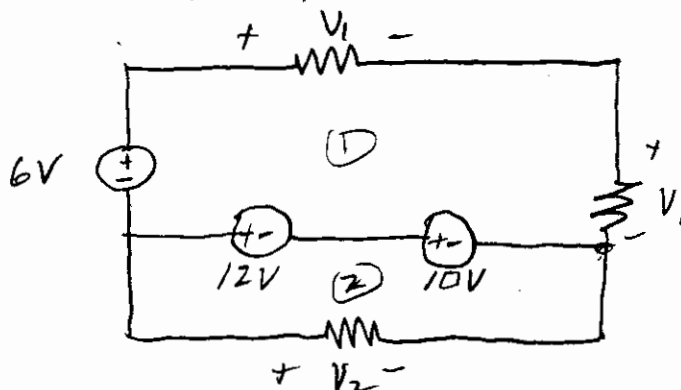2.16

Find  $V_1$  and  $V_2$  in the following ckt.



Around mesh ①

$$\sum \text{rises} = 0 \text{ CW}$$

$$2V_1 - 6 - 12 - 10 = 0$$

$$2V_1 = 28$$

$$V_1 = 14V$$

Around mesh ②

$$\sum \text{rises} = 0 \text{ CW}$$


$$10 + 12 - V_2 = 0$$

$$V_2 = 22V$$

Wk 9

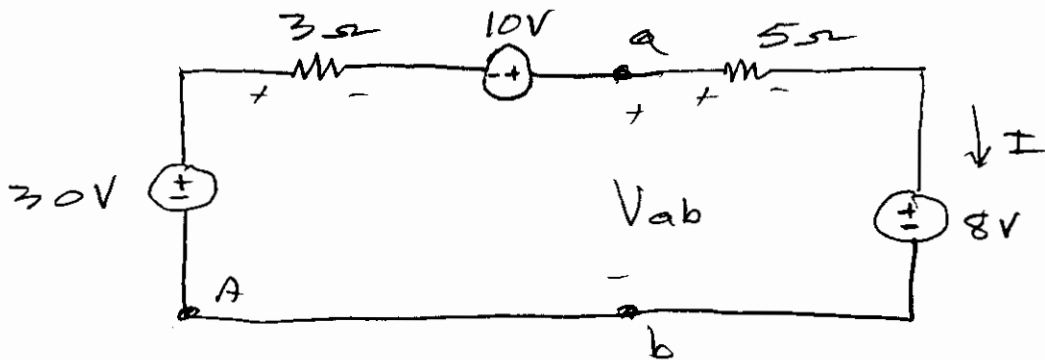2.18

Find  $I$  and  $V_{ab}$  in the ckt below.



$\sum v_{loop} = 0$ ,  
start at A, go CW

$$30 - 3I + 10 - 5I - 8 = 0$$

$$8I = 32$$

$$I = 4 \text{ A}$$

start at "b" go CW using

$$\sum v_{loop} = 0$$


$$V_{ab} - 5I - 8 = 0$$

$$V_{ab} = 5I + 8 \Big|_{I=4} = 20 + 8$$

$$V_{ab} = 28 \text{ V}$$

wky

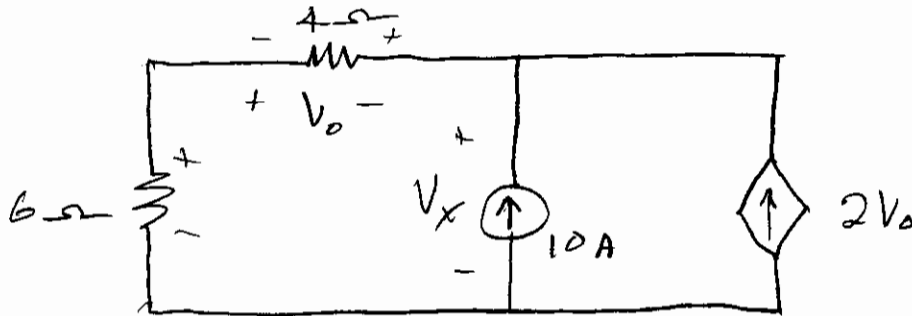2.22 Find  $V_o$  in the following ckt and the power dissipated by the controlled source.



$$V_x + V_o - 6(10 + 2V_o) = 0$$

$$V_x + V_o - 12V_o - 60 = 0$$

$$\boxed{V_x - 11V_o = 60}$$

Also,

$$V_o + 4(10 + 2V_o)$$

$$9V_o = -40$$

$$\therefore V_o = -4.44 \text{ V}$$

Also

$$V_x = 60 + 11V_o = 60 - 11 \times 4.44 = 11.16 \text{ V}$$


$$P_{\text{disp}} = (-V_x)(2V_o) = (-11.16)(2(-4.44))$$

$$\boxed{P_{\text{disp}} = 99.1 \text{ W}}$$

wtg

2,31

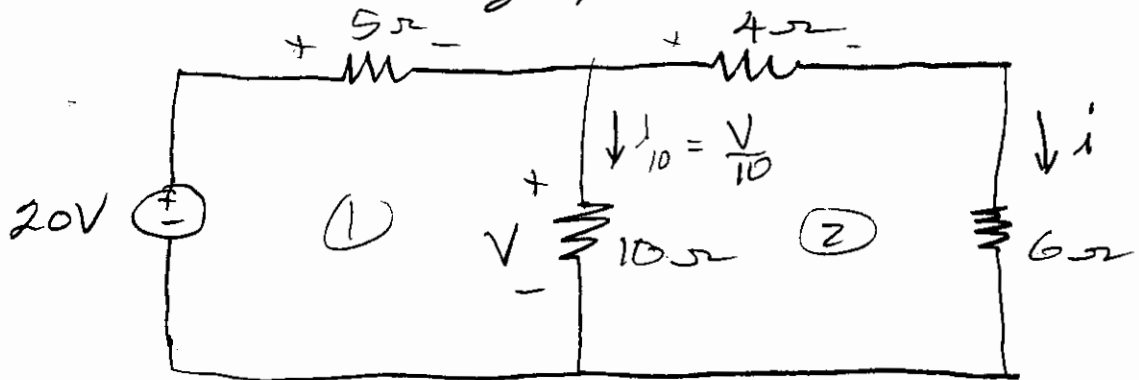Find  $V$  and  $i$  and the power absorbed by the  $4\Omega$  resistor.



Around (1)  $\sum v \cdot i = 0$ , CW

$$20 - 5 \cdot \left( \frac{V}{10} + i \right) - V = 0$$

$$-1.5V - 5i = -20$$

OR

$$\boxed{1.5V + 5i = 20} \quad \text{(A)}$$

Around (2)  $\sum v \cdot i = 0$ , CW

$$\boxed{V - 10i = 0} \quad \text{(B)}$$

Solving (A) and (B)

$$V = 10V$$


$$i = 1A$$

$$P_{\text{abs}} = i^2 R = (1)^2 \times 4 = 4W$$

wkg

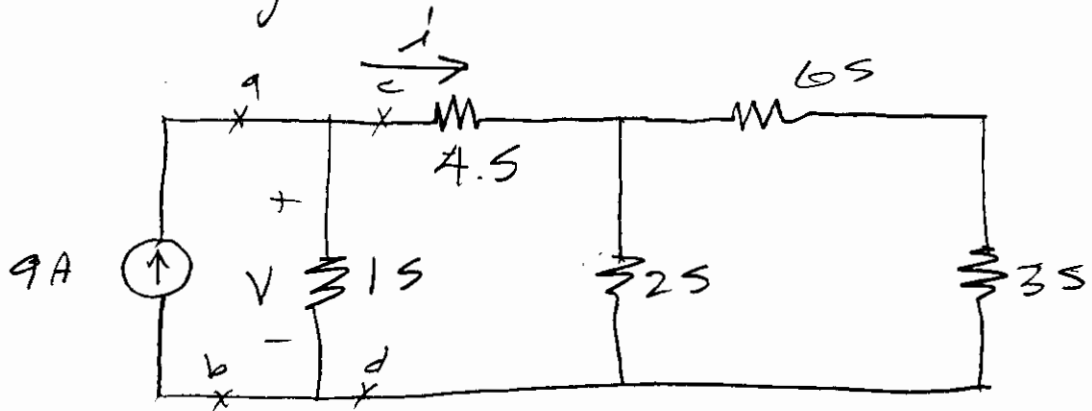2.33

Find  $V$  and  $i$  in the following circuit.



3 ohm in series with 6 ohm

$$\frac{3 \times 6}{3 + 6} = 2 \text{ ohm}$$

2 ohm in parallel with 25 ohm

$$25 + 2 = 27 \text{ ohm}$$

Then 27 ohm in series with 4.5 ohm

$$\frac{27 \times 4.5}{27 + 4.5} = 3.75 \text{ ohm}$$

Then 3.75 ohm in parallel with 15 ohm

$$Y_{ab} = 25 + 15 = 35 \text{ ohm}$$

$$V = \frac{9}{3} = 3 \text{ V}$$


$$Y_{cd} = 2 \text{ ohm}$$

$$i = V \times Y_{cd} = 3 \times 2 = 6 \text{ A}$$

wly

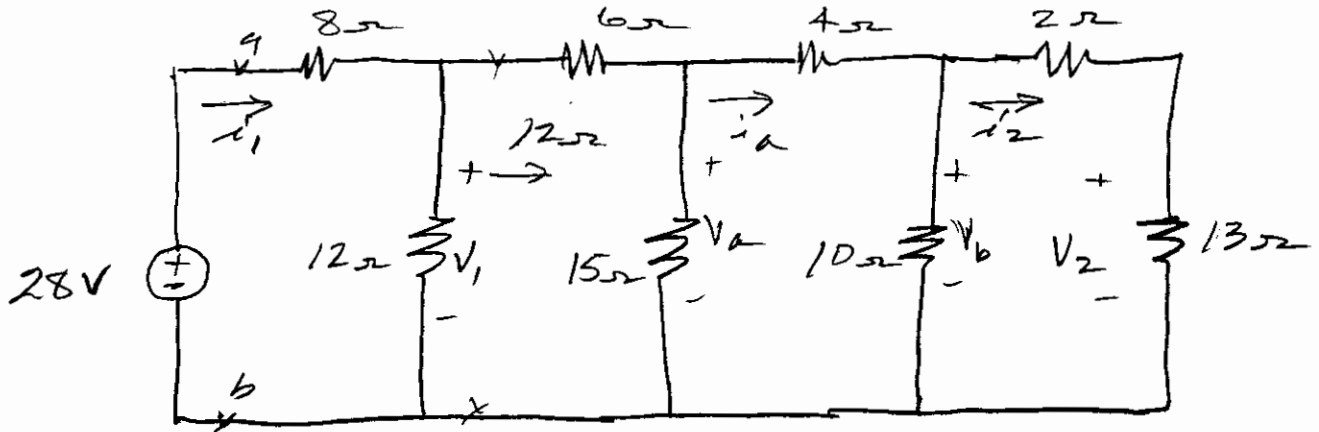2.34

Determine  $i_1$ ,  $i_2$ ,  $V_1$ , and  $V_2$  in the network below. Calculate the power dissipated in the  $2\Omega$  resistor.



Find  $R_{ab}$

$$15 \parallel 10 = \frac{15 \times 10}{25} = 6\Omega$$

$6\Omega$  in series with  $4\Omega = 10\Omega$

Then

$$10\Omega \parallel 15\Omega = 6\Omega$$

$6\Omega$  in series with  $6\Omega = 12\Omega$

$$12\Omega \parallel 12\Omega = \underline{6\Omega}$$

$6\Omega$  in series with  $8\Omega = 14\Omega$

$$\text{So } R_{ab} = 14\Omega$$

$$i_1 = \frac{28}{14} = 2A$$

alg

2

2.34 continued

$$V_1 = i_1 \times 6 = 2 \times 6 = 12 \text{ V}$$

$$\boxed{V_1 = 12 \text{ V}}$$

$$V_a = \frac{V_1 \times 6}{6+6} = \frac{V_1}{2} = \frac{12}{2} = 6 \text{ V}$$

$$V_b = \frac{6 \text{ V} \times 6}{6+4} = 3.6 \text{ V}$$

$$V_2 = \frac{(3.6)(13)}{13+2} = 3.12 \text{ V}$$

$$\boxed{V_2 = 3.12 \text{ V}}$$

$$i_2 = \frac{3.12}{13} = 0.24 \text{ A}$$

$$\boxed{i_2 = 0.24 \text{ A}}$$

$$P_{2\Omega} = (i_2^2) 2 = (0.24)^2 \times 2$$


$$\boxed{P_{2\Omega} = 0.115 \text{ W}}$$



W/h

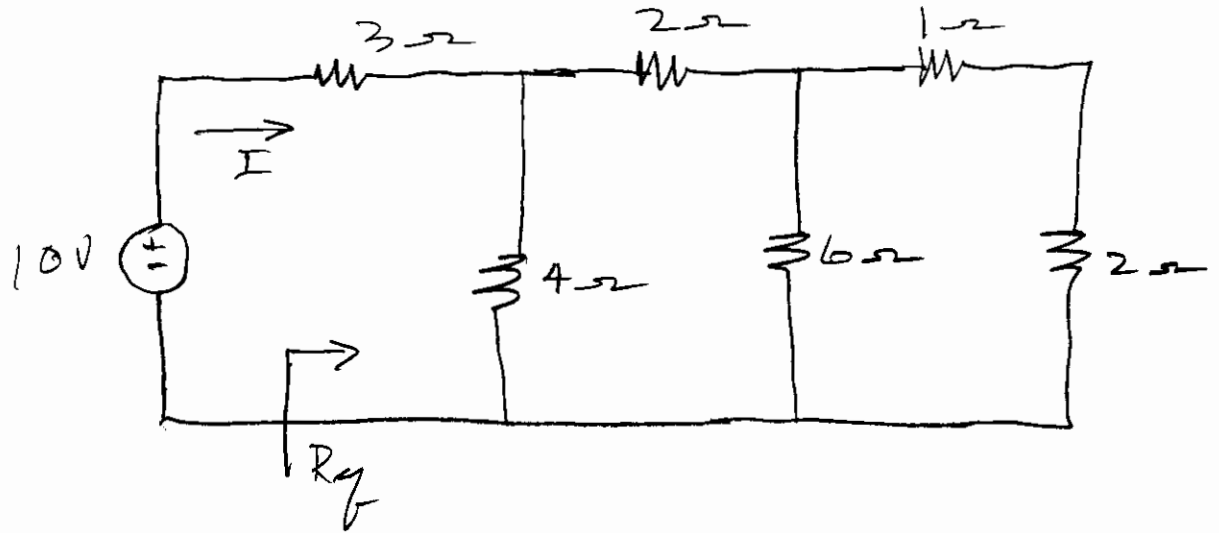2.40

FIND  $I$  and  $R_{eq}$  for the ckt below.



FOR  $R_{eq}$ , starting at the far right.

$$3 \parallel 6 = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2 \Omega$$

2 IN series with 2 =  $4 \Omega$

$$4 \parallel 4 = \frac{4 \times 4}{4 + 4} = 2 \Omega$$


$$R_{eq} = 3 + 2 = 5 \Omega$$

$$I = \frac{10V}{5} = 2A$$

WQ 7

2.43

(a) Find  $R_{ab}$  for the following

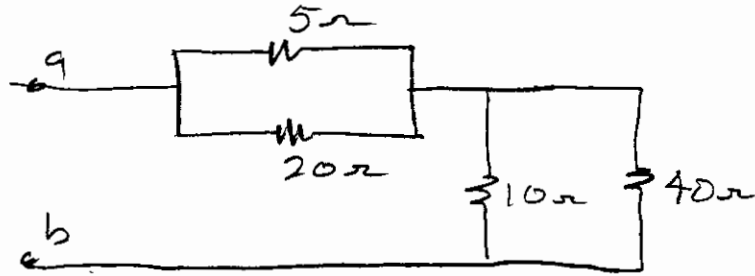


$$R_{ab} = 5 \parallel 20 + 10 \parallel 40$$

$$= \frac{5 \times 20}{20 + 5} + \frac{10 \times 40}{10 + 40}$$

$$R_{ab} = 4 \Omega + 8 \Omega = 12 \Omega$$

$$R_{ab} = 12 \Omega$$

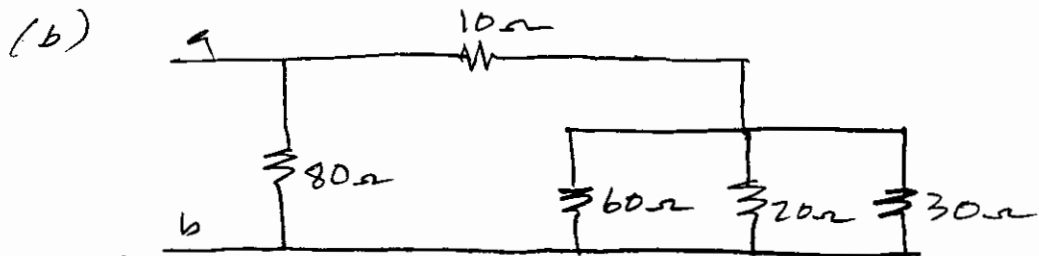

60, 20, 30 in parallel

$$\frac{20 \times 30}{20 + 30} = 12 \Omega$$

$$\frac{60 \times 12}{72} = 10 \Omega$$


$$R_{ab} = \frac{80 \times 20}{80 + 20} = 16 \Omega$$

wk 4

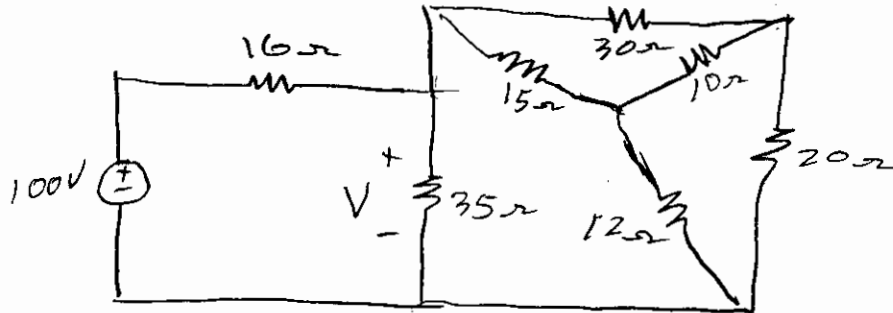
2.56

Find  $V$  in the circuit below. Since this is in the wye-delta section of the problems, I will use Y- $\Delta$ .

First I redraw the circuit identifying the Y- $\Delta$  portions, that I see.



I will use the  $\Delta$  on the right

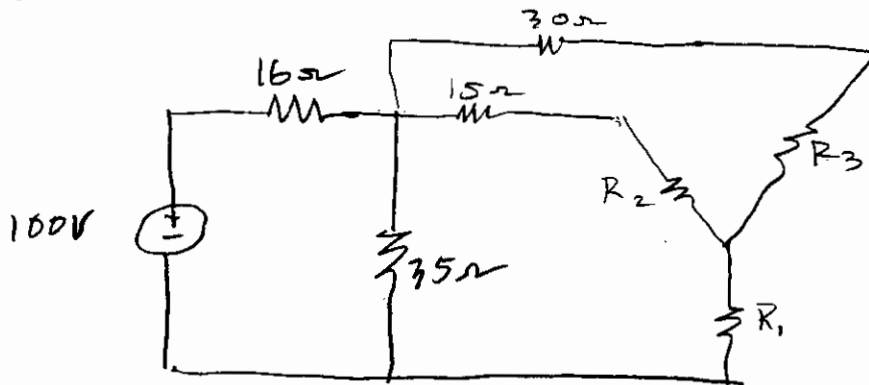

$$R_1 = \frac{12 \times 20}{12 + 20 + 10} = 5.714 \Omega$$



$$R_2 = \frac{10 \times 12}{12 + 20 + 10} = 2.86 \Omega$$

$$R_3 = \frac{10 \times 20}{12 + 20 + 10} = 4.762 \Omega$$


W/64  
2.56 CONTINUED

(2)

The ckt becomes;

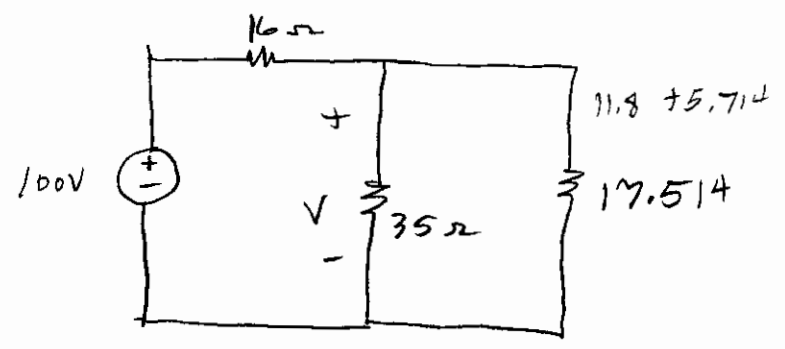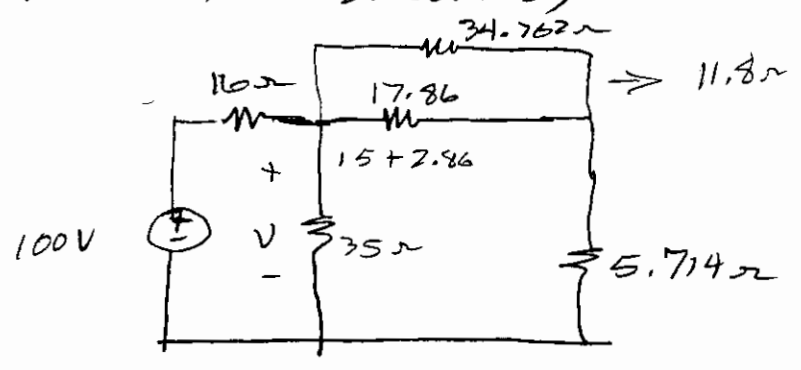
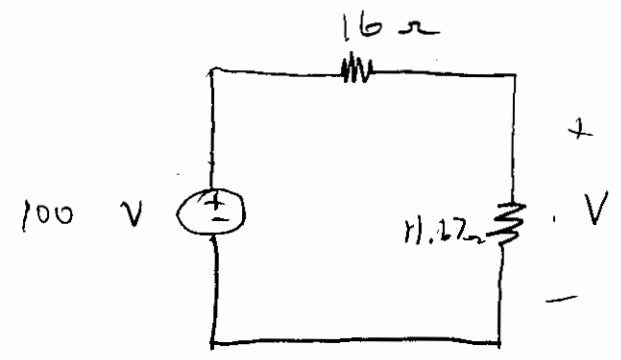
$$35 \parallel 17.514 = \frac{35 \times 17.514}{35 + 17.514} = 11.67$$




By voltage division

$$V = \frac{100 \times 11.67}{16 + 11.67} = 42.18 \text{ V}$$

w/q

2.58

Given the following

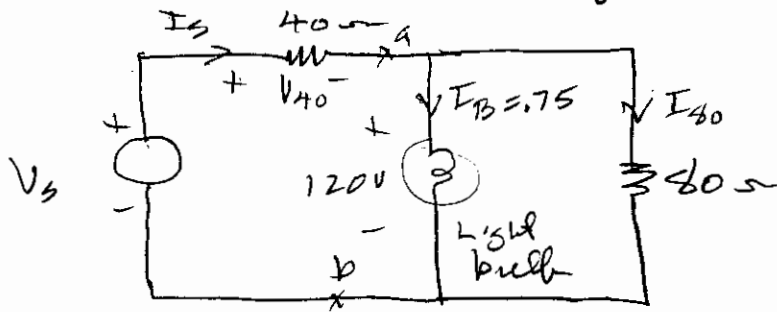

Light bulb is rated at  $120\text{V}$ ,  $0.75\text{A}$ .

I assume this means d.c. since we have not covered A.C. I further assume there is  $120\text{V}$  drop across the bulb and it is drawing  $0.75\text{A}$ .

Calculating  $I_s$

$$I_s = I_B + I_{80}$$

$$\text{where } I_{80} = \frac{120\text{V}}{80} = 1.5\text{A}$$

$$I_s = 0.75 + 1.5 = 2.25\text{A}$$

Calculating  $V_s$

$$V_s = V_{40} + 120 = 2.25 \times 40 + 120$$


$$V_s = 90 + 120$$

$$\boxed{V_s = 210\text{V}}$$

w/g

2.64

Given

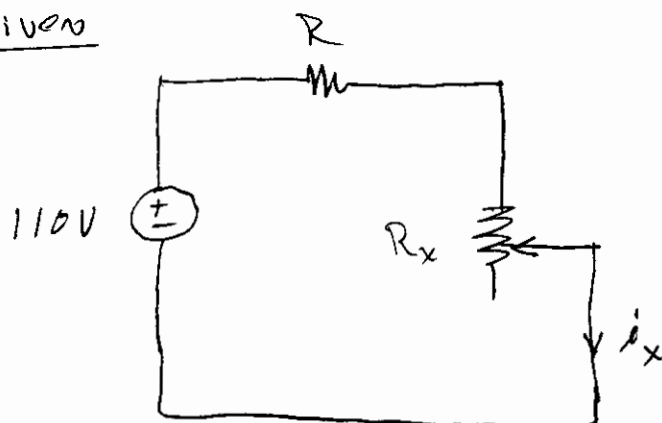

Assume High End For  $i_x$

With  $R_x$  giving zero resistance to the circuit;

$$i_x = \frac{110}{R} = 10$$

$$\therefore \boxed{R = \frac{110}{10} = 11 \Omega}$$

Assume Low End For  $i_x$

$R_x$  fully in

$$\frac{110}{11 + R_x} = 1$$

$$R_x + 11 = 110$$

$$\boxed{R_x = 99 \Omega}$$

$$R = 11 \Omega$$

$$R_x = 99 \Omega$$

with


### 2.17

Given, in large quantities

$1.8\Omega, 20\Omega, 300\Omega, 24K\Omega, 56K\Omega$

Using series & parallel combinations and a minimum number of available resistors, how would you obtain the following resistances?

(a)  $5\Omega$

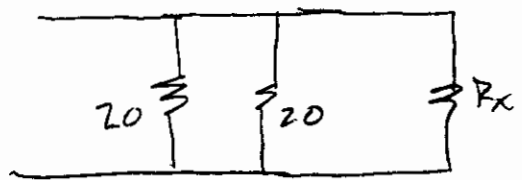

$20 \parallel 20 = 10$   
 Try  $10 \parallel R_x = 5$


$$\frac{10 R_x}{10 + R_x} = 5$$

$$10 R_x = 50 + 5 R_x$$

$R_x = 10\Omega$  can do this with


2,  $20\Omega$  resistors.

40:

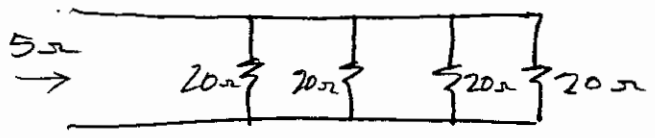

(b) Want  $311.8$



$$300 + 1.8 + 20 \parallel 20$$

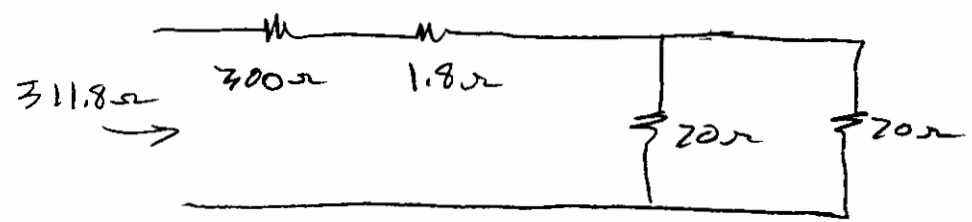

2.77 cont

(c) want 40 KΩ

want 40 KΩ

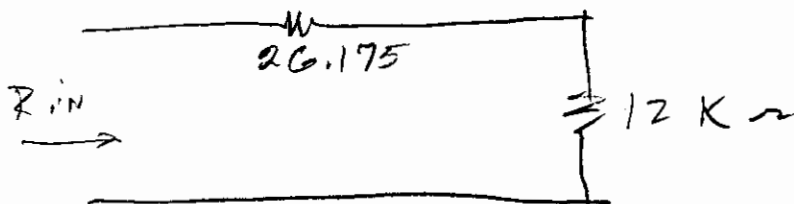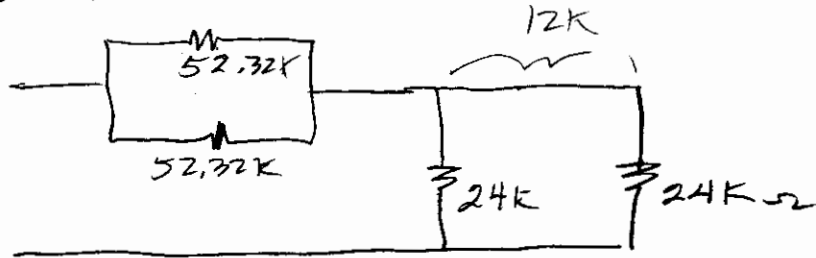

$R_{in} = 38.175 K\Omega$

Close AS I can get

with 4 or fewer resistors. You could continue with  $300\Omega$  (several) and round  $1.8\Omega$  and get close but many resistors.

Book Answer assumes we have  $56K\Omega$

with this

