
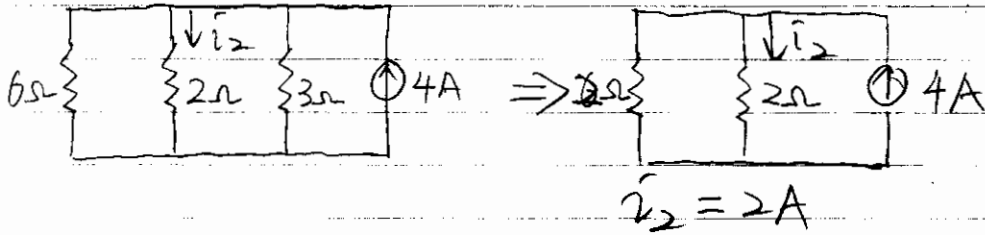




HW #4

4.11


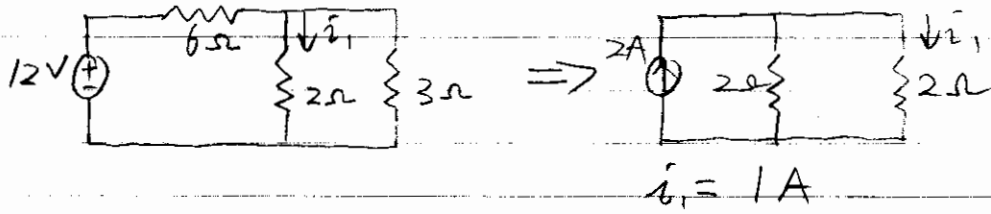


$$i = i_1 + i_2 = 3A$$


4.22

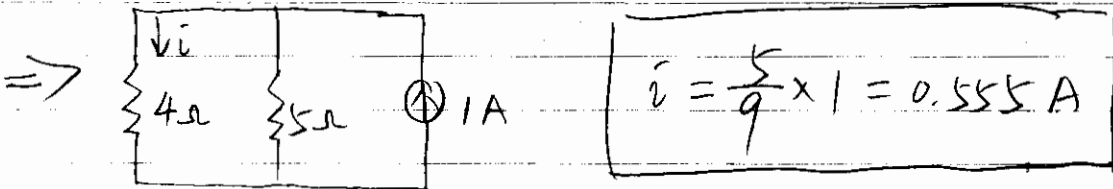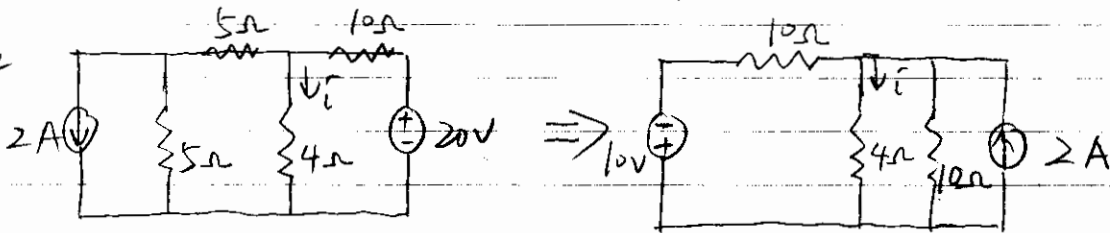

4.31

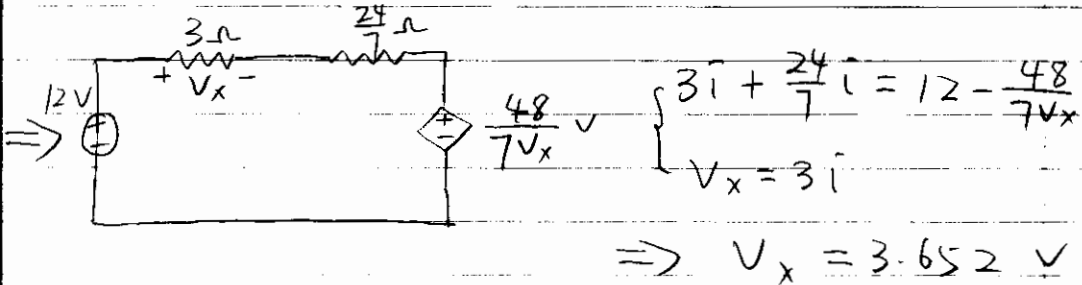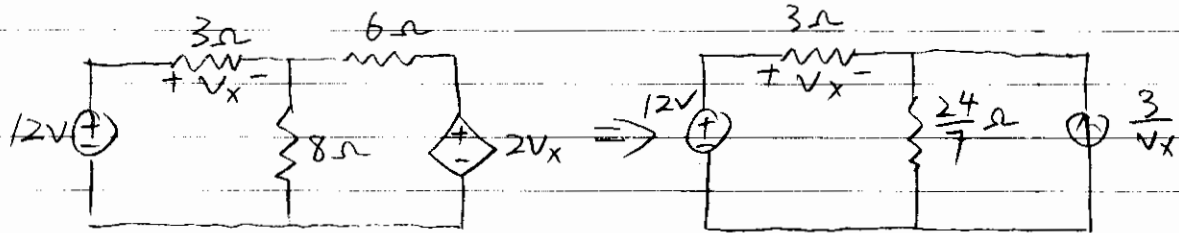

4.36




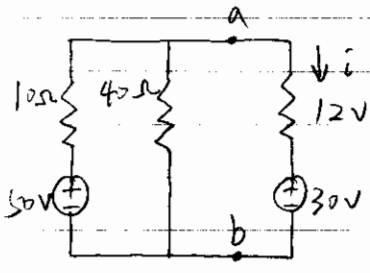


$$R_{th} = 10\Omega // 40\Omega = 8\Omega$$

$$V_{th} = 40V$$





$$i = \frac{40 - 30}{12 + 8} = 0.5 A$$

4.38

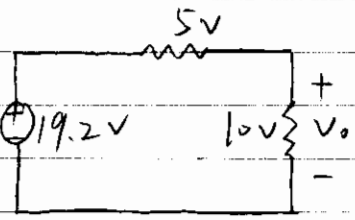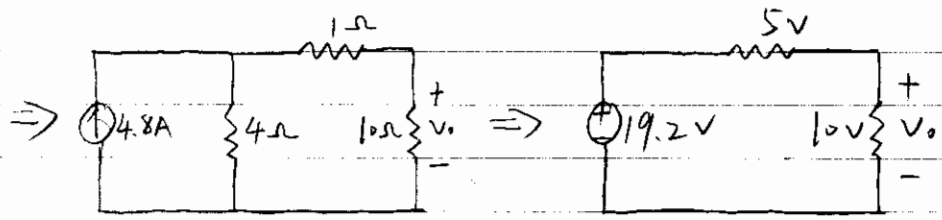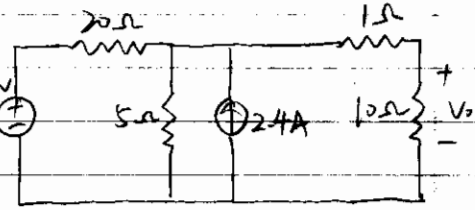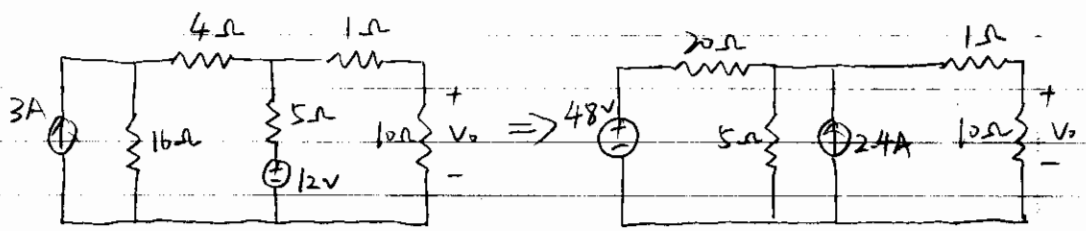

$$V_o = \frac{10}{10 + 5} \times 19.2 = 12.8 V$$

4.41

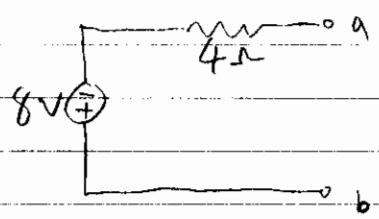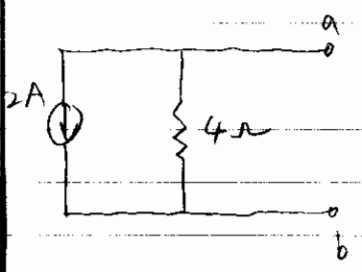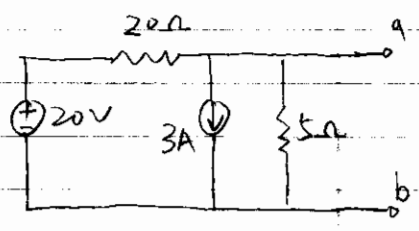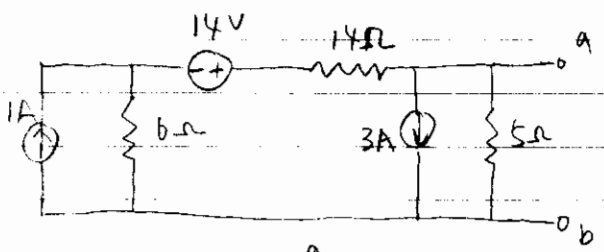


Norton

Thevenin

$$I_N = -2A, \quad R_{th} = 4\Omega, \quad V_{th} = -8V$$


4.47

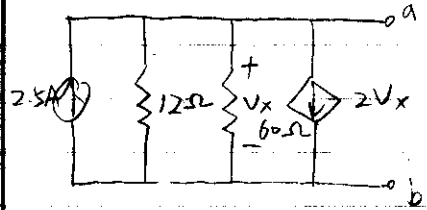

$$(2.5 - 2V_x) \cdot (12 \parallel 60) = V_x$$

$$V_x = 1.19 \text{ V}$$

$$V_{th} = V_x = 1.19 \text{ V}$$

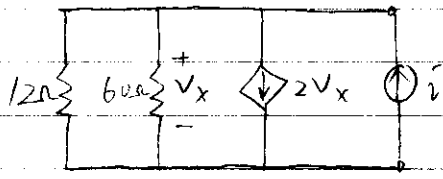


$$\frac{V_x}{12} + \frac{V_x}{60} + 2V_x = i$$

$$126V_x = 60i$$

$$i = 2.5 \text{ A}, \quad R_{th} = \frac{V_x}{i} = 0.476 \Omega$$

4.52

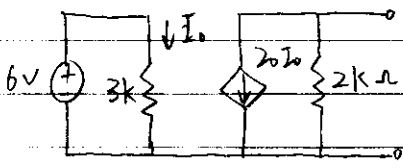


$$I_o = \frac{6}{3k} = 2 \text{ mA}$$

$$R_{th} = 2k \Omega$$


$$V_{th} = -20I_o \cdot 2k = -20 \times 2m \times 2k = -80 \text{ V}$$

4.54

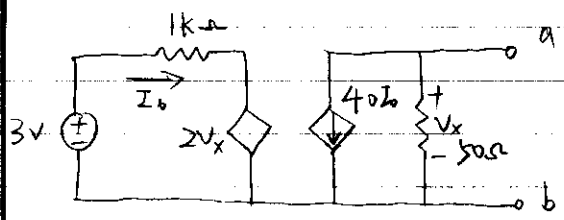

$$\begin{cases} 3 - 2V_x = 1000I_o \\ V_x = -50(40I_o) \end{cases}$$

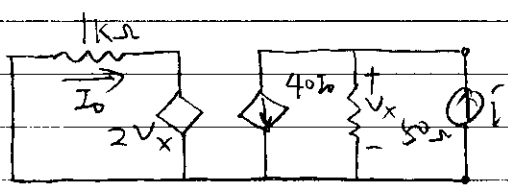
$$\Rightarrow V_{th} = V_x = 2 \text{ V}$$



$$\begin{cases} -2V_x = 1000I_o \\ \frac{V_x}{50} + i = 40I_o \end{cases}$$


$$\Rightarrow R_{th} = \frac{V_x}{i} = -16.67 \Omega$$

4.57

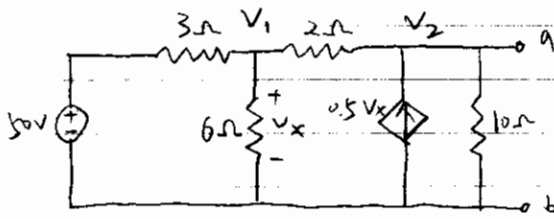

$$\begin{cases} \frac{V_1 - 50}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0 \\ \frac{V_2 - V_1}{2} + \frac{V_2}{10} - \frac{V_1}{2} = 0 \end{cases}$$
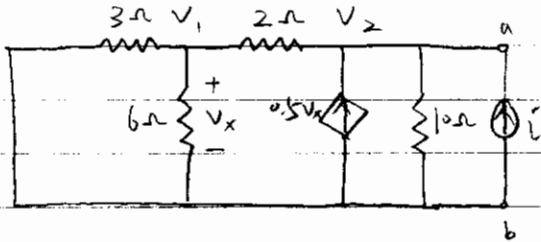
$$\Rightarrow V_{th} = V_2 = 166.67 \text{ V}$$




$$\begin{cases} \frac{V_1}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0 \\ \frac{V_2 - V_1}{2} + \frac{V_2}{10} - \frac{V_1}{2} - i = 0 \end{cases}$$

$$\Rightarrow i = 16.67 \text{ A}$$

$$R_{th} = \frac{V_{th}}{i} = \frac{166.67}{16.67} = 10 \Omega$$

4.63

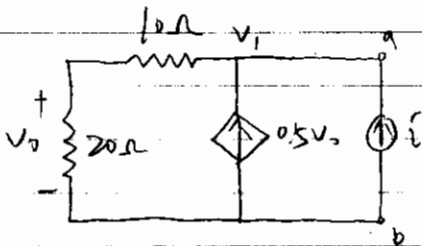

$$\begin{cases} \frac{V_1}{30} - 0.5V_0 - i = 0 \\ V_0 = \frac{2}{3} V_1 \end{cases}$$

$$R_{th} = \frac{V_1}{i} = -3.33 \Omega$$

No independent voltage source or current source,
 $V_{th} = 0$, $I_N = 0$