

Desk Copy

ECE 300  
Spring Semester, 2005  
HW Set #5

Due: February 24, 2005

wlg

AM

PM

Name Green

Print(last, first)

Use Engineering Paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers. Each problem counts 5 points.**

Work the following problems from the text. Answers to the problems, except 4.68, are in the Appendix of the text. You should visit my web site and review the power point slides on op-amps before attempting this homework.

4.68  $P_L = 1.6W, V_{TH} = 4V, R_{TH} = 0\Omega$

4.69  $-1.187kW$

4.75  $1k\Omega$

5.9 (a)  $2V, (b) 2V$

5.11  $-2V, -1mA$

5.13  $2.7V, 288\mu A$


5.15 (a)  $-(R_1 + R_3 + \frac{R_1 R_3}{R_2})$  (b)  $-92k\Omega$

5.19  $-0.375mA$


5.27 (a)  $10.2, (b) 1.471 \cos(20\pi t)$

5.31  $0.7272mA$

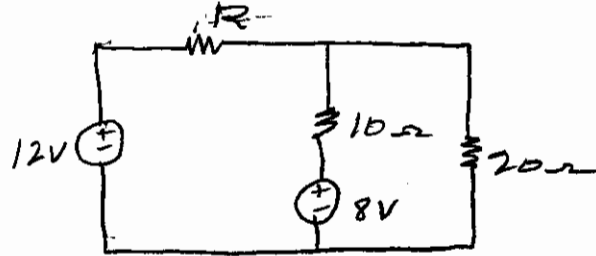
4.68 Find the value of  $R$  that results in maximum power transfer to the  $10\Omega$  resistor. Find the maximum power,



REARRANGES

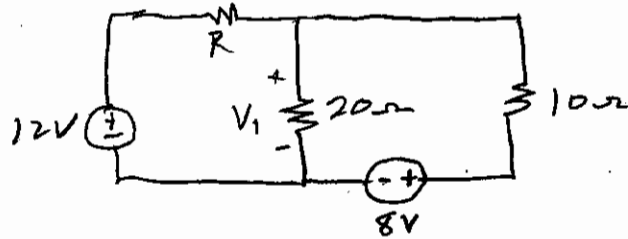

$$R_{TH} = \frac{20R}{20+R}$$

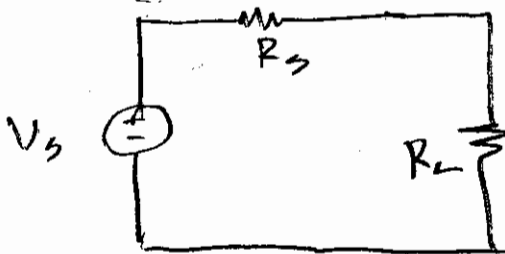

Consider  $R_s$  is the variable resistor;  $R_L$  is fixed

At the load

$$P_L = \left( \frac{V_s R_L}{R_s + R_L} \right)^2 \times \frac{1}{R_L} = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$

We see that for

$$P_L = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$


to have the largest value for fixed  $V_s$  and  $R_L$ ;  $R_s = 0$ .

4.68


$$R_s = 0 = R_{TH} = \frac{20R}{20+R}$$

Requires  $R = 0$

With  $R = 0$  we have the following;

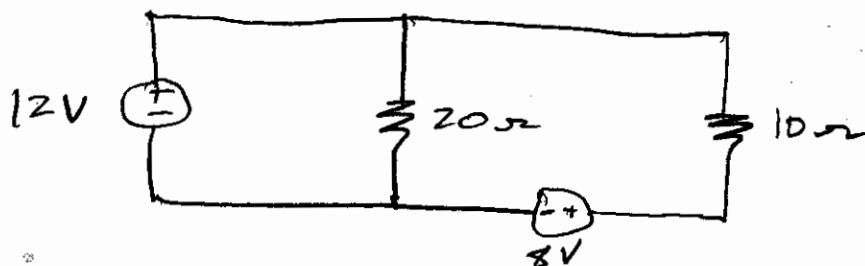

OR

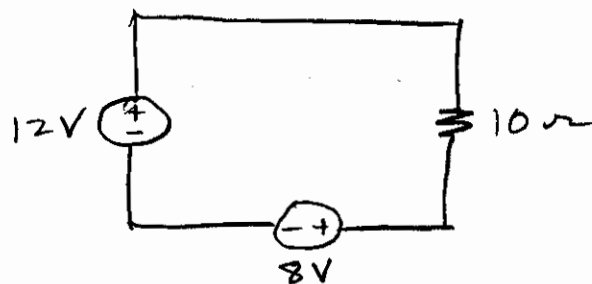

$$P_L = \frac{V_L^2}{10} = \frac{4^2}{10} = \frac{16}{10}$$


$$P_L = 1.6 \text{ W}$$

$$V_{TH} = 4 \text{ V}$$

$$R_{TH} = 0 \text{ } \Omega$$

4.69


By Pengfei Xi

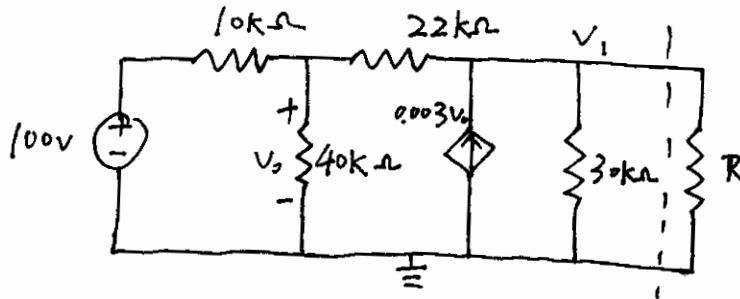

with R removed,

$$\begin{cases} \frac{V_o - 100}{10k} + \frac{V_o}{40k} + \frac{V_o - V_1}{22k} = 0 \\ \frac{V_1 - V_o}{22k} + \frac{V_1}{30k} = 0.003V_o \end{cases}$$
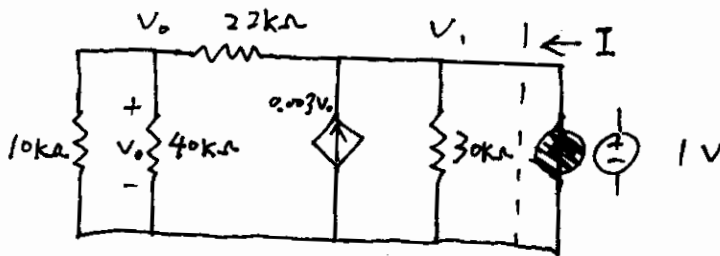
$$\Rightarrow V_o = -243.6 \text{ V} = V_{TH}$$



$$\begin{cases} \frac{V_o}{10k} + \frac{V_o}{40k} + \frac{V_o - V_1}{22k} = 0 \\ \frac{V_1 - V_o}{22k} + \frac{V_1}{30k} = 0.003V_o + I \end{cases}$$

$$V_1 = 1 \text{ V}$$


$$\Rightarrow V_o = 0.267 \text{ V}$$

$$I = -0.733 \text{ mA}$$

$$R_{TH} = \frac{1}{I} = \frac{1}{-0.733 \text{ m}} = -1.36 \text{ k}\Omega$$

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(-243.6)^2}{4 \times (-1.36 \text{ k})} = -10.9 \text{ W}$$

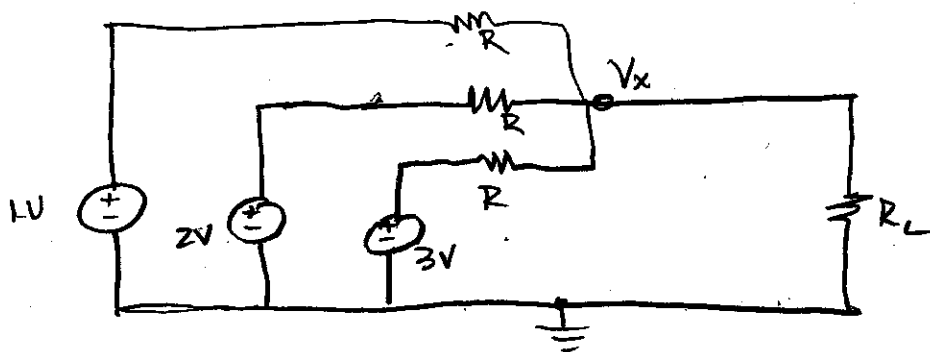4.75 Determine the value of  $R$  such that the maximum power delivered to the load is  $3\text{ mW}$ .




The Thevenin resistance is  $\frac{R}{3}$ .

With  $R_L$  removed we can write a node equation at  $V_x$ .

$$\frac{V_x - 1}{R} + \frac{V_x - 2}{R} + \frac{V_x - 3}{R} = 0$$

$$3V_x = 6$$

$$V_x = 2 = V_{TH}$$

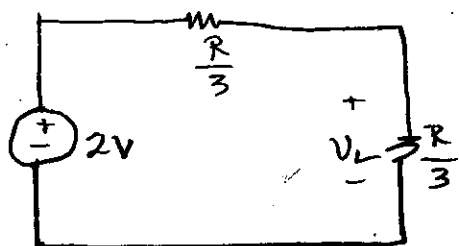


$$V_L = \frac{2 \times \frac{R}{3}}{\frac{R}{3} + \frac{R}{3}} = \frac{2}{2} = 1\text{ V} \quad \text{as expected}$$

$$P_L = \frac{V_L^2}{R/3} = 3\text{ mW} = \frac{3}{R}$$

$$R = 1\text{ k}\Omega$$

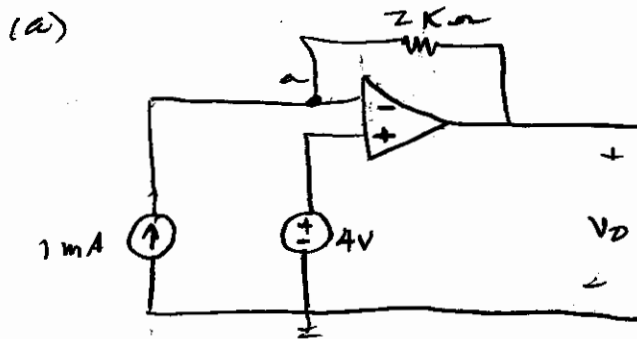5.9 Determine  $V_D$  for each of the following op-amp circuits.



At a:


$$1 \text{ mA} = \frac{4 - V_D}{2 \text{ k}}$$

OR

$$2 = 4 - V_D$$

$$\boxed{V_D = 2 \text{ V}}$$

(b)

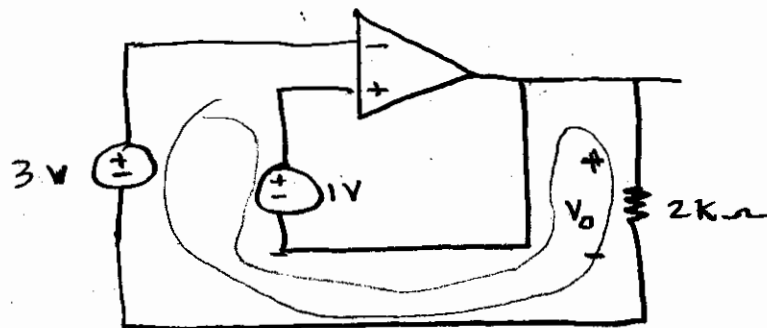


Writing KVL around the indicated path gives

$$-3 + 1 + V_D = 0$$

OR

$$\boxed{V_D = 2 \text{ V}}$$

5.11

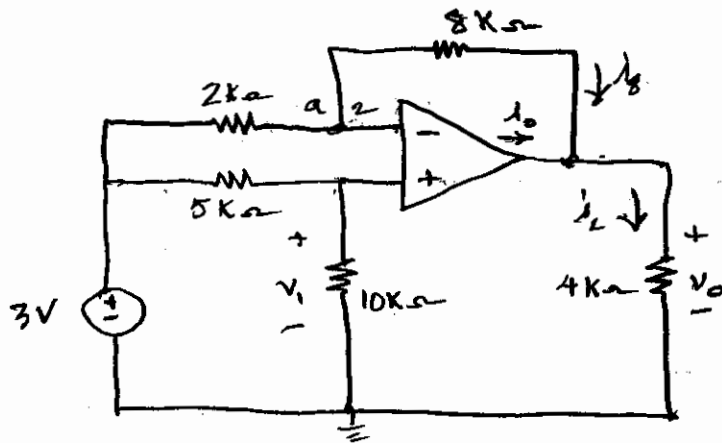Find  $V_o$  and  $i_o$  in the following ckt.

$$V_1 = \frac{3 \times 10K}{10K} = 2V$$

The voltage at node "a" is 2V. Writing a node equation at a gives

$$\frac{2-3}{2K} + \frac{2-V_o}{8K} = 0$$

$$-4 + 2 - V_o = 0$$

$$\boxed{V_o = -2V}$$


$$i_8 = \frac{2-V_o}{8K} = \frac{4}{8K} = 0.5mA$$

$$i_o + i_8 = i_L = \frac{V_o}{4K} = \frac{-2}{4K} = -0.5mA$$

$$i_o = i_L - i_8 = -0.5mA - 0.5mA$$

$$\boxed{i_o = -1mA}$$

5.13 Find  $V_o$  and  $i_o$ .

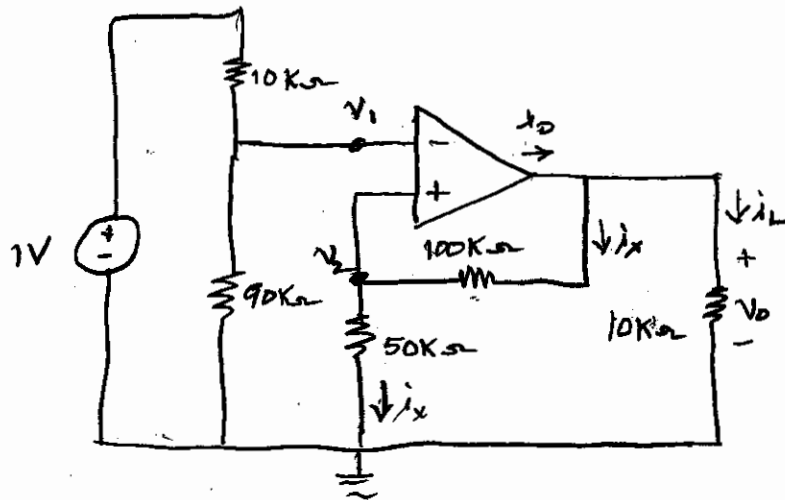

$$V_1 = \frac{1 \times 90}{100} = 0.9 \text{ V}$$

$$V_2 = 0.9 \text{ V}$$

$$i_x = \frac{0.9}{50 \text{ K}}$$

$$V_o = 0.9 + \left( \frac{0.9}{50 \text{ K}} \right) 100 \text{ K} = 2.7 \text{ V}$$

$$\boxed{V_o = 2.7 \text{ V}}$$

$$i_o = i_x + i_L = \frac{0.9}{50 \text{ K}} + \frac{2.7}{10 \text{ K}}$$

$$i_o = 0.018 \text{ mA} + 0.27 \text{ mA}$$


$$\boxed{i_o = 0.288 \text{ mA} = 288 \mu\text{A}}$$



5.15

(a) Determine  $\frac{V_o}{i_s}$  for the op-amp ckt below.

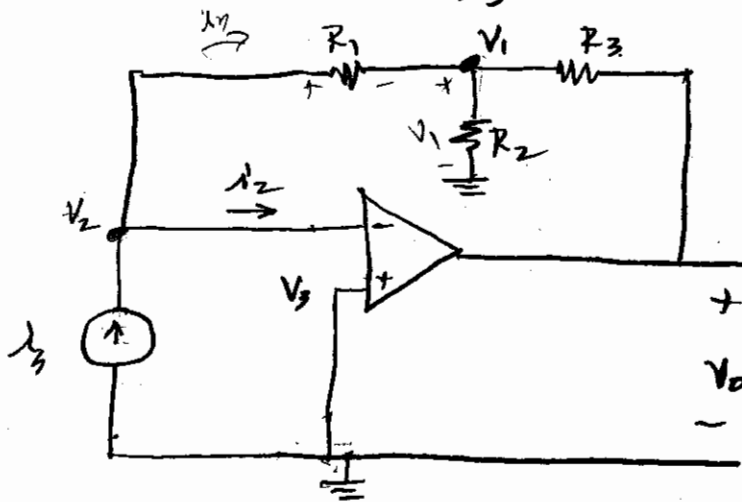(b) With  $R_1 = 20\text{K}\Omega$ ,  $R_2 = 25\text{K}\Omega$ ,  $R_3 = 40\text{K}\Omega$  evaluate  $\frac{V_o}{i_s}$ .



$$V_3 = V_2 = 0, \quad i_2 = 0$$

$$V_1 = -i_s R_1$$

Write a nodal eq at  $V_1$

$$\frac{V_1}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_o}{R_3} = 0$$


$$-\frac{V_o}{R_3} = \frac{i_s R_1}{R_1} + \frac{i_s R_1}{R_2} + \frac{i_s R_1}{R_3}$$

$$\frac{V_o}{i_s} = - \left( R_1 + R_3 + \frac{R_1 R_3}{R_2} \right)$$

with numbers


$$\frac{V_o}{i_s} = - \left( 20\text{K} + 40\text{K} + \frac{800\text{K}}{25\text{K}} \right) = \underline{\underline{-92\text{K}\Omega}}$$

5.19 Determine  $i_o$

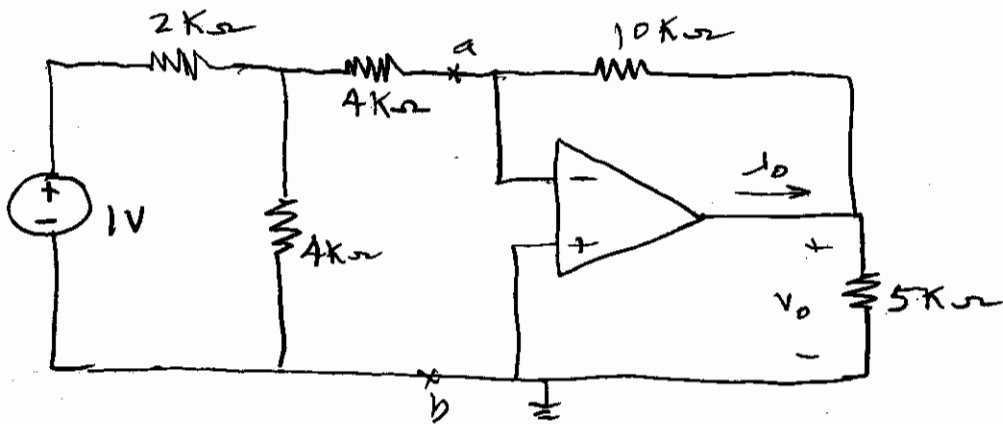

Find the THEVENIN ckt to the Left of a b
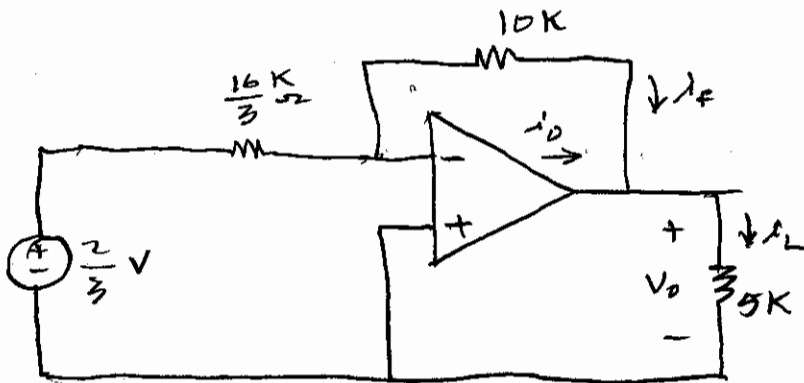
$$V_{TH} = \frac{1 \times 4}{6} = \frac{2}{3} \text{ V}, \quad R_{TH} = \frac{2 \times 4}{6} + 4 = \frac{16}{3} \Omega$$



$$V_o = -\frac{10K}{(16/3)K} \times \frac{2}{3} = \frac{20}{16} = -\frac{5}{4} \text{ V}$$

$$i_L = \frac{-5}{4.5K} = -0.25 \text{ mA}$$


$$i_f = -\frac{V_o}{10K} = +\frac{5}{4 \times 10K} = +\frac{1}{8} \text{ mA} = +0.125 \text{ mA}$$

$$i_o = i_L - i_f = -0.375 \text{ mA}$$

5.27

(a) Determine  $V_o/V_i$

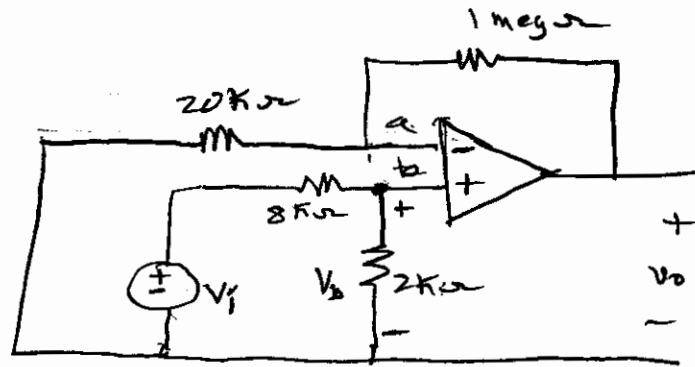(b) What value of  $V_i$  will give  $V_o = 15 \cos 120\pi t$ ?



At b:

$$V_b = \frac{V_i \cdot 2k}{10k} = 0.2V_i$$

Voltage at a is also  $0.4V_i$

Writing a nodal equation at a.

$$\frac{0 - 0.2V_i}{20k} = \frac{0.2V_i - V_o}{1 \text{ meg}}$$

$$-10V_i = 0.2V_i - V_o$$


$$\frac{V_o}{V_i} = 10.2$$

$$V_i = \frac{15 \cos 120\pi t}{10.2}$$


$$V_i = 1.47 \cos 120\pi t$$

5.31

FIND  $i_x$

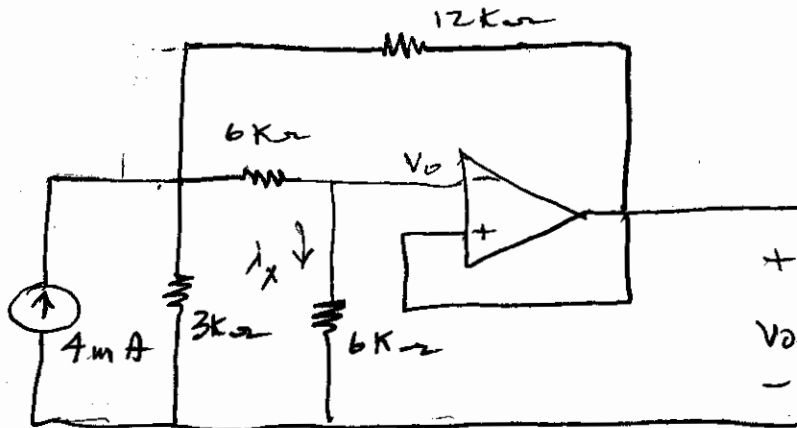

Use source transformation

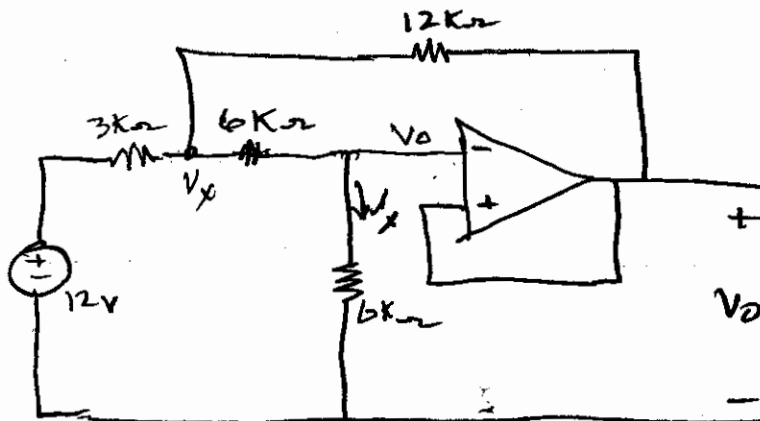

$$\frac{V_x - 12}{3K} + \frac{V_x - V_o}{6K} + \frac{V_x - V_o}{12K} = 0$$

$$4V_x - 48 + 2V_x - 2V_o + V_x - V_o = 0$$

$$7V_x - 3V_o = 48$$

$$\frac{V_o - V_x}{6K} + \frac{V_o}{6K} = 0$$

$$-V_x + 2V_o = 0$$

$$V_o = 4.364 V$$

$$i_x = \frac{V_o}{6K} = 0.7273 \text{ mA}$$