

Desk Copy

ECE 300  
Spring Semester, 2005  
HW Set #8

Due: March 29, 2005

wlg

AM

PM

Name Green  
Print(last, first)

Use Engineering Paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers. Each problem counts 5 points.**

8.6 (a)  $v_R(0^+) = 0 \text{ V}$ ,  $v_L(0^+) = 0 \text{ V}$

(b)  $\frac{dv_R(0^+)}{dt} = 0 \text{ V/s}$      $\frac{dv_L(0^+)}{dt} = \frac{V_s}{(CR_s)} \text{ V/s}$

(c)  $v_L(\infty) = 0 \text{ V}$ ,     $v_R(\infty) = \frac{v_s R}{(R+R_s)} \text{ V}$

8.8  $i(t) = 4te^{-3t} \text{ A}$

8.13  $R = 120 \text{ ohms}$

8.17  $v(t) = [64.53e^{-2.68t} - 4.641e^{-37.32t}] \text{ V}$

8.19  $v(t) = 24\sin(0.5t) \text{ V}$

8.23  $C = 40 \text{ mF}$

8.25  $v_0(t) = e^{-0.25t}[24\cos(1.984t) + 3.024\sin(1.984t)] \text{ V}$

8.26  $i(t) = [2 + 2e^{-t}\sin(2t) + ] \text{ A}$

8.41  $i(t) = e^{-2t}[0.7275\sin(4.583t)] \text{ A}$

8.49  $i(t) = \{ 3 + [e^{-2t}(3 + 6t)] \} \text{ A}$


The following is a good web site to see how other students (at Univ. of North Florida in Jacksonville, FL) have been working with the MSF430 project. See Summer 2003 in particular.

<http://www.unf.edu/~gmerckel/>

Check the following site for free samples of MSP430F449 chip (up to 3). Please order 3 to replace the ones in the kit. Thanks.

<http://focus.ti.com/docs/prod/productfolder.jhtml?genericPartNumber=MSP430F449&pfsection=samples>

(8.6)

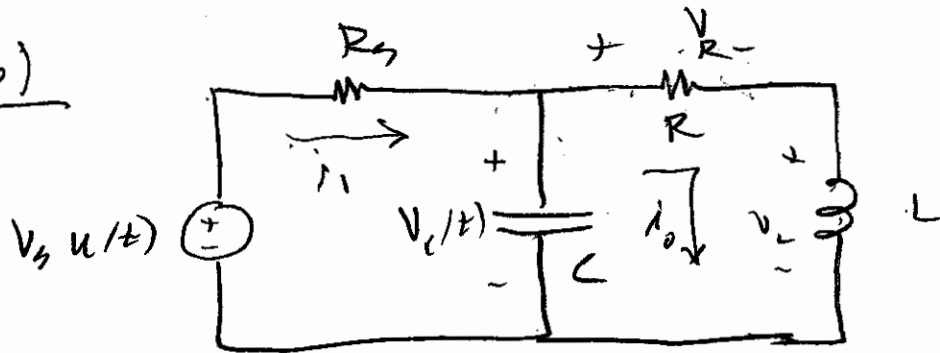

$$(a) \quad V_R(0^+); \quad V_R(0^-) = 0 \therefore V_R(0^+) = 0$$

$$i_0(0^-) = 0 \text{ and } i_0(0^+) = 0$$

$$V_L(0^+): \quad V_L(t) = L \frac{di}{dt}$$

$$V_L(0^-) = 0$$

$V_C(0) = 0$ ; Voltage across the capacitor cannot change instantly;

$$V_C(0^+) - V_R(0^+) - V_L(0^+) = 0$$

$$V_L(0^+) = V_C(0^+) - V_R(0^+) = 0 - 0 = 0$$

$$(b) \quad \frac{dV_R(0^+)}{dt}; \quad \frac{dV_L(0^+)}{dt}$$

$$\text{Now } V_L(0^+) = L \frac{di_0(0^+)}{dt} \quad \text{but } V_L(0^+) = 0$$

$$\therefore \frac{di_0}{dt} = 0 \quad \text{Note } \frac{dV_R}{dt} = R \frac{di_0}{dt}$$

$$\therefore \frac{dV_R(0^+)}{dt} = 0$$

$$(c) \quad V_C - V_R - V_L = 0 \quad \text{OR}$$

$$\frac{dV_C}{dt} - \frac{dV_R}{dt} - \frac{dV_L}{dt} = 0$$

(8.6)

2

but we know

$$\frac{dV_R(t^+)}{dt} = 0$$

We need  $\frac{dV_C(t^+)}{dt}$ ,

$$\text{Now } i(t^+) = \frac{V_s}{R_s} = C \frac{dV_C(t^+)}{dt}$$

so

$$\frac{dV_C(t^+)}{dt} = \frac{V_s}{R_s C}$$

$$\frac{dV_L(t^+)}{dt} = \frac{dV_C(t^+)}{dt} = \frac{V_s}{R_s C}$$

$$(c) V_R(\infty) = \frac{V_s \times R}{R + R_s}$$

$$V_L(\infty) = L \frac{di(\infty)}{dt} = 0$$

8.8 Given

$$\frac{d^2 i}{dt^2} + 6 \frac{di}{dt} + 9i = 0$$

$$i(0) = 0, \quad \left. \frac{di}{dt} \right|_{t=0} = 4$$

Obtain the char. Eq. & solve for  $i(t)$ :

char. Eq. is

$$s^2 + 6s + 9 = 0$$

Roots:

$$(s+3)(s+3) = 0 \quad \text{repeated roots}$$

$$i(t) = (A_1 + A_2 t) e^{-3t}$$


$$i(0) = \boxed{0 = A_1}$$

$$\left. \frac{di}{dt} \right|_{t=0} = -3A_2 t e^{-3t} + A_2 e^{-3t} \Big|_{t=0}$$

$$4 = A_2$$

$$i(t) = 4t e^{-3t} \quad A$$

8.13

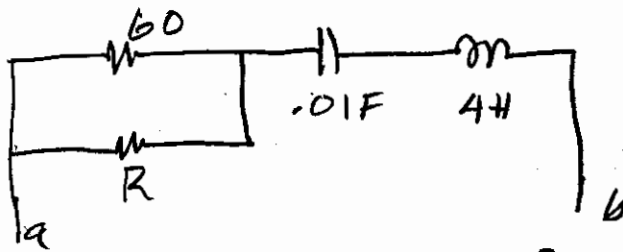

$$R_g = \frac{60R}{60+R}$$

Find  $R$  so that the char Eq has critically damped roots

It is sufficient to write KVL

$$L \frac{di}{dt} + R_g i + v_c = 0$$

$$i = C \frac{dv_c}{dt} = .01 \frac{dv_c}{dt}$$

$$4 \times .01 \times \frac{d^2 v_c}{dt^2} + \frac{.16R}{60+R} \frac{dv_c}{dt} + v_c = v_{in}$$

$$\frac{d^2 v_c}{dt^2} + \frac{.15R}{R+60} \frac{dv_c}{dt} + 25 v_c = 0$$

$$(s+5)(s+5) = 0 \quad \text{critically damped}$$


$$\frac{.15R}{R+60} = 10$$

$$.15R = 10R + 600$$

$$.15R = 600$$

$$R = 120 \Omega$$

8.17

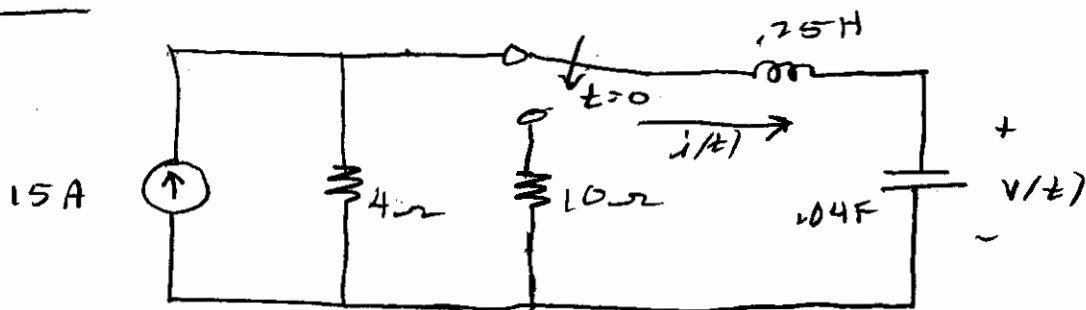

Find  $v(t)$ ,  $t \geq 0$

$t < 0$

$$i(0^-) = 0$$


$$v(0^-) = 15 \times 4 = 60V$$

We know

$$v(0^+) = v(0^-) = 60V$$

$$i(0^+) = i(0^-) = 0$$

$t > 0$

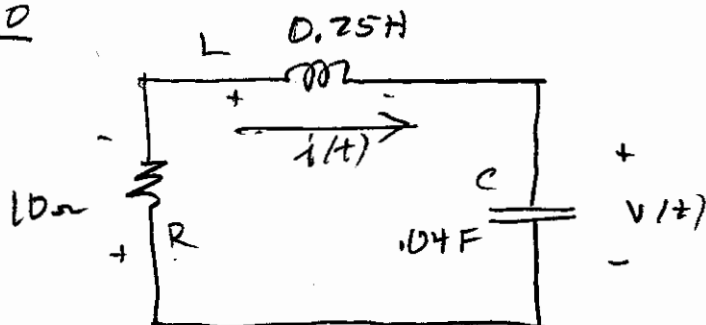

$$Ri + L \frac{di}{dt} + v = 0 \quad (1)$$

$$\text{Use } i = C \frac{dv}{dt} \quad (1a)$$

$$RC \frac{dv}{dt} + LC \frac{d^2v}{dt^2} + v = 0 \quad (2)$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = 0 \quad (3)$$

8.17

2

$$\frac{d^2v}{dt^2} + \frac{10}{.125} \frac{dv}{dt} + \frac{v}{.125 \times .04} = 0 \quad (4)$$

$$\frac{d^2v}{dt^2} + 40 \frac{dv}{dt} + 100v = 0 \quad (5)$$

Char. Eq.

$$s^2 + 40s + 100 = 0$$

$$(s + 2.68)(s + 37.3) \quad (6)$$

Now

$$v(\infty) = v_{ss} = 0 \quad \text{by}$$

inspection of the circuit and of

$$\frac{d^2v}{dt^2} + 40 \frac{dv}{dt} + 100v = 0 \quad (6')$$

The solution to the above is

$$v(t) = A_1 e^{-2.68t} + A_2 e^{-37.3t}$$

solve for  $A_1$  &  $A_2$  using  $v(0^+)$  $\frac{dv(0^+)}{dt}$ . From (1a)

$$C \frac{dv}{dt} = i \quad \text{but } i(0^+) = 0$$

$$\text{so } \boxed{\frac{dv(0^+)}{dt} = 0}$$

$$\boxed{60 = A_1 + A_2}$$

$$\frac{dv}{dt} = -2.68 A_1 e^{-2.68t} - 37.3 A_2 e^{-37.3t}$$

evaluate at  $t = 0^+$

8.17

3

$$\frac{dD/dt}{dt} = 0 = -2.68A_1 - 37.3A_2$$

40 we have

$$A_1 + A_2 = 60$$


$$-2.68A_1 - 37.3A_2 = 0$$

$$A_1 = 64.6, A_2 = -4.64$$

$$v(t) = \left[ 64.6 e^{-2.68t} - 4.64 e^{-37.3t} \right] V$$




8.19

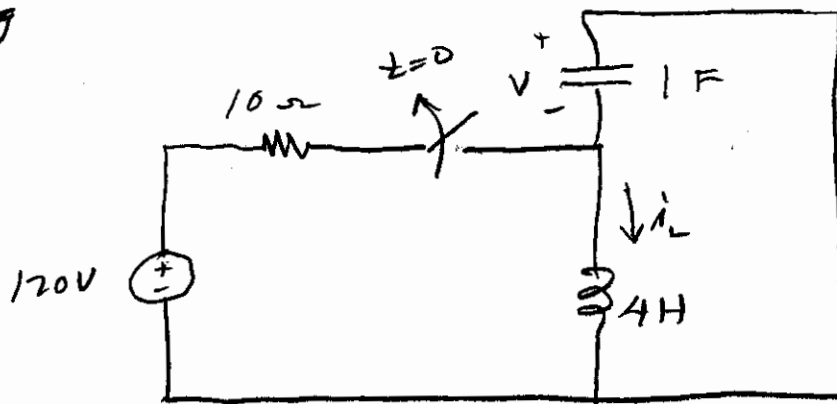

$$i_L(0^-) = i_L(0^+) = \frac{120}{10} = 12 \text{ A}$$

$$V(0^-) = 0$$

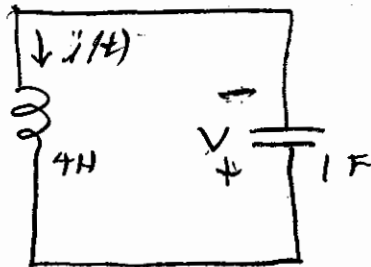 $t \geq 0$ 

$$L \frac{di_L}{dt} + V = 0 \quad \frac{di_L(0)}{dt}$$

$$LC \frac{d^2V}{dt^2} + V = 0$$

$$\frac{d^2V}{dt^2} + \frac{V}{LC} = 0$$

$$i_L(0^+) = 12 = C \frac{dV(0^+)}{dt}$$

$$\frac{dV(0^+)}{dt} = -12$$

$$\frac{d^2V(0^+)}{dt^2} = \frac{-V(0^+)}{LC} = 0$$

8.19

back to

$$\frac{d^2V}{dt^2} + \frac{V}{LC} = 0$$

Char. Eq

$$s^2 + \frac{1}{LC} = 0$$

$$s^2 + 0.25 = 0$$

$$(s + j0.5)(s - j0.5) = 0$$

$$v(t) = A_1 e^{j0.5t} + A_2 e^{-j0.5t}$$

$$\frac{dv}{dt} = j0.5A_1 e^{j0.5t} - j0.5A_2 e^{-j0.5t}$$

$$-12 = j0.5A_1 - j0.5A_2$$

$$\frac{d^2v}{dt^2} = -0.25A_1 e^{j0.5t} - 0.25A_2 e^{-j0.5t}$$


$$0 = A_1 + A_2$$

$$A_1 = -j12, \quad A_2 = +j12$$

$$v(t) = -j12 [e^{j0.5t} - e^{-j0.5t}]$$

$$v(t) = +24.5 \sin 0.5t \quad v$$

8.23

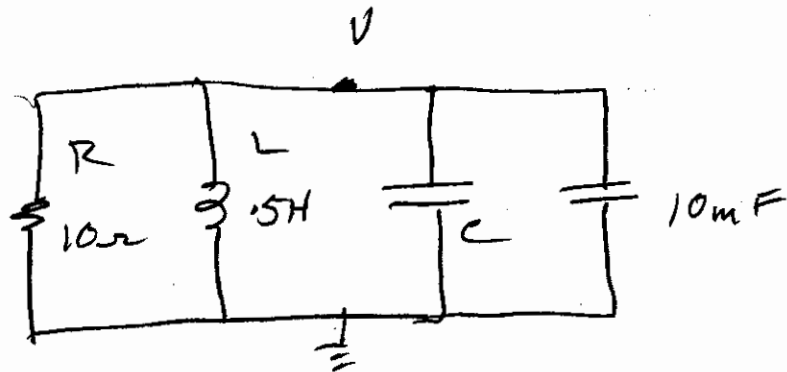

Assume unforced; want only C.E.

$$\frac{V}{R} + C \frac{dV}{dt} + \frac{1}{L} \int V dt + i(0) = 0$$

$$C \frac{d^2 V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{V}{L} = 0$$

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = 0$$

Underdamped;  $\alpha = 1$

$$s^2 + 2\alpha + \omega_0^2$$

$$\frac{j}{RC} = -2$$

$$C = \frac{1}{2R} = \frac{1}{20} = .05$$


$$10\text{mF} + C = .05$$

$$C = .05 - .01 = .04$$


$$C = 40\text{mF}$$

8.25

GIVEN

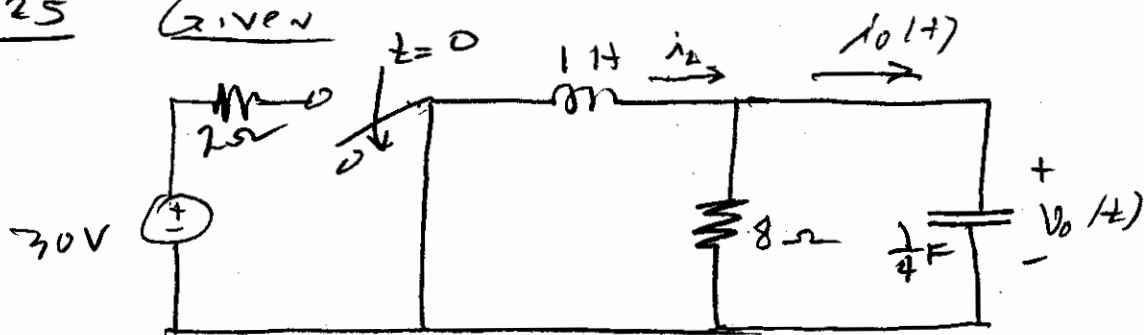

FIND  $i_L(t)$ ,  $V_o(t)$   $t \geq 0$

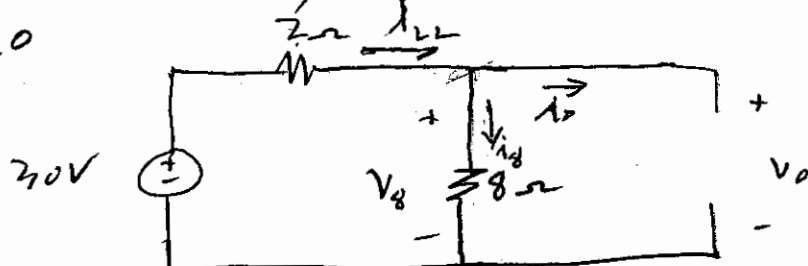


$$V_8(0^-) = 24V, \quad i_8(0^-) = 3A,$$

$$i_L(0^-) = i_L(0^+) = 3$$

$$V_o(0^-) = V_o(0^+) = 24$$

$t \geq 0$

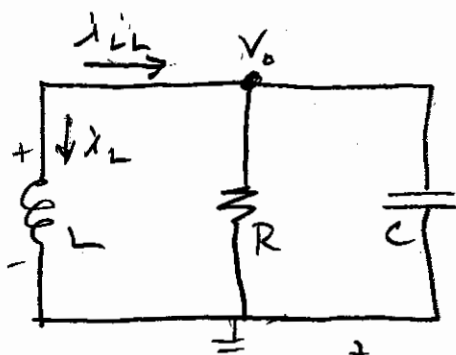

$$i_L = -\dot{V}_o$$

$$i_L(0^+) = -3$$

$$C \frac{dV_o}{dt} + \frac{V_o}{R} + \frac{1}{L} \int_0^t V_o dt + i_L(0^+) = 0$$

$$C \frac{d^2 V_o}{dt^2} + \frac{1}{R} \frac{dV_o}{dt} + \frac{V_o}{L} = 0$$

$$\frac{d^2 V_o}{dt^2} + \frac{1}{RC} \frac{dV_o}{dt} + \frac{V_o}{LC} = 0$$

8,25

2

$$\frac{d^2 v_o}{dt^2} + \frac{4}{8} \frac{dv_o}{dt} + \frac{v_o}{1} = 0$$

Char. Eq.

$$s^2 + 0.5s + 4 = 0 \quad (1)$$

$$(s + .25 + j1.9843)(s + .25 - j1.9843) = 0$$

Compare (1) to

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$2\alpha = 0.5$$

$$\alpha = 0.25$$

$$\text{by inspection } \omega_d = 1.98$$

$$\sqrt{\omega_0^2 - \alpha^2} = 1.98$$

$$v_o(t) = e^{-.25t} [A_1 \cos 1.98t + A_2 \sin 1.98t]$$

Know

$$v_o(0^+) = 24$$

To get  $\frac{dv_o(0^+)}{dt}$ 

$$C \frac{dv_o(0^+)}{dt} + \frac{v_o}{R} + \frac{1}{L} \int_0^{0^+} (v_o dt + i_L(0^+)) = 0$$

$$\frac{1}{4} \frac{dv_o(0^+)}{dt} = -\frac{v_o}{R} - i_L(0^+)$$

$$\frac{1}{4} \frac{dv_o(0^+)}{dt} = \left[ -\frac{24}{8} - (-3) \right] = -3 + 3 = 0$$

$$\frac{dv_o(0^+)}{dt} = 0$$

8.25

3

$$V_0(0^+) = 24, \quad \frac{dV_0(0^+)}{dt} = 0$$

$$24 = A_1$$

$$\frac{dV_0}{dt} = -.25e^{-.25t} [24\cos(1.98t) + A_2\sin(1.98t)] \\ + e^{-.25t} [-47.52\sin(1.98t) + 1.98A_2\cos(1.98t)]$$

Evaluate at  $0^+$ 

$$0 = -.25 [24] + 1.98A_2$$

$$A_2 = \frac{+6}{1.98} = 3.03$$

$$V_0(t) = e^{-.25t} [24\cos(1.98t) + 3.03\sin(1.98t)]$$

Then

$$i_0(t) = C \frac{dV_0}{dt}$$

8.26 Step response of RLC circuit  
given by

$$\frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + 5i = 10$$

Given  $i(0) = 2$ ,  $\frac{di(0)}{dt} = 4$  find  $i(t)$

Characteristic Eq. is;

$$s^2 + 2s + 5 = 0$$

$$(s+1+j2)(s+1-j2) = 0$$

Form of the solution will be  
(first note  $i_{ss} = 2$ )

$$i(t) = 2 + e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$$

where

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

comparing with

$$s^2 + 2s + 5$$

$$2\alpha = 2; \alpha = 1; \omega_0^2 = 5$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{5 - 1} = 2$$

$$i(t) = 2 + e^{-t} [A_1 \cos 2t + A_2 \sin 2t]$$

$$i(0) = 2 = 2 + A_1 \quad A_1 = 0$$

$$i(t) = 2 + e^{-t} A_2 \sin 2t$$

$(-1 \pm j2) / (s+1 \pm j2)$

8.26


$$\left. \frac{di}{dt} \right|_{t=0} = e^{-t} A_2 [2 \cos 2t - A_2 e^{-t} \sin 2t] \Big|_{t=0}$$

$$4 = A_2 \times 2 \quad A_2 = 2$$

$$i(t) = 2 + 2 e^{-t} \sin 2t$$




8.41

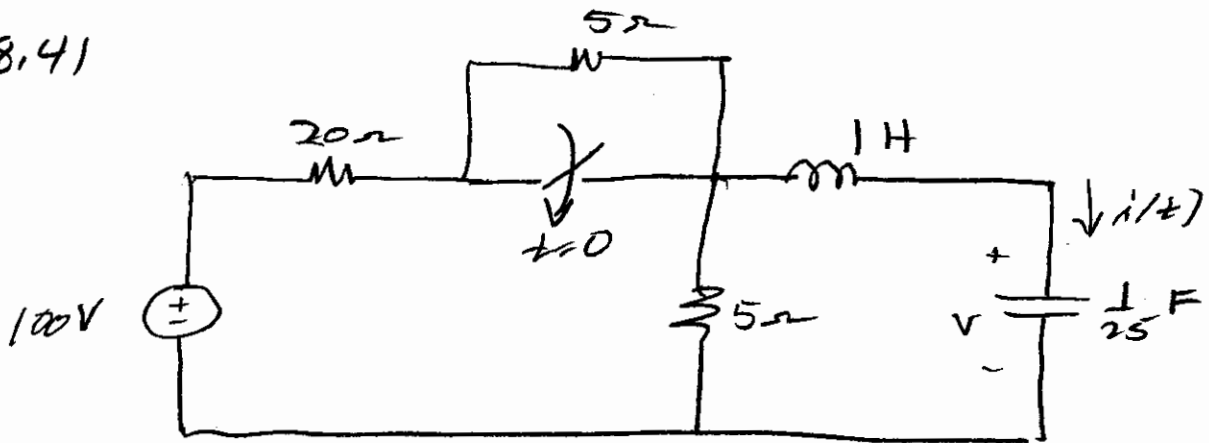

$$i(0^-) = i(0^+) = 0$$

$$v(0^-) = v(0^+) = \frac{100 \times 5}{30} = \frac{50}{3}$$


$t \geq 0$

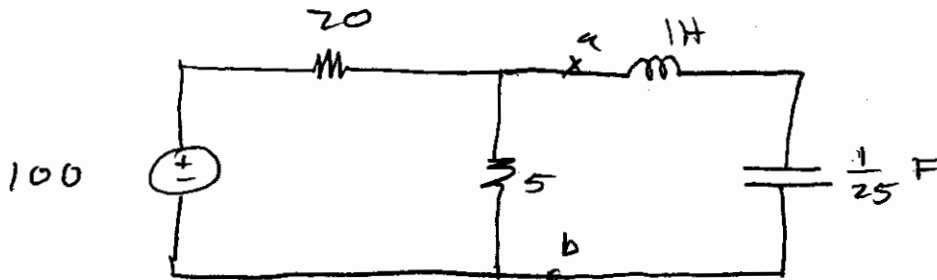

Thevenin to the left of a-b

$$V_{TH} = \frac{5 \times 100}{25} = 20V$$
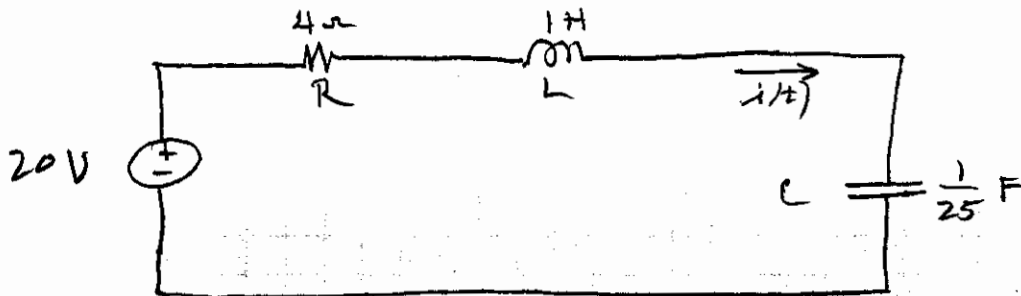
$$R_{TH} = \frac{5 \times 20}{25} = 4\Omega$$



$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i dt + v_c(0) = 20 \quad (1)$$

8.4)

$$i(0^+) = 0$$

$$L \frac{di(0^+)}{dt} = 20 - V_c(0) - Ri(0^+)$$

$$\frac{di(0^+)}{dt} = \frac{20 - \frac{50}{3}}{1H} = \frac{10}{3}$$

Differentialgleichung Eq # 1

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$\frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 25 i = 0$$

$$s^2 + 4s + 25 = 0$$

$$s^2 + 2 \times 2s + 16 = 0$$

$$(s + 2 + j4.58)(s + 2 - j4.58) = 0$$

$$i(t) = i(0) + e^{-2t} [A_1 \cos 4.58t + A_2 \sin 4.58t]$$

$$i(0) = 0$$

$$i(t) = e^{-2t} [A_1 \cos 4.58t + A_2 \sin 4.58t]$$


$$0 = A_1$$

$$\frac{di}{dt} = -2e^{-2t} [A_2 \sin 4.58t] + e^{-2t} [4.58 A_2 \cos 4.58t]$$


$$\frac{10}{3} = 4.58 A_2 \quad A_2 = 0.73$$

$$i(t) = 0.73 e^{-2t} \sin 4.58t \quad A$$

8.49

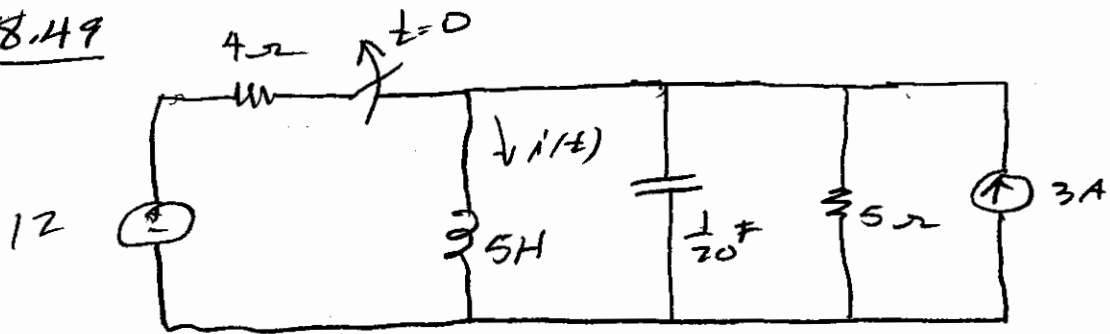


$t < 0$

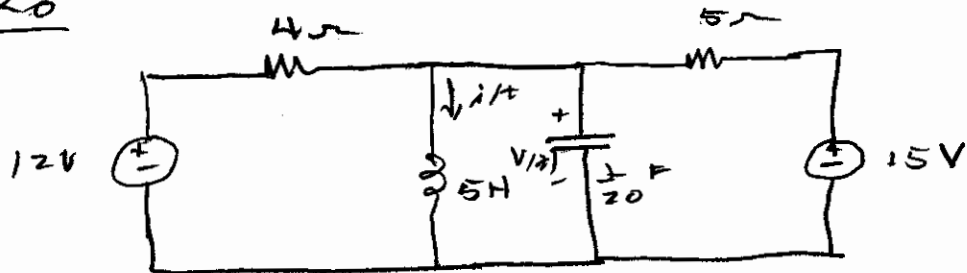

$$i(0^-) = \frac{12}{4} + \frac{15}{5} = 6A = i'(0^+)$$

$$v(0^-) = 0 = v(0^+)$$

$t > 0$

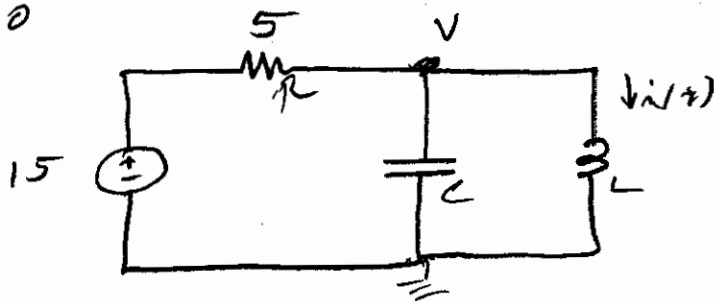

$$\frac{V-15}{R} + C \frac{dV}{dt} + i(t) = 0$$

$$V = L \frac{di'}{dt}$$

$$\frac{V}{R} + C \frac{dV}{dt} + i = \frac{15}{R}$$

$$\frac{L}{R} \frac{di'}{dt} + LC \frac{d^2 i'}{dt^2} + i' = \frac{15}{R}$$

$$\frac{d^2 i'}{dt^2} + \frac{1}{RC} \frac{di'}{dt} + \frac{i'}{LC} = \frac{15}{RLC}$$

8.49

2

$$\frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 4i = 12$$

$$s^2 + 4s + 4 = 0$$

compare

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\alpha = 2, \quad \omega_0 = 2$$

critically damped

$$i(t) = i(\infty) + (A_1 + A_2 t) e^{-2t}$$

$$i(\infty) = 3$$

$$i(t) = 3 + (A_1 + A_2 t) e^{-2t}$$

$$i(0^+) = 6$$

$$6 = 3 + A_1, \quad A_1 = 3$$

$$V_L = L \frac{di}{dt}$$

$$V_L(0^+) = 0$$

$$L \frac{di}{dt}(0^+) = 0$$

$$\frac{di}{dt} = -2(3 + A_2 t) e^{-2t} + e^{-2t} (A_2) =$$

$$0 = -6 + A_2, \quad A_2 = 6$$

$$i(t) = \left\{ 3 + e^{-2t} [3 + 6t] \right\} A$$