

Desk copy

ECE 300
Spring Semester, 2005
HW Set #9

Due: April 4, 2005
wlg

AM

PM

Name

Green
Print(last, first)

Revised: version 2

Use Engineering Paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 5 points.

9.23 (a) $v(t) = 40\cos(\omega t - 60^\circ)$ V, (b) $v(t) = 38.4\cos(\omega t + 96.8^\circ)$ V;
(c) $i(t) = 6\cos(\omega t + 80^\circ)$ A, (d) $i(t) = 11.5\cos(\omega t - 52.1^\circ)$ A

9.36 $i(t) = 26.6\cos(200t - 3.9^\circ)$ mA

9.42 $v_o(t) = 17.14\cos(200t)$ V

10.13 $V_X = 29.4\angle 62.9^\circ$ V

10.15 $I = 7.91\angle 43.5^\circ$ A ----- I got $I = 1.374\angle 104.04^\circ$ A

10.25 $i_o = 1.414\cos(2t + 45^\circ)$ A

10.29 $I_1 = 4.67\angle -20.17^\circ$ A, $I_2 = 1.79\angle 37.35^\circ$ A

10.57 $Z_N = Z_{th} = 21.6\angle -33.7^\circ \Omega$, $V_{th} = 107.3\angle 146.6^\circ$ V, $I_N = 4.96\angle -179.7^\circ$ A

10.62 $Z_{th} = 2.29\angle -103.24^\circ \Omega$, $V_{th} = 3.073\angle 140.18^\circ$ V, $V_o = 2.3\angle -163.3^\circ$ V

10.68 $v_{th} = 11.52\sin(10t - 50.2^\circ)$ V, $Z_{th} = 1.92\angle -50.19^\circ \Omega$

9.23

Give a single sinusoid for each of the following.

$$(a) \hat{V} = 40 \angle -60^\circ \text{ V}$$

$$v(t) = 40 \cos(\omega t - 60^\circ) \text{ V}$$

$$(b) \hat{V} = -30 \angle 110^\circ + 50 \angle 60^\circ \text{ V}$$

$$\hat{V} = (-45.44 + j 0.918) = 38.76 \angle 96.8^\circ \text{ V}$$

$$v(t) = 38.4 \cos(\omega t + 96.8^\circ) \text{ V}$$

$$(c) \hat{I} = j 6 e^{-j 10^\circ} \text{ A} = 6 e^{-j 10^\circ} \cdot e^{j 90^\circ}$$

$$\hat{I} = 6 e^{j 80^\circ} \text{ A}$$

$$i(t) = 6 \cos(\omega t + 80^\circ) \text{ A}$$

$$(d) \hat{I} = \frac{2}{j} + 10 \angle -45^\circ$$

$$\hat{I} = -j 2 + 10 \angle -45^\circ = 2 \angle -90^\circ + 10 \angle -45^\circ$$


$$\hat{I} = 7.07 - j 9.071 = 11.5 \angle -52.1^\circ$$

$$i(t) = 11.5 \cos(\omega t - 52.1^\circ) \text{ A}$$

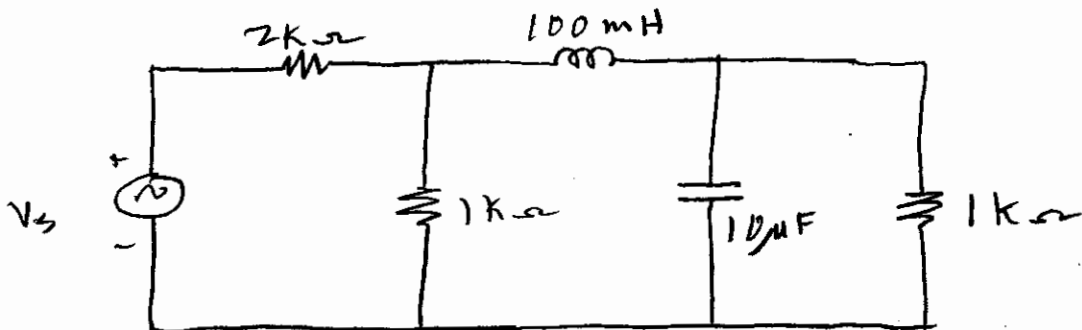9.36

In the circuit below, determine i .


Let $v_s = 60 \cos(200t - 10^\circ) \text{ V}$



Prepare the phasor circuit

$$100 \text{ mH} \rightarrow j\omega L \rightarrow j200 \times 0.1 \rightarrow j20 \Omega$$
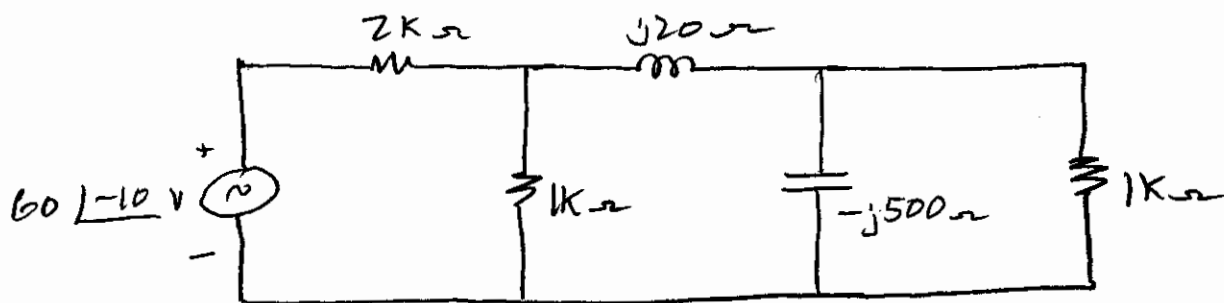
$$10 \mu\text{F} \rightarrow \frac{-j}{200 \times 10 \times 10^{-6}} \rightarrow \frac{-j}{2 \times 10^{-3}} \rightarrow -j500 \Omega$$



$$1000 \parallel (-j500) = \frac{1000(-j500)}{1000 - j500} = 200 - j400$$

Add the $j20$ to $200 - j400 = 200 - j380$

$$1000 \parallel (200 - j380) = \frac{1000(200 - j380)}{1000 + 200 - j380} = 242.6 - j239.8$$

$$Z_{in} = 2000 + 242 - j239.8 = 2242 - j239.8$$


$$\underline{I} = \frac{60 \angle -10}{(2242 - j239.8)} = 0.0266 \angle -3.895 \text{ A}$$

$$i(t) = 26.61 \cos(200t - 3.89^\circ) \text{ A}$$

Answer
book
error

9.42

Calculate $V_0(t)$ in the following ckt.

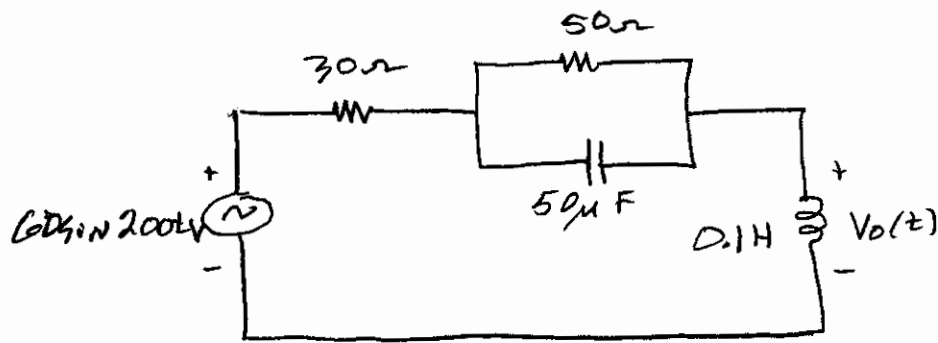


change to phasor circuit

$$0.1 \text{ H} \rightarrow j200 \times 0.1 = j20 \Omega$$

$$50 \mu\text{F} \rightarrow \frac{-j}{200 \times 50 \times 10^{-6}} \rightarrow \frac{-j}{10 \times 10^{-3}} \rightarrow -j100 \Omega$$
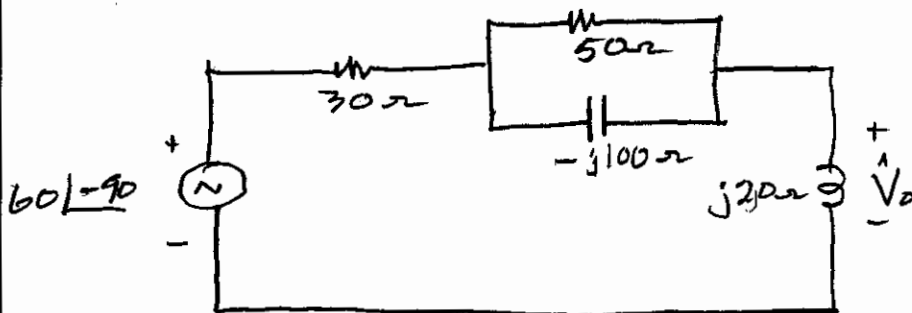
$$60 \sin 200t \rightarrow 60 \cos(200t - 90)$$



$$50 \parallel (-j100) = \frac{50(-j100)}{50 - j100} = 40 - j20$$

Using voltage division;


$$\hat{V}_0 = \frac{(60 \angle -90)(20 \angle 90)}{30 + 40 - j20 + j20} = \frac{1200 \angle 0}{70}$$

$$\hat{V}_0 = 17.14 \angle 0$$


$$V_0(t) = 17.14 \cos(200t) \text{ V}$$

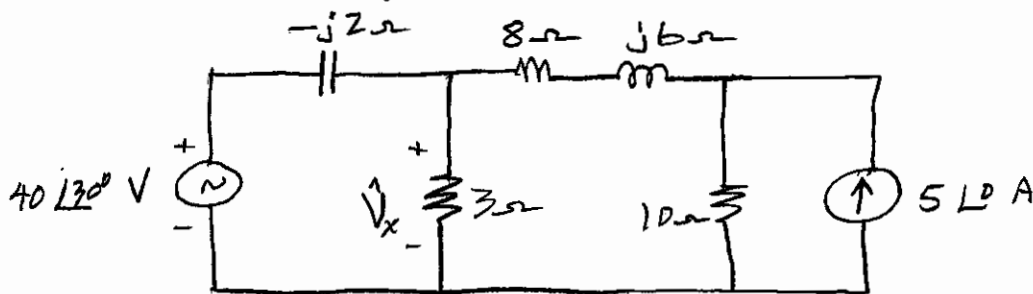10.13

Determine \hat{V}_x in the following circuit using any method of your choice.



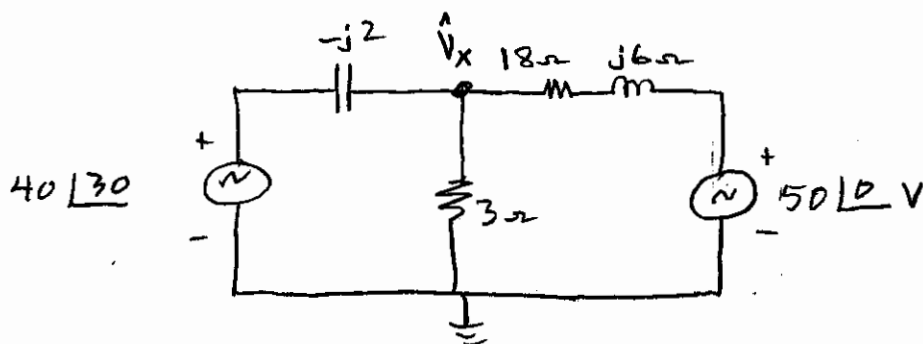Use source transformation on the right side



$$\frac{\hat{V}_x - 40\angle 30^\circ}{2\angle -90^\circ} + \frac{\hat{V}_x}{3} + \frac{\hat{V}_x - 50}{18 + j6} = 0$$

$$\frac{\hat{V}_x}{2\angle -90^\circ} + \frac{\hat{V}_x}{3} + \frac{\hat{V}_x}{18 + j6} = 20\angle 120^\circ + \frac{50}{18 + j6}$$


$$\hat{V}_x [.5\angle 90^\circ + .333 + .05 - j.0167] = 20\angle 120^\circ + 2.64\angle -18.4^\circ$$

$$\hat{V}_x [.3833 + j0.4833] = 18.11\angle 114.4^\circ$$

$$\hat{V}_x = 29.4\angle 62.9^\circ \text{ V}$$

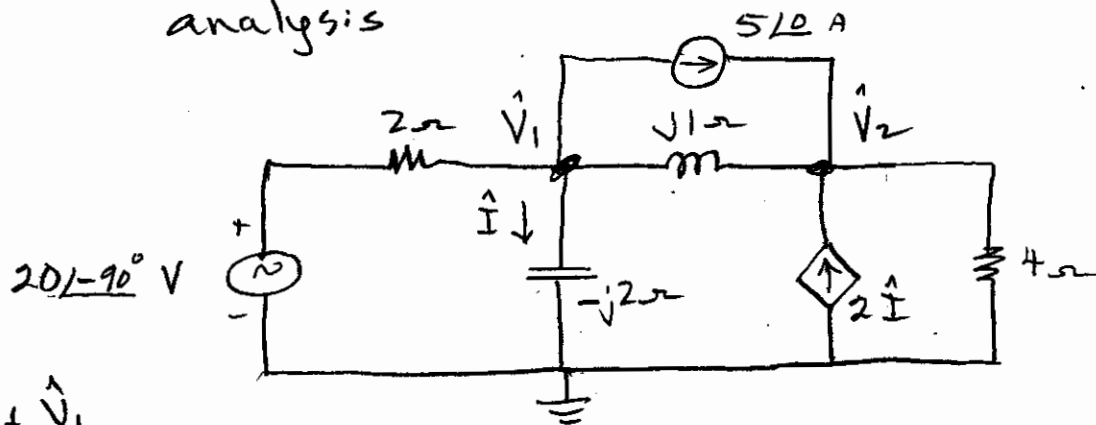10.15

Solve for the current \hat{I} using nodal analysis



At \hat{V}_1

$$\frac{\hat{V}_1 - 20\angle -90}{2} - \frac{\hat{V}_1}{j2} + \frac{\hat{V}_1 - \hat{V}_2}{j1} + 5\angle 0 = 0$$

$$V_1(0.5 + j0.5 - j) + jV_2 = -5 - j10$$

$$\boxed{(0.5 - j0.5)\hat{V}_1 + j\hat{V}_2 = -5 - j} \quad (1)$$

At \hat{V}_2

$$\frac{\hat{V}_2 - \hat{V}_1}{j1} + \frac{\hat{V}_2}{4} - 2\hat{I} = 5$$

$$\hat{I} = \frac{\hat{V}_1}{-j2} = j0.5V_1$$


$$-j\hat{V}_2 + j\hat{V}_1 + 0.25\hat{V}_2 - j\hat{V}_1 = 5$$

$$\boxed{0\hat{V}_1 - j0.75V_2 = 5}$$

$$\hat{V}_1 = 2.749 \angle 114.04^\circ \text{ V}$$

$$\boxed{\hat{I} = \frac{\hat{V}_1}{-j2} = 1.374 \angle 114.04^\circ \text{ A}}$$

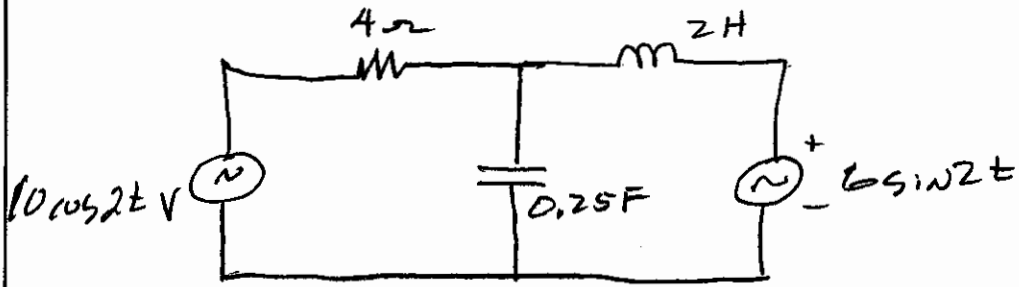
10.25 Solve for i_0 below using mesh analysis



Go to phasor circuit

$$2H \rightarrow j \times 2 \times 2 = j4\Omega$$
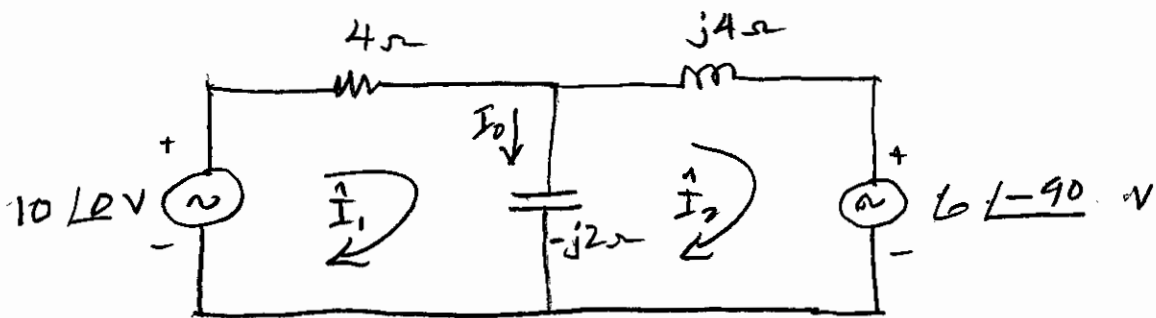
$$.25F \rightarrow \frac{-j}{2 \times .25} = -j2\Omega$$



$$\begin{bmatrix} 4-j2 & j2 \\ j2 & j2 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 6\sqrt{2} \\ -6\sqrt{2} \end{bmatrix}$$


$$\hat{I}_1 = 2 + j0.5, \quad \hat{I}_2 = 1 - j0.5$$

$$\hat{I}_0 = \hat{I}_1 - \hat{I}_2 = 2 + j0.5 - 1 + j0.5$$

$$\hat{I}_0 = 1 + j1 = 1.414 \angle 45^\circ$$

$$i_0(t) = 1.414 \cos(2t + 45^\circ)$$

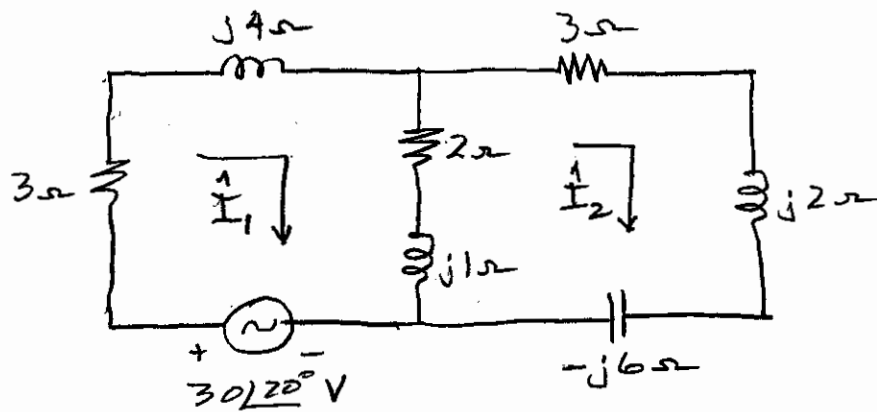10.29 Use mesh analysis to find \hat{I}_1 and \hat{I}_2 in the following circuit.



By inspection


$$\begin{bmatrix} 5+j5 & -2-j1 \\ -2-j1 & 5-j3 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 30\angle 20^\circ \\ 0 \end{bmatrix}$$

Hand calculator solution:

$$\hat{I}_1 = 4.67 \angle -20.17^\circ \text{ A} \quad \hat{I}_2 = 1.79 \angle 37.4^\circ \text{ A}$$

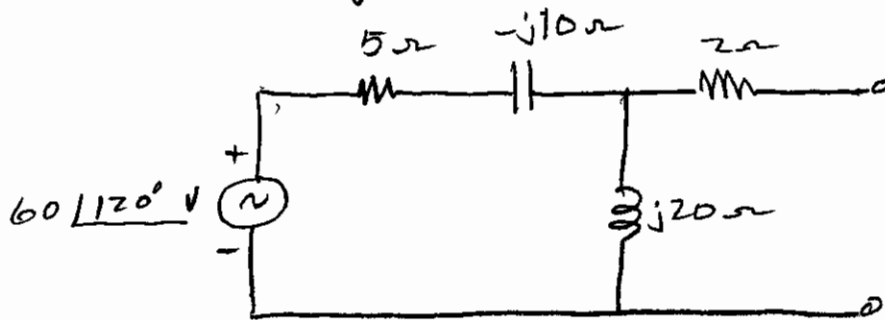10.57

Find the Thevenin equivalent \hat{v}_T , Norton equivalent circuits for the following:



$$Z_{TH} = 2 + \frac{(j20)(5-j10)}{5-j10+j20}$$

$$Z_{TH} = 2 + \frac{(20\angle 90^\circ)(5-j10)}{(5+j10)} = 2 + 16 - j12$$

$$Z_{TH} = 18 - j12 = 21.6 \angle -33.7^\circ \Omega$$


$$\hat{V}_{TH} = \frac{(60\angle 120^\circ)(20\angle 90^\circ)}{5+j10}$$

$$\hat{V}_{TH} = 107.33 \angle 146.5^\circ$$

$$\hat{I}_N = \frac{\hat{V}_{TH}}{Z_{TH}} = \frac{107\angle 146.5^\circ}{21.6 \angle -33.7^\circ}$$


$$\hat{I}_N = 4.96 \angle -179.8^\circ \text{ A}$$

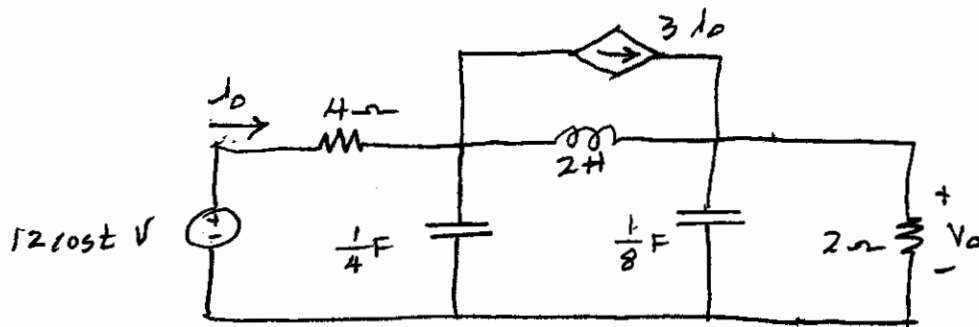10.62 Use Thevenin's theorem to find $V_o(t)$ in the following circuit.




$\omega = 1$; $\frac{1}{4}F \rightarrow -j4\Omega$; $\frac{1}{8}F \rightarrow -j8\Omega$; $2H \rightarrow j2\Omega$

Redraw as phasor circuit

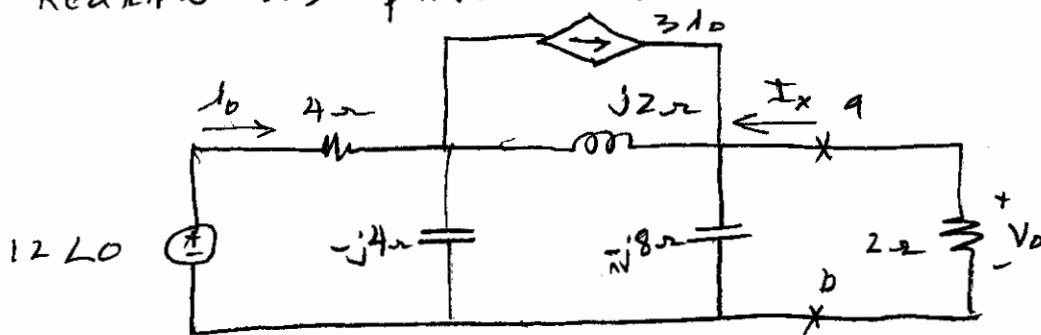

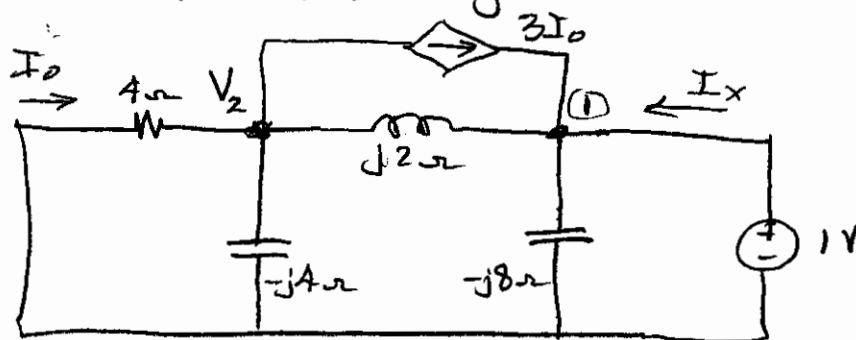Find Z_{TH} looking into ab with 2Ω resistor removed, apply a 1V source and find the resulting current.



$$\frac{V_2}{4} - \frac{V_2}{j4} + \frac{V_2 - 1}{j2} + 3I_o = 0 \quad (1)$$

$$I_o = \frac{-V_2}{4} \quad (2)$$

substitute (2) into (1).

10.62

2

$$\frac{V_2}{4} - \frac{V_2}{j4} + \frac{V_2 - 1}{j2} + \frac{3V_2}{4} = 0$$

multiply through by $j4$

$$jV_2 - V_2 + 2V_2 - 2 + j3V_2 = 0$$

$$(1 - j2)V_2 = 2$$

$$V_2 = 0.4 + j0.8 \text{ V}$$

At ①

$$-\frac{1}{j8} + \frac{1 - V_2}{j2} - 3I_0 = I_x$$

substituting in for V_2 and I_0

$$-\frac{1}{j8} + \frac{0.6 - j0.8}{j2} + \frac{(1.2 + j2.4)}{4} = I_x$$

multiply through by $j8$


$$-1 + 2.4 - j3.2 + j2.4 - 4.8 = j8 I_x$$

$$I_x = \frac{-3.4 - j0.8}{j8} = -0.1 + j0.425 \text{ A}$$

$$\therefore Z_{TH} = \frac{1}{I_x} = 2.29 \angle -103.24^\circ \Omega$$

To find V_{TH} we go back to the 2 circuit with the 2Ω resistor removed and find V_0 as indicated in the following circuit.

10.62

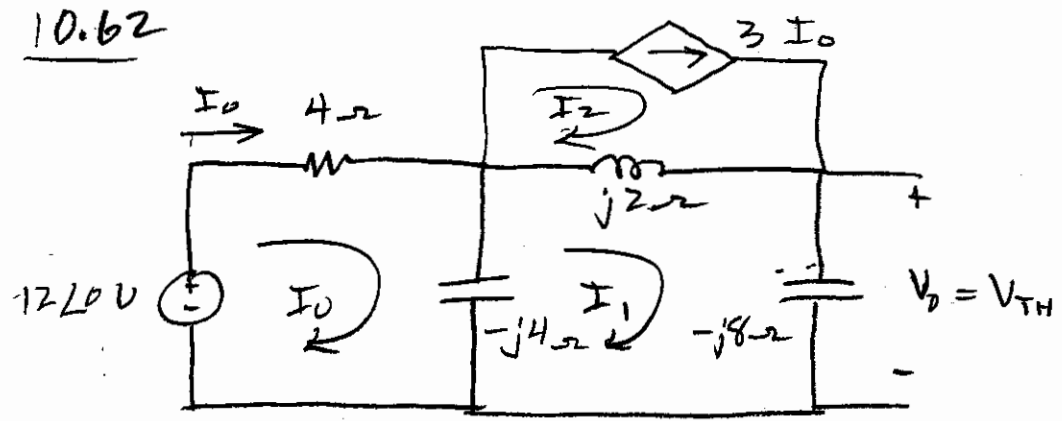

We have;

$$(4 - j4)I_0 + j4I_1 + 0I_2 = 12\angle 0$$

$$4jI_0 - j6I_1 - j2I_2 = 0$$


$$3I_0 + 0I_1 - I_2 = 0$$

$$I_0 = (1.23 + j1.48)A ; I_1 = (-0.246 - j0.295)$$

$$I_2 = (3.69 + j4.43)A$$

$$V_{TH} = (-j8)(I_1)$$

$$V_{TH} = 3.073 \angle 140.18^\circ V$$

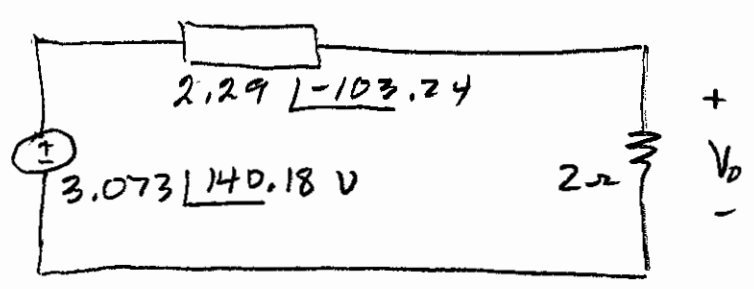


$$V_0 = \frac{(3.073 \angle 140.18) 2}{2 + 2.29 \angle -103.24} = 2.3 \angle -163.3^\circ V$$

10.62

4

By Ritz's mesh analysis

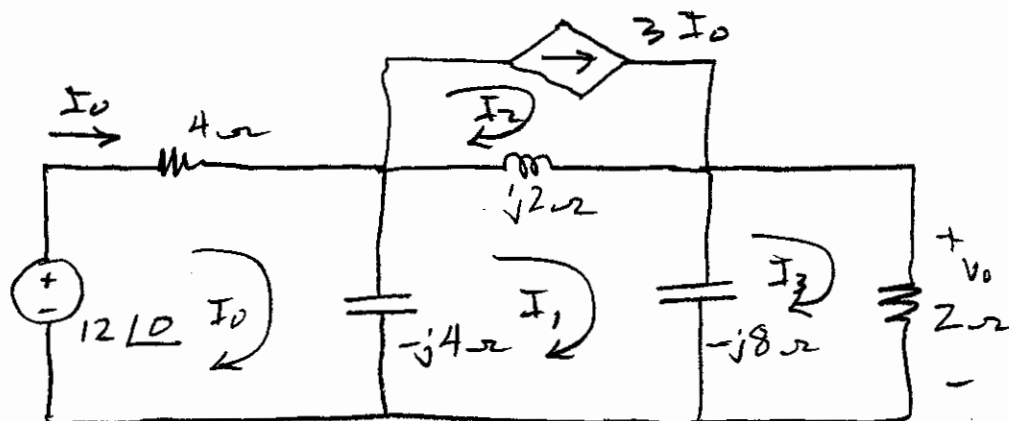

$$(4-j4)I_0 + j4I_1 + 0I_2 + 0I_3 = 12$$

$$j4I_0 - j10I_1 - j2I_2 + j8I_3 = 0$$

$$3I_0 + 0I_1 - I_2 + 0I_3 = 0$$

$$0I_0 + j8I_1 + 0I_2 + (2-j8)I_3 = 0$$

using MATLAB


$$I_3 = (-1.101 - j0.3303) = 1.149 \angle -163.3$$

$$V_0 = 2 \times I_3 = 2.3 \angle -163.3 \text{ A}$$

check

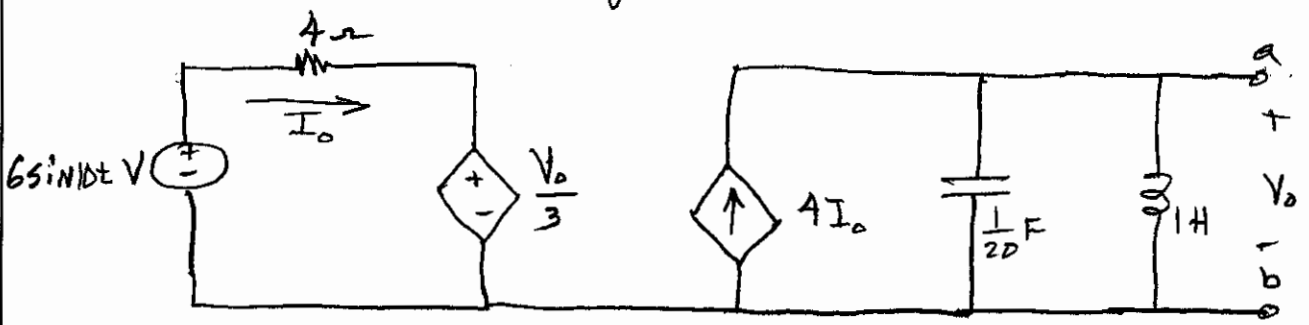
10.68

Find the Thevenin equivalent at terminals a-b



Prepare the phasor circuit:
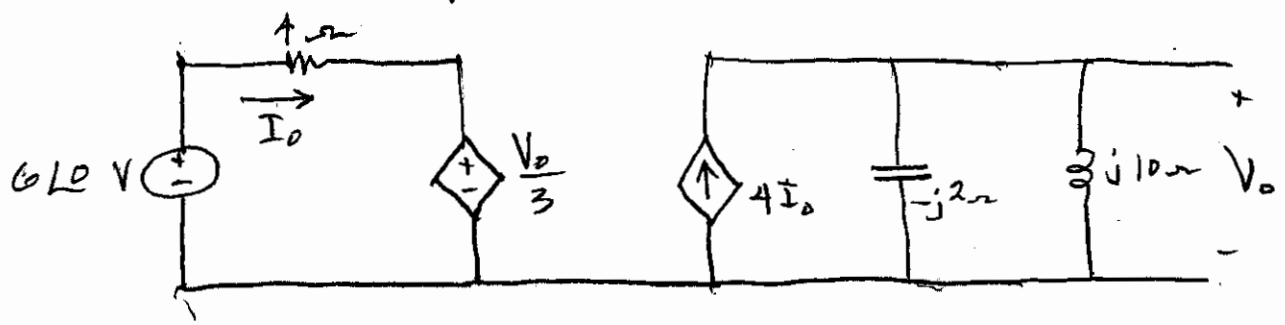
$$\frac{1}{20} F \rightarrow \frac{1}{j\omega C} = \frac{20}{j10} = -j2 \Omega \quad 1 H \rightarrow j\omega L = j10 \Omega$$



$$V_0 = V_{TH} = \left[\frac{(4I_0)(2\angle -90)}{(j10 - j2)} \right] 10\angle 90$$


$$V_0 = -j10I_0 \quad \text{but } 4I_0 = 6 - \frac{V_0}{3}$$

$$4I_0 = 6 + j\frac{10}{3}I_0$$

$$I_0 = \frac{6}{4 - j\frac{10}{3}} = 0.89 + j.74 = 1.15 \angle 39.8^\circ A$$

$$V_0 = -j10I_0 = 11.5 \angle -50.2 = V_{TH}$$

10.68

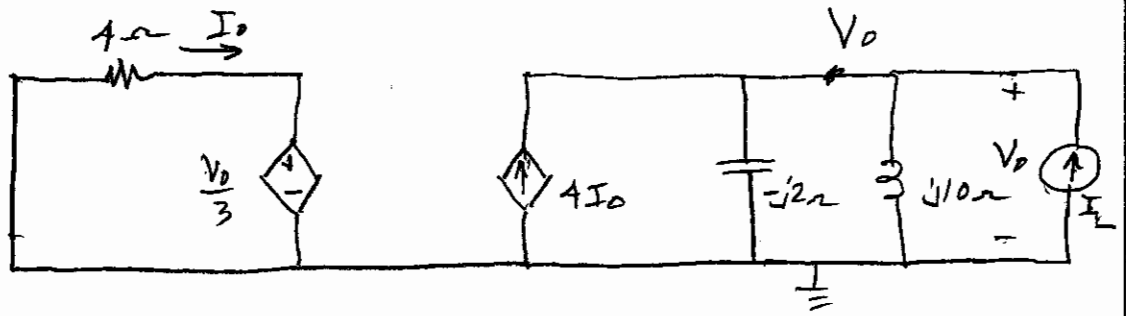

$$\frac{V_0}{j10} - \frac{V_0}{j2} = 4I_0 = I_L$$

$$I_0 = -\frac{V_0}{12}$$

$$\frac{V_0}{j10} - \frac{V_0}{j2} + \frac{V_0}{3} = I_L$$

mult by $j30$

$$3V_0 - 15V_0 + j10V_0 = j30I_L$$

$$[-12 + j10]V_0 = j30I_L$$

$$Z_{TH} = \frac{V_0}{I_L} = \frac{j30}{(-12 + j10)}$$

$$Z_{TH} = 1.92 \angle -50.19^\circ \Omega$$