

Desk Copy

ECE 300
Test #2
Spring Semester, 2005

wlg

PM Section

AM Section

Name GREEN
Print (last, first)

- (1) Develop the Thevenin equivalent circuit as seen looking into terminals a-b of the circuit of Figure 1. Using your Thevenin circuit, connect a $100\ \Omega$ resistor between terminals a-b and determine V_{ab} .

17%

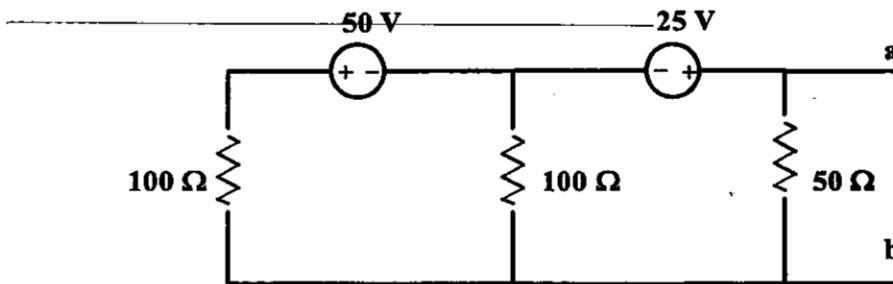


Figure 1: Circuit for problem 1.

- (2) Find I_0 in the network of Figure 2 using Thevenin's theorem.

17%

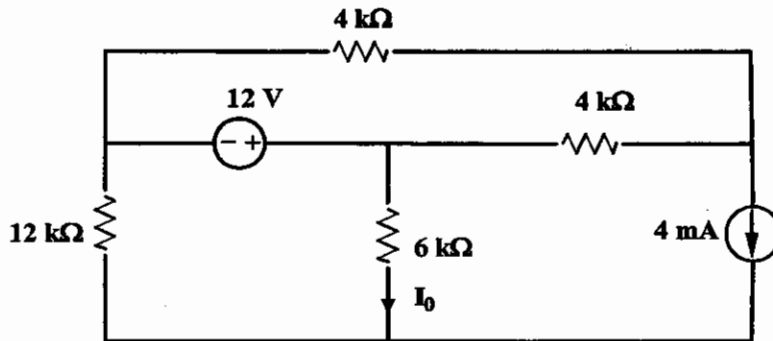


Figure 2: Circuit for problem 2.

(3) You are given the circuit of Figure 3.

- (a) Place a short across a-b and determine the current flowing from a to b. Call this I_N .
- (b) Find the Thevenin resistance looking into terminals a-b.
- (c) Draw the Norton equivalent circuit as seen by looking into terminals a-b.

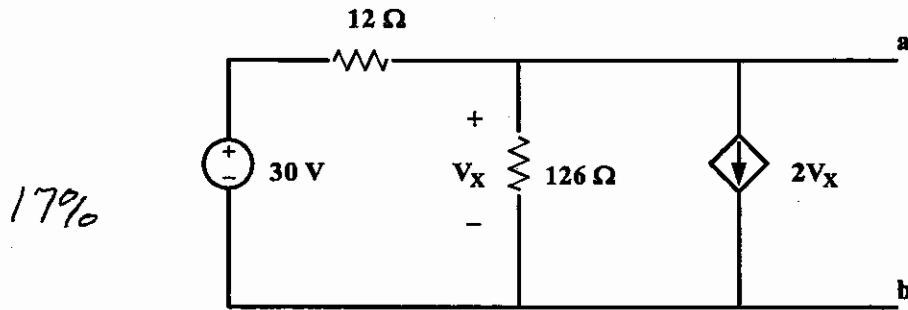


Figure 3: Circuit for problem 3.

(4) You are given the circuit of figure 4. The circuit is in steady state. In other words, I as shown in the circuit, equal 0. Find v_1 , v_2 , and v_3 . How much energy is stored in the $5\mu\text{F}$ capacitor?

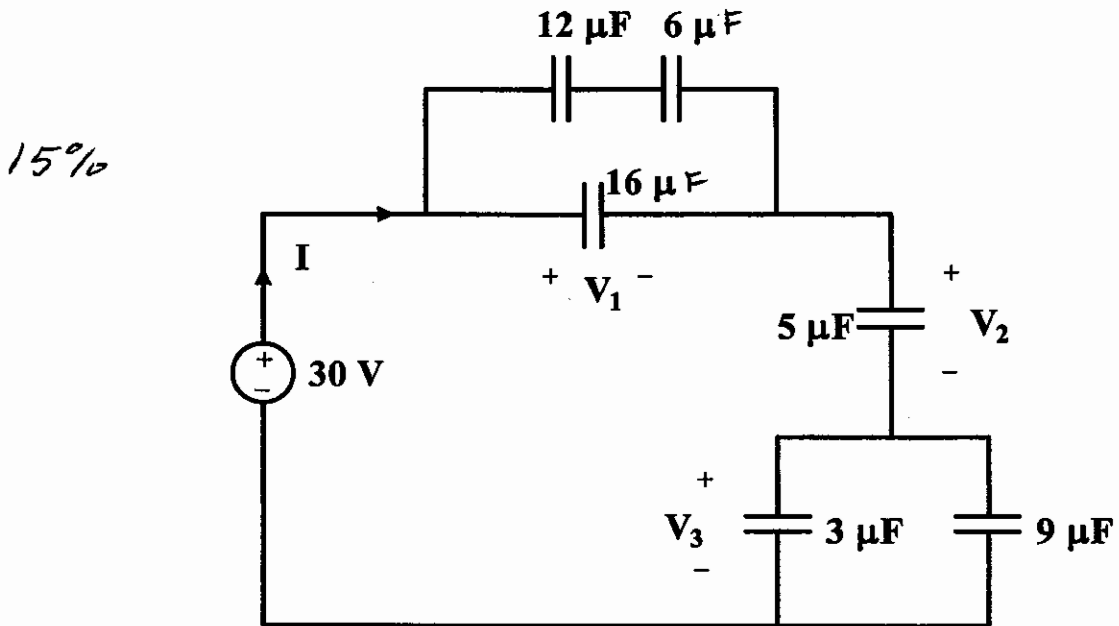


Figure 4: Circuit for problem 4.

- (5) Determine the voltage gain of V_{out}/V_{in} for the op amp circuit shown in Figure 5. Your answer should be a function of R_A , R_B , R_C , R_D .

17%

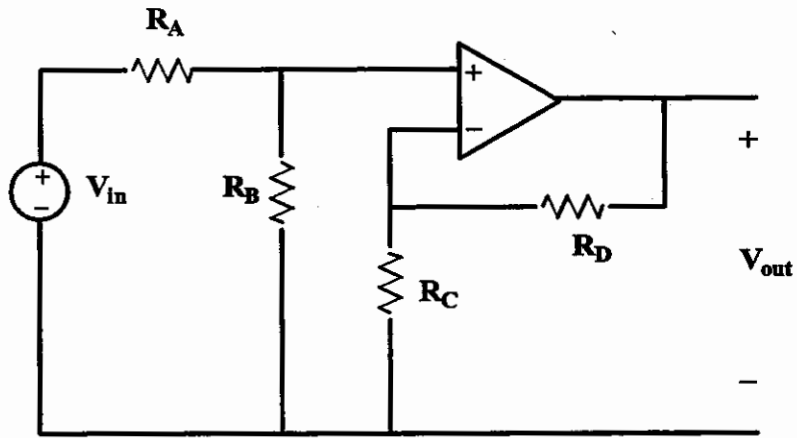


Figure 5: Circuit for problem 5.

- (6) For the op amp circuit shown in Figure 6, find the value of R_X that results in $V_{out} = 20V_{in}$.

17%


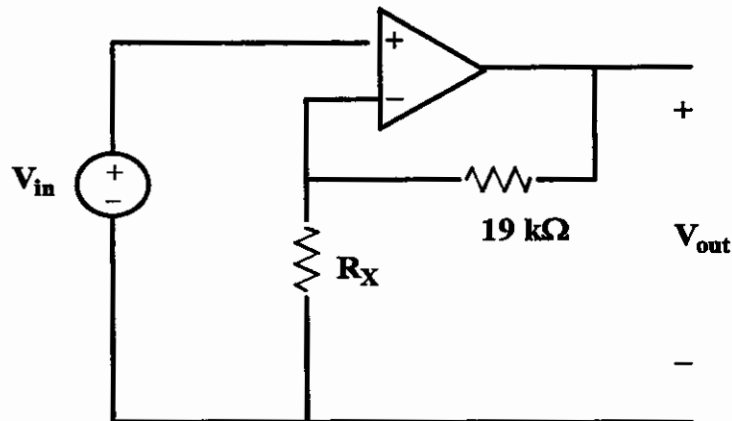



Figure 6: Circuit for problem 6

Test # 2

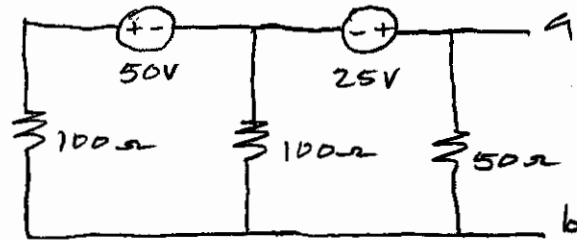(1) Find the Thevenin: Attach 100Ω , find V_{ab}



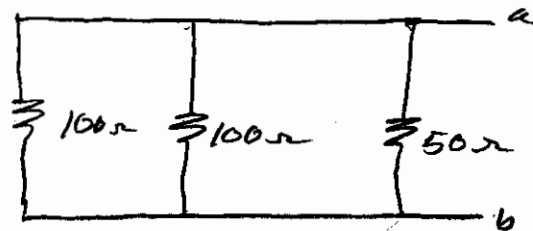
To find R_{TH} : Remove (deactivate) independent sources.



Practically by inspection


$$R_{TH} = 25\Omega$$

To find V_{TH} :

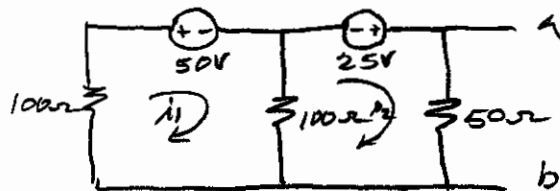


$$\begin{bmatrix} 200 & -100 \\ -100 & 150 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -50 \\ 25 \end{bmatrix} \quad \begin{array}{l} i_1 = -.25 \text{ A} \\ i_2 = 0 \end{array}$$

$$V_{TH} = i_2 \times 50 = 0$$

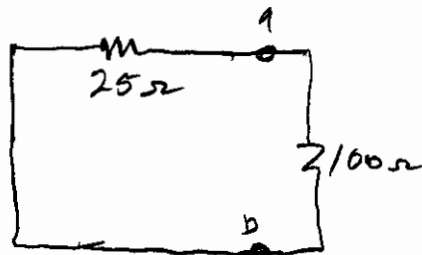


$$V_{ab} = 0$$

(2) Find I_0 using THOVENIN:

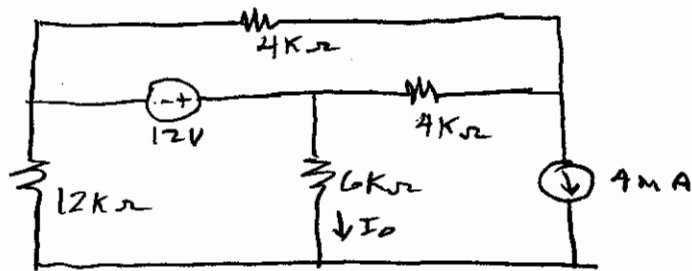


To find R_{TH}

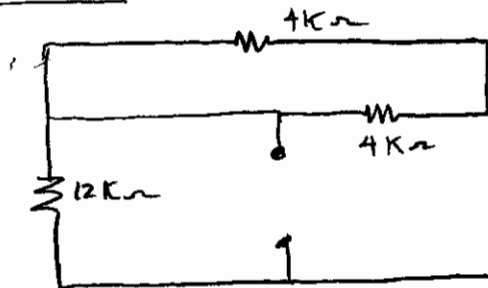

The two $4k\Omega$ are shorted out.

$$R_{TH} = 12k\Omega$$


To Find V_{TH}

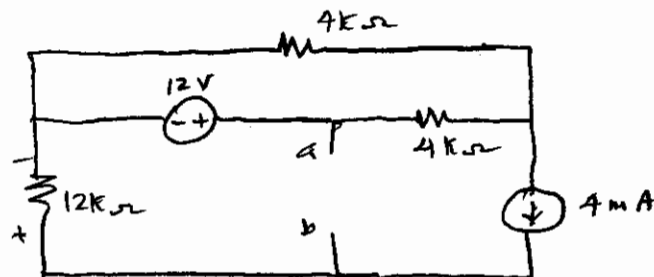

$$V_{TH} = V_{ab}$$

$$-V_{ab} + 12 - (12k)(4k^{-1}) = 0$$


$$V_{ab} = 12 - 48 = -36V$$

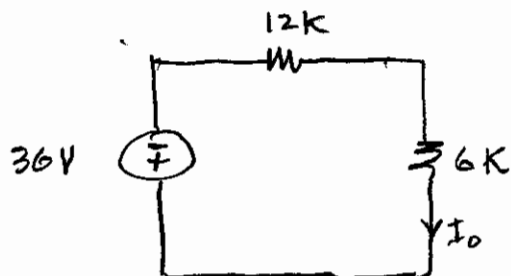

$$I_0 = \frac{-36}{18k}$$

$$I_0 = -2mA$$

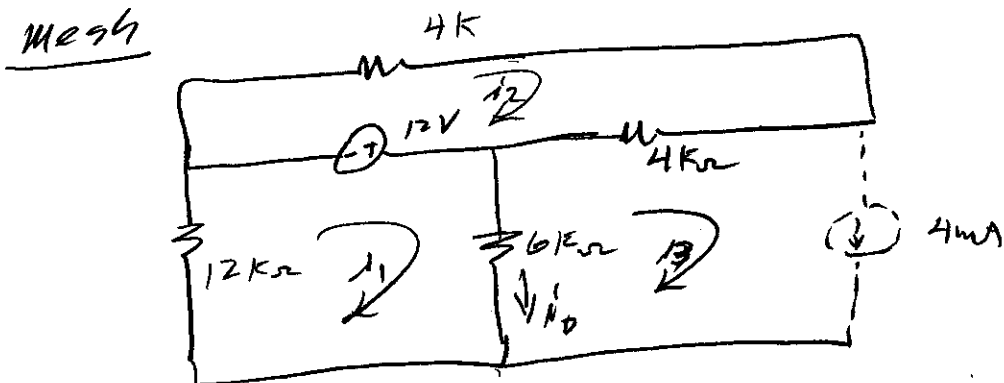(2) Alternate solution for checking purposes



$$18K i_1 + 0 i_2 - 6K i_3 = 12$$

$$0 i_1 + 8K i_2 - 4K i_3 = -12$$

$$0 i_1 + 0 i_2 + i_3 = 4 \text{ mA}$$

$$i_1 = .002 \text{ A}$$


$$i_2 = .0005 \text{ A}$$

$$i_3 = .004 \text{ A}$$


$$i_0 = i_1 - i_3 = .002 - .004$$

$$i_0 = -2 \text{ mA} \quad \text{check}$$

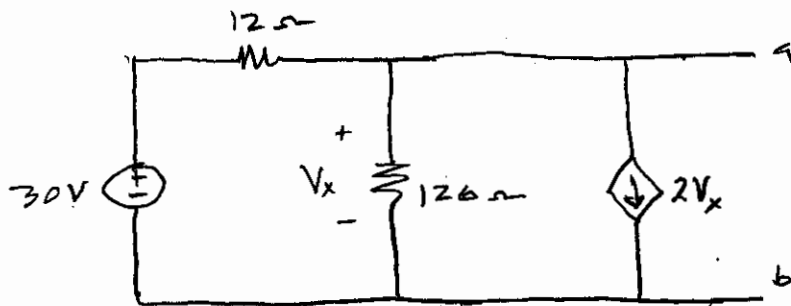
- (3) (a) Determine I_{ss}
 (b) Find Thevenin resistance.
 (c) Draw Norton ckt looking into a-b



To determine I_{ss}

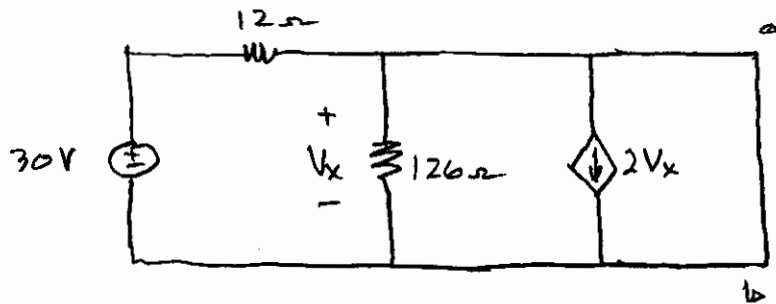

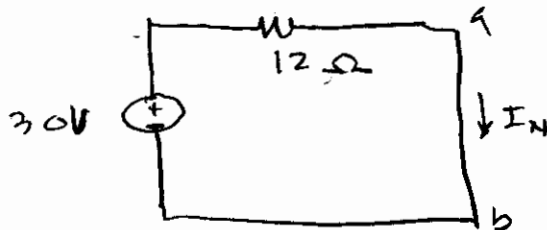Placing a short from a to b causes the 126Ω resistor to be shorted, which in turn makes $V_x = 0$. If $V_x = 0$ the current source is zero, which means open. The circuit becomes as below:



$$I_N = \frac{30}{12} = 2.5 \text{ A}$$


(3) continued

2

To find R_{TH}

Deactivate all independent sources, since we are left with a dependent source, we must place either a voltage (V_L) or current source (I_L) at the load and solve for $\frac{V_L}{I_L}$.

In this case $V_L = V_x$, by inspection

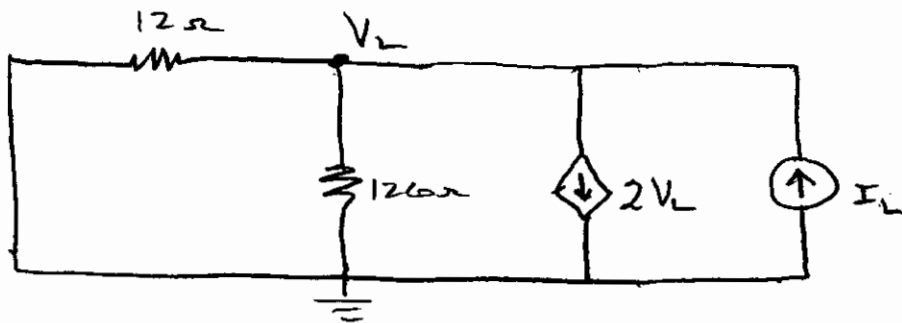


Writing a nodal equation at V_L gives

$$\frac{V_L}{12} + \frac{V_L}{126} + 2V_L = I_L$$

$$126V_L + 12V_L + 3024V_L = 1512I_L$$

$$\frac{V_L}{I_L} = \frac{1512}{3142} = 0.478 \Omega$$

$$\therefore R_{TH} = 0.478 \Omega$$

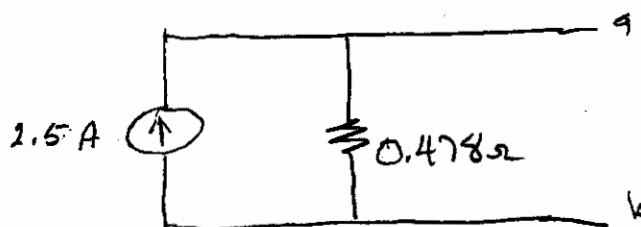

Norton
circuit


(4) Doing capacitance reduction;

$12\mu\text{F}$ in series with $6\mu\text{F}$


$$\frac{12 \times 6 \mu\text{F}}{18} = 4\mu\text{F}$$

$3\mu\text{F}$ in parallel with $9\mu\text{F} = 12\mu\text{F}$

We have

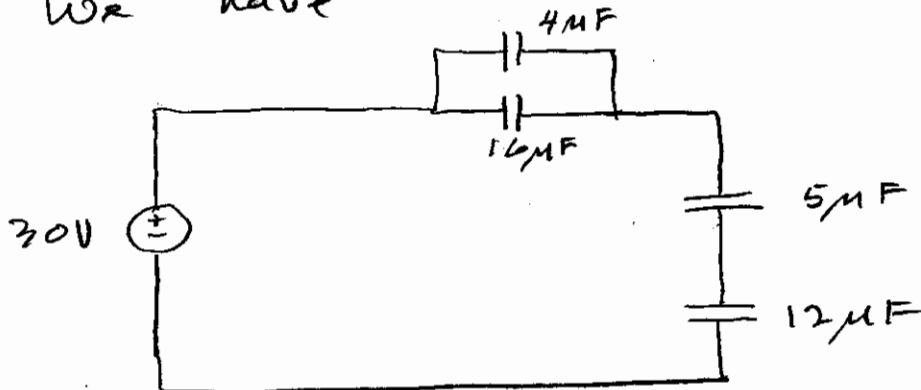

OR

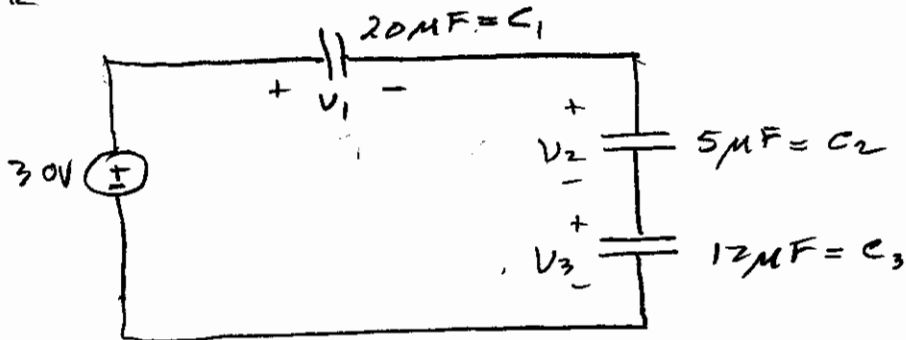

$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{5} + \frac{1}{12}$$

$$\frac{60}{C_{eq}} = 3 + 12 + 5 = 20$$

$$C_{eq} = 3\mu\text{F}$$

$$Q = C_{eq} V = (3\mu\text{F})(30\text{V}) = 90 \times 10^{-6} \text{C}$$

(7) continued

2

$$V_1 = \frac{Q}{C_1} = \frac{90 \times 10^{-6}}{20 \times 10^{-6}} = 4.5 \text{ V}$$

$$V_2 = \frac{Q}{C_2} = \frac{90 \times 10^{-6}}{5 \times 10^{-6}} = 18 \text{ V}$$

$$V_3 = \frac{Q}{C_3} = \frac{90 \times 10^{-6}}{12 \times 10^{-6}} = 7.5 \text{ V}$$

$$V_1 + V_2 + V_3 = 4.5 + 18 + 7.5$$

$$= 30 \text{ V} \quad (\text{ENCOURAGING})$$


Energy stored in the $5 \mu\text{F}$ capacitor

$$W_5 = \frac{1}{2} C_2 V_2^2$$

$$W_5 = \frac{1}{2} \times 5 \times 10^{-6} (18)^2 =$$

$$W_5 = 0.81 \text{ mJ}$$

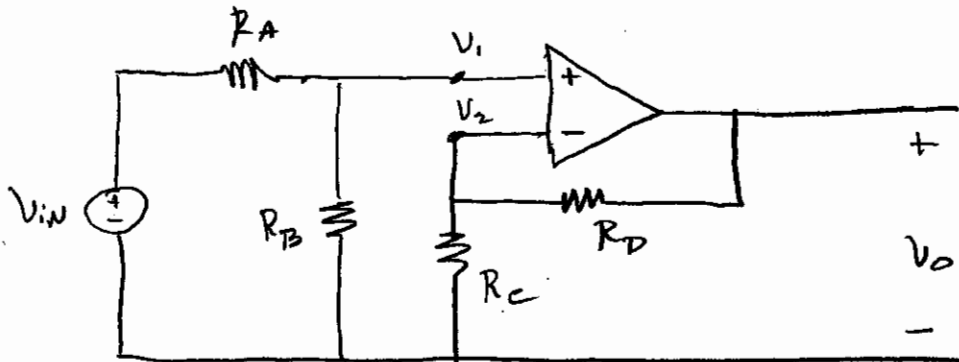(5) Determine V_{out}/V_{in} for the following op-amp circuit.



$$V_1 = \frac{V_{in} R_B}{R_A + R_B}$$

$$V_2 = \frac{V_o R_c}{R_c + R_D}$$


Now $V_1 = V_2$

$$V_o \frac{R_c}{R_c + R_D} = \frac{V_{in} R_B}{R_A + R_B}$$

so

$$\frac{V_o}{V_{in}} = \frac{R_B (R_c + R_D)}{R_c (R_A + R_B)}$$

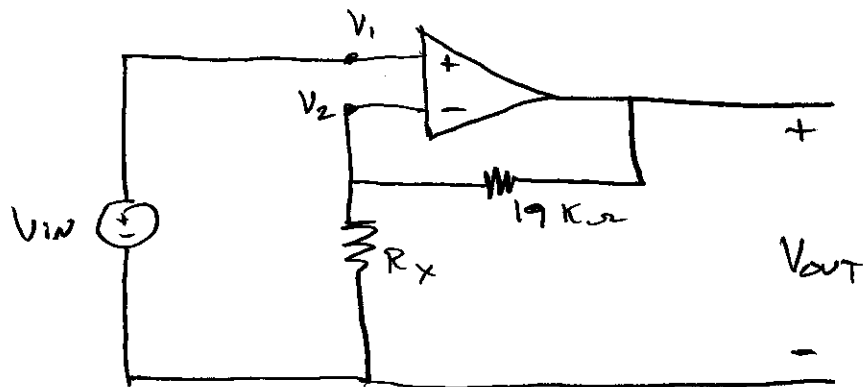(6) Find R_x that results in $V_{OUT} = 20V_{IN}$



$$V_2 = \frac{V_o \times R_x}{R_x + 19K}$$

$$V_1 = V_{in}$$

$$\text{but } V_1 = V_2$$

$$\frac{V_o R_x}{R_x + 19K} = V_{in}$$

$$V_o = \left(\frac{R_x + 19K}{R_x} \right) V_{in}$$

make

$$\frac{R_x + 19K}{R_x} = 20$$

$$R_x + 19K = 20R_x$$

$$19R_x = 19K$$

$$R_x = 1K\Omega$$