

Find the average power absorbed by the $10\ \Omega$ resistor.

$$\text{KVL: } 8\angle 20^\circ = 4I_0 + 0.1V_0$$

$$\text{KCL: } 8I_0 + \frac{V_1}{j5} + \frac{V_1}{10-j5} = 0$$

$$V_0 = \frac{10}{10-j5} V_1 \Rightarrow V_1 = \frac{10-j5}{10} V_0$$

$$8I_0 + \frac{10-j5}{j50} V_0 + \frac{V_0}{10} = 0$$

$$I_0 = j0.025 V_0$$

Substituting:


$$8\angle 20^\circ = 0.1V_0(1+j)$$

$$V_0 = \frac{80\angle 20^\circ}{1+j}$$


$$I_1 = \frac{V_0}{10} = \frac{8}{10} \angle -25^\circ = \frac{4}{5} \angle -25^\circ$$

$$P = \frac{1}{2} I^2 R$$
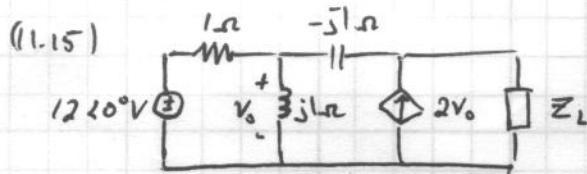
$$= \frac{1}{2} \left(\frac{64}{5} \right) (10) = \underline{\underline{160\text{ W}}}$$



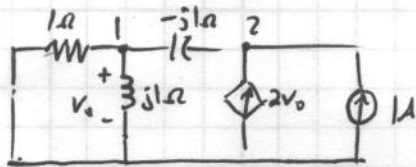- Find the value of Z_L that will absorb the maximum power and the value of the max power.



From node 1:

$$\frac{v_o}{1} + \frac{v_o}{j} = \frac{v_2 - v_o}{-j}$$

$$v_o = jv_2$$

From node 2:

$$1 + 2v_o = \frac{v_2 - v_o}{-j}$$

$$1 = jv_2 - (2+j)v_o$$

Substituting:

$$1 = jv_2 - (2+j)(j)v_2 = (1-j)v_2$$

$$v_2 = \frac{1}{1-j}$$

$$Z_{th} = \frac{v_2}{1} = \frac{1+j}{2} = 0.5 + j0.5$$

$$Z_2 = Z_{th}^* = \underline{\underline{0.5 - j0.5 \Omega}}$$

For Power: Open Z_L in figure and determine V_{th}

$$2v_o + \frac{12 - v_o}{1} = \frac{v_o}{j}$$

$$v_o = \frac{-12}{1+j}$$

$$-v_o - (-j \cdot 2v_o) + V_{th} = 0$$

$$V_{th} = (1 - j2)v_o = \frac{(-12)(1-j2)}{1+j}$$

$$P_{max} = \frac{|V_{th}|^2}{8R_L} = \frac{\left(\frac{12\sqrt{5}}{\sqrt{2}}\right)^2}{8(0.5)} = \underline{\underline{90W}}$$

(11.30) Determine the rms value of the waveform.

$$v(t) = \begin{cases} t & 0 \leq t < 2 \\ -1 & 2 \leq t < 4 \end{cases}$$

$$V_{\text{rms}}^2 = \frac{1}{4} \left[\int_0^2 t^2 dt + \int_2^4 (-1)^2 dt \right]$$

$$= \frac{1}{4} \left[\frac{8}{3} + 2 \right]$$

$$= 1.1667$$

$$V_{\text{rms}} = \underline{\underline{1.08V}}$$


(11.34)

~~(11.34)~~ Find the effective value of $s(t)$ in Fig. 11.65

$$s_{\text{rms}}^2 = \frac{1}{T} \int_0^T s^2(t) dt = \frac{1}{3} \left[\int_0^2 (3t)^2 dt + \int_2^3 6^2 dt \right]$$

$$= \frac{1}{3} \left[\frac{9t^3}{3} \Big|_0^2 + 36 \right] = 20$$
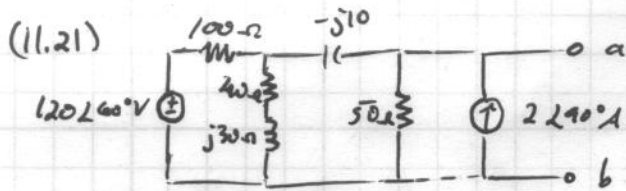
$$s_{\text{rms}} = \underline{\underline{4.472}}$$



- What load should be connected to terminals a-b of the circuits in Fig. 11.52 so that max power is transferred to the load

Assumptions:

Purely resistive load impedance.

Find Z_{th} at terminals a-b: open current source

$$Z_{th} = 50 \parallel [-j10 + 100 \parallel (40 + j30)]$$

$$\text{where } 100 \parallel (40 + j30) = \frac{(100)(40 + j30)}{140 + j30}$$

$$= 31.707 + j14.634$$

$$Z_{th} = 50 \parallel 31.707 + j14.634$$

$$= 19.5 + j1.73$$

$$R_L = |Z_{th}| = \underline{\underline{19.58 \Omega}}$$