

Solutions to Exam #1

Test B

ECE 300

Spring Semester, 2006


**University of Tennessee, Knoxville, TN
ECE Department**

Test B

Wing

- (1) You are given the circuit of Figure 1.
 (a) Find the voltage V_{fb} .
 (b) Find the power supplied by the 10 V source.

15%

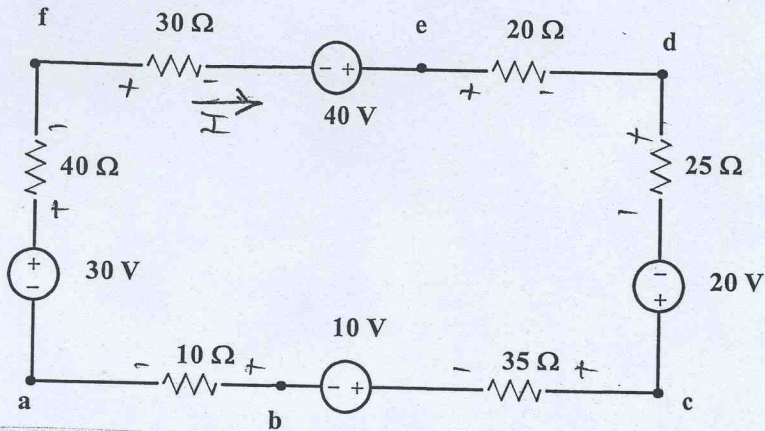

(a)

Assume I as shown. Use default sign convention. Write KVL, cw starting at "f" using drops.

$$30I - 40 + 20I + 25I - 20 + 35I + 10 + 10I - 30 + 40I = 0$$

$$160I = 80$$

$$I = 0.5 \text{ A}$$

Start at "f", cw, $\Sigma \text{drops} = 0$

$$+V_{fb} + 10I - 30 + 40I = 0$$

$$V_{fb} = 30 - 50I = 30 - 50 \times 0.5 = 30 - 25$$


$$V_{fb} = 5 \text{ V}$$

(b) $P_{\text{sup}} = -10I = -5 \text{ W}$

$$P_{\text{sup}} = -5 \text{ W}$$

(2) You are given the circuit of Figure 2. Find the voltage V_x .

15%

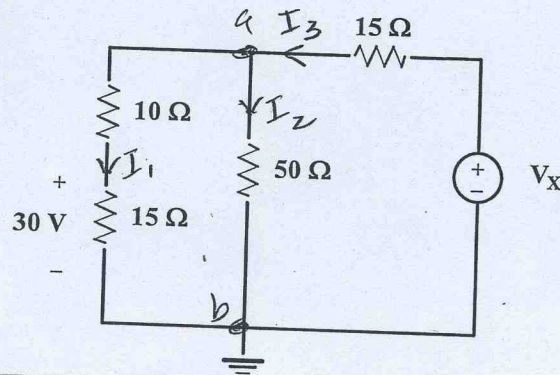

By Ohm's Law:

$$I_1 = \frac{30}{15} = 2A$$

$$V_{ab} = 2 \times 25 = 50V$$

$$I_2 = \frac{50}{50} = 1A$$

KVC $I_3 = I_1 + I_2 = 3A$

KVL $V_x = 15 I_3 + V_{ab}$


$$V_x = 45 + 50$$

$$V_x = 95V$$

B

(3) You are given the circuit shown in Figure 3. Find the resistance, R_{eq} .

15%

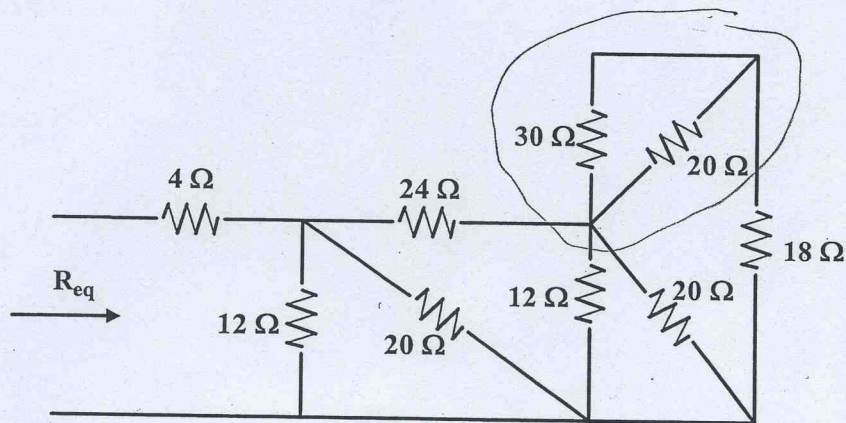


- * Starting at the right hand side you have $20 \parallel 30$ which gives 12Ω .
- * The 12Ω is in series with 18Ω giving 30Ω .
- * The 30Ω is then in parallel with 20Ω giving 12Ω .
- * The 12Ω is in \parallel with 12Ω , giving 6Ω .
- * The 6Ω is in series with 24Ω giving 30Ω .
- * The 30Ω is in parallel with 20Ω giving 12Ω .
- * The 12Ω is in \parallel with 12Ω giving 6Ω .
- * The 6Ω is in series with 4Ω giving

$$R_q = 10 \Omega$$

(4) You are given the circuit shown in Figure 4. Find the ratio of V_O/V_S (which is the gain).

15%

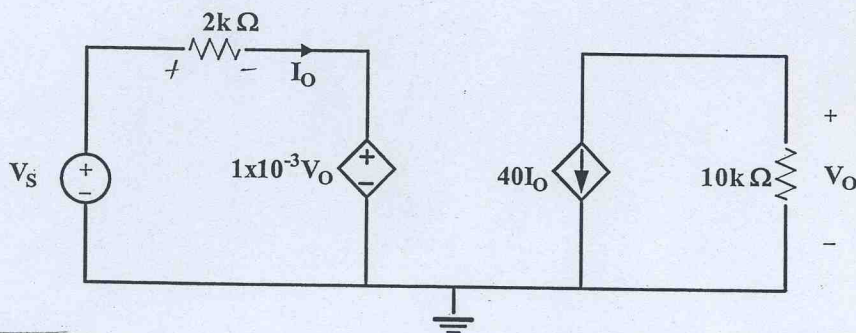

On the right side:

$$V_O = -(400k)I_O \quad (\#1)$$

On the left side,

$$-V_S + (2k)I_O + k^{-1}V_O = 0$$

$$2kI_O = V_S - k^{-1}V_O$$

$$I_O = \frac{V_S - k^{-1}V_O}{2k} \quad (\#2)$$

Substitute (#2) into (#1)

$$V_O = -400k \left[\frac{V_S - k^{-1}V_O}{2k} \right]$$

$$= -200 [V_S - k^{-1}V_O]$$

$$V_O = -200V_S + 0.2V_O$$


$$.8V_O = -200V_S$$

$$\frac{V_O}{V_S} = -250$$

B Tech

(5) You are given the circuit shown in Figure 5. Use nodal analysis to find V_1 and V_2 .

20%

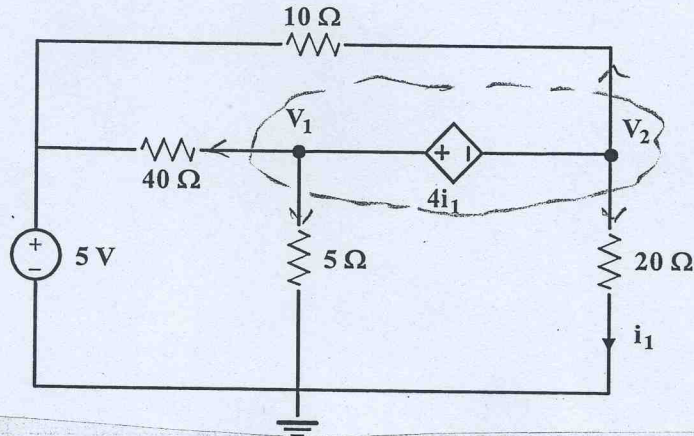

We have a super node as indicated above. For the super node we write the following equation.

$$\frac{V_1 - 5}{40} + \frac{V_1}{5} + \frac{V_2 - 5}{10} + \frac{V_2}{20} = 0$$

x40

$$V_1 - 5 + 8V_1 + 4V_2 - 20 + 2V_2 = 0$$

$$\boxed{9V_1 + 6V_2 = 25}$$

Constraint Eq.

$$V_1 - 4i_1 - V_2 = 0$$

$$i_1 = \frac{V_2}{20}$$

$$V_1 - \frac{4V_2}{20} - V_2 = 0$$

$$5V_1 - V_2 - 5V_2 = 0$$


$$\boxed{5V_1 - 6V_2 = 0}$$

$$\begin{bmatrix} 9 & 6 \\ 5 & -6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 25 \\ 0 \end{bmatrix}$$

$$\boxed{V_1 = 1.79 \text{ V}, \quad V_2 = 1.49 \text{ V}}$$

B-Tech
#5

Mesh

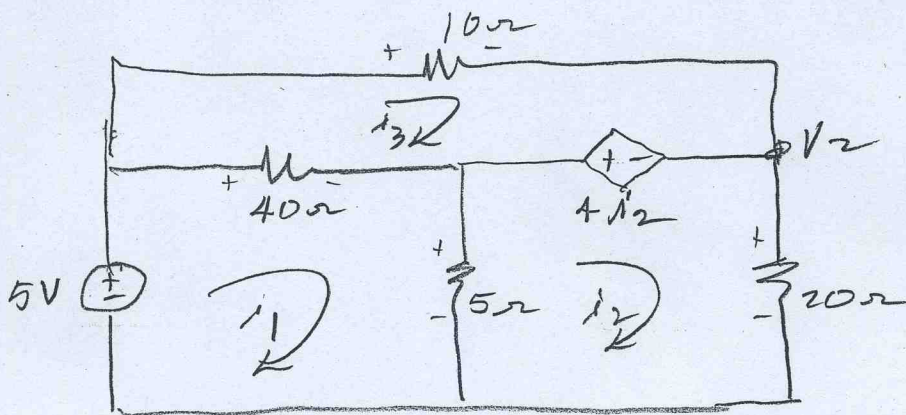

$$45i_1 - 5i_2 - 40i_3 = 5$$

$$10i_3 - 4i_2 - 40(i_1 - i_3) = 0$$

$$-40i_1 - 4i_2 + 50i_3 = 0$$

$$-5(i_1 - i_2) + 4i_2 + 20i_2 = 0$$

$$-5i_1 + 5i_2 + 24i_2 = 0$$

$$-5i_1 + 29i_2 + 0i_3 = 0$$

$$\begin{bmatrix} 45 & -5 & -40 \\ -40 & -4 & 50 \\ -5 & 29 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$i_1 = 0.432A, \quad i_2 = 0.074A, \quad i_3 = 0.351A$$

$$V_1 = 5(i_1 - i_2) = 5(0.432 - 0.074)$$


$$V_1 = 1.79V \quad \text{check}$$

$$V_2 = 20 \times i_2 = 20 \times 0.074 = 1.48V \quad \text{check}$$


B Test

(6) You are given the circuit of Figure 6. Use mesh analysis to find the current I_0 .

20%

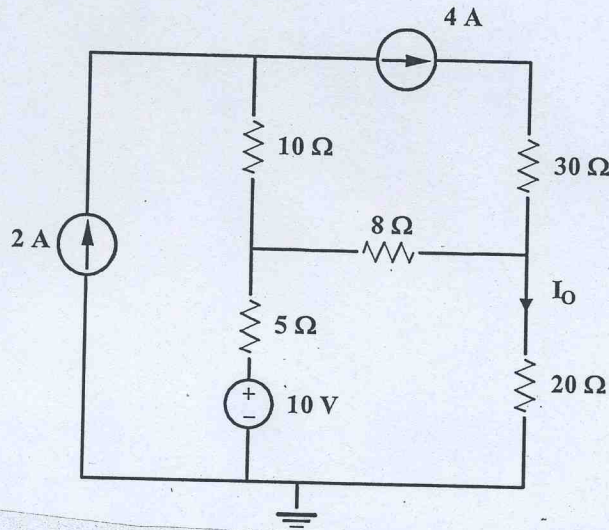

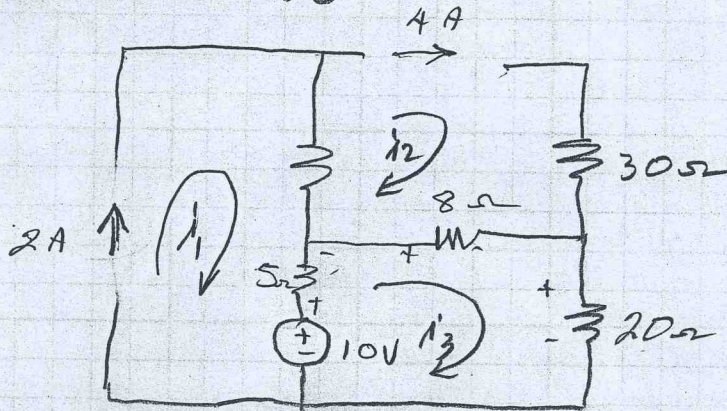Redraw the circuit with the 4A and 2A source inactive



Around mesh 3:

$$-10 + 5(i_3 - i_1) + 8(i_3 - i_2) + 20i_3 = 0$$

$$\boxed{-5i_1 - 8i_2 + 33i_3 = 10} \quad (\#1)$$

Constraint #1

$$\boxed{i_1 = 2A}$$

Constraint #2

$$\boxed{i_2 = 4A}$$

Back to (#1)

$$-10 - 32 + 33i_3 = 10$$


$$\boxed{i_3 = 1.58A}$$

$$I_0 = i_3 = 1.58A$$

$\frac{50}{33}$

B-Test
6

Nodal Analysis

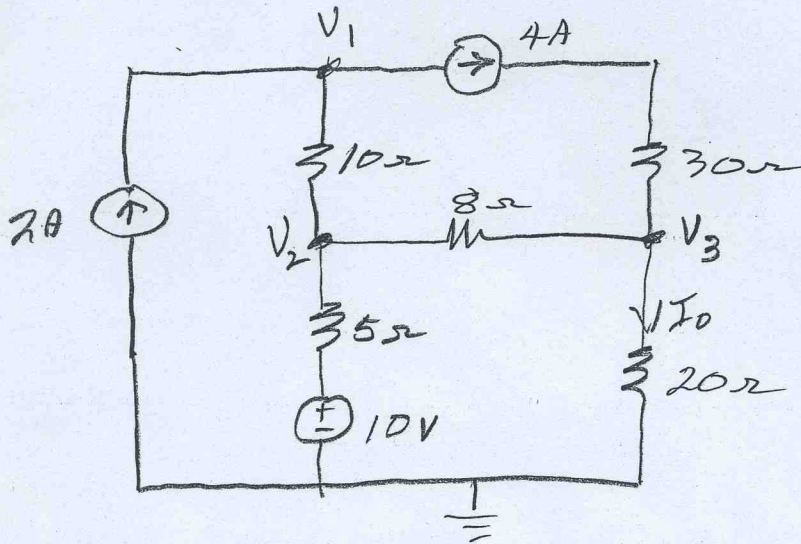

At V_1

$$\frac{V_1 - V_2}{10} + 4 - 2 = 0$$

$$\boxed{V_1 - V_2 + 0V_3 = -20}$$

At V_2

$$\times 40 \quad \frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{8} + \frac{V_2 - 10}{5} = 0$$

$$4V_2 - 4V_1 + 5V_2 - 5V_3 + 8V_2 = 80$$

$$\boxed{-4V_1 + 17V_2 - 5V_3 = 80}$$

At V_3

$$\frac{V_3 - V_2}{8} + \frac{V_3}{20} - 4 = 0$$

$\times 40$

$$5V_3 - 5V_2 + 2V_3 = 160$$

$$\boxed{0V_1 - 5V_2 + 7V_3 = 160}$$

$$V_3 = 31.52V$$

$$I_0 = \frac{31.52}{20} = 1.58A \quad \text{check}$$