

# Desk Copy

Don't

wlg

Exam B

ECE 300  
Spring Semester, 2006  
Test #2

Name wlg  
Print (last, first)

Work the exam on the space provided below the problem. Work on one side of your paper only.  
Problems 1 through 4 are 20% each. Problem 5 is 10%. Take home problem is 10%.

- (1) Determine the value of  $V_s$  in the opamp circuit of Figure 1 so that  $V_o = -2 \text{ V}$ .

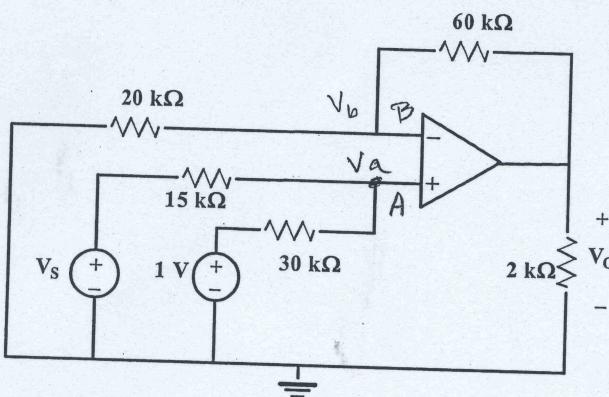


Figure 1: Circuit for problem 1.

At A

$$\frac{V_a - V_s}{15\text{k}} + \frac{V_a - 1}{30\text{k}} = 0$$

$$2V_a - 2V_s + V_a - 1 = 0$$

$$3V_a = 2V_s + 1$$

$$V_a = \left[ \frac{2V_s + 1}{3} \right] \quad (1)$$

At B

$V_b = V_a$ ; write a node equation

$$\frac{\left[ \frac{2V_s + 1}{3} \right]}{20\text{k}} + \frac{\left[ \frac{2V_s + 1}{3} - V_o \right]}{60\text{k}} = 0$$

(1) continued

$$2V_s + 1 + \frac{2V_s + 1}{3} - V_o = 0$$

$$6V_s + 3 + 2V_s + 1 - 3V_o = 0$$

$$8V_s = 3V_o - 4$$

$$V_s = \frac{3V_o - 4}{8} \quad \Big| \quad V_o = -2 \quad = \frac{-10}{8}$$

$$V_s = \frac{-10}{8} \text{ V} = -1.25 \text{ V}$$

- (2) You are given the circuit shown in Figure 2.
- Find the Thevenin equivalent circuit, with respect to terminals a-b.
  - Draw the Thevenin equivalent circuit: include  $V_{TH}$  and  $R_{TH}$ .
  - What resistor placed between terminals a-b will give maximum power transfer to this resistor? Determine the value of this power.


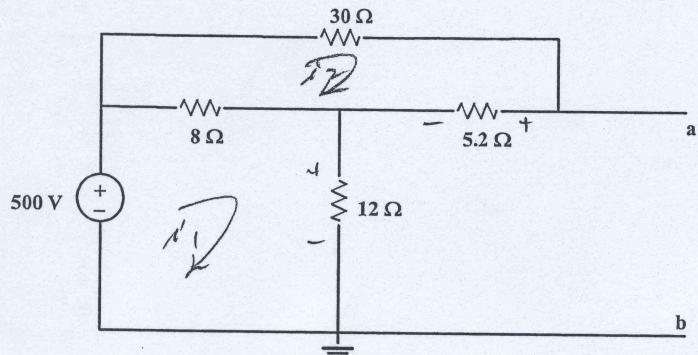


Figure 2: Circuit for problem 2.

(a) First find  $R_{TH}$ .

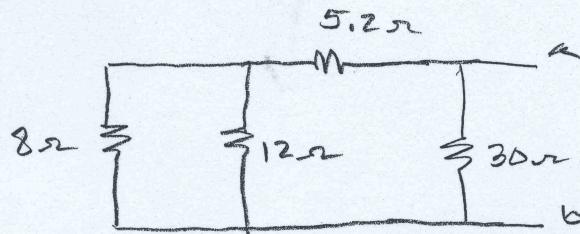

$$8 \parallel 12 = \frac{8 \times 12}{20} = 4.8\Omega$$

$$R_{TH} = 30 \parallel 4.8 = \frac{30 \times 4.8}{40} = 7.5\Omega$$

$$\boxed{R_{TH} = 7.5\Omega}$$

using mesh

$$\begin{bmatrix} 20 & -8 \\ -8 & 43.2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 500 \\ 0 \end{bmatrix}$$


$$i_1 = 27A \quad i_2 = 5A$$

(2) cont.


$$\begin{aligned}V_{ab} &= 12i_1 + 5.2i_2 \\&= 12 \times 27 + 5.2 \times 5 \\&= 350 \text{ V}\end{aligned}$$

$$V_{ab} = V_{TH} = 350 \text{ V}$$

(b)

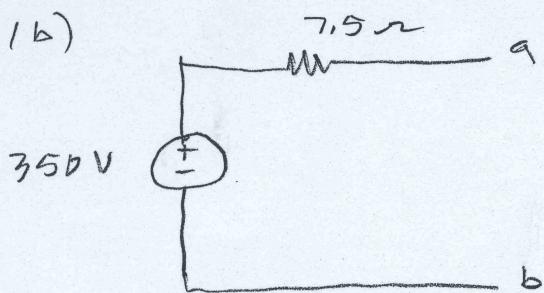

(c) For max pwr xfr.

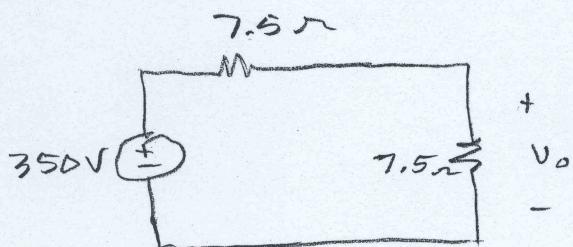

$$P_o = \frac{V_o^2}{7.5}$$

$$V_o = \frac{350}{2} = 175 \text{ V}$$

$$P_o = \frac{175^2}{7.5} = 4083 \text{ W}$$

$$P_o = 4083 \text{ W}$$

(3) You are given the circuit of Figure 3.

- Find the Norton equivalent circuit with respect to terminals a-b. You are required to find  $I_{NORTON}$  by actually finding the short circuit current.
- Draw your Norton equivalent circuit showing the  $I_{NORTON}$ ,  $R_{TH}$  and terminals a-b.



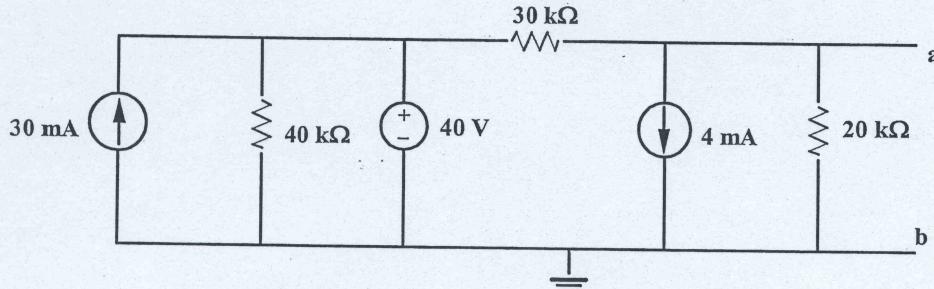


Figure 3: Circuit for problem 3.

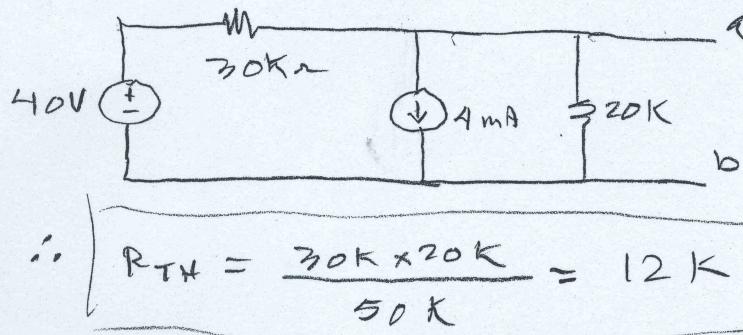(a) The circuit can be redrawn as follows




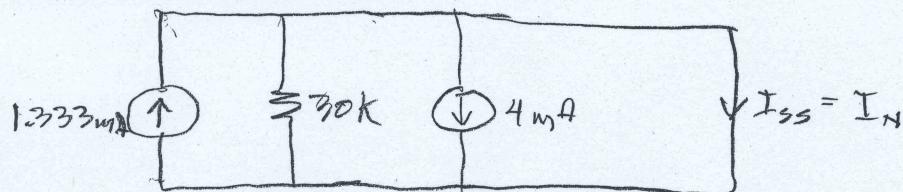shorting a-b, shorts out the 20kΩ resistor.  
The circuit becomes (with a source transformation)



$$I_N = -4 + 1.333 = -2.667mA$$

(b)

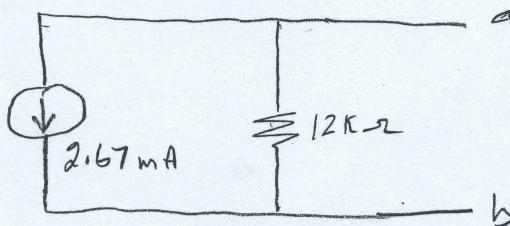

Norton  
Equivalent Circuit

(4) You are given the circuit of Figure 4.

- (a) Give the value of the Thevenin voltage seen looking into terminals a-b.
- (b) Determine the resistance  $R_{TH}$  seen looking into terminals a-b.

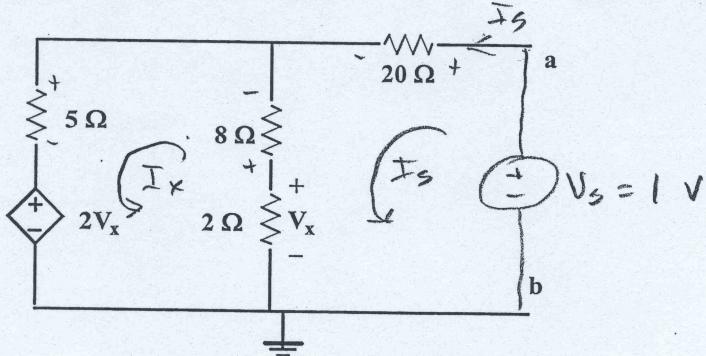


Figure 4: Circuit for problem 4.

(a) Since there are no independent sources,  
 $V_{TH} = 0$ . (It is a dead circuit).

(b) Apply a source,  $V_s = 1V$ , as shown in the diagram. Determine  $I_s$ . Then

$$R_{TH} = \frac{V_s}{I_s} = \frac{1}{I_s}$$

For mesh  $I_x$

$$-V_x + 8(I_x - I_s) + 5I_x + 2V_x = 0$$

$$13I_x - 8I_s + V_x = 0 \quad (1)$$

$$\text{but } V_x = 2(I_s - I_x) = 2I_s - 2I_x \quad (2)$$

Substitute (2) into (1)

$$13I_x - 8I_s + 2I_s - 2I_x = 0$$

$11I_x - 6I_s = 0$

(3)

(4) continued

For mesh  $I_s$

$$-1 + 30I_s - 10I_x = 0$$


$$-10I_x + 30I_s = 1 \quad (4)$$

$$\begin{bmatrix} 11 & -6 \\ -10 & 30 \end{bmatrix} \begin{bmatrix} I_x \\ I_s \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$I_s = 0.0407 \text{ A}$$

$$R_{TH} = \frac{1}{0.0407} \approx 24.5 \Omega$$

(c)

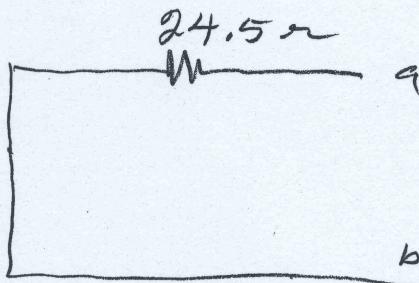

Thévenin  
Circuit

B

- (5) Find the voltage across each capacitor in the circuit shown in Figure 5.

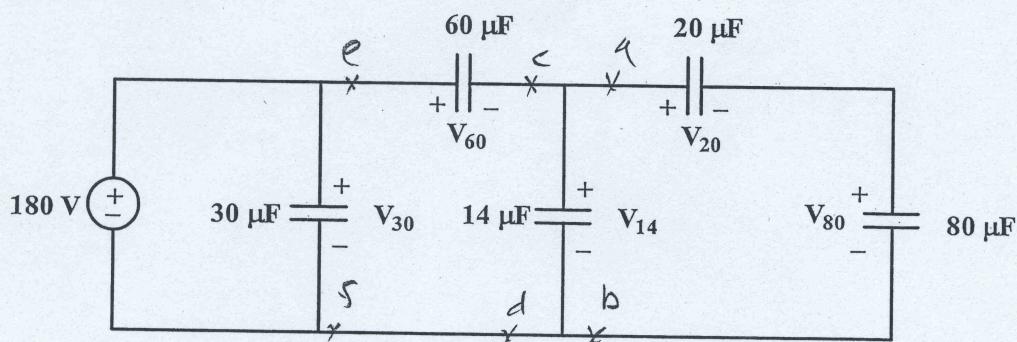


Figure 5: Circuit for problem 5.

$$C_{ab} = \left( \frac{20 \times 80}{20 + 80} \right) \mu F = 16 \mu F$$

$$C_{cd} = 14 \mu F + 16 \mu F = 30 \mu F$$

$$C_{ce} = \frac{60 \times 30}{60 + 30} \mu F = 20 \mu F$$

$$\boxed{V_{30} = 180 V}$$

$$\boxed{V_{60} = \left( \frac{180 \times 30}{30 + 60} \right) = 60 V}$$

$$\boxed{V_{14} = 180 - V_{60} = 120 V}$$

$$\boxed{V_{20} = \frac{V_{14} \times 80}{80 + 20} = 96 V}$$

$$\boxed{V_{80} = V_{14} - 96 = 24 V}$$