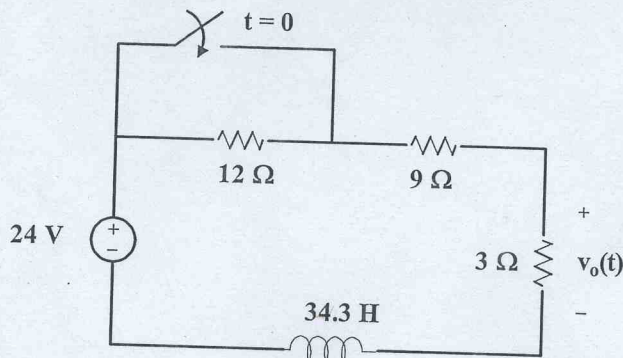


ECE 300
Test #3 A
Spring 2006

WR g:

- (1) The circuit shown in Figure 1 is at steady state before the switch closes at time $t = 0$. **Determine** the output voltage, $v_o(t)$, for $t \geq 0$.



Recall:

$$v_o(t) = v_o(\infty) + [v_o(0^+) - v_o(\infty)] e^{-\frac{t}{\tau}}$$


For $t < 0$

$$v_o(0^-) = \frac{24 \times 3}{12 + 9 + 3} = 3V$$

Since there is an inductor in this series circuit, $i(0^+) = i(0^-)$. Therefore, $v_o(0^+) = v_o(0^-)$

$$\boxed{v_o(0^+) = 3V}$$

For $t > 0$

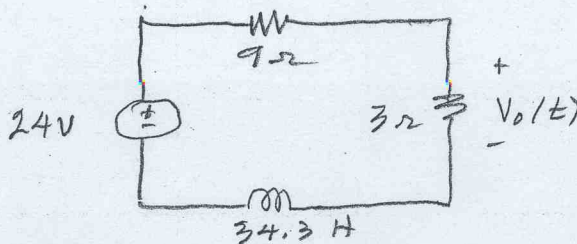

By inspection, $v_o(\infty) = 6V$

$$\tau = \frac{L}{R_T} = \frac{34.3}{12} = 2.86s; \quad \frac{1}{\tau} = 0.35 s^{-1}$$


$$\boxed{v_o(t) = [6 - 3e^{-0.35t}] V}$$

TouBA

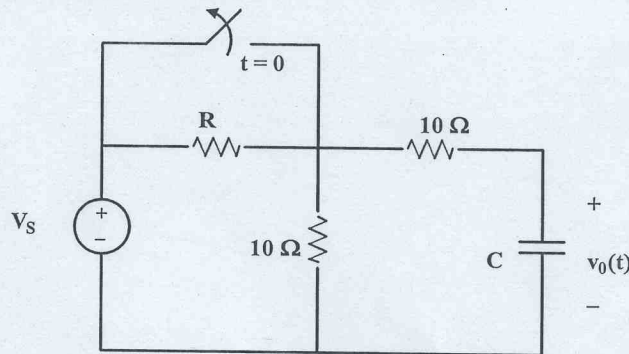- (2) The circuit shown in Figure 2 is at steady state before the switch opens at $t = 0$. V_S is a constant dc voltage source. The output of the circuit is the voltage across the capacitor, $v_o(t)$. This output voltage is given by;

$$v_o(t) = 2 + 8e^{-0.5t} \text{ V}; \quad t \geq 0$$

Required: Determine (a) the value of the input voltage, V_S ; (b) the value of the capacitor, C ; (c) the value of the resistor, R .



For $t < 0$

$$v_o(0^-) = V_S$$

For $t > 0$

$$v_o(0^+) = v_o(0^-) = V_S = 2 + 8e^{-0.5t} \Big|_{t=0} = 10 \text{ V}$$

$$\boxed{V_S = 10 \text{ V}}$$

$$v_o(\infty) = 2 + 8e^{-0.5t} \Big|_{t=\infty} = 2 \text{ V}$$

$$v_o(\infty) = \frac{V_S \times 10}{R + 10} = \frac{10 \times 10}{R + 10} = 2$$

$$100 = 2R + 20$$

$$\boxed{R = 40 \text{ } \Omega}$$

$$\tau = R_{eq} C = 2$$

(2) Tent 3B

$$R_{eq} = 10 + 40 \parallel 10 = 18 \Omega$$

$$R_{eq} C = 2$$

$$C = \frac{2}{18} = \frac{1}{9} F$$

40;


$$V_s = 10 V$$

$$R = 40 \Omega$$

$$C = \frac{1}{9} F$$

(3) T3A & T3B

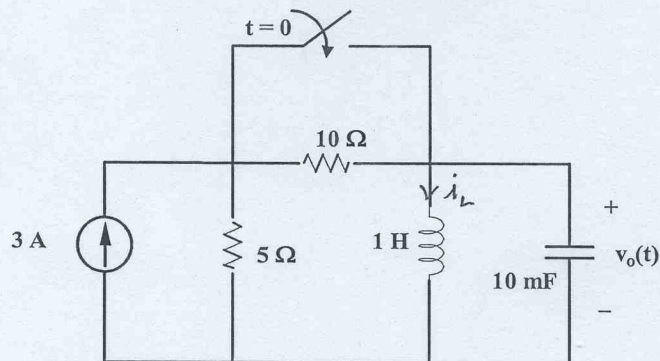(3) You are given the circuit of Figure 3. **Determine** the expression for the voltage $v_o(t)$.




FOR $t < 0$

$$i_L(0^+) = i_L(0^-) = \frac{3 \times 5}{10 + 5} = 1A$$

$$v_o(0^+) = v_o(0^-) = 0$$

FOR $t > 0$

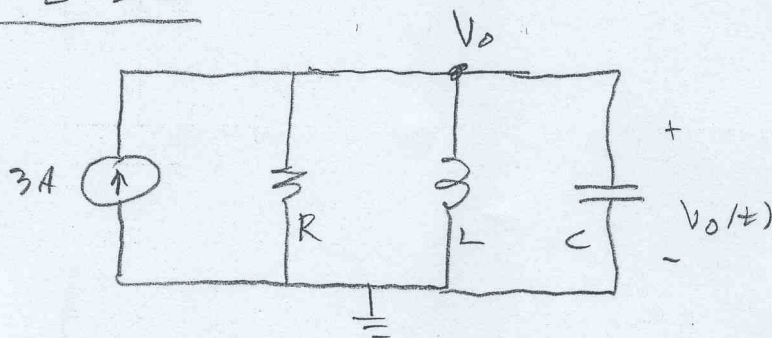

Parallel
RLC CKT

Using nodal:

$$\frac{v_o}{R} + C \frac{dv_o}{dt} + \frac{1}{L} \int_0^t v_o dt + 1 = 3 \quad (1)$$

$i_C = i_L(0^+)$

Will need $\frac{dv_o(0^+)}{dt}$ in solving the D.E.

Go ahead and get it now from (1)

(3)

2

$$C \frac{dV(0^+)}{dt} = 3 - 1 - \frac{V_0(0^+)}{R}$$

$$\frac{dV(0^+)}{dt} = \frac{2}{C} = \frac{2}{10 \times 10^{-3}} = 200 \text{ V/s}$$

so; $V_0(0^+) = 0$, $\frac{dV_0(0^+)}{dt} = 200 \text{ V/s}$ (2)

Go to (1) and take $\frac{d(\cdot)}{dt}$, this gives

$$\frac{1}{R} \frac{dV_0}{dt} + C \frac{d^2 V_0}{dt^2} + \frac{V_0}{L} = 0$$

$$\frac{d^2 V_0}{dt^2} + \frac{1}{RC} \frac{dV_0}{dt} + \frac{V_0}{LC} = 0$$

Put in values;

$$\frac{d^2 V_0}{dt^2} + 20 \frac{dV_0}{dt} + 100 V_0 = 0$$

$$s^2 + 20s + 100 = 0$$

$$(s+10)(s+10) = 0$$

$$V_0 = (A + Bt)e^{-10t} \quad (3)$$

$$V_0(0) = A = 0$$

$$V_0(t) = Bt e^{-10t}$$

$$\left. \frac{dV_0}{dt} \right|_{t=0} = 200 = \left[-10Bt e^{-10t} + B e^{-10t} \right] \Big|_{t=0}$$


$$B = 200$$

$$V_0(t) = 200t e^{-10t} \text{ V}$$

Ans

Test 3A

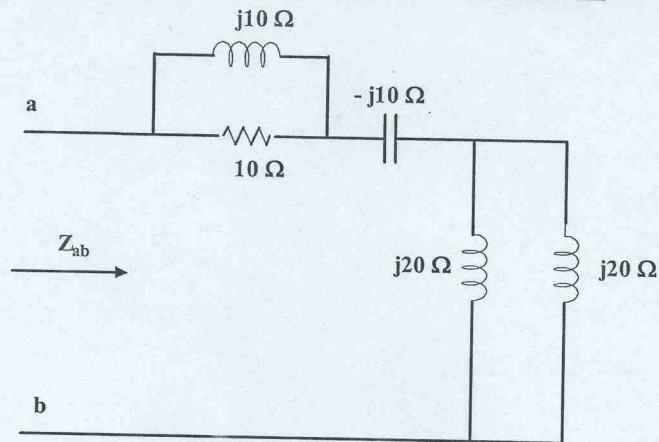(4) You are given the circuit shown in Figure 4. Determine the input impedance, Z_{ab} ,



$$j20 \parallel j20 = \frac{(j20)(j20)}{j20 + j20} = j10 \Omega$$


$j10 \Omega$ in series with $-j10 \Omega = 0$

So

$$Z_{ab} = \frac{10 (j10)}{10 + j10}$$

$$Z_{ab} = 5 + j5 = 7.07 \angle 45^\circ \Omega$$

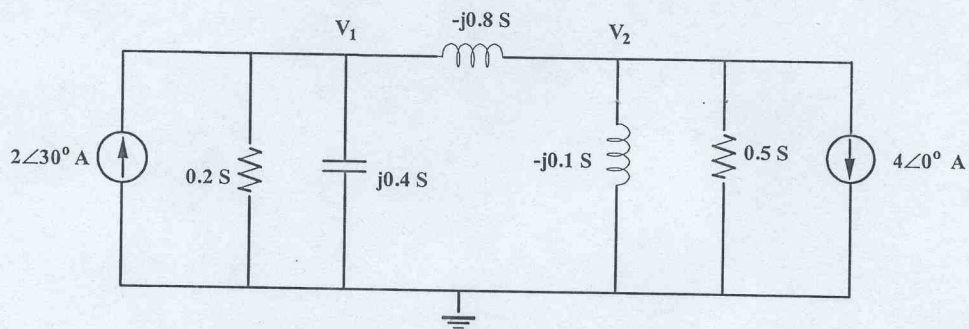- (5) You are given the circuit of Figure 5. **Solve** for the phasor voltages V_1 and V_2 . Express your answers in polar form. **Note:** The unit for the circuit parameters is given in Seiman (S).




By inspection

$$\begin{bmatrix} (0.2 - j0.4) & j0.8 \\ j0.8 & (0.5 - j0.9) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \angle 30^\circ \\ -4 \angle 0^\circ \end{bmatrix}$$

$$V_1 = 5.16 \angle 95.45^\circ \text{ V}$$

$$V_2 = 0.4 \angle 135^\circ \text{ V}$$

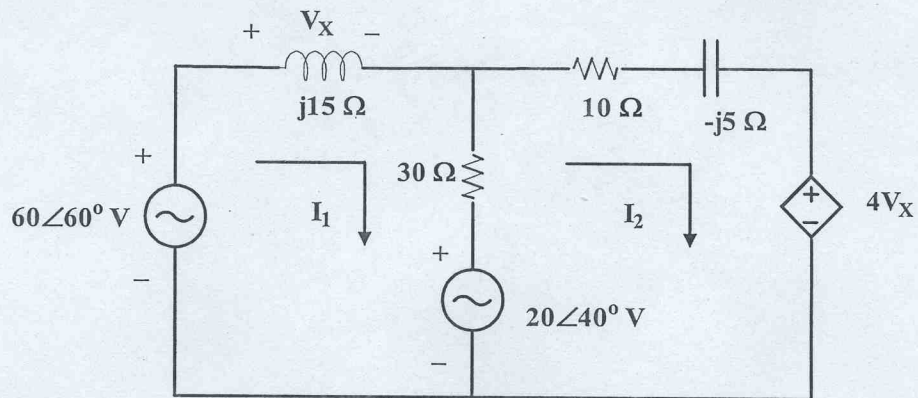- (6) **Solve** for the phasor currents I_1 and I_2 indicated in the circuit of Figure 6. Express your answers in polar form.



$$(30 + j15)I_1 - 30I_2 = 60\angle 60^\circ - 20\angle 40^\circ$$

$$-30I_1 + (40 - j5)I_2 = 20\angle 40^\circ - 4V_x$$

$$= 20\angle 40^\circ - 4(j15)I_1$$

$$(-30 + j60)I_1 + (40 - j5)I_2 = 20\angle 40^\circ$$

$$\begin{bmatrix} 30 + j15 & -30 \\ -30 + j60 & 40 - j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 60\angle 60^\circ - 20\angle 40^\circ \\ 20\angle 40^\circ \end{bmatrix}$$

$$I_1 = 0.99 \angle -24.04^\circ \text{ A}$$

$$I_2 = 1.40 \angle -63.98^\circ \text{ A}$$