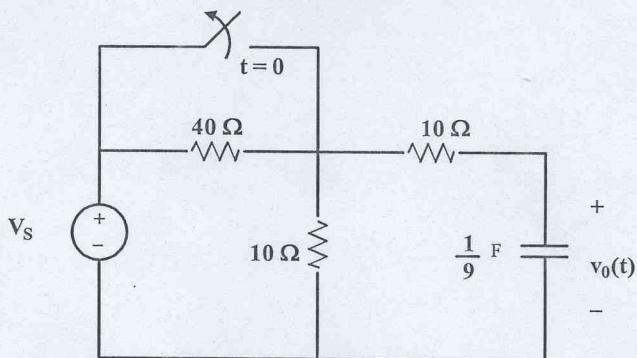


- (1) The circuit shown in Figure 1 is in steady state before the switch opens at $t = 0$. The input is 10 V, constant. The output is the voltage across the capacitor, $v_o(t)$.

Required: Determine the expression for the output voltage $v_o(t)$ for $t \geq 0$.



For $t < 0$

$$v_o(0^-) = v_s = 10\text{ V}$$

For $t > 0$

Voltage across the capacitor cannot change instantaneously so: $v_o(0^+) = v_o(0^-) = 10\text{ V}$

$$v_o(\infty) = \frac{v_s \times 10}{40+10} = \frac{10 \times 10}{50} = 2\text{ V}$$

$$R_{eq} = 10 + \frac{40 \times 10}{40+10} = 18\text{ }\Omega$$

$$T = R_{eq}C = \frac{18}{9} = 2$$

$$v_o(t) = v_o(\infty) + [v_o(0^+) - v_o(\infty)] e^{-\frac{t}{T}}$$


$$v_o(t) = 2 + 8e^{-0.5t}, \text{ V}$$

Test B

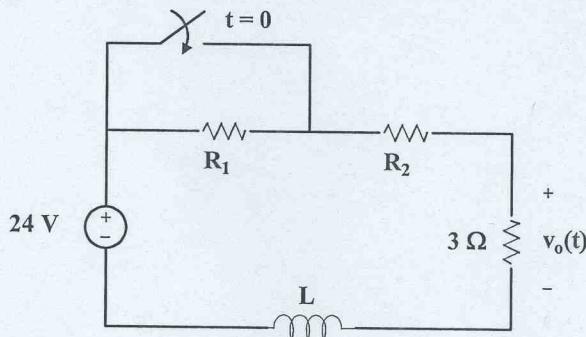- (2) The circuit shown in Figure 2 is in steady state before the switch closes at $t = 0$. The input to the circuit is a constant dc voltage of 24 V. The output, $v_o(t)$, is the voltage across the 3Ω resistor and is given by

$$v_o(t) = 6 - 3e^{-0.35t} \text{ V; } t \geq 0$$

Determine the (a) value of the inductor L , (b) the values of the resistor R_1 and R_2 .



Look at $v_o(\infty)$

$$v_o(\infty) = 6 - 3e^{\frac{-0.35t}{\infty}} = 6 \text{ V}$$

From the eqt;

$$v_o(\infty) = \frac{24 \times 3}{R_2 + 3} = 6$$

$$72 = 6R_2 + 18$$

$$\boxed{R_2 = 9 \Omega}$$

Look at $v_o(0^-) = v_o(0^+)$

From the equation, $v_o(0^-) = 6 - 3e^{\frac{-0.35t}{0^-}} = 6$

$$v_o(0^-) = v_o(0^+) = 3 \text{ V}$$

but $v_o(0^-) = \left(\frac{24}{R_1 + R_2 + 3} \right) \times 3 = 3$

Tcat B

2

(2)

R_0

$$\frac{24}{R_1 + 9 + 3} = 1$$

$$24 = R_1 + 12$$

$$\boxed{R_1 = 12 \Omega}$$

$$\gamma = \frac{1}{.35} = \frac{L}{R_{eq}}$$

$$R_{eq} = R_2 + 3 = 9 + 3 = 12 \Omega$$

$$\gamma = 2.86 = \frac{L}{12}$$

$$\boxed{L = 12 \times 2.86 = 34.32 H}$$


" $R_1 = 12 \Omega$

$$R_2 = 9 \Omega$$

$$L = 34.32 H$$

(3) T3A & T3B

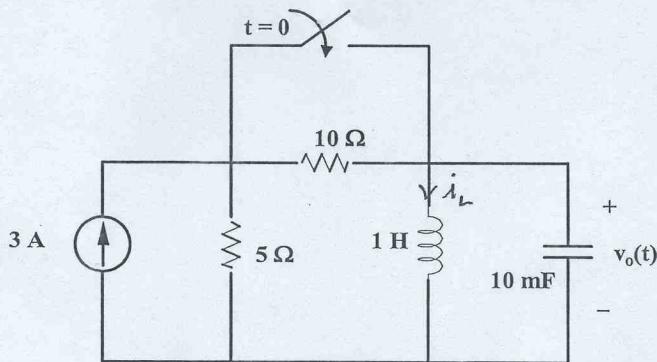(3) You are given the circuit of Figure 3. Determine the expression for the voltage $v_o(t)$.




For $t < 0$

$$i_L(0^+) = i_L(0^-) = \frac{3 \times 5}{10+5} = 1A$$

$$v_o(0^+) = v_o(0^-) = 0$$

For $t > 0$

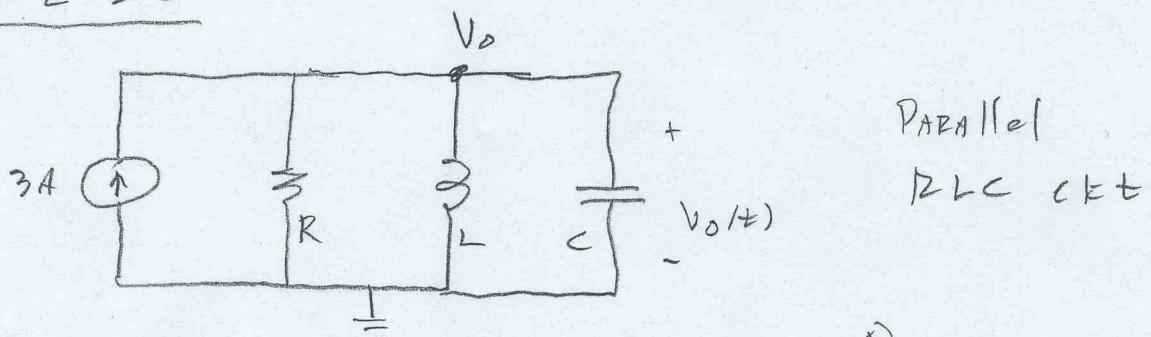

Using nodal:

$$\frac{V_o}{R} + C \frac{dV_o}{dt} + \frac{1}{L} \int_0^t V_o dt + 1 = 3 \quad (1)$$

Will need $\frac{dV_o(0^+)}{dt}$ in solving the D.E.

Go ahead and get it now from (1)

(13)

2

$$C \frac{dV(0^+)}{dt} = 3 - 1 - \frac{V_o(0^+)}{R}$$

$$\frac{dV(0^+)}{dt} = \frac{2}{C} = \frac{2}{10 \times 10^{-3}} = 200 \text{ V/s}$$

so;

$$V_o(0^+) = 0, \quad \frac{dV(0^+)}{dt} = 200 \text{ V/s} \quad (2)$$

Go to (1) and take $\frac{d(\cdot)}{dt}$, this gives

$$\frac{1}{R} \frac{dV_o}{dt} + C \frac{d^2 V_o}{dt^2} + \frac{V_o}{L} = 0$$

$$\frac{d^2 V_o}{dt^2} + \frac{1}{RC} \frac{dV_o}{dt} + \frac{V_o}{LC} = 0$$

Put in values;

$$\frac{d^2 V_o}{dt^2} + 20 \frac{dV_o}{dt} + 100 V_o = 0$$

$$s^2 + 20s + 100 = 0$$

$$(s+10)(s+10) = 0$$

$$V_o = (A + Bt)e^{-10t} \quad (3)$$

$$V_o(0) = A = 0$$

$$V_o(t=) = Bt e^{-10t}$$

$$\left. \frac{dV_o}{dt} \right|_{t=0} = 200 = \left[-10Bt e^{-10t} + Be^{-10t} \right]_{t=0}$$


$$B = 200$$

$$V_o(t) = 200t e^{-10t}$$

Ans

Test 3B

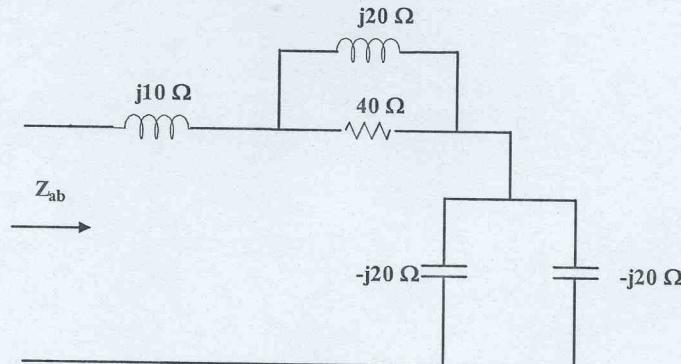- (4) You are given the circuit of Figure 4. Determine the impedance, Z_{ab} .



$$(-j20) \parallel (-j20) = \frac{(-j20)(-j20)}{-j20 - j20} = -j10$$


$-j10$ in series with $+j10 = 0$

so

$$Z_{ab} = 40 \parallel j20 = \frac{40(j20)}{40 + j20}$$

$$Z_{ab} = 8 + j16 = 17.89 \angle 63.43^\circ \Omega$$

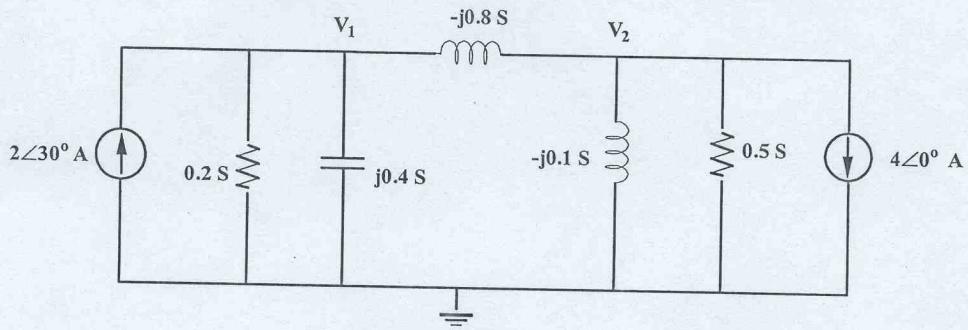- (5) You are given the circuit of Figure 5. Solve for the phasor voltages V_1 and V_2 . Express your answers in polar form. Note: The unit for the circuit parameters is given in Seiman (S).




By inspection

$$\begin{bmatrix} (0.2 - j0.4), & j0.8 \\ j0.8, & (0.5 - j0.1) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2\angle 30^\circ \\ -4\angle 0^\circ \end{bmatrix}$$

$$V_1 = 5.16 \angle 95.45^\circ \text{ V}$$

$$V_2 = 0.4 \angle 135^\circ \text{ V}$$

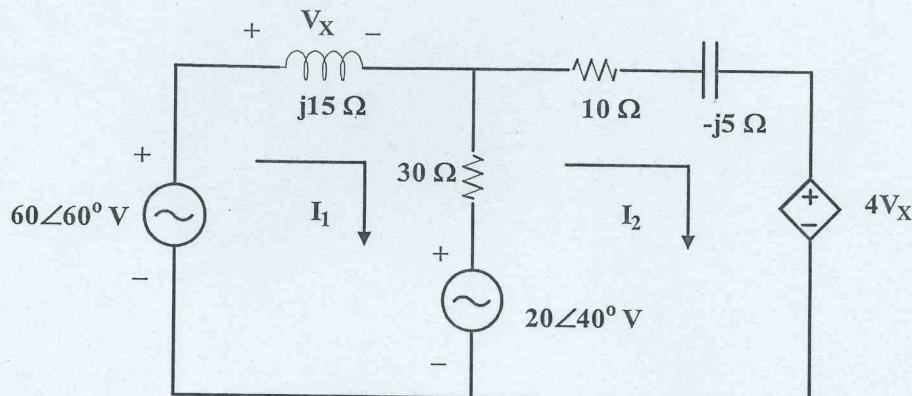- (6) Solve for the phasor currents I_1 and I_2 indicated in the circuit of Figure 6. Express your answers in polar form.



$$(30 + j15) \vec{I}_1 - 30 \vec{I}_2 = 60 \angle 60^\circ - 20 \angle 40^\circ$$

$$-30 \vec{I}_1 + (40 - j5) \vec{I}_2 = 20 \angle 40^\circ - 4V_x$$

$$= 20 \angle 40^\circ - 4(j15) \vec{I}_1$$

$$(-30 + j60) \vec{I}_1 + (40 - j5) \vec{I}_2 = 20 \angle 40^\circ$$

$$\begin{bmatrix} 30 + j15, & -30 \\ -30 + j60, & (40 - j5) \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 60 \angle 60^\circ - 20 \angle 40^\circ \\ 20 \angle 40^\circ \end{bmatrix}$$

$$\vec{I}_1 = 0.99 \angle -24.04^\circ A$$

$$\vec{I}_2 = 1.40 \angle -63.98^\circ A$$