
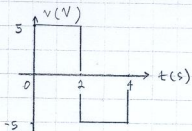


H. W. # 1
ECE 300
Spring, '07

B.S.

1.16

Given :

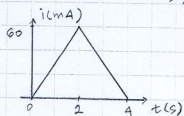


(a) sketch the power delivered to the device for $t > 0$

Solution :

$$i(t) = \begin{cases} 30t \text{ mA}, & 0 < t < 2 \\ (120 - 30t) \text{ mA}, & 2 < t < 4 \end{cases}$$

$$v(t) = \begin{cases} 5 \text{ V}, & 0 < t < 2 \\ -5, & 2 < t < 4 \end{cases}$$

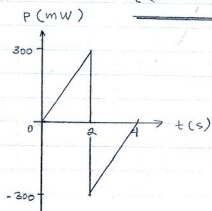
$$\Rightarrow p(t) = \begin{cases} 150t \text{ mW}, & 0 < t < 2 \\ (-600 + 150t) \text{ mW}, & 2 < t < 4 \end{cases}$$



(b). Total energy absorbed by the device:

$$W = \int_0^4 p \, dt = \underline{\underline{0 \text{ J}}}$$

2.9 Given :

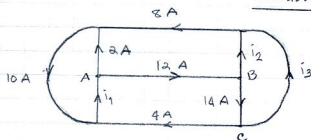

Solution: At node A:

$$12 + 2 = i_1 \quad \rightarrow \quad \underline{\underline{i_1 = 14 \text{ A}}}$$

At node B:


$$12 = i_2 + 14 \quad \rightarrow \quad \underline{\underline{i_2 = -2 \text{ A}}}$$

At node C:

$$14 = i_3 + 4 \quad \rightarrow \quad \underline{\underline{i_3 = 10 \text{ A}}}$$

Find i_1, i_2, i_3 .

2.02 Given :

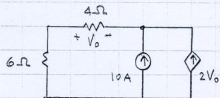

Find V_o and the power dissipated by the controlled source.

Solution :

At the node, KCL Requires that:

$$\frac{V_o}{4} + 10 + 2V_o = 0 \rightarrow \underline{V_o = -4.444 \text{ V}}$$


The current through the controlled source :

$$i = 2V_o = -8.888 \text{ A}$$

and the voltage across it :

$$\begin{aligned} V &= (6+4) i_o, \quad i_o = \frac{V_o}{4} = -1.111 \text{ A} \\ &= 10 \times (-1.111) \\ &= -11.111 \text{ V} \end{aligned}$$
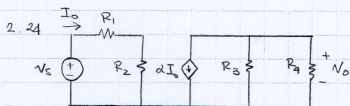
$$\begin{aligned} \therefore \text{POWER} &= (-8.888 \text{ A}) (-11.111 \text{ V}) \\ &= \underline{98.75 \text{ W}} \end{aligned}$$



Find $\frac{V_o}{V_s}$ in terms of α, R_1, R_2, R_3 and R_4

If $R_1 = R_2 = R_3 = R_4$, what value of α will produce $|\frac{V_o}{V_s}| = 10$?

Solution

$$(a) \quad I_o = \frac{V_s}{R_1 + R_2}$$


(b) If $R_1 = R_2 = R_3 = R_4$.

$$\begin{aligned} V_o &= -\alpha I_o (R_3 \parallel R_4) \\ &= -\alpha \frac{V_s}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4} \end{aligned}$$

$$\left| \frac{V_o}{V_s} \right| = \frac{\alpha}{2R} \cdot \frac{R}{2} = \frac{\alpha}{4} = 10 \rightarrow \underline{\alpha = 40}$$

$$\therefore \underline{\underline{\frac{V_o}{V_s} = \frac{-\alpha R_3 R_4}{(R_1 + R_2)(R_3 + R_4)}}}$$

2.21. Given:

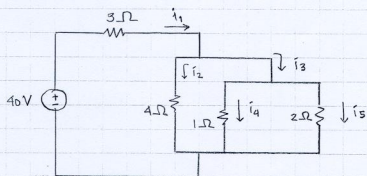

Determine i_1 to i_5

Solution

$$R_{eq} = 3 + 4 // 1 // 2 = 3 + \frac{1}{\frac{1}{4} + \frac{1}{1} + \frac{1}{2}} = 3.5714 \Omega$$

$$i_1 = \frac{40}{3.5714} = \underline{\underline{11.2 A}}$$

$$V_1 = 0.5714 i_1 = 6.4 V$$


$$i_2 = \frac{V_1}{4} = \underline{\underline{1.6 A}}$$

$$i_4 = \frac{V_1}{1} = \underline{\underline{6.4 A}}$$

$$i_5 = \frac{V_1}{2} = \underline{\underline{3.2 A}}$$

$$i_3 = i_4 + i_5 = \underline{\underline{9.6 A}}$$

2.35 Given:

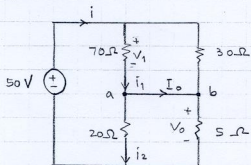

Solution:

Combining the resistors in parallel:

$$70 // 30 = \frac{70 \times 30}{70 + 30} = 21 \Omega$$

$$20 // 5 = \frac{20 \times 5}{20 + 5} = 4 \Omega$$

Calculate V_0 and I_0

$$i = \frac{90}{21+4} = 2 \text{ A}$$

$$V_1 = 21 i = 42 \text{ V}$$

$$V_0 = 4 i = \underline{8 \text{ V}}$$


$$i_1 = \frac{V_1}{70} = 0.6 \text{ A}$$

$$i_2 = \frac{V_0}{20} = 0.4 \text{ A}$$

At node a, KCL must be satisfied.

$$i_1 = i_2 + I_0 \rightarrow 0.6 = 0.4 + I_0 \rightarrow \underline{I_0 = 0.2 \text{ A}}$$

2.39 Evaluate R_{eq} .

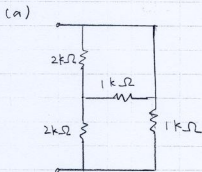

The top $2 \text{ k}\Omega$ is parallel with the first $1 \text{ k}\Omega$:


$$2 // 1 = \frac{2}{3} = 0.667 \text{ k}\Omega$$

The $0.667 \text{ k}\Omega$ is in series with the second $2 \text{ k}\Omega$ give

$$0.667 + 2 = 2.667 \text{ k}\Omega$$

The $2.667 \text{ k}\Omega$ is in parallel with the second $1 \text{ k}\Omega$
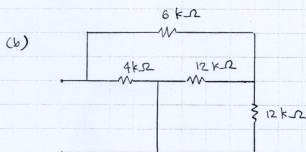
$$\therefore R_{eq} = \frac{2.667 \times 1}{3.667} = 0.7273 \text{ k}\Omega = \underline{727.3 \Omega}$$



The two $12 \text{ k}\Omega$ are in parallel

$$12 // 12 = 6 \text{ k}\Omega$$


The $6 \text{ k}\Omega$ is in series with the top $6 \text{ k}\Omega$

gives $6 + 6 = 12 \text{ k}\Omega$.

This $12 \text{ k}\Omega$ is in parallel with the $4 \text{ k}\Omega$

$$\therefore R_{eq} = \frac{12 \times 4}{16} = \underline{3 \text{ k}\Omega}$$


3.5

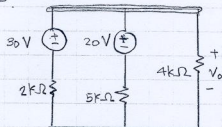Calculate V_o Solution

Applying KCL to the top node

$$\frac{30 - V_o}{2k} + \frac{20 - V_o}{5k} = \frac{V_o}{4k} \rightarrow \underline{V_o = 20V}$$


3.6

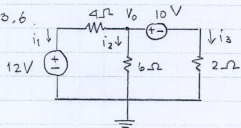Find V_o using nodal analysis.Solution

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_o - 12}{4} + \frac{V_o}{6} + \frac{V_o - 10}{2} = 0 \rightarrow \underline{V_o = 8.727V}$$

3.11

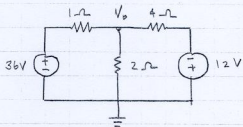Find V_o & power dissipated in all resistors.Solution:

At the top node, KVL gives


$$\frac{V_o - 36}{1} + \frac{V_o}{2} + \frac{V_o + 12}{4} = 0 \rightarrow \underline{V_o = 18.857V}$$

$$P_{1\Omega} = \frac{(36 - 18.857)^2}{1} = \underline{293.9W}$$

$$P_{2\Omega} = \frac{18.857^2}{2} = \underline{177.79W}$$

$$P_{4\Omega} = \frac{(18.857 + 12)^2}{4} = \underline{238W}$$

3.14.

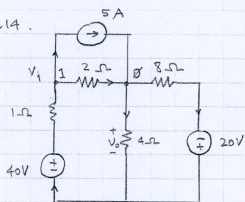Use nodal analysis to find V_o Solution

$$\text{At node 1: } \frac{V_1 - V_o}{2} + 5 = \frac{40 - V_1}{1} \longrightarrow 3V_1 - V_o = 70 \quad \text{--- (1)}$$

$$\text{At node } \phi: \frac{V_1 - V_o}{2} + 5 = \frac{V_o}{4} + \frac{V_o + 20}{8} \longrightarrow 4V_1 - 7V_o = -20 \quad \text{--- (2)}$$

$$\text{Solving (1) and (2) : } \underline{\underline{V_o = 20 \text{ V}}}$$