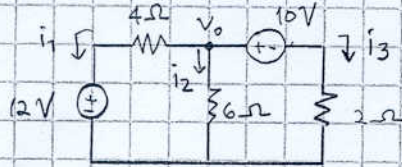


# HW #2 SOLUTION

ECE 300  
SPRING '07

# 3.6

GIVEN:



USE NODAL ANALYSIS TO OBTAIN  $V_0$


Solution:

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_0 - 12}{4} + \frac{V_0}{6} + \frac{V_0 - 10}{2} = 0 \implies V_0 = \underline{\underline{8.727 \text{ V}}}$$


# 3.8

GIVEN:

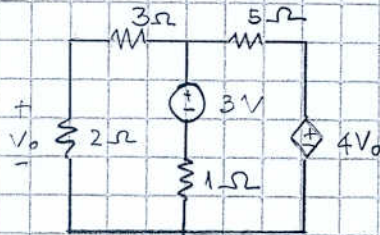

FIND  $V_0$  USING NODAL ANALYSIS.

Solution:

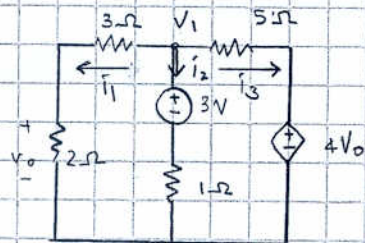

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_1}{3+2} + \frac{V_1-3}{1} + \frac{V_1-4V_0}{5} = 0$$

Also,  $\frac{V_0}{2} = \frac{V_1}{5} \implies V_0 = \frac{2}{5} V_1$

So,  $\frac{V_1}{5} + \frac{V_1-3}{1} + \frac{V_1 - \frac{8}{5} V_1}{5} = 0$

$$V_1 + 5V_1 - 15 + V_1 - \frac{8}{5} V_1 = 0$$

$$\frac{27}{5} V_1 = 15$$


$$V_1 = 2.778 \text{ V}$$

$$\implies V_0 = \underline{\underline{1.111 \text{ V}}}$$



# 3.12

Given :

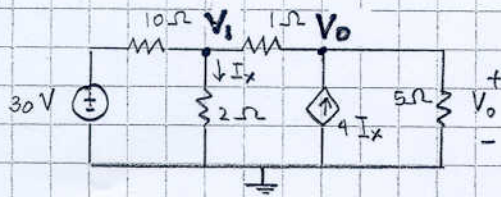

FIND  $V_0$  USING NODAL ANALYSIS

Solution :

$$\text{At node 1 : } \frac{V_1 - 30}{10} + \frac{V_1}{2} + \frac{V_1 - V_0}{1} = 0$$

$$16V_1 - 10V_0 = 30 \quad \text{--- ①}$$

$$\text{At NODE 2 : } \frac{V_0 - V_1}{1} - 4I_x + \frac{V_0}{5} = 0$$

$$-5V_1 + 6V_0 - 20I_x = 0 \quad \text{--- ②}$$


$$I_x = \frac{V_1}{2} \rightarrow \text{② : } -15V_1 + 6V_0 = 0$$

$$V_1 = 0.4V_0 \quad \text{--- ③}$$

$$\text{① \& ③ : } 16(0.4V_0) - 10V_0 = 30 \longrightarrow \underline{\underline{V_0 = -8.333 \text{ V}}}$$

# 3.23

Given :

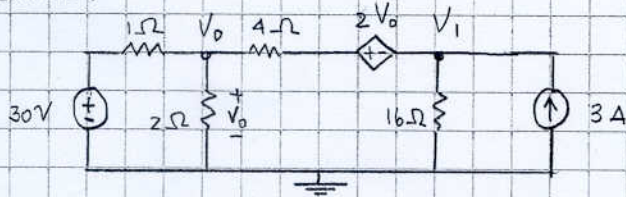

FIND  $V_0$  USING NODAL ANALYSIS

Solution :

$$\text{At NODE 0 : } \frac{V_0 - 30}{1} + \frac{V_0}{2} + \frac{V_0 - (2V_0 + V_1)}{4} = 0$$

$$1.25V_0 - 0.25V_1 = 30 \quad \text{--- ①}$$

$$\text{At NODE 1 : } \frac{(2V_0 + V_1) - V_0}{4} + \frac{V_1}{16} - 3 = 0$$

$$5V_1 + 4V_0 = 48 \quad \text{--- ②}$$


① & ② :

$$\underline{\underline{V_0 = 22.34 \text{ V}}}$$



# 3.38

Given:

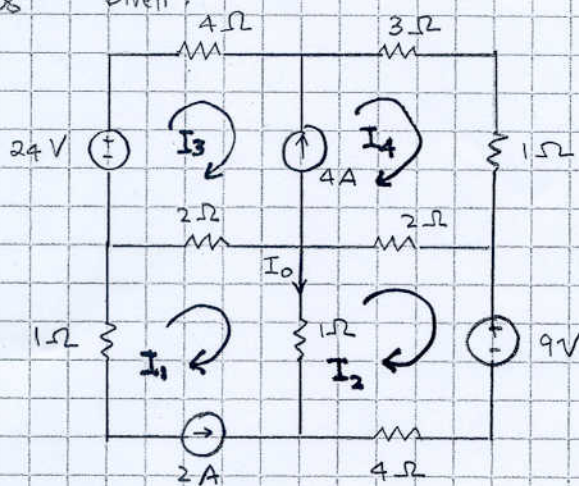FIND  $I_0$  USING MESH ANALYSIS

Solution:

$$\text{Mesh 1: } I_1 = -2 \text{ A} \quad \text{--- (1)}$$

$$\text{Mesh 2: } 1(I_2 - I_1) + 2(I_2 - I_4) + 9 + 4I_2 = 0$$

$$7I_2 - I_4 = -11 \quad \text{--- (2)}$$

$$\text{SUPER MESH: } -24 + 4I_3 + 3I_4 + 1I_4 + 2(I_4 - I_2) + 2(I_3 - I_1) = 0$$

$$-2I_2 + 6I_3 + 6I_4 = 20 \quad \text{--- (3)}$$

Constraint Equation:

$$-I_3 + I_4 = 4$$

Solving the unknowns:

$$\begin{bmatrix} 7 & 0 & -1 \\ -2 & 6 & 6 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -11 \\ 20 \\ 4 \end{bmatrix}$$

$$\text{USING MATLAB, WE FOUND } I_2 = -0.55$$

$$I_3 = -4$$

$$I_4 = 7.15$$

$$\text{So, } I_0 = I_1 - I_2 = -2 - (-0.55)$$

$$\underline{\underline{I_0 = -1.45 \text{ A}}}$$


Checking the SUPER MESH (3):

$$1.1 - 24 + 42.9 \checkmark = 20$$



# 3.39

Given

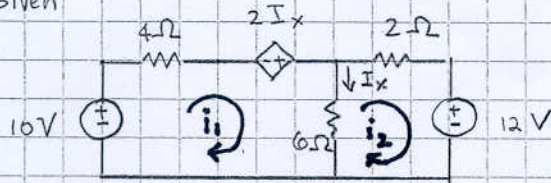

FIND  $i_1$  AND  $i_2$

Solution :

$$\begin{aligned} \text{Mesh 1 : } & -10 + 4I_1 - 2I_x + 6(I_1 - I_2) = 0 \\ & -10 + 10I_1 - 2I_x - 6I_2 = 0 \end{aligned}$$

$$I_x = I_1 - I_2 ;$$


$$\begin{aligned} 10 &= -2I_1 + 2I_2 + 10I_1 - 6I_2 \\ 5 &= 4I_1 - 2I_2 \quad \text{--- ①} \end{aligned}$$

$$\begin{aligned} \text{Mesh 2 : } & 12 + 8I_2 - 6I_1 = 0 \\ & 6 = 3I_1 - 4I_2 \quad \text{--- ②} \end{aligned}$$

$$\text{Solving ① \& ② : } \begin{aligned} I_1 &= 0.8 \text{ A} \\ I_2 &= -0.9 \text{ A} \end{aligned}$$

# 3.50

GIVEN :

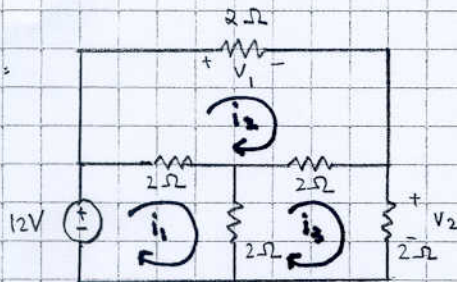

FIND  $V_1$  \&  $V_2$

$$\begin{aligned} \text{Loop 1 : } & 2(i_1 - i_2) + 2(i_1 - i_3) = 12 \\ & 4i_1 - 2i_2 - 2i_3 = 12 \\ & 2i_1 - i_2 - i_3 = 6 \quad \text{--- ①} \end{aligned}$$

$$\begin{aligned} \text{Loop 2 : } & 2(i_2 - i_1) + 2i_2 + 2(i_2 - i_3) = 0 \\ & -2i_1 + 6i_2 - 2i_3 = 0 \\ & -i_1 + 3i_2 - i_3 = 0 \quad \text{--- ②} \end{aligned}$$



$$\begin{aligned} \text{Loop 3: } 2(i_3 - i_1) + 2(i_3 - i_2) + 2i_3 &= 0 \\ -2i_1 - 2i_2 + 6i_3 &= 0 \\ -i_1 - i_2 + 3i_3 &= 0 \quad \text{--- (3)} \end{aligned}$$

From (1), (2), & (3) in MATRIX FORM:

$$\begin{bmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned} \text{We found } i_1 &= 6 \text{ A} \\ i_2 &= 3 \text{ A} \\ i_3 &= 3 \text{ A} \end{aligned}$$


Thus,

$$V_1 = 2i_2 = \underline{\underline{6 \text{ V}}}$$

$$V_2 = 2i_3 = \underline{\underline{6 \text{ V}}}$$

# 3.60

Given:

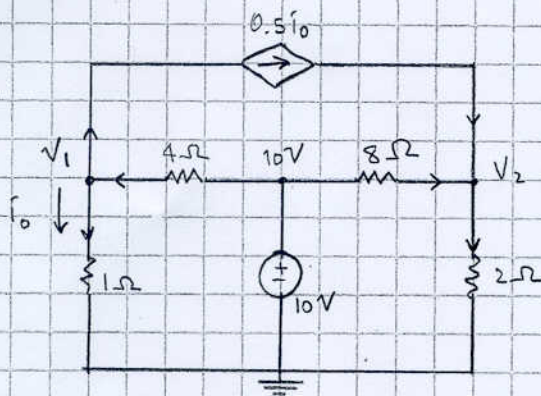

Calculate the power dissipated in each resistor.

$$i_0 = \frac{V_1}{1}$$

Solution:

$$\text{At NODE 1: } \frac{V_1}{1} + 0.5 \frac{V_1}{1} - \frac{V_1 - 10}{4} = 0 \quad \longrightarrow \quad V_1 = \frac{10}{7}$$

$$\text{At NODE 2: } \frac{V_2}{2} - \frac{10 - V_2}{8} - 0.5 \frac{V_1}{1} = 0 \quad \longrightarrow \quad V_2 = \frac{22}{7}$$

$$P_{1\Omega} = \frac{(V_1)^2}{1} = \underline{\underline{2.041 \text{ WATTS}}}$$

$$P_{4\Omega} = \frac{(10 - V_1)^2}{4} = \underline{\underline{18.38 \text{ WATTS}}}$$


$$P_{2\Omega} = \frac{(V_2)^2}{2} = \underline{\underline{4.939 \text{ WATTS}}}$$

$$P_{8\Omega} = \frac{(10 - V_2)^2}{8} = \underline{\underline{5.88 \text{ WATTS}}}$$



# 3.68

Given.

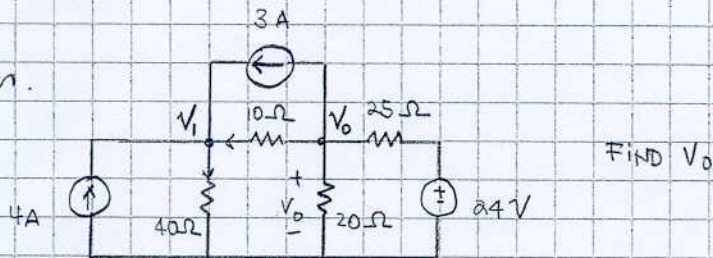

Solution.

At NODE 1 :  $\frac{V_1}{40} - \frac{V_0 - V_1}{10} - 4 - 3 = 0$

$$\frac{V_1}{40} - \frac{V_0 - V_1}{10} = 7$$

$$V_1 - 4(V_0 - V_1) = 280$$

$$-4V_0 + 5V_1 = 280 \quad \text{--- (1)}$$

At NODE 0 :  $\frac{V_0}{20} + \frac{V_0 - 24}{25} + \frac{V_0 - V_1}{10} + 3 = 0$

$$5V_0 + 4(V_0 - 24) + 10(V_0 - V_1) = -300$$


$$19V_0 - 10V_1 = -204 \quad \text{--- (2)}$$

Solve (1) & (2) :

$$V_0 = 32.36 \text{ V}$$

$$V_1 = 81.89 \text{ V}$$

# 3.84 Given :

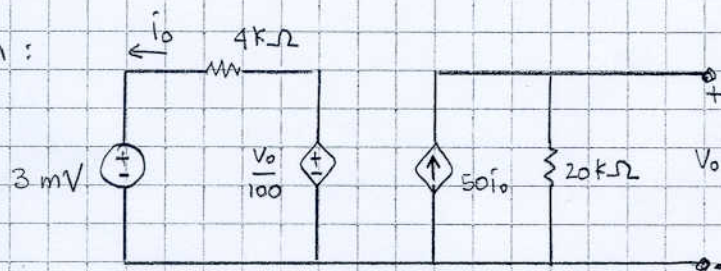

Calculate  $V_0$  &  $i_0$

Solution :

From output loop :  $V_0 = 50i_0 \times 20 \times 10^3 = 10^6 i_0 \quad \text{--- (1)}$

From input Loop :  $3 \times 10^{-3} + 4 \times 10^3 i_0 - \frac{V_0}{100} = 0 \quad \text{--- (2)}$

Solving (1) & (2) we get  $i_0 = 0.5 \text{ mA}$  AND  $V_0 = 0.5 \text{ V}$