

Desk copy

ECE 300  
Spring Semester, 2007  
HW Set #5

Due: February 22, 2007: Version 2  
wlg

Name wlg  
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

5.7 Ans:  $V_0 = -10\text{mV}$ ,  $V_d = 100\text{ nV}$

5.10 Ans  $\frac{V_o}{V_s} = 2$

5.14 Ans:  $V_o = -2.5\text{ V}$

5.15 Ans: (a)  $\frac{V_o}{i_s} = -\left[ R_1 + R_3 + \frac{R_1 R_3}{R_2} \right]$ , (b)  $\frac{V_o}{i_s} = -92\text{ k}\Omega$

5.23 Ans:  $\frac{V_o}{V_s} = \frac{-R_f}{R_i}$

5.30 Ans:  $i_x = 10\text{ }\mu\text{A}$ ,  $P = 2\text{ }\mu\text{W}$

5.32 Ans:  $i_x = 600\text{ nA}$ ,  $V_o = 12\text{ mV}$ ,  $P = 2.4\text{ nW}$


5.58 Ans:  $V_o = -2.738\text{ V}$   $i_o = 0.6848\text{ mA}$

5.58XX Simulate 5.58 with pspice and verify  $i_o$ . Use the  $\mu\text{A741}$  op amp

N.W. #5  
ECE 300  
Spring '07

Wly

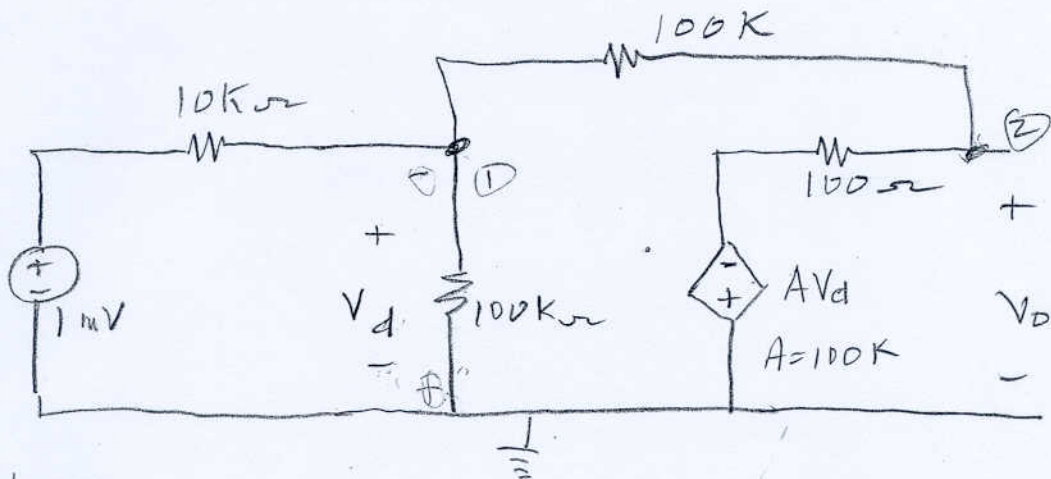5.7 Redraw the circuit in the text using the op amp model.



At ①

$$\frac{V_d - 1 \times 10^{-3}}{10 \text{K}} + \frac{V_d}{100 \text{K}} + \frac{V_d - V_o}{100 \text{K}} = 0$$

$$10 V_d - 10 \times 10^{-3} + V_d + V_d - V_o = 0$$

$$\boxed{12 V_d - V_o = 10 \times 10^{-3}} \quad (1)$$

At ②

$$\frac{V_o - V_d}{100 \text{K}} + \frac{V_o + 100 \text{K} V_d}{100} = 0$$

$$V_o - V_d + 1000 V_o + 100 \times 10^6 V_d = 0$$

$$\boxed{100 \times 10^6 V_d + 1001 V_o = 0} \quad (2) \quad \text{solve (1) \& (2)}$$


$$\underline{V_d = 100 \text{ nV}}$$

$$V_o = -.00999987 \text{ V}$$

$$\underline{V_o \approx -10 \text{ mV}}$$

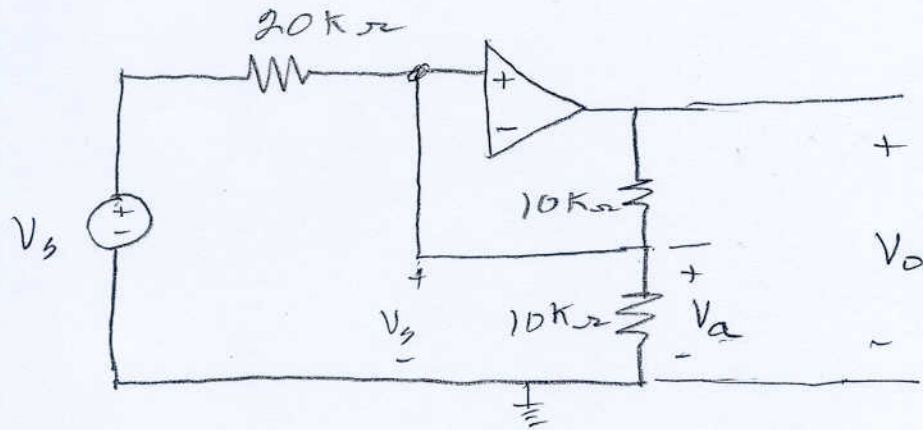5.10

FIND  $\frac{V_o}{V_s}$  for the following  
OP-AMP circuit.



$$V_a = \frac{V_o \times 10\text{K}}{10\text{K} + 10\text{K}} = \frac{V_o}{2}$$


but  $V_a = V_s$

$\therefore$

$$V_s = \frac{V_o}{2}$$

$$\boxed{\frac{V_o}{V_s} = 2}$$

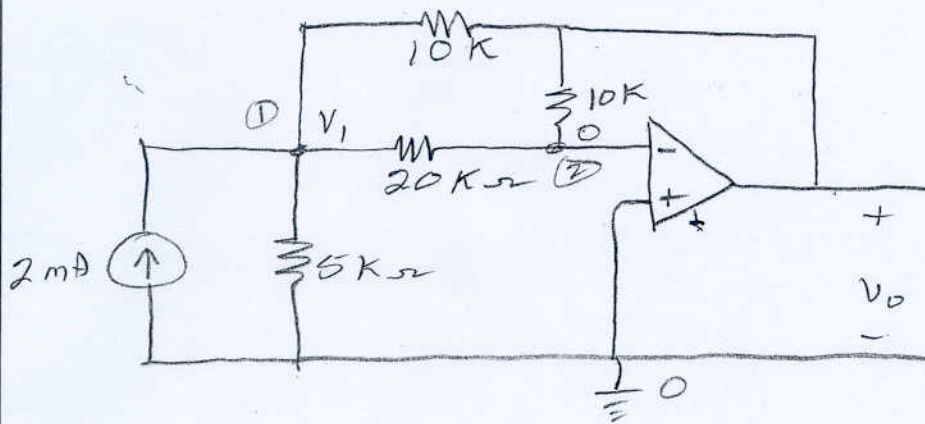5.14 Determine  $V_o$  for the following op-Amp circuit.



At ①

$$\frac{V_1}{5K} + \frac{V_1 - V_o}{10K} + \frac{V_1 - 0}{20K} = 2 \times 10^{-3}$$

$$4V_1 + 2V_1 - 2V_o + V_1 = 40$$

$$7V_1 - 2V_o = 40$$

At ②

$$\frac{0 - V_1}{20K} + \frac{0 - V_o}{10K} = 0$$

$$-V_1 - 2V_o = 0$$

$$V_1 = 5V \quad V_o = -2.5V$$


$$V_o = -2.5V$$

5.15 For the following op-amp configuration

(a) determine  $V_o/i_s$

(b) evaluate the ratio for  $R_1 = 20k\Omega$

$R_2 = 25k\Omega$ ,  $R_3 = 40k\Omega$

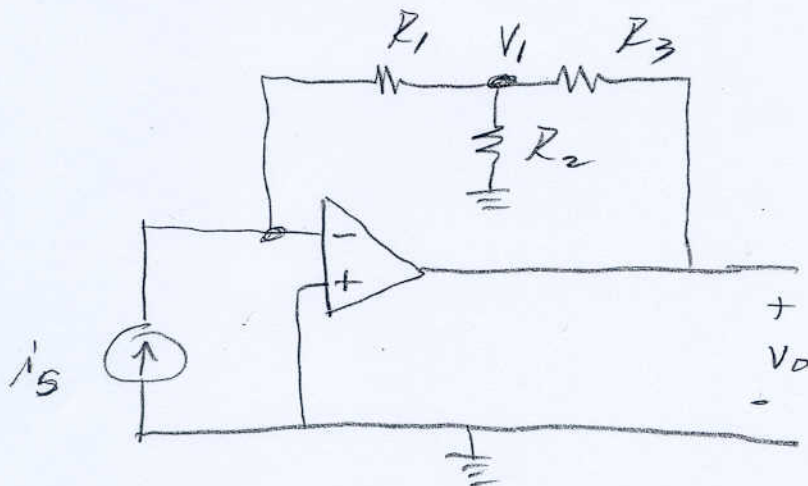

$$-i_s + \frac{V_1}{R_2} + \frac{V_1 - V_o}{R_3} = 0$$

$$\text{but } i_s = -\frac{V_1}{R_1} \quad \text{OR} \quad V_1 = -i_s R_1$$

so

$$-i_s - \frac{i_s R_1}{R_2} - \frac{i_s R_1 - V_o}{R_3} = 0$$

$$-i_s \left[ 1 + \frac{R_1}{R_2} + \frac{R_1}{R_3} \right] = \frac{V_o}{R_3}$$

$$-i_s \left[ R_3 + \frac{R_1 R_3}{R_2} + R_1 \right] = V_o$$

5.15 cont


2

$$\frac{V_o}{i_s} = - \left[ R_1 + R_3 + \frac{R_1 R_3}{R_2} \right]$$

$$= - \left[ 20K + 40K + \frac{(40K)(20K)}{25K} \right]$$

$$\frac{V_o}{i_s} = -92K \Omega$$

5.23

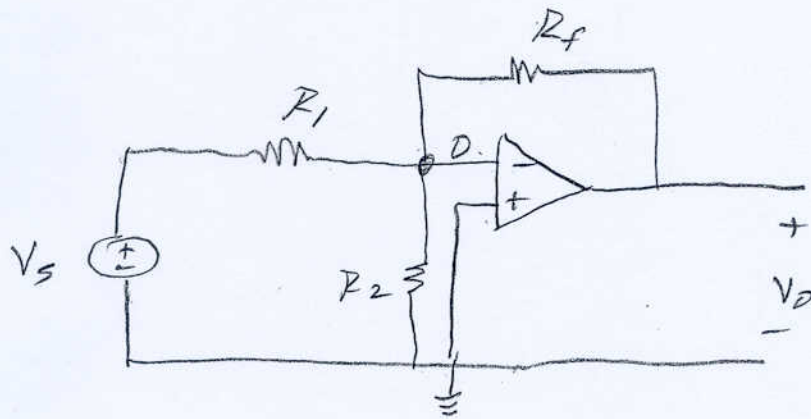FIND the voltage gain for  $\frac{V_o}{V_s}$ .


$$\frac{0 - V_s}{R_1} + \frac{0 - V_o}{R_f} + \frac{0}{R_2} = 0$$

$$-\frac{V_s}{R_1} - \frac{V_o}{R_f} = 0$$

$$\frac{V_o}{V_s} = -\frac{R_f}{R_1}$$

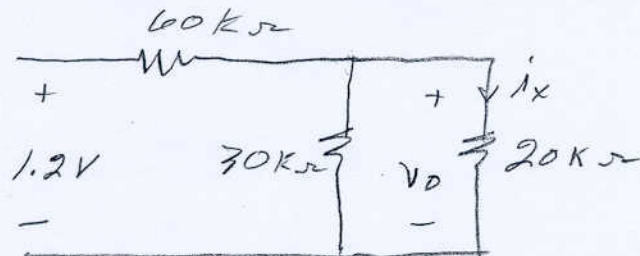5.30

Circuit is arranged as a voltage follower. This means it is necessary to analyze the following



$$V_D = \frac{1.2 \times 12K}{60K + 12K}$$

$$30K \parallel 20K = 12K \Omega$$

$$V_D = 0.2V$$

$$i_x = \frac{V_D}{20K} = \frac{0.2}{20} \times 10^{-3}$$


$$i_x = 10 \times 10^{-6} A = 10 \mu A$$

$$P_{20K} = \frac{V_D^2}{20K} = \frac{(0.2)^2}{20K} = 2 \times 10^{-6} W$$

$$P_{20K} = 2 \mu W$$



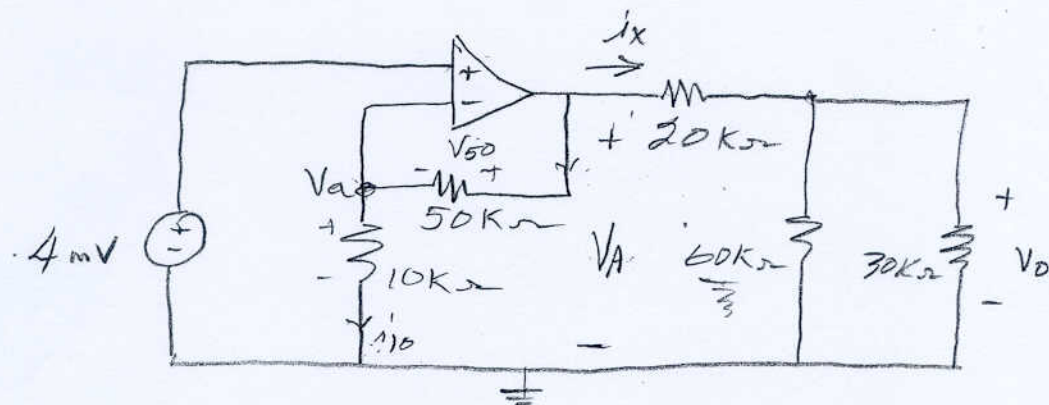5.32 Calculate  $i_x$  and  $V_o$  in the circuit below. Also find the power dissipated in the  $60\text{-k}\Omega$  resistor.



$$V_a = 4\text{ mV}$$

$$i_{10} = \frac{4 \times 10^{-3}}{10 \times 10^3} = .4 \times 10^{-6}\text{ A}$$

$$V_A = (4 \times 10^{-6})(50 \times 10^3) + 4 \times 10^{-3}$$

$$V_A = 20 \times 10^{-3} + 4 \times 10^{-3}$$

$$V_A = 24\text{ mV}$$


$$30\text{ k}\Omega \parallel 60\text{ k}\Omega = 20\text{ k}\Omega$$

$$V_o = \frac{V_A \times 20\text{ k}\Omega}{20\text{ k}\Omega + 20\text{ k}\Omega} = 12\text{ mV}$$

$$i_x = \frac{V_A}{40\text{ k}\Omega} = 600\text{ nV}$$

$$P_{60\text{ k}\Omega} = \frac{V_o^2}{60\text{ k}\Omega} = \frac{(0.012)^2}{60\text{ k}\Omega} = 2.4\text{ nW}$$

5.54

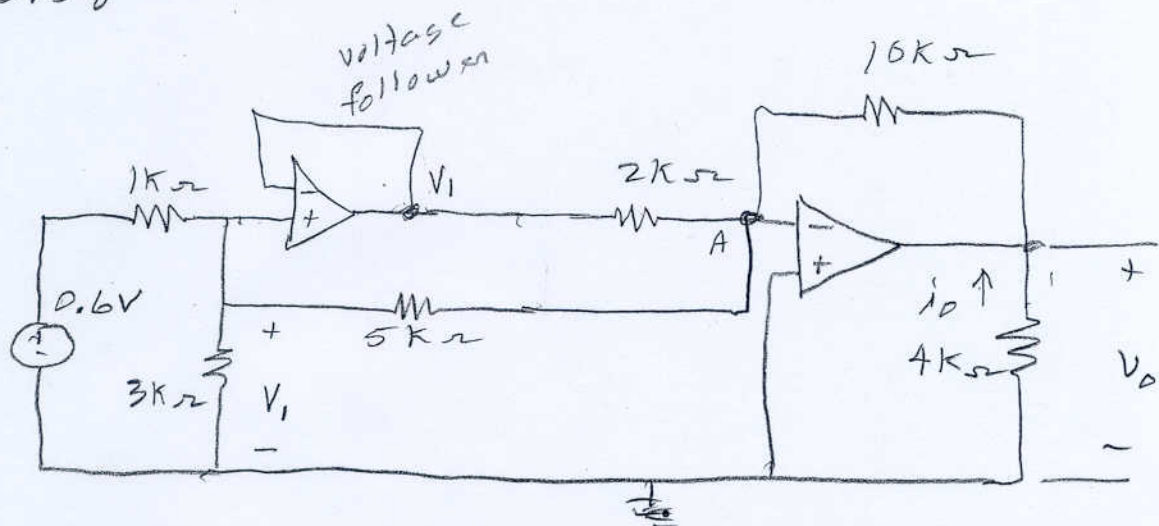

Point A is at ground. Therefore

$$V_1 = \frac{0.6 \times 3k \parallel 5k}{1k + 3k \parallel 5k} = \frac{0.6 \times 1.875k}{2.875k}$$

$$V_1 = 0.3913 \text{ V}$$


$\therefore$

$$V_0 = - \left( \frac{10k}{2k} + \frac{10k}{5k} \right) V_1$$

$$V_0 = -2.739 \text{ V}$$

$$i_0 = \frac{-V_0}{4k} = \frac{2.739}{4k}$$

$$i_0 = 684.8 \mu\text{A}$$

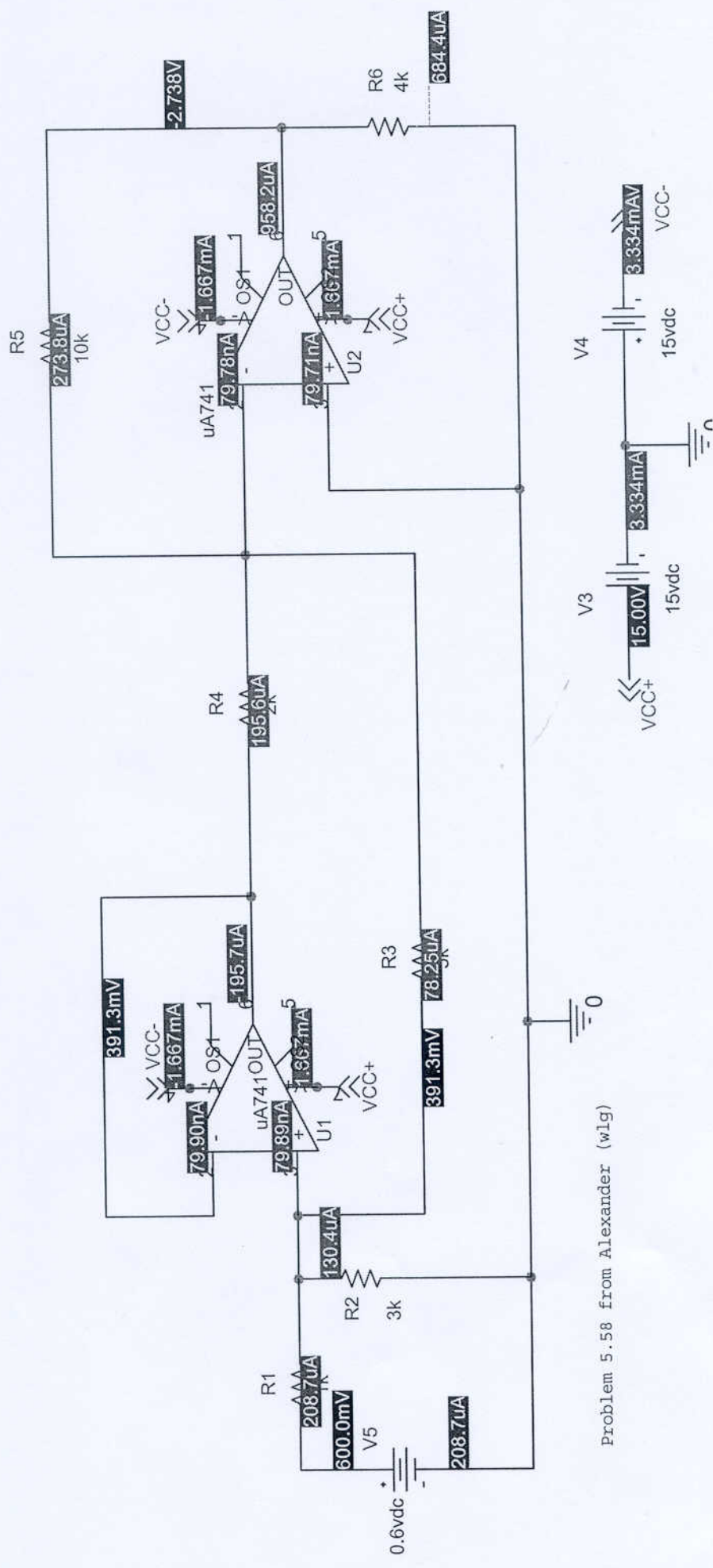

Problem 5.58 from Alexander (wlg)