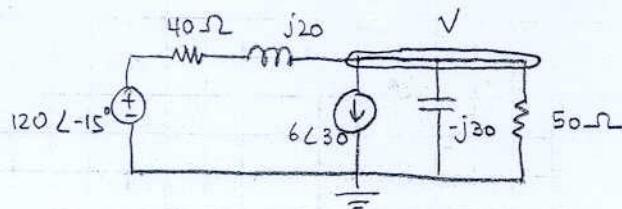


4/17/2007

HW #11 Solution

10.7




FIND V using Nodal analysis

$$\frac{V - (120 \angle -15^\circ)}{40 + j20} + 6 \angle 30^\circ + \frac{V}{50} + \frac{V}{-j30} = 0$$

$$\begin{aligned} \frac{V}{40 + j20} + \frac{V}{50} + \frac{V}{-j30} &= -6 \angle 30^\circ + \frac{120 \angle -15^\circ}{40 + j20} \\ &= -3.2 - j4.78 \\ &= 5.75 \angle -123.80^\circ \end{aligned}$$

$$\begin{aligned} V &= -111.7 - j59.34 \\ &= 124.22 \angle -154.06^\circ \text{ V} \end{aligned}$$

10.15

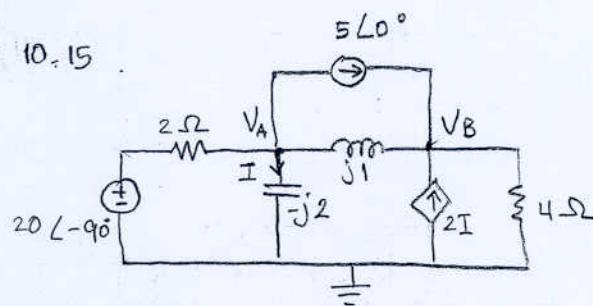

FIND I using nodal analysis

$$\text{NODE A : } \frac{V_A - (20L - 90^\circ)}{2} + 5L 0^\circ + \frac{V_A}{j2} + \frac{V_A - V_B}{j1} = 0$$

$$\frac{V_A}{2} + \frac{V_A}{j2} + \frac{V_A}{j1} - \frac{V_B}{j1} = -5L 0^\circ + 10L -90^\circ$$

$$\left(\frac{1}{2} - j\frac{1}{2}\right)V_A + jV_B = -5 - j10 \quad \text{--- ①}$$

$$\text{NODE B : } \frac{V_B}{4} - 2I - 5L 0^\circ + \frac{V_B - V_A}{j1} = 0 \quad \text{but } I = \frac{V_A}{j2}$$

$$\frac{V_B}{4} - 2 \frac{V_A}{j2} + \frac{V_B}{j1} - \frac{V_A}{j1} = 5L 0^\circ$$

$$\left(\frac{1}{4} - j\right)V_B = 5L 0^\circ \quad \text{--- ②}$$

Solving for egn ① & ② :


$$\begin{bmatrix} \frac{1}{2} - j\frac{1}{2} & j \\ 0 & \frac{1}{4} - j \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} -5 - j10 \\ 5 \end{bmatrix}$$

$$V_A = 10.88 - j11.47$$

$$V_B = 1.18 + j4.7$$

$$\therefore I = \frac{V_A}{j2} = 7.90 L 43.49^\circ A$$

10.19

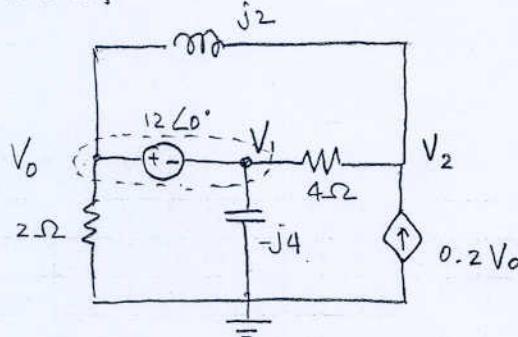

FIND V_0 using nodal analysis.

$$\text{At supernode: } \frac{V_0}{2} + \frac{V_0 - V_2}{j2} + \frac{V_1 - V_2}{4} + \frac{V_1}{-j4} = 0$$

$$\frac{V_0}{2} + \frac{V_0}{j2} + \frac{V_1}{4} + \frac{V_1}{-j4} - \frac{V_2}{j2} - \frac{V_2}{4} = 0$$

$$(\frac{1}{2} - j\frac{1}{2})V_0 + (\frac{1}{4} + j\frac{1}{4})V_1 + (-\frac{1}{4} + j\frac{1}{2})V_2 = 0 \quad \textcircled{1}$$

$$\text{At node } V_2: -0.2V_0 + \frac{V_2 - V_1}{4} + \frac{V_2 - V_0}{j2} = 0$$

$$-\frac{1}{5}V_0 - \frac{V_0}{j2} - \frac{V_1}{4} + \frac{V_2}{4} + \frac{V_2}{j2} = 0$$

$$(-\frac{1}{5} + j\frac{1}{2})V_0 - \frac{1}{4}V_1 + (\frac{1}{4} - j\frac{1}{2})V_2 = 0 \quad \textcircled{2}$$

Also,

$$V_0 - V_1 = 12 \quad \textcircled{3}$$

Solving for $\textcircled{1}, \textcircled{2}, \frac{1}{2}\textcircled{3}$:

$$\begin{bmatrix} \frac{1}{2} - j\frac{1}{2} & \frac{1}{4} + j\frac{1}{4} & -\frac{1}{4} + j\frac{1}{2} \\ -\frac{1}{5} + j\frac{1}{2} & -\frac{1}{4} & \frac{1}{4} - j\frac{1}{2} \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 12 \end{bmatrix}$$


#10, 19 cont'd

$$V_0 = 4.91 + j5.9 = \underline{\underline{7.682 \angle 50.19^\circ V}}$$

$$V_1 = -7.08 + j5.9 = 9.22 \angle 140.2^\circ$$

$$V_2 = 1.42 + j3.62 = 3.89 \angle 68.58^\circ$$

#10, 28

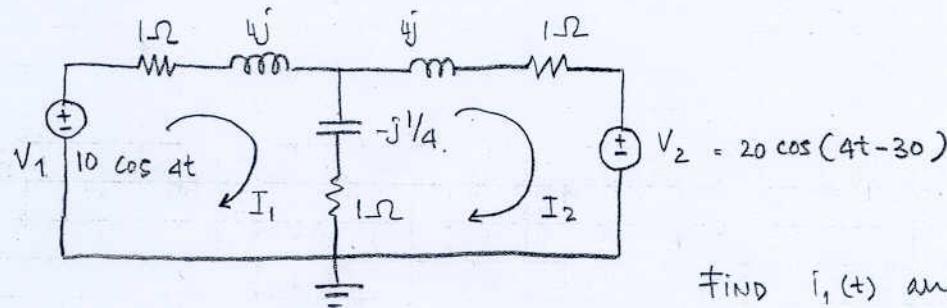

FIND $i_1(t)$ and $i_2(t)$

$$\omega = 4.$$

$$\text{Mesh 1: } -10 \angle 0^\circ + (1+4j)I_1 + (1-j/4)(I_1 - I_2) = 0$$

$$(1+4j)I_1 + (1-j/4)I_1 + (-1+j/4)I_2 = 10 \angle 0^\circ$$

$$(2+j3.75)I_1 + (-1+j0.25)I_2 = 10 \angle 0^\circ \quad \textcircled{1}$$

$$\text{Mesh 2: } 20 \angle -30^\circ + (1-j/4)(I_2 - I_1) + (1+4j)I_2 = 0$$

$$(-1+j/4)I_1 + (2+j3.75)I_2 = -20 \angle -30^\circ \quad \textcircled{2}$$


Solving FOR $\textcircled{1} \& \textcircled{2}$:

$$\begin{bmatrix} 2+j3.75 & -1+j0.25 \\ -1+j0.25 & 2+j3.75 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ -20 \angle -30^\circ \end{bmatrix}$$

$$I_1 = 2.74 \angle -41.07^\circ \rightarrow i_1(t) = 2.74 \cos(4t - 41.07^\circ) A$$

$$I_2 = 4.11 \angle 92^\circ \rightarrow i_2(t) = 4.11 \cos(4t + 92^\circ) A$$

10.33

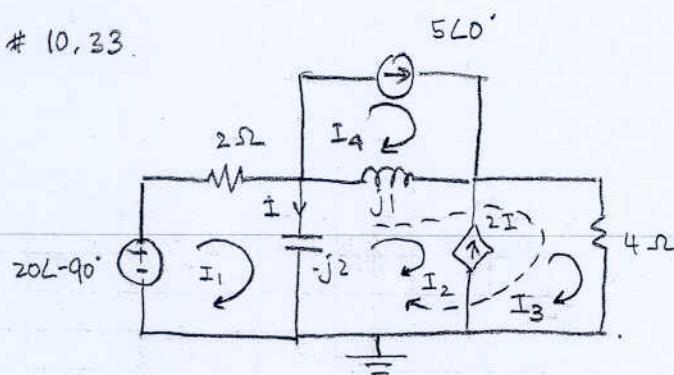

FIND I using Mesh analysis.

$$\text{Mesh 1 : } -20\angle-90^\circ + 2I_1 - j_2(I_4 - I_2) = 0$$

$$(2 - j_2)I_1 + j_2(I_2) = 20 \angle-90^\circ \quad \text{--- (1)}$$

SUPERNESH :

$$j_1(I_2 - I_4) + 4I_3 - j_2(I_2 - I_1) = 0 \quad \text{but } I_4 = 5$$

$$j_1(I_2 - 5) + 4I_3 - j_2(I_2 - I_1) = 0$$

$$j_2I_1 + (-j_1)I_2 + 4I_3 = j_5 \quad \text{--- (2)}$$

Constraint :

$$I_2 - I_3 = -2I \quad \text{AND} \quad I = I_1 - I_2 \\ = -2(I_1 - I_2)$$

$$\Rightarrow 2I_1 - I_2 - I_3 = 0 \quad \text{--- (3)}$$

SOLVING for ①, ②, & ③ :

$$\begin{bmatrix} 2 - j_2 & j_2 & 0 \\ j_2 & -j_1 & 4 \\ 2 & -1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 20 \angle-90^\circ \\ j_5 \\ 0 \end{bmatrix}$$


$$I_1 = 6.91 \angle -141.9^\circ$$

$$I_2 = 14.8 \angle -139^\circ$$

$$I_3 = 1.21 \angle 76^\circ$$

$$\therefore I = I_1 - I_2 = 7.9 \angle 43.49^\circ \text{ A}$$

10.39

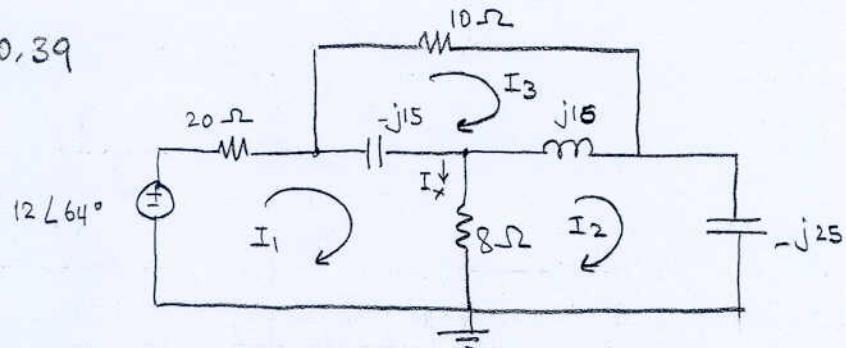

FIND All I's

$$\text{Mesh 1 : } -12\angle 64^\circ + 20 I_1 - j15 (I_1 - I_3) + 8 (I_1 - I_2) = 0$$

$$(28 - j15) I_1 - 8 I_2 + j15 I_3 = 12\angle 64^\circ \quad \text{--- (1)}$$

$$\text{Mesh 2 : } 8 (I_2 - I_1) + j16 (I_2 - I_3) - j25 I_2 = 0$$

$$-8 I_1 + (8 - j9) I_2 - j16 I_3 = 0 \quad \text{--- (2)}$$

$$\text{Mesh 3 : } -j15 (I_3 - I_1) + 10 I_3 + j16 (I_3 - I_2) = 0$$

$$j15 I_1 - j16 I_2 + (10 + j) I_3 = 0 \quad \text{--- (3)}$$

Solving eqn (1), (2) & (3) :

$$\begin{bmatrix} 28 - j15 & -8 & j15 \\ -8 & 8 - j9 & -j16 \\ j15 & -j16 & 10 + j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12\angle 64^\circ \\ 0 \\ 0 \end{bmatrix}$$


$$I_1 = 0.38 \angle 109.6^\circ$$

$$I_2 = 0.344 \angle 124.4^\circ$$

$$I_3 = 8.145 \angle -60.42^\circ$$

$$I_x = I_1 - I_2 = 0.1 \angle 48.5^\circ$$


H10, 50

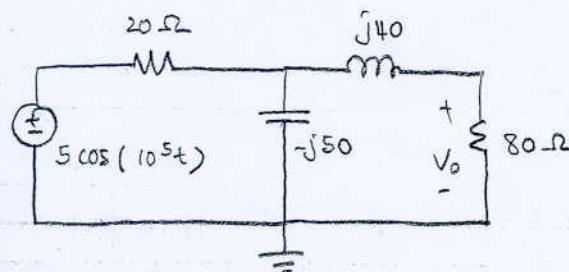

$$\omega = 10^5$$

FIND V_o USING SOURCE TRANSFORMATION.



(i)

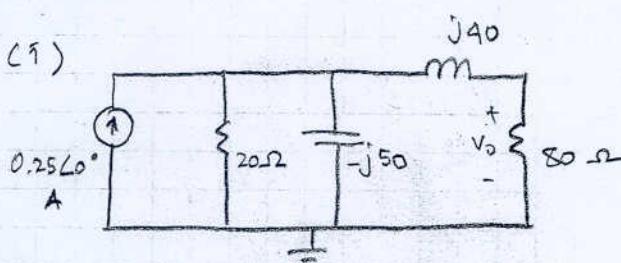

Let :

$$z_1 = 20 // -j50 = \frac{(20)(-j50)}{20 - j50} = 17.24 - j6.9$$

(ii)

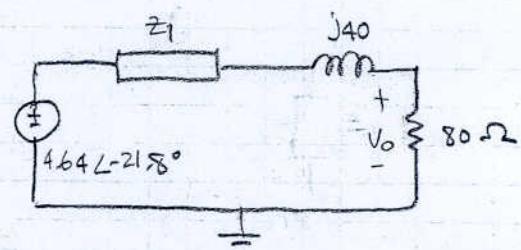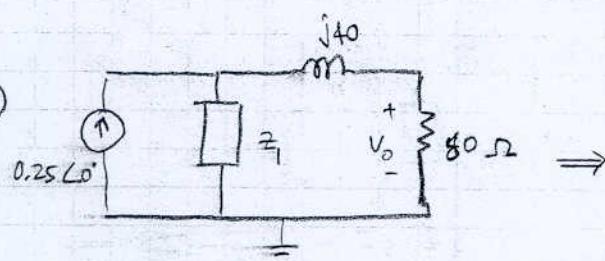

$$V_s = (0.25 \angle 0^\circ)(17.24 - j6.9)$$

$$= 4.31 - j1.72$$


$$= 4.64 \angle -21.8^\circ \text{ V}$$

(iii) USING VOLTAGE DIVISION :

$$V_o = (4.64 \angle -21.8^\circ) \frac{80}{80 + j40 + (17.24 - j6.9)}$$

$$\Rightarrow V_o = \underline{3.615 \angle -40.6^\circ \text{ V}} \Rightarrow V_o(t) = 3.615 \cos(10^5 t - 40.6^\circ) \text{ V}$$

10, 56 (a)

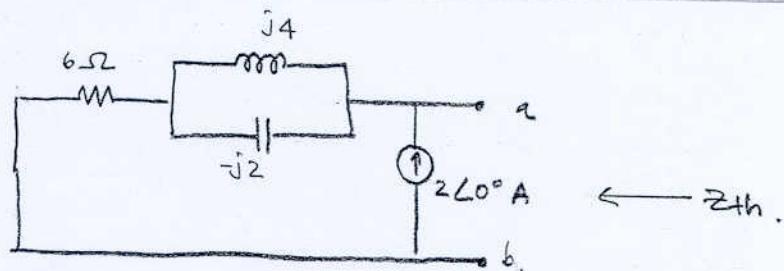

$$\begin{aligned} z_{TH} &= 6 + (j4// -j2) \\ &= 6 + \frac{(j4)(-j2)}{j4 - j2} \\ &= 6 + \frac{8}{j2} = 6 - j4 = 7.211 \angle -33.68^\circ \Omega \end{aligned}$$


By placing a short circuit at terminal a-b,

$$I_N = 2\angle 0^\circ A$$

$$\therefore V_{TH} = z_{TH} \cdot I_N = (7.211 \angle -33.68^\circ)(2\angle 0^\circ)$$

$$\underline{\underline{V_{TH} = 14.42 \angle -33.69^\circ V}}$$

10.61.

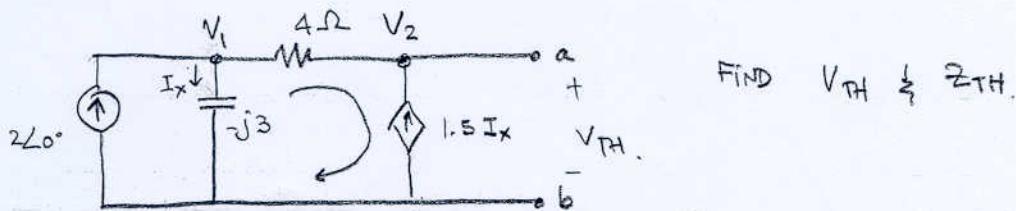

FIND $V_{TH} \neq Z_{TH}$.

(i) to find V_{TH} .

At node V_1 , using KCL:

$$-2 + I_x - 1.5 I_x = 0$$

$$-0.5 I_x = 2$$

$$I_x = -4A$$

then. we apply KVL:


$$-I_x(-j3) - 1.5 I_x(4) + V_{TH} = 0$$

$$V_{TH} = I_x(-j3) + 1.5 I_x(4)$$

$$= (-4)(-j3) + 1.5(-4)(4)$$

$$\therefore \underline{V_{TH} = -24 + j12 \text{ Volts}}$$

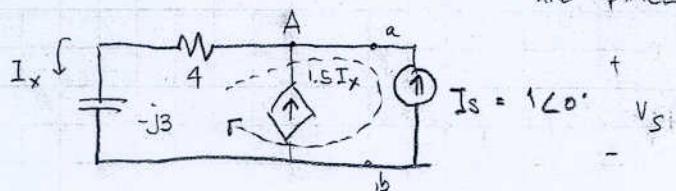(ii) to find Z_{TH} , we deactivate the independent source and place 1A at terminal ab:



At node A : $I_x = 1.5 I_x + I_s$

$$-0.5 I_x = 1A$$

$$I_x = -2A$$

Apply KVL on outer loop clockwise direction:

$$(4-j3)(-I_x) + V_s = 0$$

$$V_s = I_x(4-j3)$$

$$= (-2)(4-j3) = (-8+j6)V$$

$$\therefore \underline{Z_{TH} = \frac{V_s}{I_s} = (-8+j6) \Omega}$$