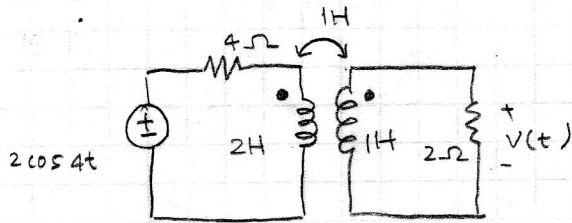


#13.8


HW SET #13

SOLUTION

FIND $v(t)$

$$\omega = 4$$

REDRAW THE CKT DIAGRAM:

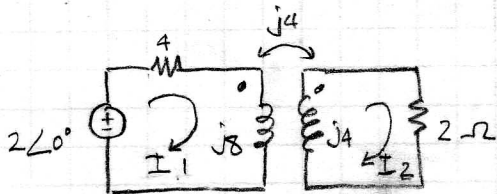

$$\begin{aligned} \text{Loop 1: } -2\angle 0^\circ + (4 + j8) I_1 - j4 I_2 &= 0 \\ (4 + j8) I_1 - j4 I_2 &= 2\angle 0^\circ \quad \text{--- ①} \end{aligned}$$

$$\text{Loop 2: } -j4 I_1 + (2 + j4) I_2 = 0 \quad \text{--- ②}$$

Solving for EQN ① & ②

$$\begin{bmatrix} 4 + j8 & -j4 \\ -j4 & 2 + j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 2\angle 0^\circ \\ 0 \end{bmatrix}$$


$$I_1 = (0.206 - j0.176) \text{ A} = 0.271 \angle -40.6^\circ \text{ A}$$

$$I_2 = (0.235 - j0.0588) \text{ A} = 0.243 \angle -14.04^\circ \text{ A}$$

$$\begin{aligned} V_{2\Omega} &= 2 I_2 = 0.471 - j0.118 \text{ V} \\ &= 0.485 \angle -14.04^\circ \text{ V} \end{aligned}$$

$$v(t) = 0.485 \cos(4t - 14.04^\circ)$$

#13.13

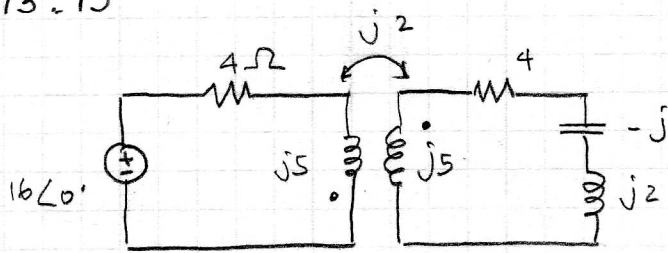


$$Z_{in} = Z_{LEFT COIL} + \frac{\omega^2}{Z_{RIGHT COIL}}$$

$$= 4 + j5 + \frac{2^2}{j5 + 4 - j + j2}$$

$$= 4 + j5 + \frac{4}{4 + j6}$$


$$= \underline{\underline{(4.308 + j4.54) \Omega}}$$

13-34

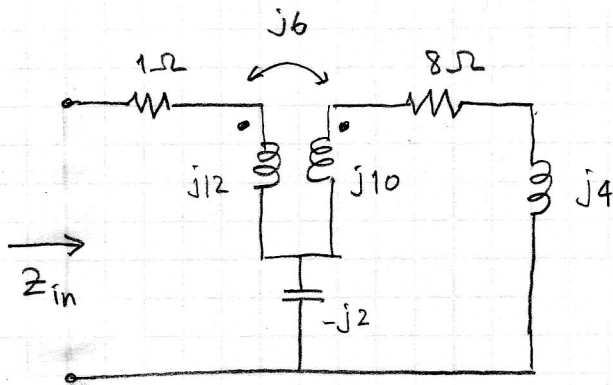

FIND THE INPUT IMPEDANCE OF THE CIRCUIT.

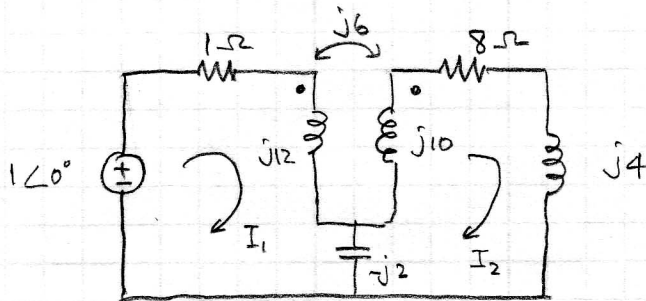Let INSERT IV SOURCE at the input terminal.



$$\text{Loop 1: } (1 + j12) I_1 - j2 (I_1 - I_2) - j6 I_2 = 1\angle 0^\circ$$

$$(1 + j10) I_1 - j4 I_2 = 1\angle 0^\circ \quad \text{--- ①}$$

$$\text{Loop 2: } -j6 I_1 - j2 (I_2 - I_1) + (8 + j4 + j10) I_2 = 0$$

$$-j4 I_1 + (8 + j12) I_2 = 0 \quad \text{--- ②}$$


Solving EQUATIONS ① & ②, WE GET:

$$I_1 = 0.019 - j0.107 = 0.108 \angle -79.9^\circ \text{ A}$$

$$I_2 = 0.021 - j0.022 = 0.03 \angle -46.22^\circ \text{ A}$$

$$\therefore Z_{in} = \frac{V}{I_1} = \frac{1\angle 0^\circ}{0.108 \angle -79.9^\circ} = \underline{\underline{9.22 \angle 79.9^\circ}}$$


13.45

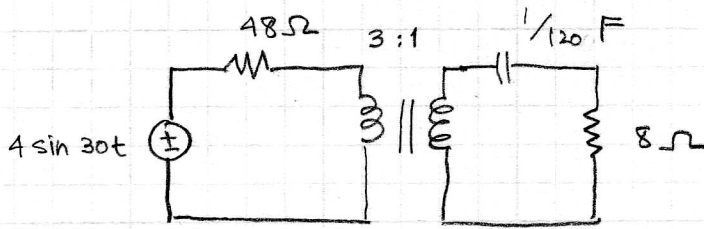

FIND THE AVERAGE POWER absorbed by 8Ω


REDRAW THE CIRCUIT IN FREQUENCY DOMAIN.

$$\omega = 30$$

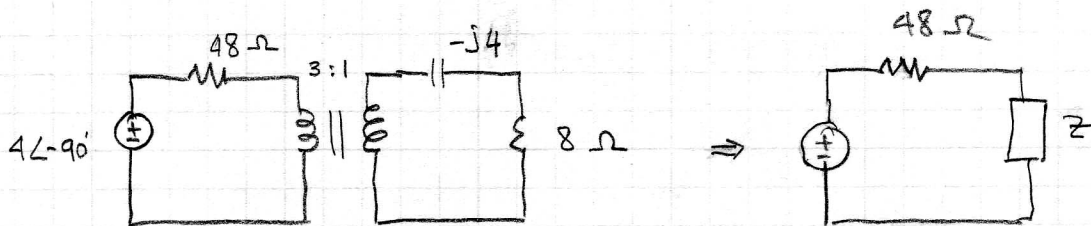

$$n = \frac{1}{3}$$



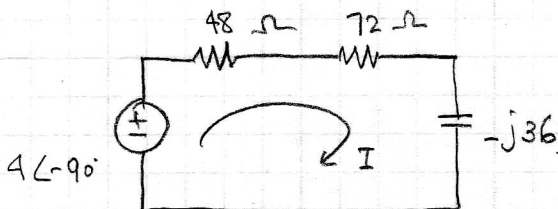
$$Z = \frac{(8 - j4)}{\left(\frac{1}{3}\right)^2} = 9(8 - j4) = 72 - j36$$



$$I = \frac{4\angle-90^\circ}{48 + 72 - j36} = \frac{4\angle-90^\circ}{120 - j36} = 0.03193 \angle -73.3^\circ$$


$$\begin{aligned} \therefore P_{8\Omega} &= \left| \frac{I^2}{2} \right| (72) = 0.0367 \text{ W} \\ &= \underline{\underline{36.7 \text{ mW}}} \end{aligned}$$

13.50

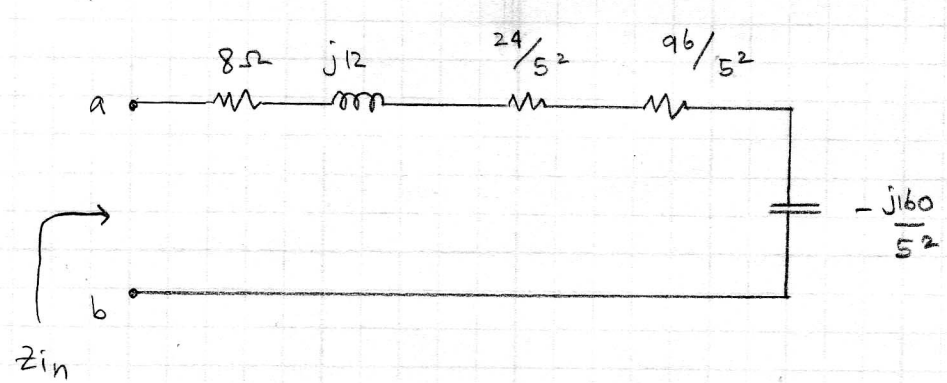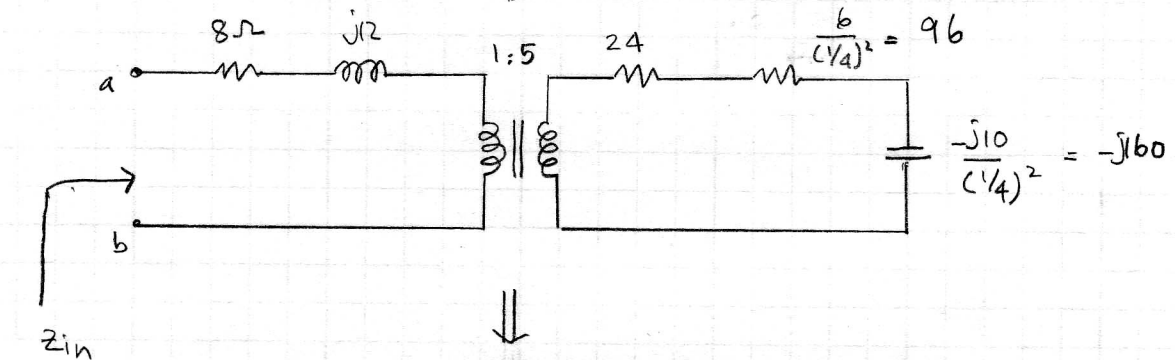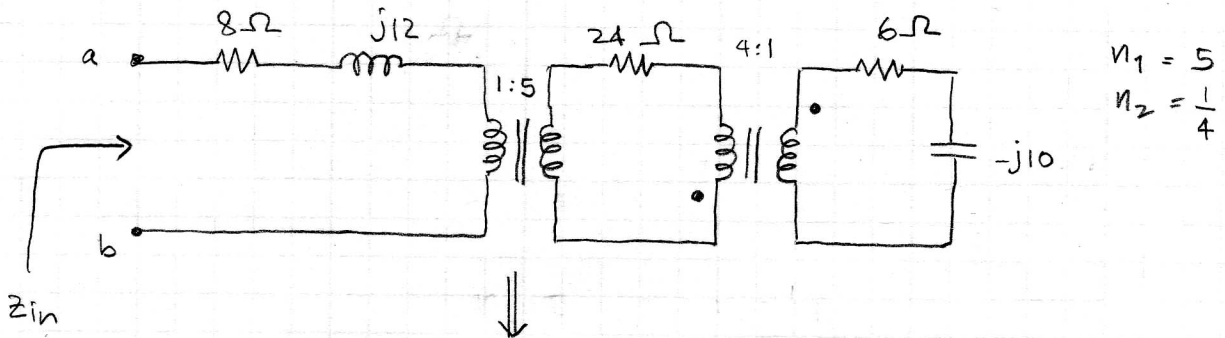

$$\begin{aligned}
 \therefore Z_{in} &= 8 + \frac{24}{25} + \frac{96}{25} + j12 - \frac{j160}{25} \\
 &= \frac{320}{25} + j \frac{140}{25} \\
 &= \underline{\underline{(12.8 + j5.6) \Omega}}
 \end{aligned}$$


13.53

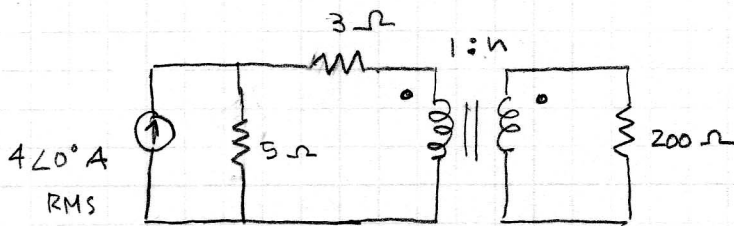


(a) Find n for maximum power supplied to 200Ω load.

(b) Determine the power in 200Ω load if $n = 10$.

(a) REDRAW THE CIRCUIT :

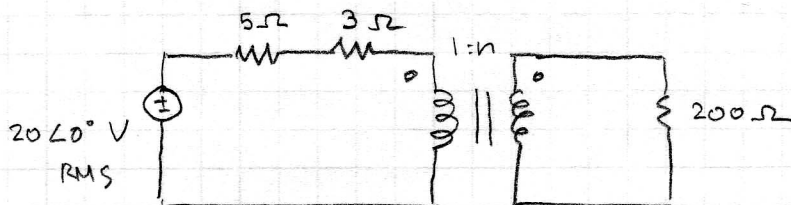

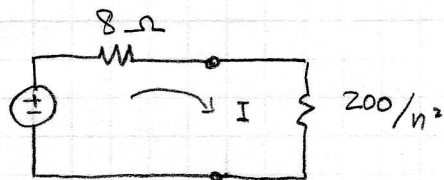THE THEVENIN EQUIVALENT CKT TO THE LEFT OF THE TRANSFORMER :



FOR MAX POWER TRANSFER : $R = 200/n^2$

$$\therefore n = 5$$

(b) If $n = 10$: $Z_L = \frac{200}{10^2} = 2 \Omega$

$$\therefore I = \frac{20}{8+2} = 2$$

$$P = I^2 Z_L = (2)^2 (2) = \underline{\underline{8W}}$$