

Due: January 22, 2005
wlg Version 2

Name Wlg
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

Work the following problems from the text.

2.37 Ans: $R = 2.5$ ohms

2.61 Use combinations R_1 and R_2 , R_1 and R_3 , R_2 and R_3 . Answer on your own.

2.74 Ans: $R_1 = 4 \Omega$, $R_2 = 0.8 \Omega$, $R_3 = 1.17 \Omega$

2.80 Ans: 30 W

P.P. 2.6

P.P. 2.7

P.P. 2.8

P.P. 2.9

P.P. 2.13

P.P. 2.15

2.XX You are given the circuit shown in Figure 2.XX.

- Use branch circuit analysis to find the current I_1 and I_2 . Ans: $I_1 = 0.0741$ A, $I_2 = 1.111$ A
- Determine the power absorbed by the three resistors. $P_{15} = 21.07$ W, $P_{30} = 0.165$ W, $P_{20} = 24.69$ W.
- Determine the power supplied by the two sources. $P_{\text{sup } 20} = 1.482$ W, $P_{\text{sup } 40} = 44.44$ W
- Does power supplied equal to power absorbed? Verify.


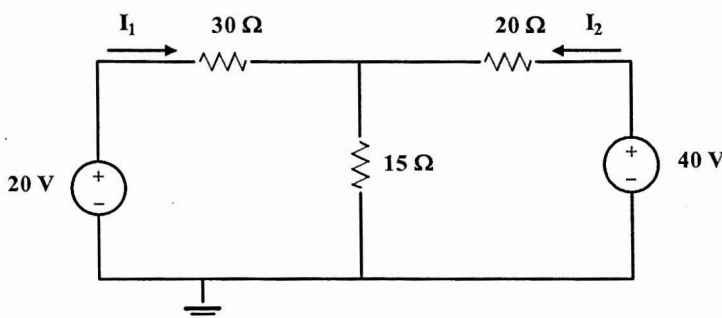


Figure 2.XX: Circuit for problem 2.XX.

ECE 300
HW #1
Spring 2008

Wg

2.37 Find R for the following circuit.

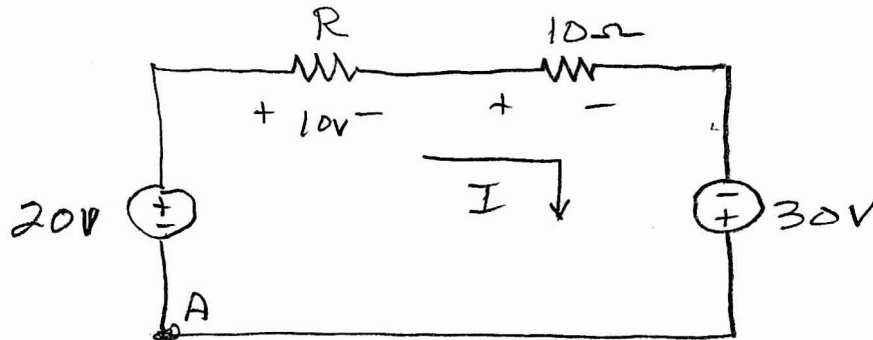

$\sum \text{drops} = 0$, from A, cw

$$-20 + 10 + 10I - 30 = 0$$

$$10I = 40$$

$$I = 4 \text{ A}$$

Then the drop across the resistor R , being 10V, must equal $4R$.

$$4R = 10$$


$$R = 2.5 \Omega$$

2.61

2.61 As a design engineer, you are asked to design a lighting system consisting of a 70-W power supply and two lightbulbs as shown in Fig. 2.124. You must select the two bulbs from the following three available bulbs.

- $R_1 = 80 \Omega$, cost = \$0.60 (standard size)
- $R_2 = 90 \Omega$, cost = \$0.90 (standard size)
- $R_3 = 100 \Omega$, cost = \$0.75 (nonstandard size)

The system should be designed for minimum cost such that lies within the range $I = 1.2 \text{ A} \pm 5 \text{ percent}$.

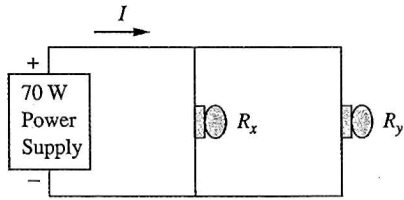

Case I

With: $R_1 = 80 \Omega$, $R_2 = 90 \Omega$

$$R_{eq} = \frac{80 \times 90}{80 + 90} = 42.35 \Omega$$

$$P = I^2 R_{eq}$$

$$I = \sqrt{\frac{70}{42.35}} = 1.28 \text{ A}$$

$$5\% \times 1.2 = .06$$

$$I_{accept} = 1.28 - .06 = 1.22 \text{ A (out of range)}$$

#

Case II
 R_1 & R_3

$$R_{eq} = \frac{80 \times 100}{80 + 100} = 44.44$$

$$I = \sqrt{\frac{70}{44}} = 1.255$$

$$I_{accept} = 1.2 + .06 = 1.26 \quad \text{OK}$$

$$\text{Cost} = 90.6 + 90.75 = \underline{\underline{\$1.35}}$$

2.61 (continued)

2

With R_2 & R_3
CASE II $R_{eq} = \frac{90 \times 100}{90 + 100} = 47.368 \Omega$

$$I = \sqrt{\frac{70}{47.368}} = 1.2156 \text{ A}$$

$$I_{\text{Accept}} = 1.2 + 0.06 = 1.26 \text{ A}$$

Since 1.2156 A is less than 1.26 A
this is acceptable.


Cost

$$\text{Cost} = \$0.9 + 0.75 = \$1.65$$

CASE II is best; R_1 & R_3 bulbs

2.74

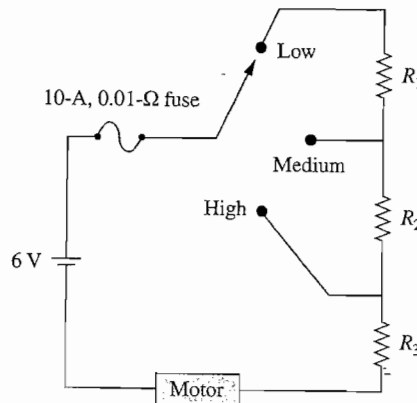2.74 The circuit in Fig. 2.134 is to control the speed of a motor such that the motor draws currents 5 A, 3 A, and 1 A when the switch is at high, medium, and low positions, respectively. The motor can be modeled as a load resistance of 20 m Ω . Determine the series dropping resistances R_1 , R_2 , and R_3 .



Start with the switch set on high, R_3 in the circuit. We have

$$-6 + (0.01 + 0.02) \times 5 + 5R_3 = 0$$

$$5R_3 = 6 - 5 \times 0.03 = 5.85$$

$$\underline{R_3 = 1.17 \Omega}$$

With R_2 and R_3 in the circuit;

$$-6 + 0.03 \times 3 + 3(1.17) + 3R_2 = 0$$

$$3R_2 = 2.5$$

$$\underline{R_2 = 0.8 A}$$

With R_1 , R_2 and R_3 in the circuit

$$-6 + 0.03 \times 1 + 1(1.17 + 0.8) + 1 \times R_1 = 0$$

$$R_1 = 6 - 0.03 - 1.97 = 4 \Omega$$

$$\underline{R_1 = 4 \Omega}$$

2.80

- 2.80 A loudspeaker is connected to an amplifier as shown in Fig. 2.139. If a $10\text{-}\Omega$ loudspeaker draws the maximum power of 12 W from the amplifier, determine the maximum power a $4\text{-}\Omega$ loudspeaker will draw.



with 10Ω

$$P_{10} = 12 = \frac{V_{\text{source}}^2}{10}$$

$$V_{\text{source}}^2 = 120$$

$$V_{\text{source}} = 10.954\text{ V}$$


with 4Ω

$$P_4 = \frac{V_{\text{source}}^2}{4} = \frac{120}{4}$$

$$P_4 = 30\text{ W}$$

PP 2.6

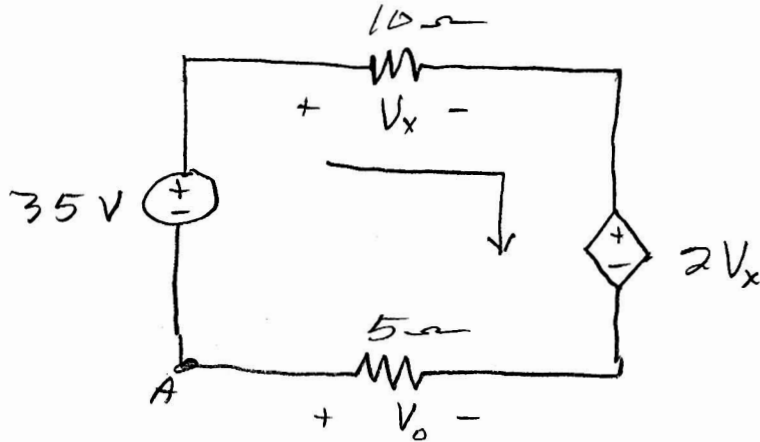Find V_x and V_o in the following circuit.



Assume I as shown. Write KVL, CCWS, CW, A

$$-35 + 10I + 2V_x + 5I = 0$$

$$\text{but } V_x = 10I, \text{ so}$$

$$-35 + 10I + 20I + 5I = 0$$

$$35I = 35$$

$$I = 1A$$


\therefore

$$\underline{V_x = 10I = 10V}$$

$$\underline{V_o = -5I = -5V}$$

PP.2.7

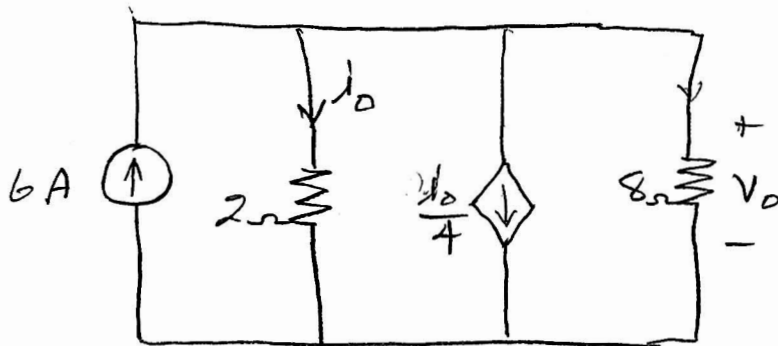Find V_o and i_o in the following circuit.



$$V_o = 2i_o$$

no

$$6 = i_o + \frac{i_o}{4} + \frac{V_o}{8}$$

$$6 = i_o + \frac{i_o}{4} + \frac{2i_o}{8}$$

$$6 = i_o + 0.5i_o$$


$$\underline{i_o = 4A}$$

$$V_o = 2i_o = 8V$$

$$\underline{V_o = 8V}$$

PP 2.8

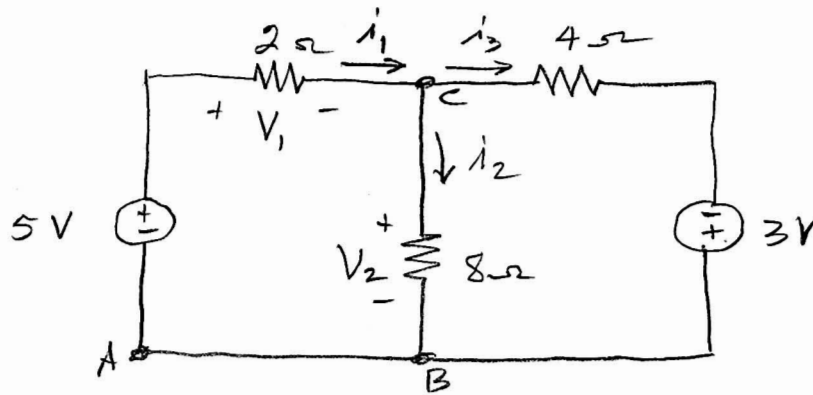Find the indicated voltages and currents in the following circuit.



Start at A, cw, Σ drops = 0

$$-5 + 2i_1 + 8i_2 + 0i_3 = 0$$

$$\boxed{2i_1 + 8i_2 + 0i_3 = 5}$$

Start at B, cw, Σ drops = 0

$$-8i_2 + 4i_3 - 3 = 0$$

$$\boxed{0i_1 - 8i_2 + 4i_3 = 3}$$

KCL @ C

$$\boxed{i_1 - i_2 - i_3 = 0}$$


$$\begin{bmatrix} 2 & 8 & 0 \\ 0 & -8 & 4 \\ 1 & -1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 3 \\ 0 \end{bmatrix}$$

$$\underline{i_1 = 1.5 \text{ A}}, \quad \underline{i_2 = 0.25 \text{ A}}, \quad \underline{i_3 = 1.25 \text{ A}}$$

$$\underline{V_1 = 2i_1 = 3 \text{ V}}; \quad \underline{V_2 = 8i_2 = 2 \text{ V}}; \quad \underline{V_3 = 4i_3 = 5 \text{ V}}$$

PT 2.9

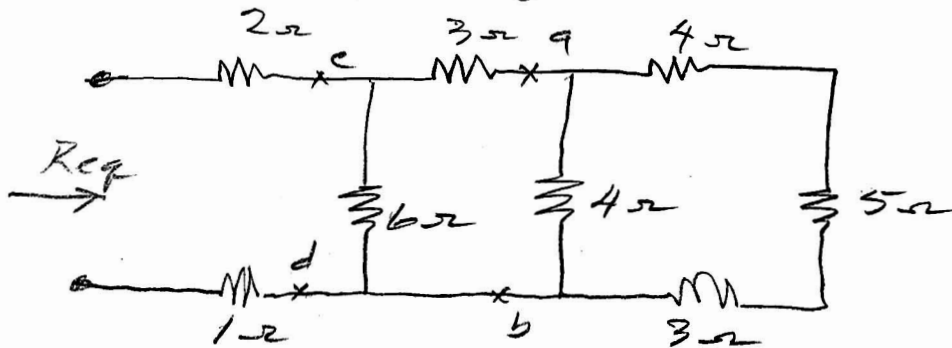By combination of resistors, find R_{eq} for the following circuit.



$$R_{ab} = 4 \parallel (4 + 5 + 3) = \frac{4 \times 12}{4 + 4 + 5 + 3} = 3 \Omega$$

$$R_{cd} = 6 \parallel (3 + R_{ab}) = \frac{6(3 + 3)}{3 + 3 + 6} = 3 \Omega$$

$$R_{eq} = 2 + R_{cd} + 1 = (2 + 3 + 1) \Omega$$

$$R_{eq} = 6 \Omega$$


PP 2.13

For the following circuit find:

(a) V_1 and V_2

(b) P dissipated in $3k\Omega$ & $20k\Omega$ resistors

(c) P supplied by current source.

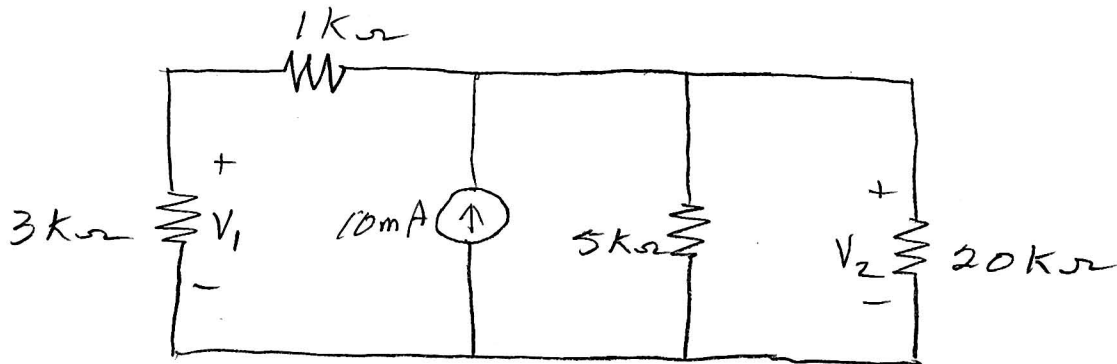

$$V_2 = 10\text{mA} \times R_{eq}$$

$$R_{eq} = 4k \parallel (5k \parallel 20k)$$

$$= \frac{4k \parallel (5k \times 20k)}{5k + 20k} = 4k \parallel 4k = 2k\Omega$$

$$\underline{V_2 = (10k^{-1})(2k) = 20V}$$

by voltage division;

$$V_1 = \frac{V_2 \times 3k}{3k + 1k} = \frac{20 \times 3}{4} = 15V$$

$$\underline{V_1 = 15V}$$

PP 2.13 continued

2

(b)

$$P_{3k} = \frac{V_1^2}{3k} = \frac{15^2}{3k} = 75 \text{ mW}$$

$$\underline{P_{3k} = 75 \text{ mW}}$$

$$\underline{P_{20k} = \frac{V_2^2}{20k} = \frac{20^2}{20k} = 20 \text{ mW}}$$

$$P_{5k} = \frac{V_2^2}{5k} = \frac{20^2}{5k} = 80 \text{ mW}$$

$$V_{1k} = \frac{20 \times 1k}{4k} = 5 \text{ V}$$

$$P_{1k} = \frac{5^2}{1k} = 25 \text{ mW}$$

$$\Sigma P_{\text{dissipated}} = (75 + 20 + 80 + 25) \text{ mW}$$

$$\Sigma P_{\text{dissipated}} = 200 \text{ mW} = P_{\text{sup } 10\text{mA}}$$



$$P_{10\text{mA supplied}} = (10k^{-1}) V_2 = 10k^{-1} \times 20$$

$$\underline{P_{10\text{mA supplied}} = 200 \text{ mW}}$$

checks

DP 2.15

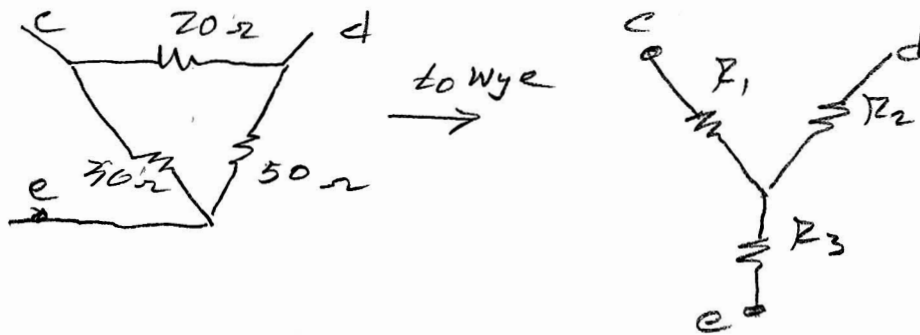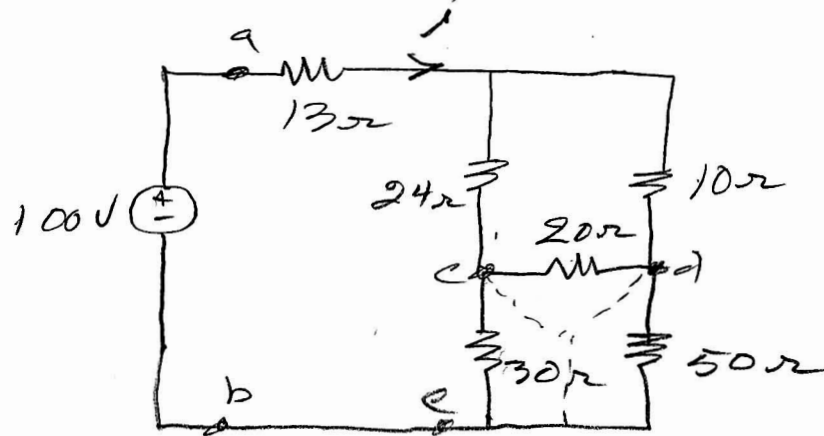
For the bridge network below,
find R_{ab} and i .



$$R_1 = \frac{20 \times 30}{20 + 30 + 50} = 7.6 \Omega$$

$$R_2 = \frac{20 \times 50}{100} = 10 \Omega$$

$$R_3 = \frac{30 \times 50}{100} = 15 \Omega$$

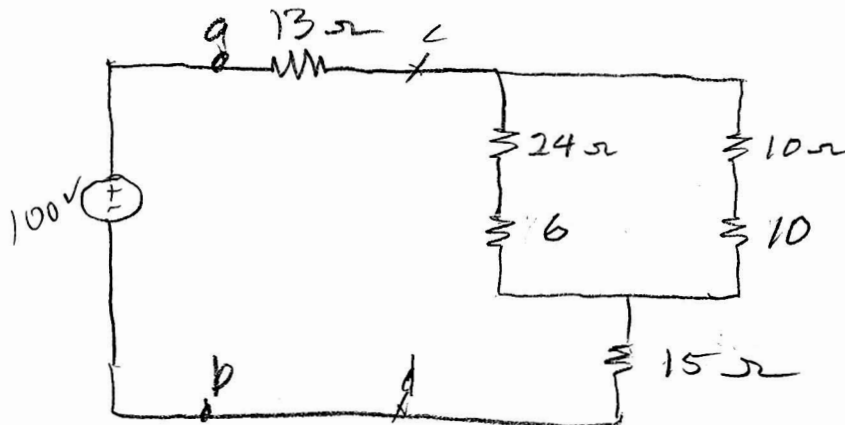

PD 2.15

2

$$R_{cd} = 30 \parallel 20 + 15 = 12 + 15$$

$$R_{cd} = 27 \Omega$$

$$R_{ab} = 13 \Omega + 27 \Omega$$

$$\underline{\underline{R_{ab} = 40 \Omega}}$$

$$\underline{\underline{i = \frac{100}{40} = 2.5 \text{ A}}}$$

2.XX You are given the circuit shown in Figure 2.XX.

- Use branch circuit analysis to find the current I_1 and I_2 . Ans: $I_1 = 0.0741$ A, $I_2 = 1.111$ A
- Determine the power absorbed by the three resistors. $P_{15} = 21.07$ W, $P_{30} = 0.165$ W
 $P_{20} = 24.69$ W.
- Determine the power supplied by the two sources. $P_{\text{sup } 20} = 1.482$ W, $P_{\text{sup } 40} = 44.44$ W
- Does power supplied equal to power absorbed? Verify.

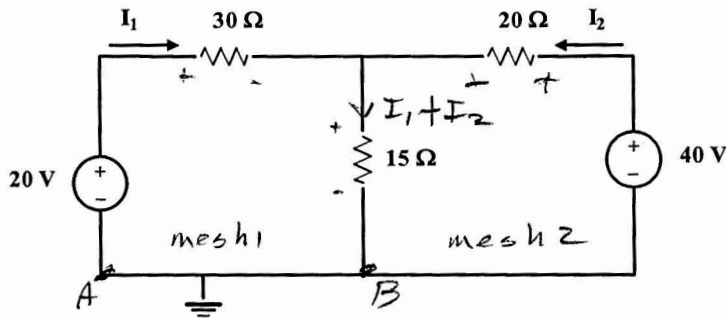


Figure 2.XX: Circuit for problem 2.XX.

(a) AROUND mesh 1: start at A, cw, Σ drops = 0

$$-20 + 30I_1 + 15(I_1 + I_2) = 0$$

$$\boxed{45I_1 + 15I_2 = 20}$$

AROUND mesh 2: start at B, cw, Σ drops = 0

$$-15(I_1 + I_2) - 20I_2 + 40 = 0$$

$$\boxed{-15I_1 - 35I_2 = -40}$$

$$\begin{bmatrix} 45 & 15 \\ 15 & 35 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 40 \end{bmatrix}$$

$$I_1 = 0.07407 \text{ A} \quad I_2 = 1.111 \text{ A}$$

2. XX cont. v. u. e. p

1b)

$$P_{30} = I_1^2 \times 30 = (0.07407)^2 \times 30$$

$$P_{30} = 0.16459 \text{ W} = .165 \text{ W}$$

$$\underline{P_{30} = 0.165 \text{ W}}$$

$$P_{20} = I_2^2 \times 20 = 24.67 \text{ W}$$

$$\underline{P_{20} = 24.69 \text{ W}}$$

$$P_{15} = (I_1 + I_2)^2 \times 15 = (1.185)^2 \times 15$$

$$P_{15} = 21.06 \text{ W}$$

$$\Sigma P_{\text{abs}} = (0.165 + 24.69 + 21.06) \text{ W}$$

$$\boxed{\Sigma P_{\text{abs}} = 45.92 \text{ W}}$$

$$P_{\text{sup}}_{20} = 20 \times I_1 = 1.482 \text{ W}$$

$$P_{\text{sup}}_{40} = 40 \times I_2 = 44.44$$

$$\Sigma P_{\text{sup}} = 1.482 + 44.44$$

$$\boxed{\Sigma P_{\text{sup}} = 45.92 \text{ W}}$$

clocks