

*Desk copy*

Due: January 29, 2005

Name wlg  
 Print (last, first)

wlg

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

2.XX You are given the circuits shown in Figures 2.XX(a), 2.XX(b), 2.XX(c). You are to find node voltages  $V_1, V_2, V_3$  for each diagram. You are to find currents  $I_A, I_B, I_C$  and  $I_D$  for each diagram. You are to also find  $V_A, V_B, V_C$  for each diagram. From this study, state what you have learned about changing reference points in nodal analysis.

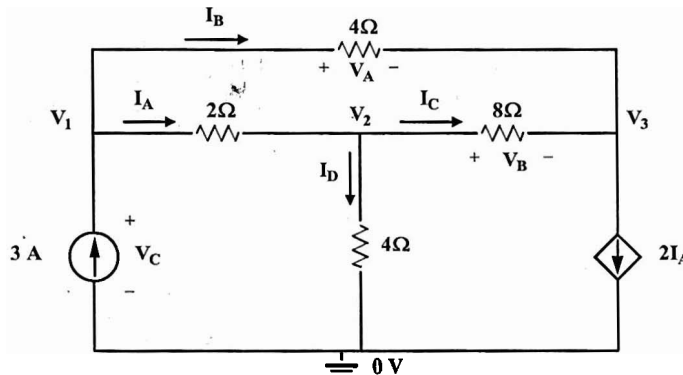


Figure 2.XX(a)

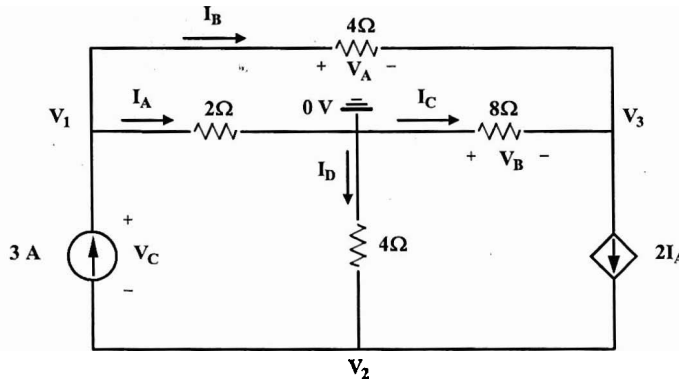


Figure 2.XX(b)

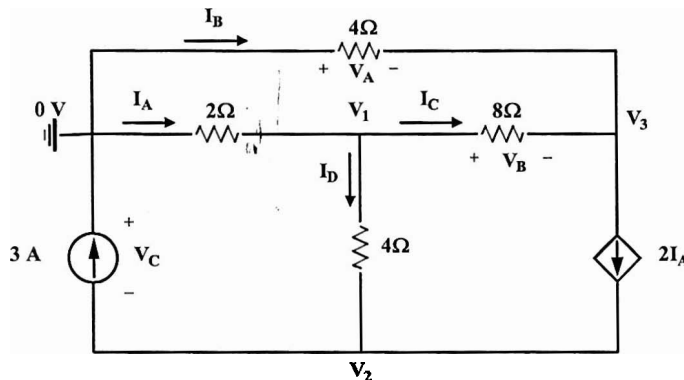


Figure 2.XX(c)

ECE 300  
H.W. #2  
Spring 2008

2.XX You are given the circuits shown in Figures 2.XX(a), 2.XX(b), 2.XX(c). You are to find node voltages  $V_1, V_2, V_3$  for each diagram. You are to find currents  $I_A, I_B, I_C$  and  $I_D$  for each diagram. You are to also find  $V_A, V_B, V_C$  for each diagram. From this study, state what you have learned about changing reference points in nodal analysis.

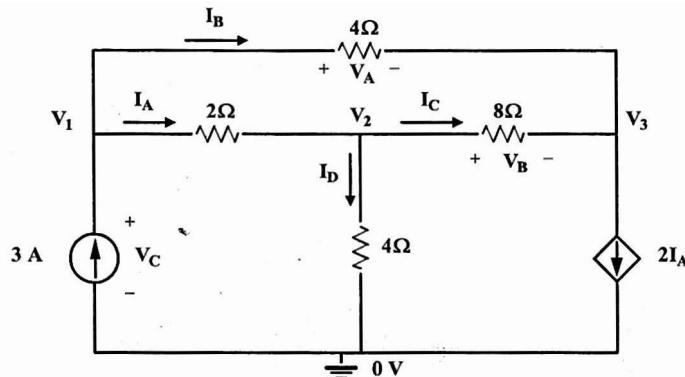


Figure 2.XX(a)

First determine  $V_1, V_2, V_3$ .

At  $V_1$

$$4 \left( \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} \right) - 3 = 0$$

$$2V_1 - 2V_2 + V_1 - V_3 = 12$$

$$3V_1 - 2V_2 - V_3 = 12$$

At  $V_2$

$$\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{8} + \frac{V_2}{4} = 0$$

$$-4V_1 + 7V_2 - V_3 = 0$$

At  $V_3$

$$\frac{V_3 - V_2}{8} + \frac{V_3 - V_1}{4} + 2I_A = 0$$

$$I_A = \frac{V_1 - V_2}{2}$$

$$8 \left( \frac{V_3 - V_2}{8} + \frac{V_3 - V_1}{4} + 2 \left( \frac{V_1 - V_2}{2} \right) = 0 \right)$$

$$V_3 - V_2 + 2V_3 - 2V_1 + 8V_1 - 8V_2 = 0$$

$$\boxed{6V_1 - 9V_2 + 3V_3 = 0}$$

$$\begin{bmatrix} 3 & -2 & -1 \\ -4 & 7 & -1 \\ 6 & -9 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$V_1 = 4.8 \text{ V}; \quad V_2 = 2.4 \text{ V}; \quad V_3 = -2.4 \text{ V}$$

$$\underline{I_A} = \frac{V_1 - V_2}{2} = \underline{1.2 \text{ A}}$$

$$\underline{I_B} = \frac{V_1 - V_3}{4} = \frac{7.2}{4} = \underline{1.8 \text{ A}}$$

$$\underline{I_C} = \frac{V_2 - V_3}{8} = \frac{2.4 + 2.4}{8} = \underline{0.6 \text{ A}}$$

$$\underline{I_D} = \frac{V_2}{4} = \underline{0.6 \text{ A}}$$

(A)  
summary  
(A)

$$\underline{I_A = 1.2 \text{ A}; \quad I_B = 1.8 \text{ A}; \quad I_C = 0.6 \text{ A}; \quad I_D = 0.6 \text{ A}}$$

2.XX

3

For  $V_A$

$$V_1 - V_A - V_3 = 0$$

$$V_A = V_1 - V_3 = 4.8 - (-2.4)$$

$$\underline{V_A = 7.2 V}$$

For  $V_B$

$$V_2 - V_B - V_3 = 0$$

$$V_B = V_2 - V_3 = 2.4 - (-2.4)$$

$$\underline{V_B = 4.8 V}$$

For  $V_C$

$$V_C = V_1$$

$$\underline{V_C = 4.8 V}$$

Summary (A)

$$\underline{V_A = 7.2 V \quad V_B = 4.8 V; \quad V_C = 4.8 V}$$

2.XX (b)

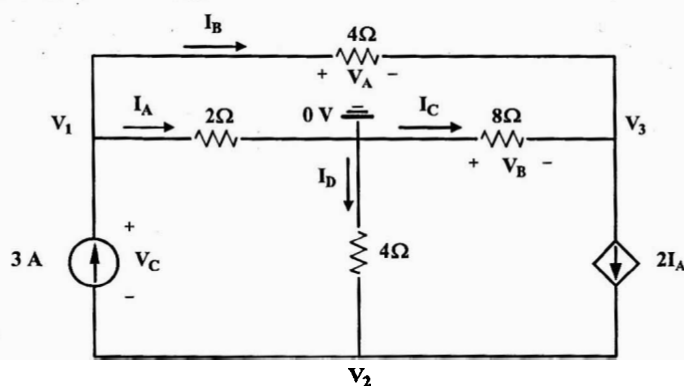


Figure 2.XX(b)

2.XX

4

(b) At  $V_1$

$$4\left(\frac{V_1}{2} + \frac{V_1 - V_3}{4} - 3 = 0\right)$$

$$2V_1 + V_1 - V_3 = 12$$

$$\boxed{-3V_1 + 0V_2 - V_3 = 12}$$

At  $V_2$

$$\frac{V_2}{4} + 3 - 2I_A = 0$$

$$I_A = \frac{V_1}{2}$$

$$4\left(\frac{V_2}{4} + 3 - 2\left(\frac{V_1}{2}\right) = 0\right)$$

$$V_2 + 12 - 4V_1 = 0$$

$$\boxed{-4V_1 + V_2 + 0V_3 = -12}$$

At  $V_3$

$$\frac{V_3}{4} + \frac{V_3 - V_1}{4} + 2I_A = 0$$

$$I_A = \frac{V_1}{2}$$

$$4\left(\frac{V_3}{4} + \frac{V_3 - V_1}{4} + 2\left(\frac{V_1}{2}\right) = 0\right)$$

2.XX

5

$$V_3 + 2V_3 - 2V_1 + 8V_1 = 0$$

$$\boxed{6V_1 + 0V_2 + 3V_3 = 0}$$

$$(b) \begin{bmatrix} 3 & 0 & -1 \\ -4 & 1 & 0 \\ 6 & 0 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 12 \\ -12 \\ 0 \end{bmatrix}$$

$$V_1 = 2.4V; \quad V_2 = -2.4V; \quad V_3 = -4.8V$$

$$I_A = \frac{V_1}{2} = 1.2A$$

$$I_B = \frac{V_1 - V_3}{4} = \frac{2.4 + 4.8}{4} = 1.8A$$

$$I_C = \frac{-V_3}{8} = \frac{4.8}{8} = 0.6A$$

$$I_D = \frac{-V_2}{4} = \frac{2.4}{4} = 0.6A$$

Summary (b)

$$I_A = 1.2A; \quad I_B = 1.8A; \quad I_C = 0.6A; \quad I_D = 0.6A$$

For  $V_A$

$$V_A = I_B \times 4 = 1.8 \times 4 = 7.2V$$

For  $V_B$

$$V_B = 8I_C = 4.8V$$

For  $V_3$  :  $V_1 - V_3 - V_2 = 0$

$$V_3 = V_1 - V_2 = 2.4 - (-2.4) = \underline{4.8V}$$

2.47 (c)

6

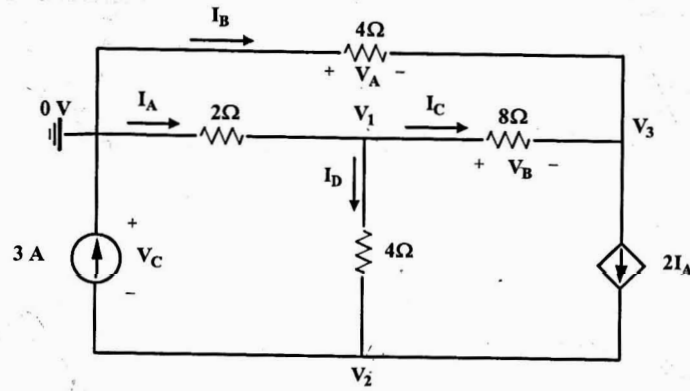


Figure 2.XX(c)

Part (c)

At  $V_1$

$$4 \left( \frac{V_1 - V_2}{4} + \frac{V_1 - V_3}{8} + \frac{V_1}{2} = 0 \right)$$

$$2V_1 - 2V_2 + V_1 - V_3 + 4V_1 = 0$$

$$\boxed{7V_1 - 2V_2 - V_3 = 0}$$

At  $V_2$

$$\frac{V_2 - V_1}{4} + 3 - 2I_A = 0$$

$$4 \left( \frac{V_2 - V_1}{4} + 3 - 2 \left( \frac{-V_1}{2} \right) = 0 \right)$$

$$V_2 - V_1 + 12 + 4V_1 = 0$$

$$\boxed{3V_1 + V_2 + 0V_3 = -12}$$

2.XY

7

At  $V_3$

$$4 \left( \frac{V_3 - V_1}{8} + \frac{V_3}{4} + 2I_A = 0 \right)$$

$$I_A = -\frac{V_1}{2}$$

$$4 \left( \frac{V_3 - V_1}{8} + \frac{V_3}{4} + 2 \left( -\frac{V_1}{2} \right) = 0 \right)$$

$$V_3 - V_1 + 2V_3 - 8V_1 = 0$$

$$\boxed{-9V_1 + 0V_2 + 3V_3 = 0}$$

$$\begin{bmatrix} 7 & -2 & -1 \\ 3 & 1 & 0 \\ -9 & 0 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -12 \\ 0 \end{bmatrix}$$

$$V_1 = -2.4V$$

$$V_2 = -4.8V$$

$$V_3 = -7.2V$$

$$\underline{I_A} = \frac{-V_1}{2} = \frac{2.4}{2} = \underline{1.2A}$$

$$\underline{I_B} = \frac{-V_3}{4} = \frac{-(-7.2)}{4} = \underline{1.8A}$$

$$I_C = \frac{V_1 - V_3}{8} = \frac{-2.4 - (-7.2)}{8} = 0.6A$$

$$I_D = \frac{V_1 - V_2}{4} = \frac{-2.4 + 4.8}{4} = 0.6A$$



2. XY

8

FOR VA

$$V_A = I_B \times 4 = 1.8 \times 4 = 7.2 \text{ V}$$

FOR VB

$$V_B = I_C \times 8 = 0.6 \times 8 = 4.8 \text{ V}$$

FOR VC

$$V_C = -V_2 = -(-4.8) = 4.8 \text{ V}$$

Overall Summary


	PART A	PART B	PART C
$V_1$	4.8V	2.4V	-2.4V
$V_2$	2.4V	-2.4V	-4.8V
$V_3$	-2.4V	-4.8V	-7.2V
$I_A$	1.2A	1.2A	1.2A
$I_B$	1.8A	1.8A	1.8A
$I_C$	0.6A	0.6A	0.6A
$I_D$	0.6A	0.6A	0.6A
$V_A$	7.2V	7.2V	7.2V
$V_B$	4.8V	4.8V	4.8V
$V_C$	4.8V	4.8V	4.8V

Conclusion

Changing reference nodes, changes the reference node voltages. However, All currents and voltages across elements remain the same.

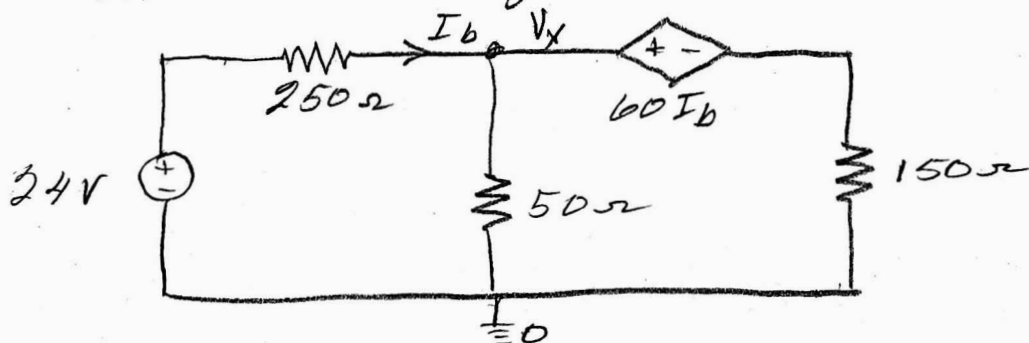3.9

Determine  $I_b$  for the following circuit.  
Use nodal analysis.



At  $V_x$ :  $\sum i \text{ leaving} = 0$ ; using KCL.

$$75 \left( \frac{V_x - 24}{250} + \frac{V_x}{50} + \frac{V_x - 60I_b}{150} = 0 \right)$$

$$3V_x - 72 + 15V_x + 5V_x - 300I_b = 0$$

$$I_b = \frac{24 - V_x}{250}$$

so

$$23V_x - 300 \left( \frac{24 - V_x}{250} \right) = 72$$

$$23V_x - 28.8 + 1.2V_x = 72$$

$$24.2V_x = 100.8$$


$$V_x = 4.165 \text{ V}$$

$$I_b = \frac{24 - V_x}{250} = \frac{24 - 4.165}{250} = 79.3 \text{ mA}$$

$$I_b = 79.3 \text{ mA}$$

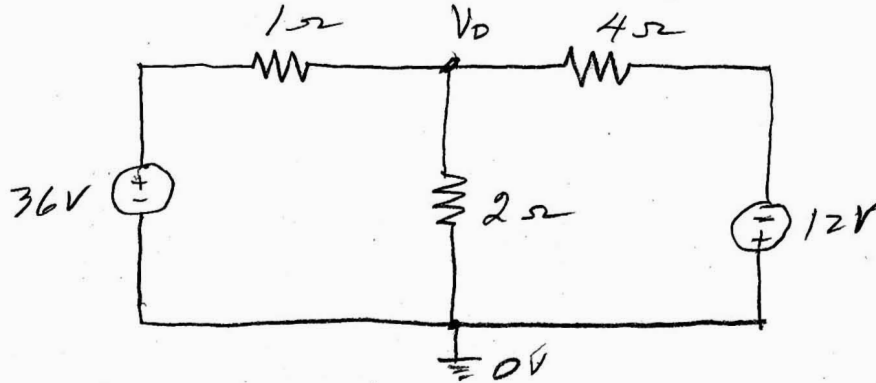3.11

Find  $V_0$  and the power dissipated in all the resistors in the following circuit.



At  $V_0$ :  $\sum i$  leaving = 0; use resistors.

$$4 \left( \frac{V_0 - 36}{1} + \frac{V_0}{2} + \frac{V_0 + 12}{4} = 0 \right)$$

$$4V_0 - 144 + 2V_0 + V_0 + 12 = 0$$

$$7V_0 = 132$$

$$V_0 = 18.86V = 18.9V$$


$$\underline{P_{1\Omega}} = (V_0 - 36)^2 \times 1 = \underline{292.4W} \quad \text{close enough}$$

$$\underline{P_{2\Omega}} = \frac{V_0^2}{2} = \underline{178.6W}$$

$$\underline{P_{4\Omega}} = \frac{(V_0 + 12)^2}{4} = \frac{V^2}{R} = \underline{238.7W}$$

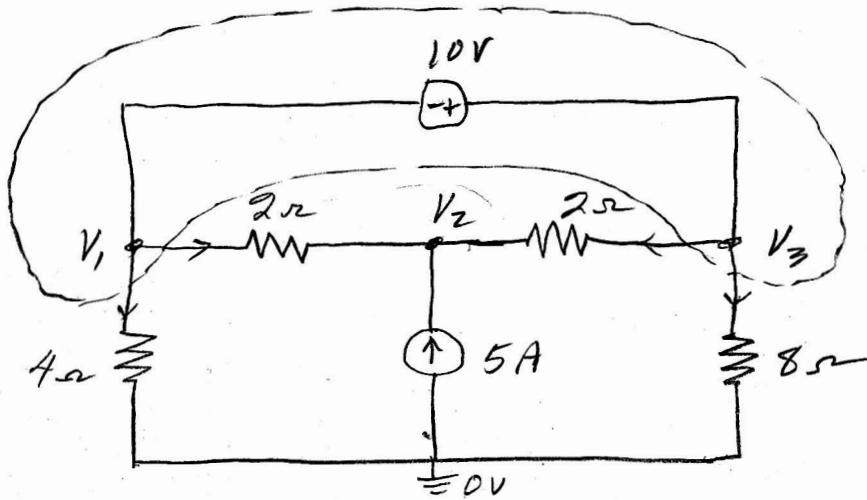3.18

Use nodal analysis to determine the node voltages in the following circuit.



There is a super node as indicated.

$\Sigma i$  leaving; using voltage rises.  
At the super node:

$$\left( \frac{V_1}{4} + \frac{V_1 - V_2}{2} + \frac{V_3 - V_2}{2} + \frac{V_3}{8} = 0 \right)$$

$$2V_1 + 4V_1 - 4V_2 + 4V_3 - 4V_2 + V_3 = 0$$

$$\boxed{6V_1 - 8V_2 + 5V_3 = 0}$$

At  $V_2$ :

$$\left( \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2} - 5 = 0 \right)$$

$$V_2 - V_1 + V_2 - V_3 - 10 = 0$$

$$\boxed{-V_1 + 2V_2 - V_3 = 10}$$

3.18 continued

Constraint Equation

$$V_1 + 10 - V_3 = 0$$

$$\boxed{V_1 + 0V_2 - V_3 = -10}$$


$$\begin{bmatrix} 6 & -8 & 5 \\ -1 & 2 & -1 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 10 \\ -10 \end{bmatrix}$$

$$V_1 = 10 \text{ V}; \quad V_2 = 20 \text{ V}; \quad V_3 = 20 \text{ V}$$

3.22

Determine  $V_1$  and  $V_2$  in the following circuit.

Will use nodal analysis.

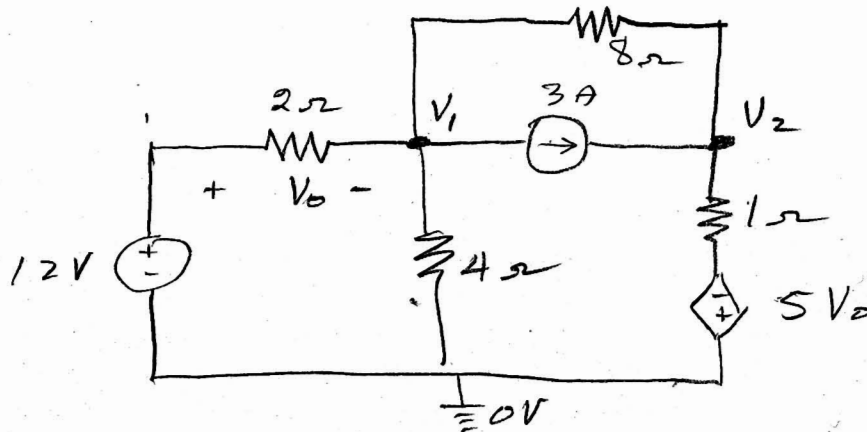

At  $V_1$ :  $\sum i_{\text{leaving}} = 0$ ; use voltage rises.

$$8 \left( \frac{V_1 - 12}{2} + \frac{V_1 - V_2}{8} + 3 + \frac{V_1}{4} = 0 \right)$$

$$4V_1 - 48 + V_1 - V_2 + 24 + 2V_1 = 0$$

$$\boxed{7V_1 - V_2 = +24}$$

At  $V_2$

$$8 \left( \frac{V_2 - V_1}{8} + \frac{V_2 + 5V_0}{1} - 3 = 0 \right)$$

$$V_2 - V_1 + 8V_2 + 40V_0 - 24 = 0$$

$$\text{But } V_1 + V_0 - 12 = 0$$

$$V_0 = 12 - V_1$$

3.22 cont.

2

$$-V_1 + 9V_2 + 40(12 - V_1) = 24$$


$$\boxed{-41V_1 + 9V_2 = -456}$$

$$\begin{bmatrix} 7 & -1 \\ -41 & 9 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} +24 \\ -456 \end{bmatrix}$$


$$V_1 = -10.91 \text{ V} ; \quad V_2 = -100.36 \text{ V}$$

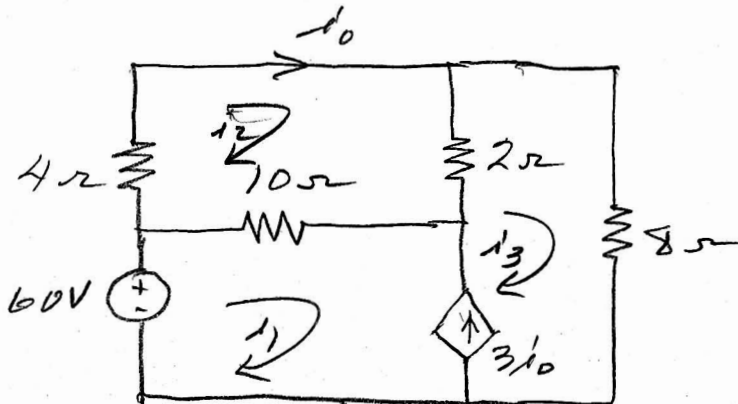3.50

Use mesh analysis to find current  $i_0$  in the circuit below.



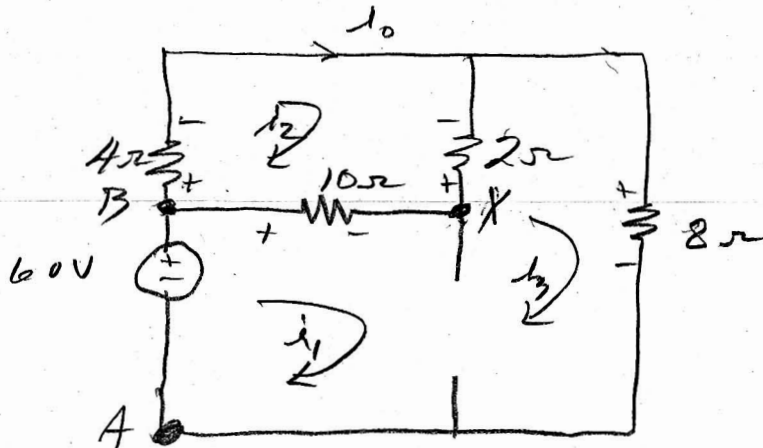Assign mesh current as shown above. Then redraw as shown below with current source omitted.



Write the following mesh equations.

At A:  $\sum \text{drops} = 0$ , c.w.

$$-60 + 10(i_1 - i_2) + 2(i_3 - i_2) + 8i_3 = 0$$

$$\boxed{10i_1 - 12i_2 + 10i_3 = 60}$$



3.50 cont.

At B

$\sum \text{drops} = 0$ , C.W.

$$4i_2 - 2(i_3 - i_2) - 10(i_1 - i_2) = 0$$

$$\boxed{-10i_1 + 16i_2 - 2i_3 = 0}$$

At X: KCL:  $\sum i \text{ entering} = 0$

$$i_2 - i_3 + i_1 - i_2 + 3i_0 = 0$$

$$i_1 - i_3 + 3i_0 = 0$$

$$\text{but } i_0 = i_2$$

$$\boxed{i_1 + 3i_2 - i_3 = 0}$$

$$\begin{bmatrix} 10 & -12 & 10 \\ -10 & 16 & -2 \\ 1 & 3 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 0 \\ 0 \end{bmatrix}$$


$$i_1 = 1.44 \text{ A}; \quad i_2 = 1.73 \text{ A}; \quad i_3 = 6.63 \text{ A}$$

$$\boxed{i_0 = i_2 = 1.73 \text{ A}}$$

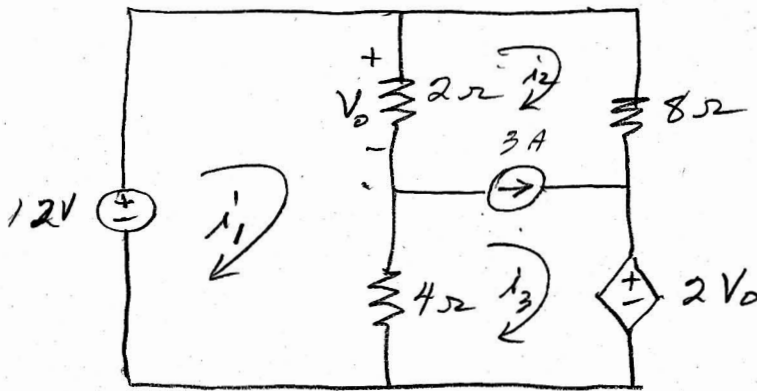
3.52

Use mesh analysis to find  $i_1, i_2, i_3$  in the following circuit.

First assign mesh currents as shown below.



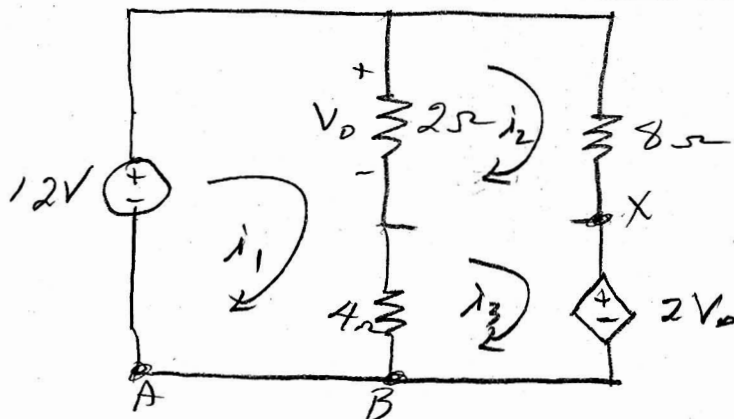Now remove the current source and write the equations.



At A: KVL; use drops, c.w.

$$-12 + 2(i_1 - i_2) + 4(i_1 - i_3) = 0$$

$$\boxed{6i_1 - 2i_2 - 4i_3 = 12}$$

3.52 cont.

At B: KVL;  $\sum drops = 0$ , e.w.

$$4(i_3 - i_1) + 2(i_2 - i_1) + 8i_2 + 2V_0 = 0$$

$$-6i_1 + 10i_2 + 4i_3 + 2V_0 = 0$$

but  $V_0 = 2(i_1 - i_2)$

$$-6i_1 + 10i_2 + 4i_3 + 2 \times 2(i_1 - i_2) = 0$$

$$\boxed{-2i_1 + 6i_2 + 4i_3 = 0}$$

At X: KCL:  $\sum i \text{ entering} = 0$

$$i_2 + 3 - i_3 = 0$$

$$\boxed{0i_1 + i_2 - i_3 = -3}$$


$$\begin{bmatrix} 6 & -2 & -4 \\ -2 & 6 & 4 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ -3 \end{bmatrix}$$

$$\boxed{i_1 = 3.5 \text{ A}; i_2 = -0.5 \text{ A}; i_3 = 2.5 \text{ A}}$$


3.63

FIND  $v_x$  and  $i_x$  IN the following circuit using mesh analysis.

Assign mesh currents as follows:

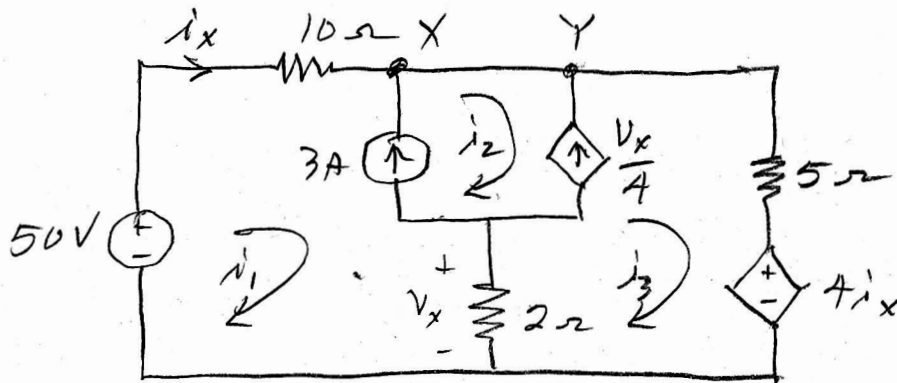

Now redraw with current sources removed.

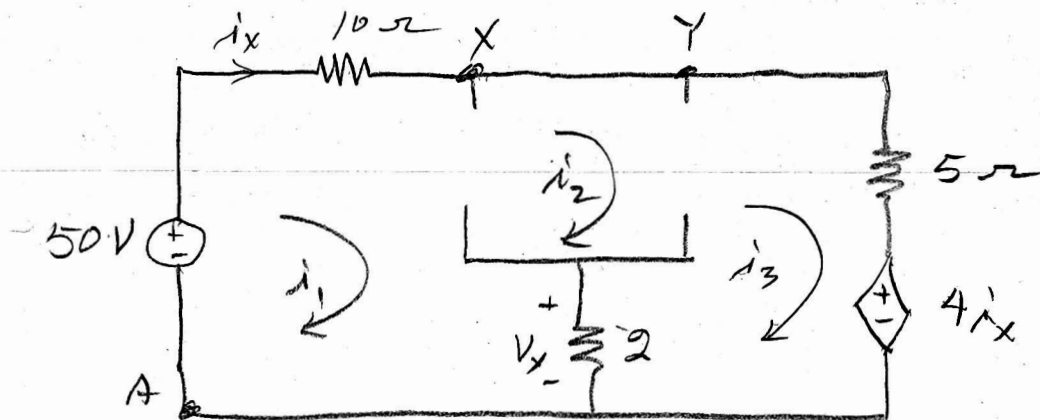

At A: KVL:  $\sum \text{drops} = 0$ , C.W.

$$-50 + 10i_1 + 5i_3 + 4i_1 = 0$$

(note;  $i_x = i_1$ )

$$14i_1 + 0i_2 + 5i_3 = 50$$

At X:  $\sum i$  entering = 0

$$i_1 - i_2 + 3 = 0$$

$$i_1 - i_2 + 0i_3 = -3$$

3.63 cont.

2

At Y;  $\sum i_{\text{entering}} = 0$

$$i_2 + \frac{V_x}{4} - i_3 = 0$$

$$V_x = 2(i_1 - i_3)$$

$$i_2 + \frac{2(i_1 - i_3)}{4} - i_3 = 0$$

$$i_2 + 0.5i_1 - 0.5i_3 - i_3 = 0$$

$$0.5i_1 + i_2 - 1.5i_3 = 0$$

$$\begin{bmatrix} 14 & 0 & 5 \\ 1 & -1 & 0 \\ 0.5 & 1 & -1.5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 3 \\ 0 \end{bmatrix}$$

$$i_1 = 2.11 \text{ A}; \quad i_2 = 5.11 \text{ A}; \quad i_3 = 4.11 \text{ A}$$


$$i_x = i_1 = 2.11 \text{ A}$$

$$V_x = 2(i_1 - i_3) = 2(2.11 - 4.11)$$

$$V_x = -4 \text{ V}$$

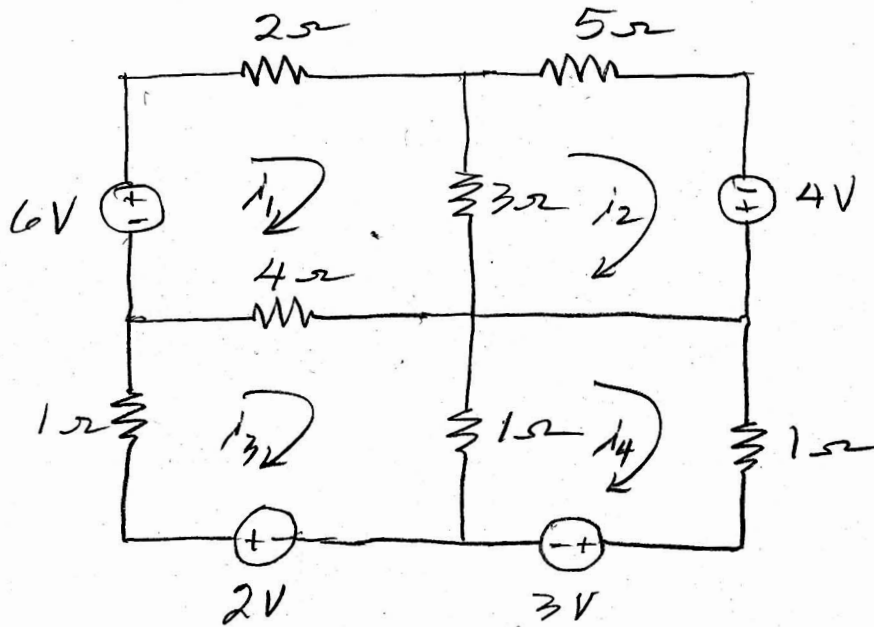3.73

Use inspection to write and solve for the mesh currents as shown in the following circuit.



$$\begin{bmatrix} 9 & -3 & -4 & 0 \\ -3 & 8 & 0 & 0 \\ -4 & 0 & 6 & -1 \\ 0 & 0 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 6 \\ 4 \\ 2 \\ -3 \end{bmatrix}$$

$$i_1 = 1.58 \text{ A}$$

$$i_2 = 1.09 \text{ A}$$

$$i_3 = 1.24 \text{ A}$$

$$i_4 = -0.88 \text{ A}$$