

ECE 300
Spring Semester, 2008
HW Set #5

Due: February 26, 2008

wlg

Name _____
Print (last, first)

Check according to your section: _____ 8:10 AM; _____ 11:10 AM

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

From the text:

PP 6.7

6.13 Ans: $v_1 = 30 \text{ V}$, $v_2 = 40 \text{ V}$


6.26 Ans: (a) $C_{eq} = 35 \mu\text{F}$; (b) $Q_1 = 0.75 \text{ mC}$, $Q_2 = 1.5 \text{ mC}$, $Q_3 = 3 \text{ mC}$; (c) $W = 393.8 \text{ mJ}$

6.46 Ans: $I_L = 2 \text{ A}$; $v_c = 0 \text{ V}$; $W_L = 1 \text{ J}$; $W_C = 0 \text{ J}$

6.61 Ans: (a) $L_{eq} = 6.67 \text{ mH}$, $i_{1(t)} = e^{-t} \text{ mA}$, $i_{2(t)} = 2e^{-t} \text{ mA}$; (b) $v_o(t) = -20e^{-t} \mu\text{V}$; (c) $W = 1.35 \text{ nJ}$

EE 300 SPRING 08
HW #5 SOLUTION

PP 6.7:

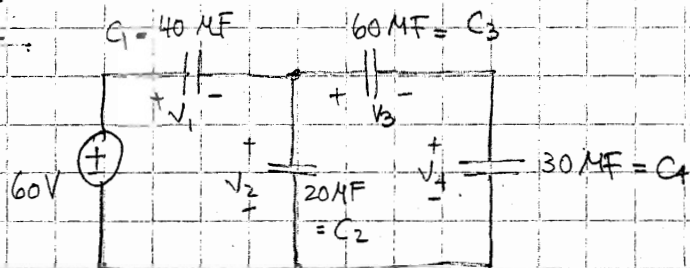

Find voltage across each capacitor

Solution:

First, we need to find C_{eq}

$$\frac{1}{C_{eq,3,4}} = \frac{1}{60\text{ nF}} + \frac{1}{30\text{ nF}} \Rightarrow C_{eq,3,4} = 20\text{ nF}$$

$$C_{eq,2,3,4} = 20\text{ nF} + 20\text{ nF} = 40\text{ nF}$$


$$\frac{1}{C_{eq}} = \frac{1}{40\text{ nF}} + \frac{1}{40\text{ nF}} \Rightarrow \underline{C_{eq} = 20\text{ nF}}$$

The total charge is

$$q = V \cdot C_{eq} = 60 \times 20 \times 10^{-6} \text{ C} = 12 \times 10^{-4} \text{ C}$$

At C_1 : capacitor;
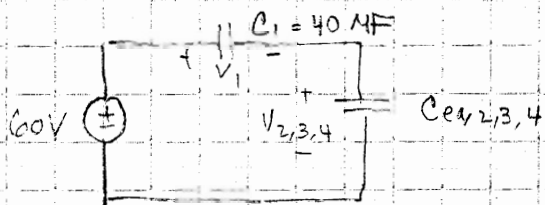
$$q_1 = q = 12 \times 10^{-4} \text{ C} \Rightarrow V_1 = \frac{q}{C_1} = \frac{12 \times 10^{-4} \text{ C}}{40 \times 10^{-6} \text{ F}} = \underline{30\text{ V}}$$



Apply KVL:

$$-60 + V_1 + V_{2,3,4} = 0$$

$$\begin{aligned} V_{2,3,4} &= 60 \text{ V} - V_1 \\ &= 60 \text{ V} - 30 \text{ V} \\ &= 30 \text{ V} \end{aligned}$$

At \$C_2\$:

Since \$C_2\$ is parallel with \$C_3\$ and \$C_4\$,

$$V_2 = V_{2,3,4} = \underline{\underline{30 \text{ V}}}$$

At capacitors \$C_3\$ and \$C_4\$:

$$\begin{aligned} q_{3,4} &= q_1 - q_2, \text{ where } q_2 = C_2 V_2 \\ &= (12 - 6) \times 10^{-4} \text{ C} &= 20 \times 10^{-6} \times 30 \\ &= 6 \times 10^{-4} \text{ C} &= 6 \times 10^{-4} \text{ C} \end{aligned}$$


So, since \$C_3\$ and \$C_4\$ are in series, \$q_{3,4} = q_3 = q_4\$:

$$\begin{aligned} V_3 &= \frac{q_3}{C_3} \\ &= \frac{6 \times 10^{-4}}{60 \times 10^{-6}} = \underline{\underline{10 \text{ V} = V_3}} \end{aligned}$$

$$\begin{aligned} V_4 &= \frac{q_4}{C_4} \\ &= \frac{6 \times 10^{-4}}{60 \times 10^{-6}} = \underline{\underline{20 \text{ V} = V_4}} \end{aligned}$$

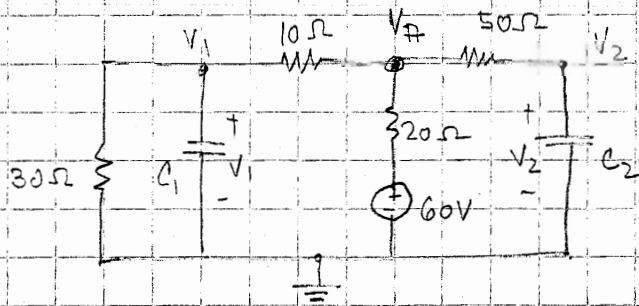Q.13

Find the voltage across the CAPACITORS in the ckt under dc condition.



Solution :

At dc condition, the capacitors are open ckt's

KCL at node V_A :

$$\frac{V_A - V_1}{10} + \frac{V_A - 60}{20} + \frac{V_A - V_2}{50} = 0$$

$$\Rightarrow 10(V_A - V_1) + 5(V_A - 60) + 2(V_A - V_2) = 0$$
$$17V_A - 10V_1 - 2V_2 = 300 \quad \text{--- (1)}$$

at node V_1 :

$$\frac{V_1 - V_A}{10} + \frac{V_1}{30} = 0$$

$$\Rightarrow 40V_1 - 30V_A = 0 \quad \text{--- (2)}$$

at node V_2

$$\frac{V_2 - V_A}{50} = 0$$

$$\Rightarrow -V_A + V_2 = 0 \quad \text{--- (3)}$$

Solving eqns (1), (2), & (3), we have

$$V_A = 40 \text{ V}$$

$$V_1 = 30 \text{ V}$$

$$V_2 = 40 \text{ V}$$

$$\therefore V_1 = 30 \text{ V}$$

$$V_2 = 40 \text{ V}$$


Q.26

Three capacitors $C_1 = 5\text{MF}$, $C_2 = 10\text{MF}$, $C_3 = 20\text{MF}$ are connected in parallel across a 150V voltage source.

- Find (a) total capacitance
(b) charge of each capacitor
(c) total energy stored in the parallel combination

Solution:
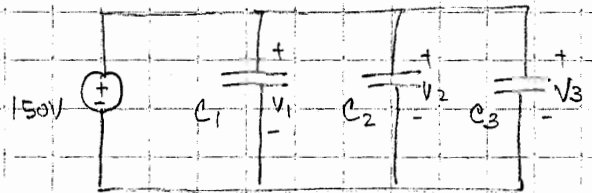
$$\begin{aligned} \text{(a)} \quad C_{eq} &= C_1 + C_2 + C_3 \\ &= (5 + 10 + 20) \text{ MF} \\ &= \underline{\underline{35 \text{ MF}}} \end{aligned}$$



$$\begin{aligned} \text{(b)} \quad q_1 &= C_1 V_1 \quad , \quad V_1 = V_2 = V_3 = V \text{ since they are in parallel} \\ &= (5 \times 10^{-6})(150) \\ &= 7.5 \times 10^{-4} \text{ C} = \underline{\underline{0.75 \text{ mC}}} \end{aligned}$$

$$\begin{aligned} q_2 &= C_2 V_2 \\ &= (10 \times 10^{-6})(150) \\ &= 15 \times 10^{-4} \text{ C} = \underline{\underline{1.5 \text{ mC}}} \end{aligned}$$


$$\begin{aligned} q_3 &= C_3 V_3 \\ &= (20 \times 10^{-6})(150) \\ &= 30 \times 10^{-4} \text{ C} = \underline{\underline{3 \text{ mC}}} \end{aligned}$$

(c) Total energy stored:


$$\begin{aligned} W &= \frac{1}{2} C_{eq} V^2 \\ &= \frac{1}{2} (35 \times 10^{-6})(150)^2 \\ &= 0.39375 \text{ J} \\ &\approx \underline{\underline{393.75 \text{ mJ}}} \end{aligned}$$

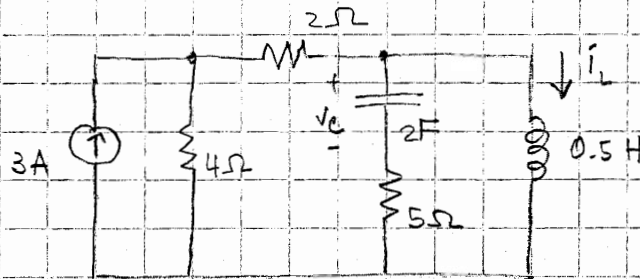Q. 46.

Find V_C , i_L and the energy stored in the capacitor & inductor in the circuit below Under dc condition



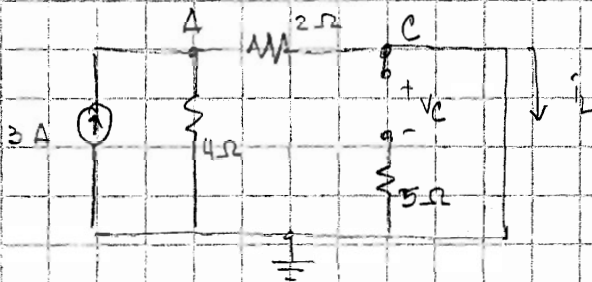Solution Under dc condition, capacitor is replaced by open ckt & inductor by short ckt



By observation, node C is connected directly to the reference (gnd) therefore $V_C = 0$

Since there is no current flows through 5Ω , we can apply current division:

$$i_L = i_{2\Omega} = (3A) \frac{4}{4+2}$$


$$i_L = \underline{\underline{2A}}$$

Energy stored :

$$W_C = \frac{1}{2} C V_C^2 = \frac{1}{2} (2) (0)^2 = \underline{\underline{0J}}$$

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (0.5) (2)^2 = \underline{\underline{1J}}$$

6.61

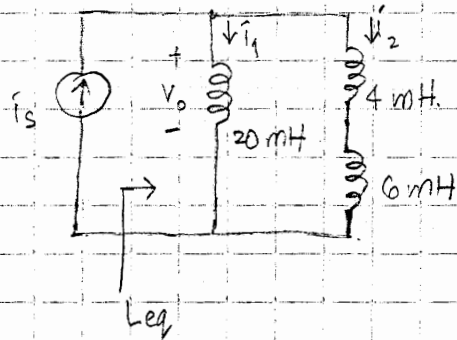

Find:

- (a) L_{eq} , $i_1(t)$, $i_2(t)$ if $i_s = 3e^{-t}$ mA
 (b) $v_o(t)$
 (c) energy stored in the 20 mH at $t = 1$ sec.

Solution

$$(a) \quad L_{eq} = 20 \text{ mH} \parallel (4+6) \text{ mH}$$

$$= \frac{20 \times 10}{20+10} = \underline{\underline{6.667 \text{ mH}}}$$

By CURRENT DIVISION:

$$i_1(t) = i_s \frac{(4+6)}{(4+6+20)}$$

$$= (3e^{-t} \text{ mA}) \left(\frac{10}{30} \right)$$

$$i_1(t) = \underline{\underline{e^{-t} \text{ mA}}}$$

$$i_2(t) = (3e^{-t} \text{ mA}) \frac{20}{30}$$

$$= \underline{\underline{2e^{-t} \text{ mA}}}$$

$$(b) \quad v_o(t) = L_{20} \frac{di_1(t)}{dt} = 20 \times 10^{-3} \frac{d}{dt} (e^{-t} \times 10^{-3})$$

$$= -20 e^{-t} \times 10^{-6} \text{ V}$$

$$v_o(t) = \underline{\underline{-20 e^{-t} \mu\text{V}}}$$

(c) Energy stored at $t = 1$ sec in 20 mH inductor:

$$W_{20} = \frac{1}{2} L_{20} (i_1(t))^2 \Big|_{t=1} = \frac{1}{2} (20 \times 10^{-3}) (e^{-1} \times 10^{-3})^2$$

$$= 1.35 \times 10^{-9} \text{ J} = \underline{\underline{1.35 \text{ nJ}}}$$