

Best copy

ECE 300  
Spring Semester, 2008  
HW Set #6

Due: March 4, 2008  
wlg  
Version 2.0

Name wlg  
Print (last, first)

Check according to your section: \_\_\_\_\_ 8:10 AM; \_\_\_\_\_ 11:10 AM

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 15 points.

From the text:

7.6 Ans:  $v(t) = 4e^{-12.5t}$  V;  $t \geq 0$

7.8 Ans: (a)  $R = 50 \Omega$ ,  $C = 5$  mF; (b)  $\tau = 0.25$  s; (c)  $W_c = 250$  mJ; (d)  $t_{\text{disp}} = 86.6$  msec

7.17 Ans:  $v_o(t) = -2e^{-16t}$  u(t) V

Also use p-spice to simulate and plot  $v_o(t)$ . Show a caption below your p-spice diagram that Says CIRCUIT USED TO PLOT  $V_o$  ( give your full name here)

PP 7.3

7.22 Ans  $i(t) = 10e^{-2.5t}$  A  $t \geq 0$   
 $v(t) = -40e^{-2.5t}$  V  $t \geq 0$


w/g

ECE 300


H.W. #6

Spring Semester 2008

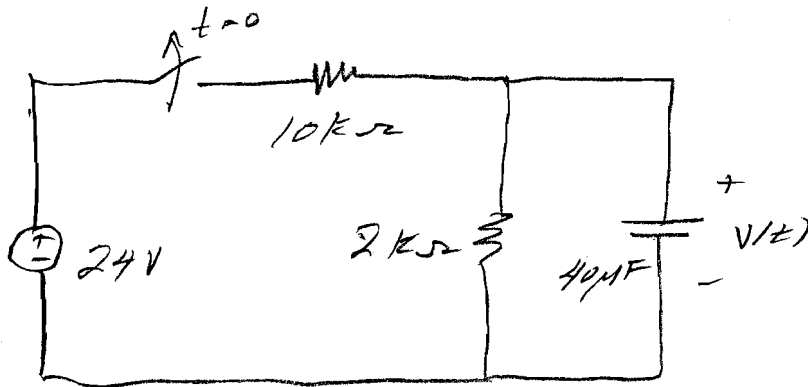7.6 The switch in the circuit below has been closed for a very long time and is opened at  $t=0$ . Find  $V(t)$  for  $t \geq 0$ .



For  $t < 0$

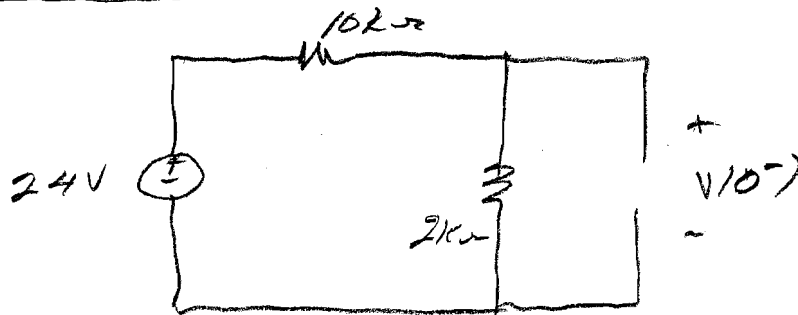

$$V(0^-) = \frac{24 \times 2k}{10k + 2k} = 4V$$


Voltage across the capacitor does not change instantaneously - so

$$V(0^+) = V(0^-) = 4V$$

7.6 cont.

2

$$t > 0$$

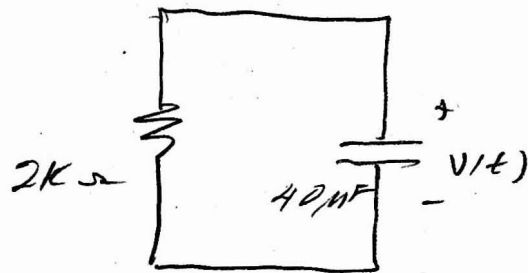

$$R_{eq} = 2k\Omega \quad C = 40\mu F$$

$$\tau = RC = 2 \times 10^3 \times 40 \times 10^{-6} = 80 \times 10^{-3}$$

$$\tau = 0.08 \text{ sec.}$$

From having solved the above circuit  
from we know

$$V(t) = V(0) e^{-\frac{t}{\tau}}$$


$$V(t) = 4 e^{-\frac{t}{0.08}}$$

$$V(t) = 4 e^{-12.5t} \quad t \geq 0$$

7.8 Given the following circuit. It is known that

$$v(t) = 10e^{-4t} \text{ V}$$

$$i(t) = 0.2e^{-4t} \text{ A}$$

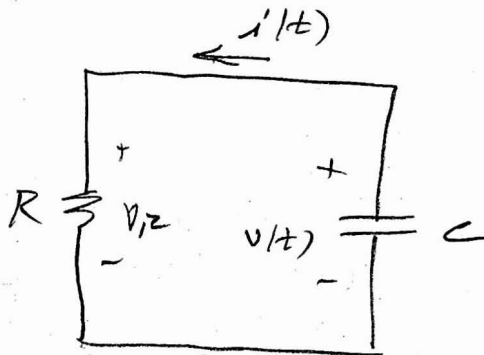

(a) Find  $R$  and  $C$

$$i = -C \frac{dv}{dt} = -C \frac{d}{dt} 10e^{-4t} = +4C \times 10e^{-4t}$$

$$i(0) = 0.2$$

$$0.2 = +4 \times 10 \times C$$

$$C = \frac{0.2}{40} = 0.005 \text{ F} = 5 \text{ mF}$$

$$v_R = v(t) = Ri(t)$$

$$v_R(0) = 10e^{-4t} \Big|_{t=0} = 10 = i(0)R = 0.2R$$

$$R = \frac{10}{0.2} = 50 \Omega$$

(b)  $T = RC = 50 \times 5 \times 10^{-3} = 250 \times 10^{-3} = 0.25 \text{ sec}$

(c)  $W_C = \frac{1}{2} C v^2(0) = \frac{1}{2} \times 5 \times 10^{-3} \times 10^2 = 0.25 \text{ J}$

(d) Energy will be dissipated in  $R$ .

7.8 part

$$W_R = \frac{1}{2} \left[ \frac{1}{2} C V_c^2(0) \right] = \frac{0.25}{2} = 0.125 \text{ J}$$

$$W_R = \int P_R dt = \int i^2 R dt$$

$$W_R = \int_0^{t_0} (0.2 e^{-4t})^2 \times 50 dt = 2 \int_0^{t_0} e^{-8t} dt$$

$$= \frac{2}{-8} [t_0 - 1] = .25 [1 - e^{-8t_0}]$$

$$0.125 = 0.25 [1 - e^{-8t_0}]$$

$$0.5 = 1 - e^{-8t_0}$$

$$e^{-8t_0} = 1 - 0.5 = 0.5$$


$$-8t_0 \ln e = \ln(0.5) = -0.693$$

$$t_0 = \frac{0.693}{8} = 0.08664 \text{ sec}$$


$$t_0 = 86.6 \text{ m sec}$$

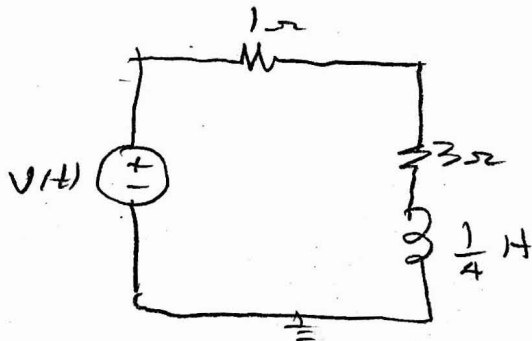7.17

Consider the circuit below. Find  $v_o(t)$   
 if  $i(t) = 2A$  and  $v(t) = 0$ .



With  $v(t) = 0$

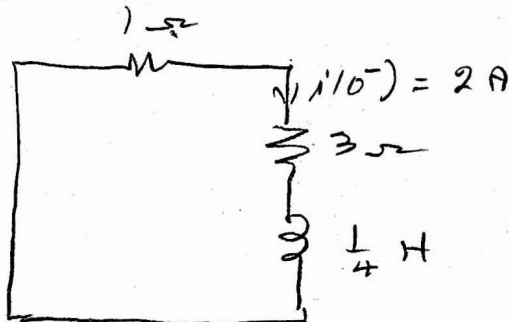

$$R_{eq} = 4 \Omega$$

$$i(t) = i(0) e^{-\frac{t}{\tau}}$$


$$\tau = \frac{L}{R} = \frac{1}{4 \times 4} = \frac{1}{16}$$

$$i(t) = 2 e^{-16t} \text{ A}$$

$$v_o(t) = -1 \times i(t) = -2 e^{-16t} \text{ A}$$

Simulation next.


Call it LC7-17

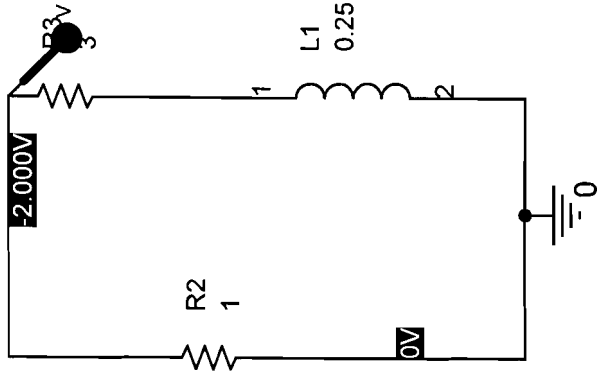

Positive IC is from 1 to 2

We want to go 2 to 1 so we use -2


Simulation for Problem 7\_17 (LC7\_17) Walter Green

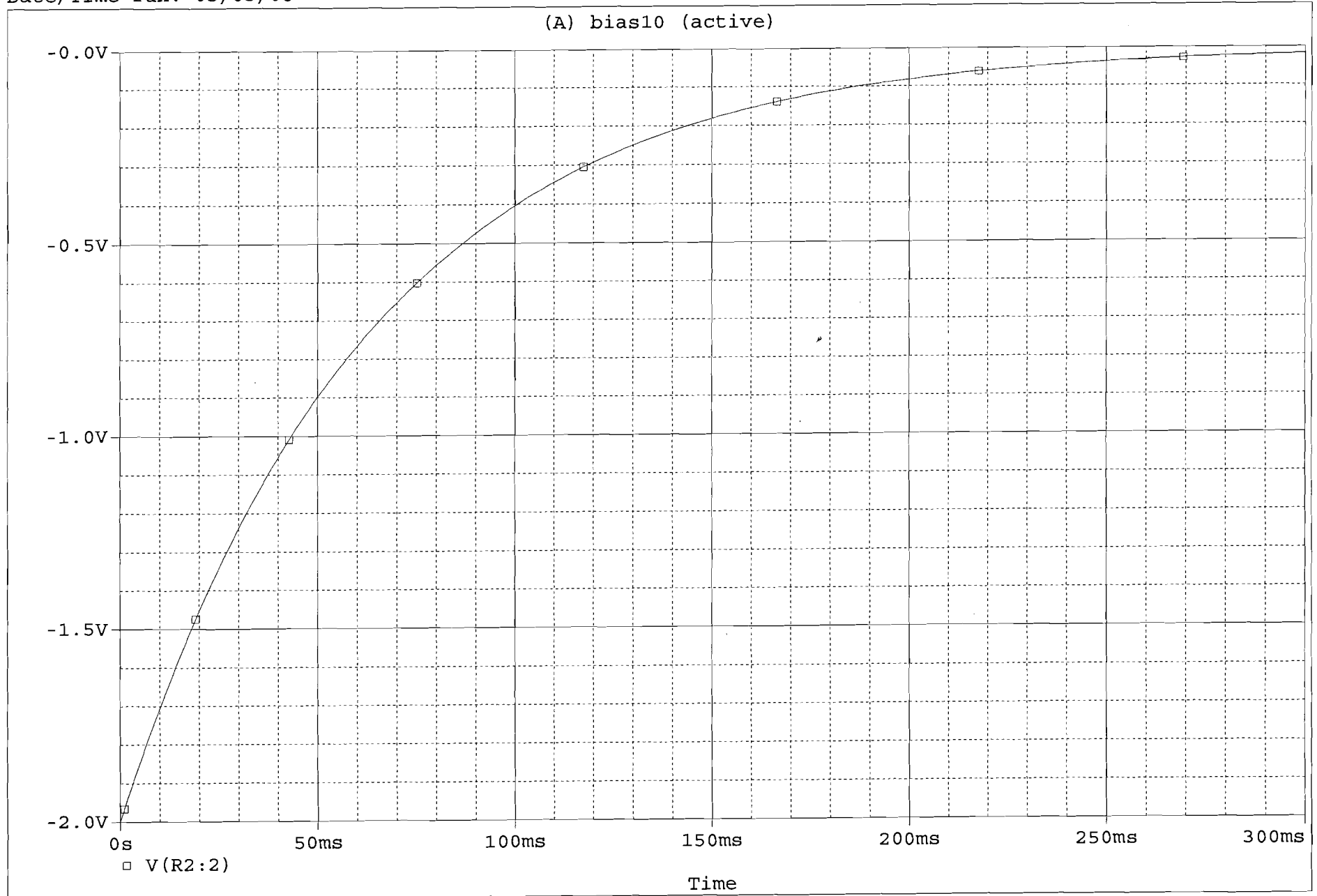



PP 7.3

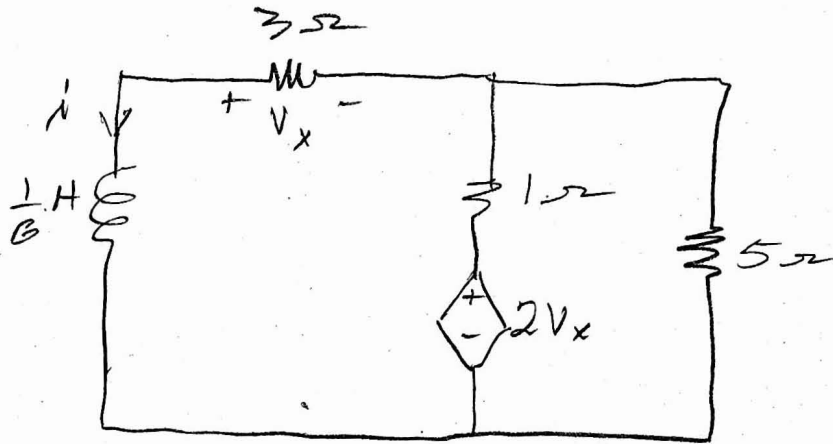
FIND  $i(t)$  and  $V_x(t)$  in the following circuit. Let  $i(0^+) = 5A$



We know that  $i(t)$  will be of the form  $i(t) = I_0 e^{-\frac{R_{eq} t}{L}}$

$I_0$  given as 5A

We must find  $R_{eq}$

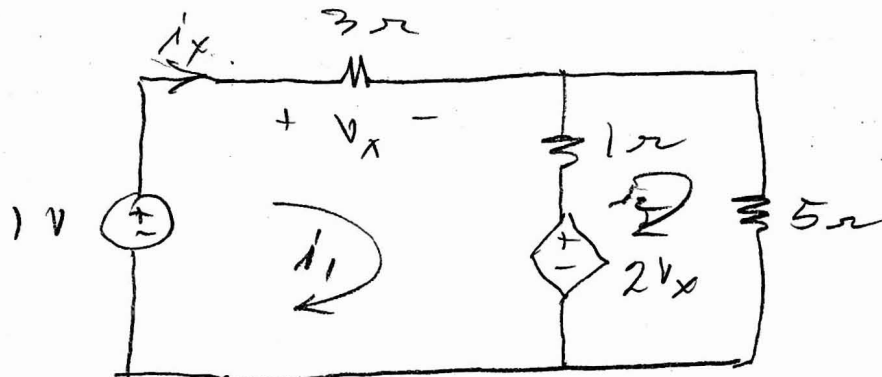

$$R_{eq} = \frac{1}{i_x}$$

P.P. 7.3 cont.

Writing mesh equations

$$-1 + 4i_1 - i_2 + 2V_x = 0$$

$$V_x = 3i_1$$

$$-1 + 4i_1 - i_2 + 6i_1 = 0$$

$$\boxed{10i_1 - i_2 = 1}$$

$$-2V_x + 6i_2 - i_1 = 0$$

$$-6i_1 + 6i_2 - i_1 = 0$$

$$\boxed{-7i_1 + 6i_2 = 0}$$

$$\begin{bmatrix} 10 & -1 \\ -7 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$i_1 = 0.1132 \text{ A}$$

$$I_q = \frac{1}{0.1132} = 8.83$$

$$\frac{R_q}{s} = \frac{8.83}{1/6} = 53$$


$$\therefore \boxed{i_x(t) = 5e^{-53t} \text{ A}}$$

$$V_x = -3i_x$$

$$\boxed{V_x = -15e^{-53t} \text{ V}}$$

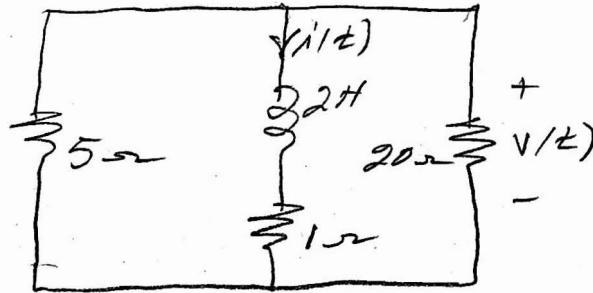7.22

Find  $i(t)$  and  $v(t)$  for  $t > 0$  in the following circuit. Assume  $i(0) = 10\text{A}$




$$R_{eq} = 1 + 5 \parallel 20$$

$$5 \parallel 20 = \frac{5 \times 20}{25} = 4 \Omega$$

$$R_{eq} = 5 \Omega$$
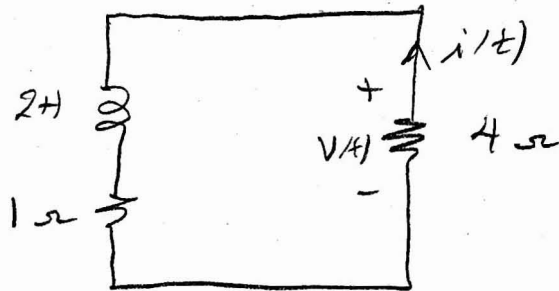
$$i(t) = i(0) e^{-\frac{R_{eq} t}{L}} = 10 e^{-2.5t} \text{ A}$$



$$v(t) = -4 i(t)$$

$$v(t) = -40 e^{-2.5t} \text{ V}$$