

Desk Copy

ECE 300
Spring Semester, 2008
HW Set #11

Due: April 3, 2008

Name wlg
Print (last, first)

wlg

Check according to your section: _____ 8:10 AM; _____ 11:10 AM

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10%, except problem (10.55) counts 20%.

This is a minimum problem set. You will probably want to work other problems to refine your understanding of A.C. circuit analysis.

(9.42) Basic Concepts: Voltage Division

Ans: $v_o(t) = 17.14\cos(200t)$ V

(9.47) Basic Concepts: Impedance

Ans: $i_s(t) = 460.7\cos(2000t + 52.6^\circ)$ mA

(9.50) Basic Concepts: Current Division

Ans: $v_x(t) = 50\cos(100t - 50^\circ)$ V

(9.60) Basic Concepts: Impedance (calculator exercise)

Ans: $Z_{in} = (51.1 + j9.88) \Omega$

(9.64) Basic Concepts: Impedance

Ans: $Z_T = (19 - j5) \Omega$, $I = 1.53\angle 104.7^\circ$ A

✓ (10.14) Nodal Analysis

Ans: $V_1 = 28.9\angle 135.4^\circ$ V; $V_2 = 49.18\angle 124.1^\circ$ V

✓ (10.17) Nodal Analysis

Ans: $I_o = 9.25\angle -162.1^\circ$ A

✓ (10.31) Mesh Analysis

Ans: $I_o = 2.18\angle 61.4^\circ$ A

✓ (10.38) Mesh Analysis

Ans: $I_o = 3.35\angle 174.3^\circ$ A

✓ (10.55) Thevenin and Norton


In finding the Norton circuit, you are to do so by finding the open-circuit voltage and short-circuit Current. Draw both the Thevenin and Norton equivalent circuits.

Ans: (a) $Z_{TH} = Z_N = 22.36\angle -63.4^\circ \Omega$; $V_{TH} = -50\angle 30^\circ$ V; $I_N = 2.24\angle 273.4^\circ$ A

(b) $Z_{TH} = Z_N = 10\angle 26^\circ \Omega$; $V_{TH} = 33.92\angle 58^\circ$ V; $I_N = 3.39\angle 32^\circ$ A


HW # 11 Solution
ECE 300 Sp 08

9.42

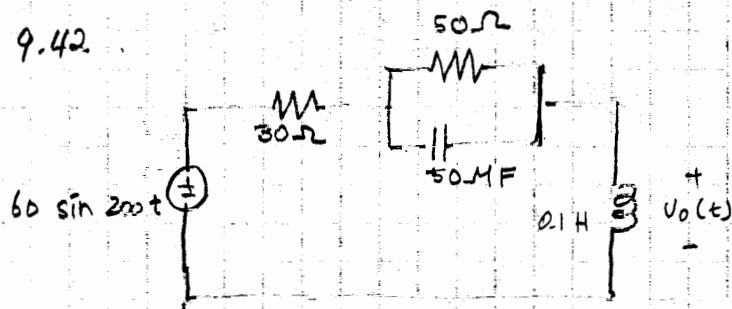

Calculate $v_o(t)$

In phasor representation: $\omega = 200$

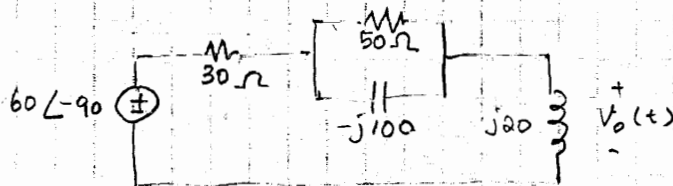

$$50 \parallel -j100 = \frac{(50)(-j100)}{50 - j100} = 40 - j20$$

$$V = \frac{j20}{30 + j20 + 40 - j20}$$


$$(60 \angle -90^\circ) = 60 \angle -90^\circ$$

$$= \frac{j20}{70} (60 \angle -90^\circ)$$

$$= 17.14 \angle 0^\circ$$


$$\therefore v_o(t) = 17.14 \cos(200t) \text{ V}$$

9.47

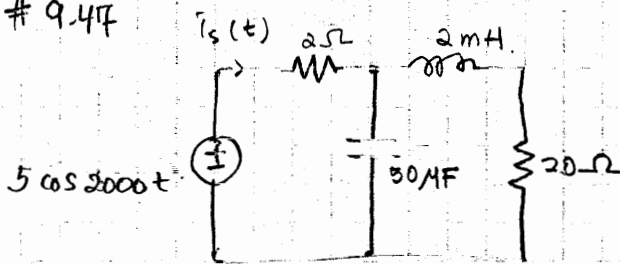

Calculate $i_s(t)$

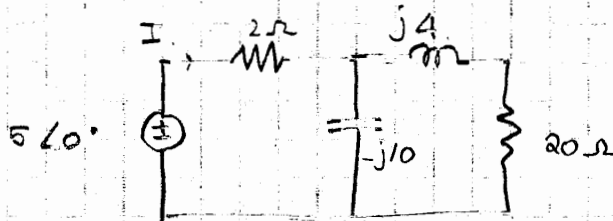In PHASOR REPRESENTATION: $\omega = 2000$




$$-j10 \parallel (20 + j4) = \frac{(-j10)(20 + j4)}{20 - j6} = 4.59 - j8.62$$

$$Z = 2 + (4.59 - j8.62) \\ = 6.59 - j8.62$$

$$I = \frac{V}{Z} = \frac{5 \angle 0}{6.59 - j8.62} = 0.28 + j0.37 \\ = 0.46 \angle 52.6^\circ$$


$$\therefore i_s(t) = 0.46 \cos(2000t + 52.6^\circ) \text{ A}$$

#9. 50

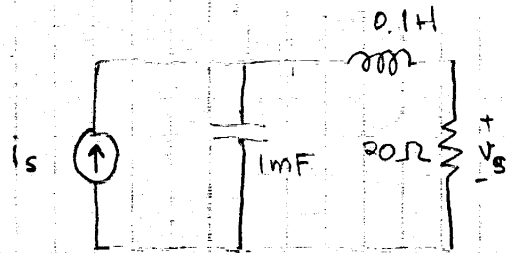

Determine v_s ,
given $i_s(t) = 5 \cos(100t + 40^\circ) \text{ A}$

In phasor: $\omega = 100$

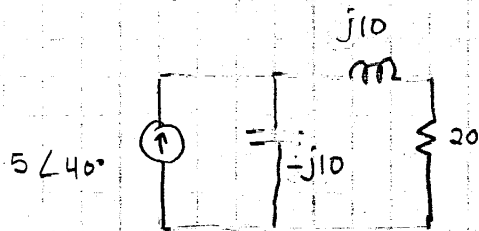


$$\begin{aligned} I \text{ flows through } j10 \text{ and } 20 \Omega &= (5 \angle 40^\circ) \frac{-j10}{-j10 + j10 + 20} \\ &= (5 \angle 40^\circ) \frac{-j10}{20} \\ &= 2.5 \angle -50^\circ \end{aligned}$$

$$\begin{aligned} V_{20} &= 20 (-2.5 \angle -50^\circ) \\ &= 50 \angle -50^\circ \end{aligned}$$

$$\therefore v_s(t) = 50 \cos(100t - 50^\circ) \text{ V}$$

9,60

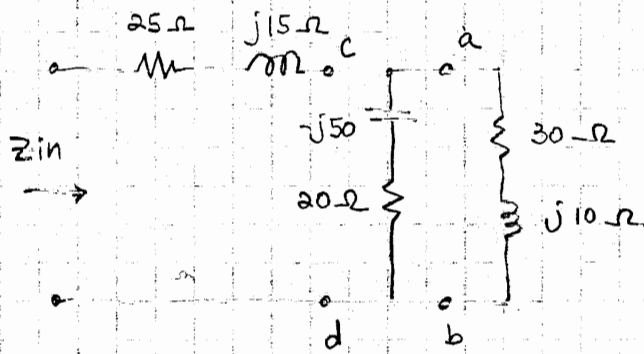

Calculate Z_{in}

$$Z_{ab} = (30 + j10) \Omega$$

$$Z_{cd} = (30 + j10) // (20 - j50)$$


$$= \frac{(30 + j10)(20 - j50)}{(30 + j10) + (20 - j50)}$$

$$= (26.1 - j5.12) \Omega$$

$$\therefore Z_{in} = (25 + j15) + (26.1 - j5.12) \Omega$$

$$= \underline{\underline{(51.1 + 9.88j) \Omega}}$$

9.64 FIND Z_T and I .

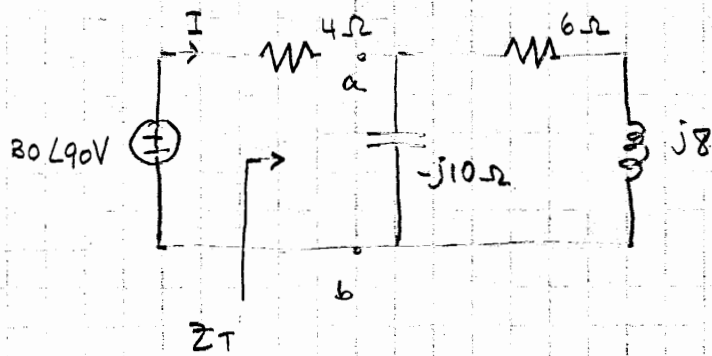


$$Z_{ab} = (-j10) \parallel (6 + j8) = \frac{(-j10)(6 + j8)}{6 + j8 - j10}$$
$$= (15 - j5) \Omega$$

$$\therefore Z_T = 4 + (15 - j5)$$
$$= (19 - j5) \Omega$$
$$= \underline{\underline{\hspace{2cm}}}$$

$$I = \frac{V}{R} = \frac{30 \angle 90^\circ}{19 - j5}$$
$$= (-0.388 + j1.48) \text{ A}$$
$$= \underline{\underline{1.53 \angle 104.74 \text{ A}}}$$

Wlg

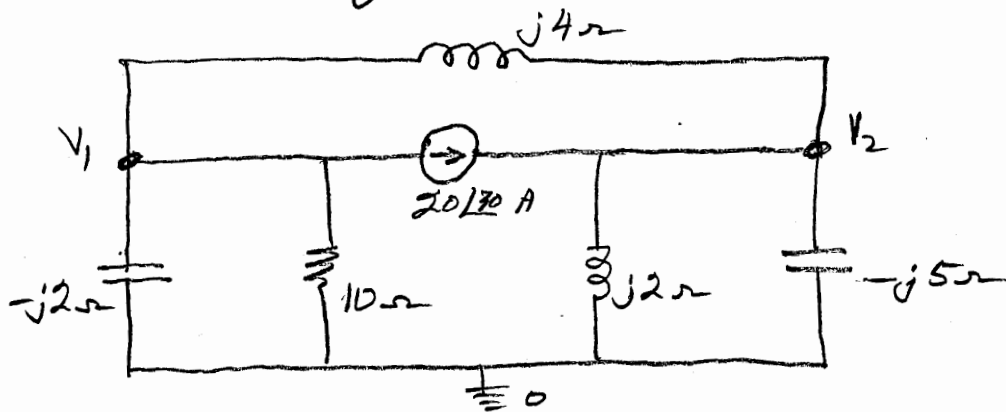(10.14) Determine node voltages V_1 & V_2 in the following circuit.



At V_1

$$-\frac{V_1}{j2} + \frac{V_1}{10} + \frac{V_1 - V_2}{j4} = -20 \angle 30^\circ$$

$$j0.5V_1 + 0.1V_1 - j0.25V_1 + j0.25V_2 = -20 \angle 30^\circ$$

$$\boxed{(0.1 + j0.25)V_1 + j0.25V_2 = -20 \angle 30^\circ}$$

At V_2

$$\frac{V_2}{j2} - \frac{V_2}{j5} + \frac{V_2 - V_1}{j4} = 20 \angle 30^\circ$$

$$-j0.5V_2 + j0.2V_2 - j0.25V_2 + j0.25V_1 = 20 \angle 30^\circ$$


$$\boxed{j0.25V_1 - j0.55V_2 = 20 \angle 30^\circ}$$

$$\begin{bmatrix} 0.1 + j0.25 & j0.25 \\ j0.25 & -j0.55 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -20 \angle 150^\circ \\ 20 \angle 30^\circ \end{bmatrix}$$

$$V_1 = 28.9 \angle 135.4^\circ \text{ V} \quad V_2 = 49.17 \angle 124.1^\circ \text{ V}$$

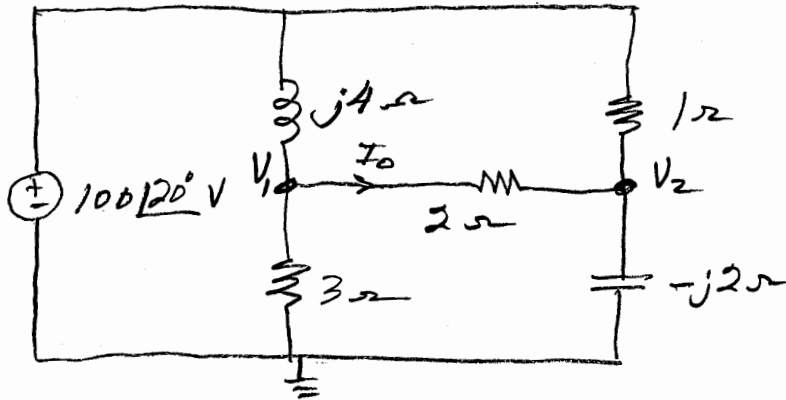(10.17)

Use nodal analysis to find current I_0 in the following circuit.



At V_1

$$\frac{V_1 - 100\angle 20^\circ}{j4} + \frac{V_1}{3} + \frac{V_1 - V_2}{2} = 0$$

$$-j0.25V_1 + j25\angle 20^\circ + 0.3333V_1 + 0.5V_1 - 0.5V_2 = 0$$

$$(0.833 - j0.25)V_1 - 0.5V_2 = -j25\angle 20^\circ = 25\angle -70^\circ$$

At V_2

$$\frac{-V_2}{j2} + \frac{V_2 - 100\angle 20^\circ}{1} + \frac{V_2 - V_1}{2} = 0$$

$$j0.5V_2 + V_2 - 100\angle 20^\circ + 0.5V_2 - 0.5V_1 = 0$$

$$-0.5V_1 + (1.5 + j0.5)V_2 = 100\angle 20^\circ$$

(10.17) cont

$$\begin{bmatrix} 0.833 - j0.25 & -0.5 \\ -0.5 & 1.5 + j0.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 25 \angle -70^\circ \\ 100 \angle 20^\circ \end{bmatrix}$$


$$V_1 = 63.066 - j14.657 \text{ V} \quad V_2 = 80.676 - j8.976 \text{ V}$$

$$V_1 = 64.75 \angle -13.08^\circ \text{ V} \quad V_2 = 81.17 \angle -6.35^\circ \text{ V}$$

$$I_0 = \frac{V_1 - V_2}{2} = 9.25 \angle -162.13^\circ \text{ A}$$

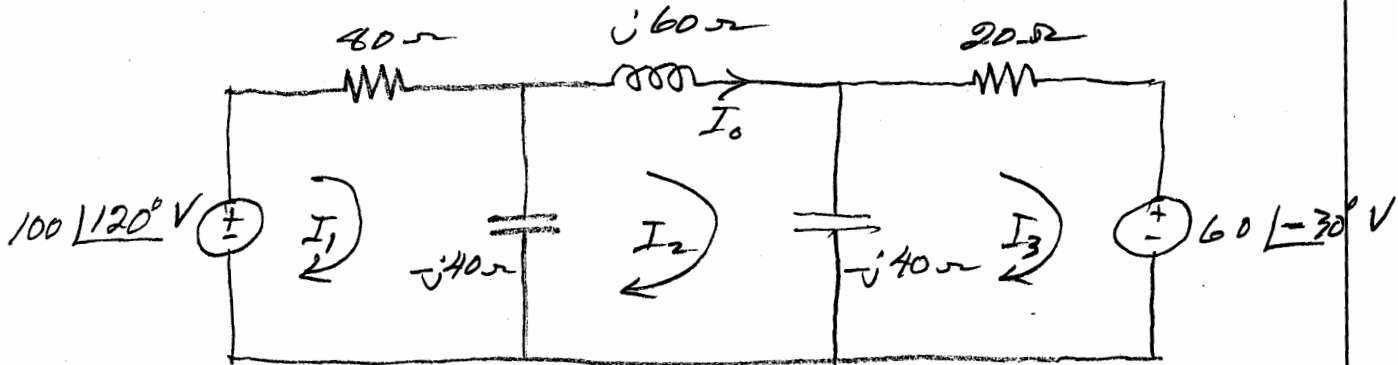(10.31)

Use mesh analysis to determine the current I_0 in the following circuit.



Assign mesh currents I_1 , I_2 and I_3 .
Write the 3 mesh equations. Solve for
 I_1 , I_2 and I_3 . Then $I_0 = I_2$

Mesh 1

$$(80 - j40)I_1 + j40I_2 = 100 \angle 120^\circ \quad (1)$$

Mesh 2

$$-j40(I_2 - I_1) + j60I_2 - j40(I_2 - I_3) = 0$$

$$j40I_1 - j20I_2 + j40I_3 = 0 \quad (2)$$

Mesh 3

$$-j40(I_3 - I_2) + 20I_3 + 60 \angle -30^\circ$$

$$j40I_2 + (20 - j40)I_3 = -60 \angle -30^\circ \quad (3)$$

(10.31) cont

From equations (1), (2), (3)

$$\begin{bmatrix} 30 - j40 & j40 & 0 \\ j40 & -j20 & j40 \\ 0 & j40 & 20 - j40 \end{bmatrix} \begin{bmatrix} \underline{I_1} \\ \underline{I_2} \\ \underline{I_3} \end{bmatrix} = \begin{bmatrix} 100 \angle 120^\circ \\ 0 \\ 60 \angle 150^\circ \end{bmatrix}$$


$$\underline{I_1} = (0.0412 + j0.5819) \text{ A}$$

$$\underline{I_2} = (1.0424 + j1.914) \text{ A} = 2.179 \angle 61.43^\circ \text{ A}$$


$$\underline{I_3} = (0.4800 + j0.3752) \text{ A}$$

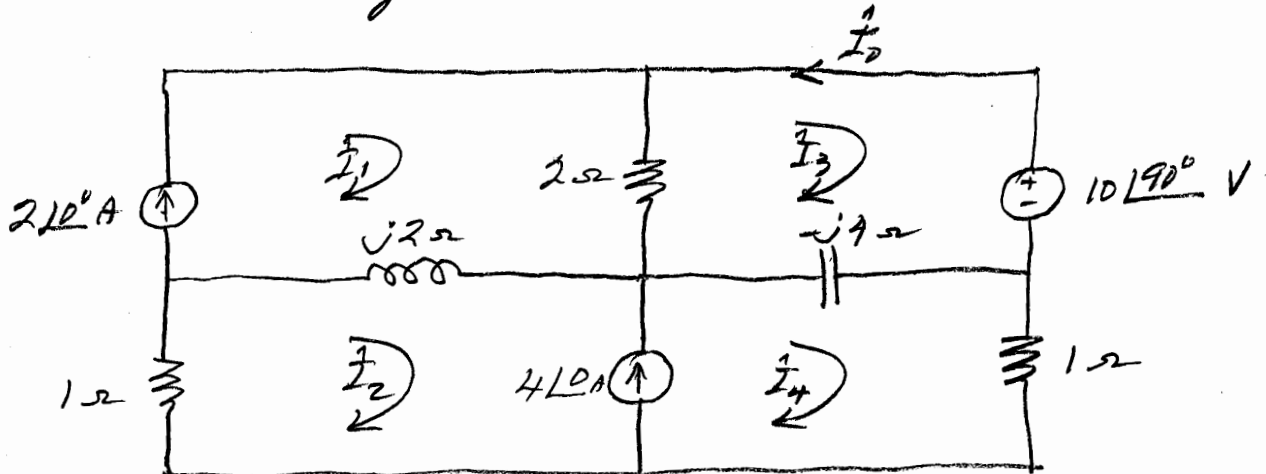(10.38)

Use mesh analysis to find current I_0 in the following circuit.



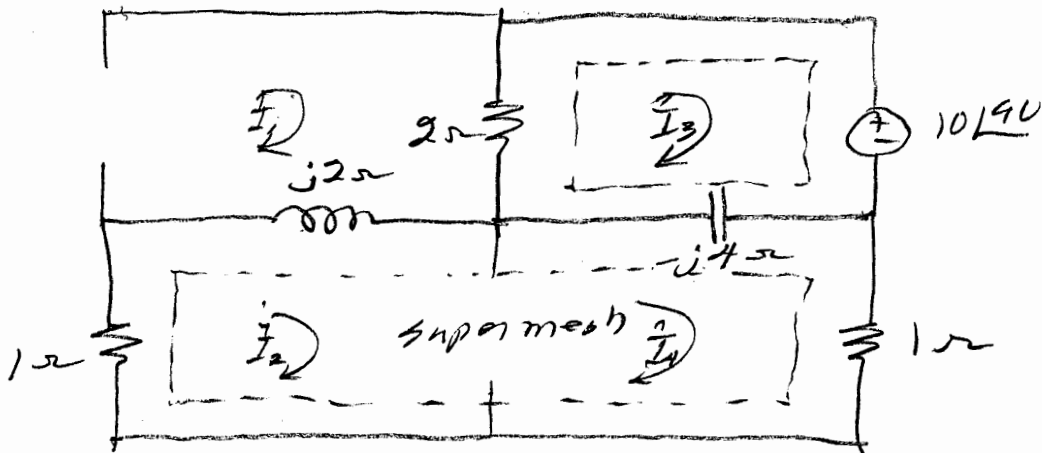Assign the mesh currents as shown above. Remove current sources $2\angle 0^\circ \text{ A}$ and $4\angle 0^\circ \text{ A}$. Redraw the circuit.



Write mesh equation for mesh 3 and the supermesh.

Impose the two constraint equations

$$I_1 = 2\angle 0 \quad (1)$$

$$I_4 - I_2 = 4\angle 0 \quad (2)$$

(10.38)

Mesh 3

$$2(I_3 - I_1) + 10 \angle 90^\circ - j4(I_3 - I_4) = 0$$

$$\boxed{-2I_1 + 0I_2 + (2-j4)I_3 + j4I_4 = -10 \angle 90^\circ} \quad (3)$$

Supermesh

$$I_2 + j2(I_2 - I_1) - j4(I_4 - I_3) + I_4 = 0$$

$$\boxed{-j2I_1 + (1+j2)I_2 + j4I_3 + (1-j4)I_4 = 0} \quad (4)$$

Combine (3) and (4) with (1) and (2)

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1 \\ -2 & 0 & 2-j4 & j4 \\ -j2 & 1+j2 & j4 & 1-j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 2 \angle 0 \\ 4 \angle 0 \\ 10 \angle -90 \\ 0 \end{bmatrix} \begin{matrix} (1) \\ (2) \end{matrix}$$

Left my TI 86 at home. TI 68 not enough memory.

Solved by using MATLAB. Program on the following page.

(10.38) cont

3

C:\MATLAB6p5\work\HW10_38.m
March 31, 2008

Page 1
10:23:29 AM

```
% Homework problem 10.38 from Alexander  
% March 31, 2008. Office PC: Program HW10_38.m  
% By: W. Green for ECE 300 Spring 2008
```

```
B = [2;4;-j*10;0];
```

```
A = [1, 0, 0, 0;0, -1, 0, 1;-2, 0, 2-j*4 ,j*4; -j*2, 1+j*2, j*4, 1-j*4];
```

```
I = inv(A)*B;
```

```
I1 = I(1)
```

```
I2 = I(2)
```

```
I3 = I(3)
```

```
I4 = I(4)
```

```
Io = -I3
```

```
magIo = abs(Io)
```

```
%gives the magnitude of Io
```

```
angIo = 57.3*phase(Io)
```

```
%angle of Io converted from radians to degrees
```

```
>> HW10_38
```

```
I1 =
```

```
2
```

```
I2 =
```

```
-3.0000 + 0.3333i
```

```
I3 =
```

```
3.3333 - 0.3333i
```

```
I4 =
```

```
1.0000 + 0.3333i
```

```
Io =
```

```
-3.3333 + 0.3333i
```

```
magIo =
```

```
3.3500
```

```
angIo =
```

```
174.3022
```

(10.55)

Find the Thevenin and Norton for the following circuit.

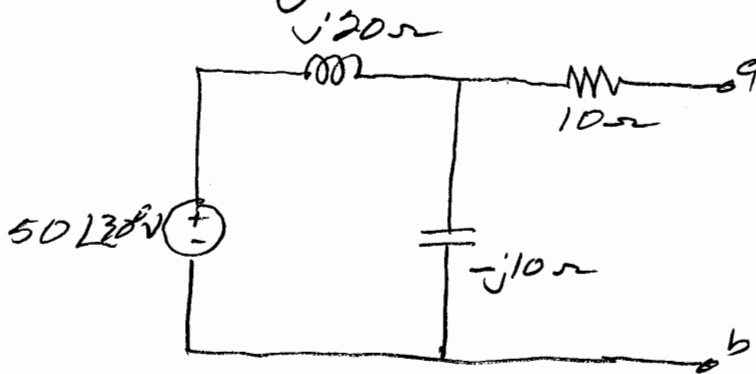


Figure 1

Thevenin Solution

V_{ab} open circuit = V_{TH} .

(a) V_{TH} is the voltage across the $-j10\Omega$ impedance of Figure 1.

$$V_{TH} = \frac{(50\angle 30^\circ) \times (-j10)}{-j10 + j20} = \frac{(50\angle 30^\circ)(10\angle -90^\circ)}{10\angle 90^\circ}$$

$$\underline{V_{TH} = 50\angle -150^\circ = -50\angle 30^\circ \text{ V}}$$

Find Z_{TH} from the following

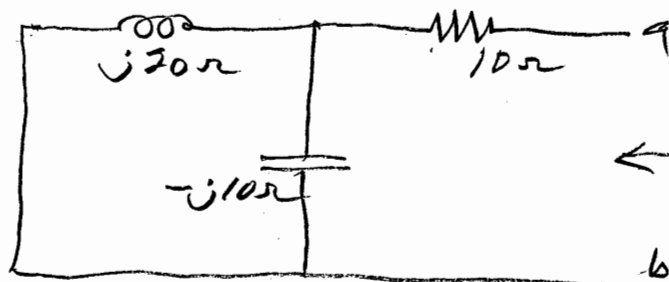


Figure 2

$$Z_{TH} = 10 + \frac{(20\angle 90^\circ)(10\angle -90^\circ)}{20\angle 90^\circ + 10\angle -90^\circ} = 22.36\angle -63.4^\circ \Omega$$

(10.55)

(a) cont

The Thevenin circuit is given below

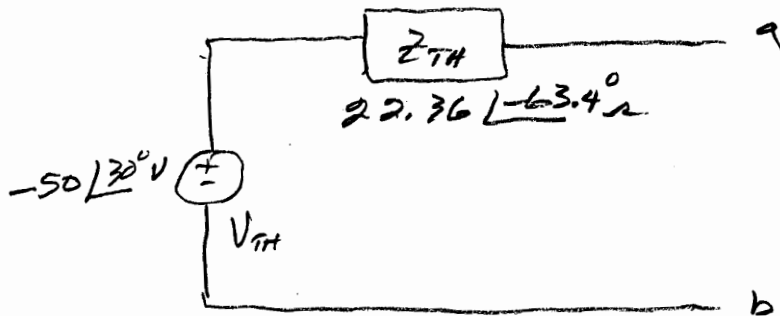


Figure 3
Thevenin circuit
for part (a)

(a) Norton:

Find $I_{sc} = I_N$ and V_{oc}

Referring to Figure 1 with terminals a-b shorted,

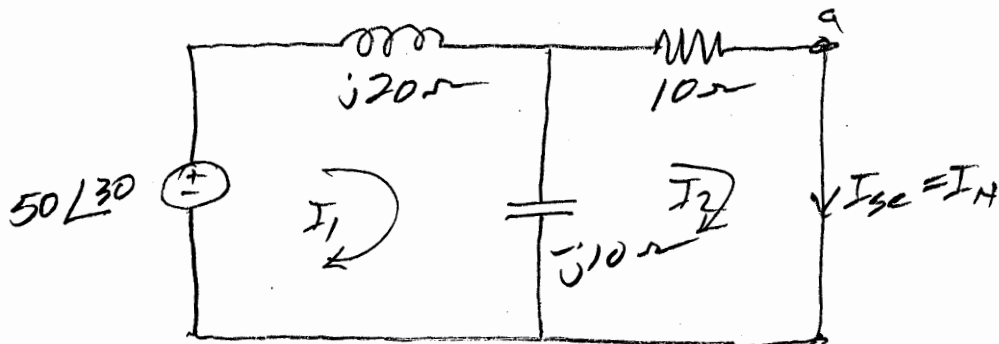


Figure 4: Circuit for finding I_N , part (a)

$$j10I_1 + j10I_2 = 50 \angle -150^\circ \quad (1)$$

$$j10I_1 + (10 - j10)I_2 = 0 \quad (2)$$

(10.55) cont.

solving (1) and (2)

$$\begin{bmatrix} j/0 & j/0 \\ j/0 & 10-j/0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \angle 30 \\ 0 \end{bmatrix}$$

$$I_1 = -2.366 + j2.098 \text{ A}$$

$$I_2 = I_N = 2.24 \angle -86.6^\circ$$

$$\therefore I_N = 2.24 \angle 273.4^\circ$$

Z_{TH} same as above.

$$\text{As a check } Z_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{V_{TH}}{I_N} = \frac{-50 \angle 30}{2.24 \angle 273.4}$$

$$Z_{TH} = 22.3 \angle -63.4^\circ \Omega \text{ check}$$

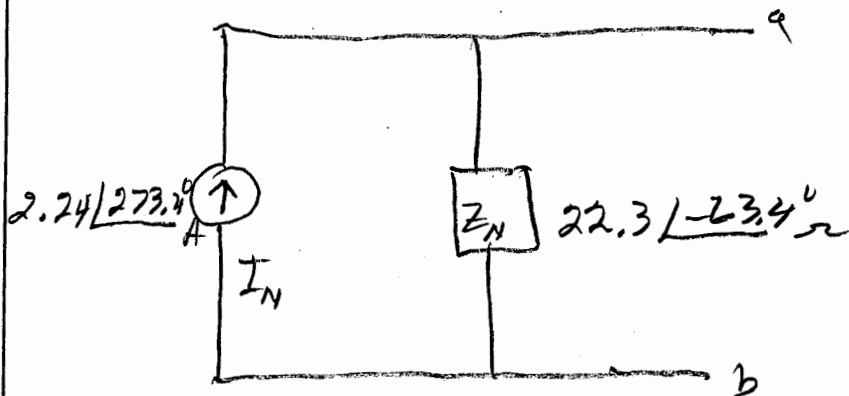


Figure 5: Norton equivalent ckt, part (a)

(10.55) cont

4

Part (b)

Find the Thevenin and Norton equivalent circuits for the circuit shown below.

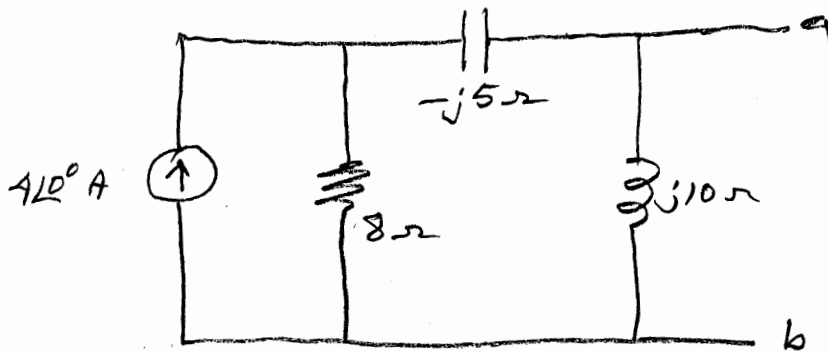


Figure 6: Circuit for part (b)

Thevenin Part (b)

Using current division;

$$V_{ab} = V_{TH} = \left(\frac{(4\angle 0)(8\angle 0)}{8 - j5 + j10} \right) (j10)$$

$$V_{TH} = 33.92 \angle 58^\circ \text{ V}$$

Use the following circuit to find Z_{TH} .

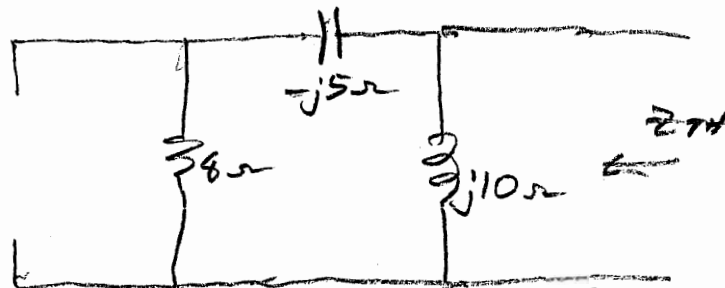


Figure 7: Circuit for finding Z_{TH} , part (b)

(1055) cont
part 1b)

$$Z_{TH} = \frac{(j10)(8-j5)}{j10 + 8 - j5} = 10 \angle 26^\circ \Omega$$


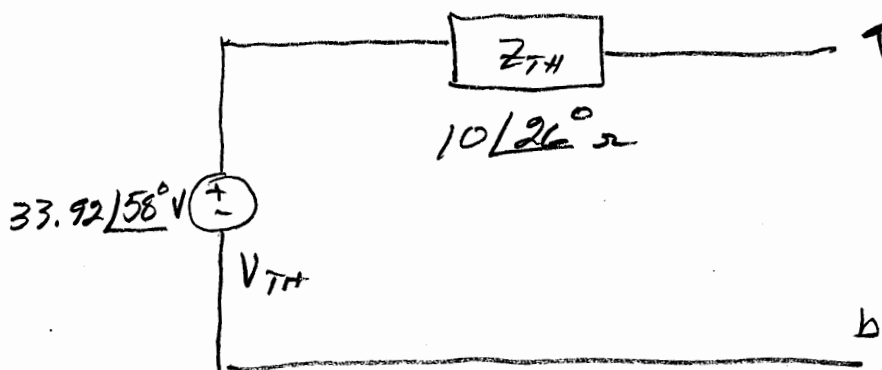


Figure 8: Thevenin circuit for part (b)

1b) Norton circuit

To get I_N , find I_{sc} below

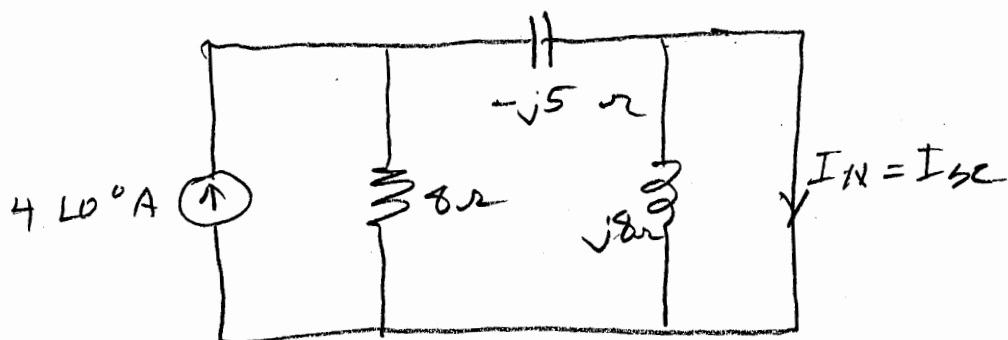

The $j8 \Omega$ coil is shorted out.

Find I_N then as shown in
Figure 9.

(10.55) cont.
part (b)

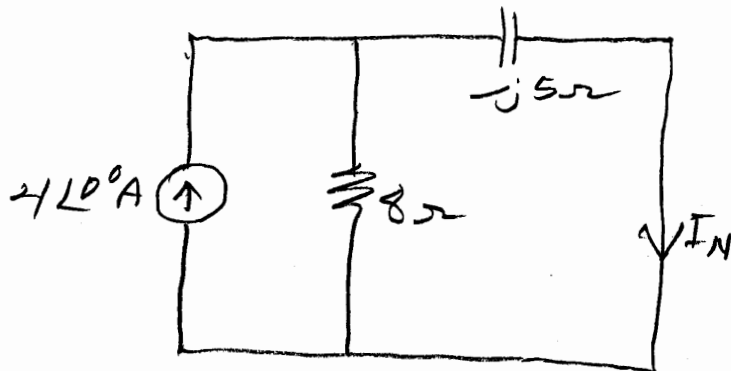


Figure 9: circuit for finding I_N , part (b)

$$I_N = \frac{4 \times 8}{8 - j5} = 3.39 \angle 32^\circ \text{ A}$$

$$Z_N = Z_{TH} = 10 \angle 26^\circ \Omega$$

As a check

$$Z_N = Z_{TH} = \frac{V_{TH}}{I_N} = \frac{33.92 \angle 56^\circ}{3.39 \angle 32^\circ}$$

$$Z_N = Z_{TH} = 10 \angle 26^\circ \Omega \text{ check}$$

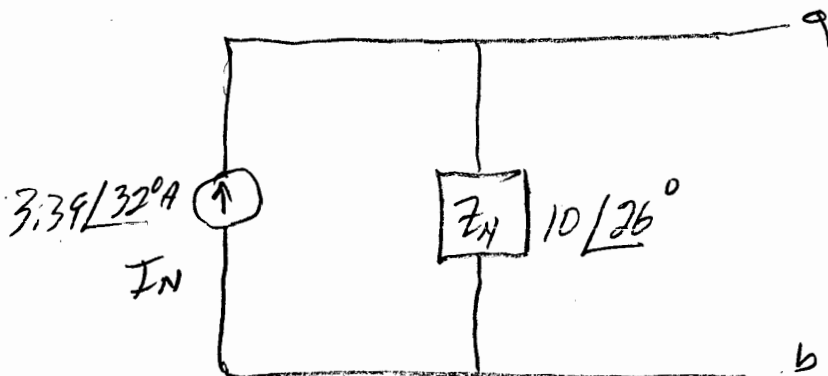


Figure 10: Norton Circuit, part (b)