

ECE 300
Spring Semester, 2008
Test #1


wlg: Test A : Section I: 11:10 AM

Name _____
 Print (last, first)

Work the exam on your own engineering paper. Work on one side of your paper only. Attach your work to the back of this exam sheet and staple in the top left hand corner. Each problem 20%. Be sure to give units for all your answers.

(1) You are given the circuit of Figure 1. Use mesh analysis in working this problem.

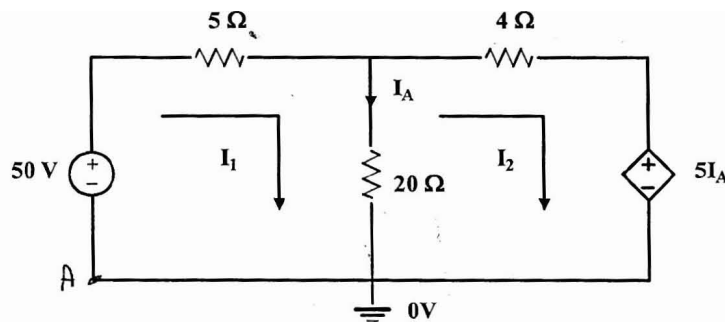- (a) Find the currents I_1 and I_2 .
 (b) Determine how much power is being supplied by the dependent source.



$$(a) -50 + 5I_1 + 20(I_1 - I_2) = 0$$

$$25I_1 - 20I_2 = 50$$

$$20(I_2 - I_1) + 4I_2 + 5(I_1 - I_2) = 0 \rightarrow (I_A = I_1 - I_2)$$

$$-15I_1 + 19I_2 = 0$$

$$\begin{bmatrix} 25 & -20 \\ -15 & 19 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \end{bmatrix}$$

$$\underline{I_1 = 5.43 A}; \quad \underline{I_2 = 4.29 A}$$

Test A

2

(1) continued

(6)

$$P_{sup} = (5I_A)(-I_2)$$


$$= 5(I_1 - I_2)(-I_2)$$

$$= 5(5.43 - 4.29)(-4.29)$$

$$P_{sup} = \underline{\underline{-24.45 \text{ W}}}$$

Test A

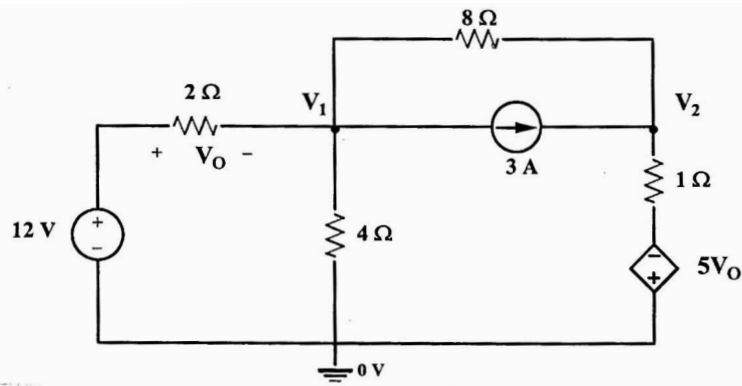(2) Determine V_1 and V_2 for the circuit of Figure 2. Use any method you desire.



Homework Problem

Easiest by nodal analysis

At V_1

$$8 \left(\frac{V_1 - 12}{2} + \frac{V_1}{4} + \frac{V_1 - V_2}{8} + 3 = 0 \right)$$

$$4V_1 - 48 + 2V_1 + V_1 - V_2 + 24 = 0$$

$$\boxed{7V_1 - V_2 = 24}$$

At V_2

$$\frac{V_2 - V_1}{8} - 3 + \frac{V_2 + 5V_0}{1} = 0$$

but $12 - V_0 - V_1 = 0$

$$V_0 = 12 - V_1$$

$$V_1 = -10.9V$$

$$V_2 = -100.36V$$

$$\frac{V_2 - V_1}{8} - 3 + V_2 + 5(12 - V_1) = 0$$

$$V_2 - V_1 - 24 + 8V_2 + 480 - 40V_1 = 0$$

$$\boxed{-41V_1 + 9V_2 = -456}$$

Test A

2

(2) cont.

$$\begin{bmatrix} 7 & -1 \\ -41 & 9 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 24 \\ -456 \end{bmatrix}$$

$$v_1 = -10.91 \text{ V}; \quad v_2 = -100.36 \text{ V}$$

Test A

(3) You are given the circuit of Figure 3. The following is known:

$$V_A = 7 \text{ V}; \quad V_B = 0.5 \text{ V}$$

Use these values in answering the following questions.

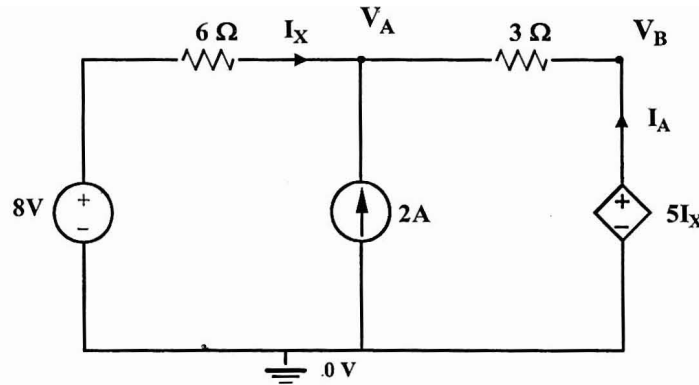


Figure 3: Circuit for problem 3.

- Determine the current I_X .
- Determine the power supplied by the dependent voltage source.
- Determine the power supplied by the independent current source.
- Determine the power supplied by the independent voltage source.
- Determine the power absorbed by the 6Ω resistor.
- Determine the power absorbed by the 3Ω resistor.

Case 1: Using the above circuit, $V_A \neq 7V$,
 $V_B \neq 0.5V$. (WRONG label on dependent source)
So we solve for V_A & V_B .

At V_A

$$\frac{V_A - 8}{6} + \frac{V_A - V_B}{3} - 2 = 0$$

Constraint:

$$V_B - 5I_X = 0$$

$$\text{OR } V_B - 5\left(\frac{8 - V_A}{6}\right) = 0$$

$$\text{Solving gives: } \underline{V_A = 7.14V}; \quad \underline{V_B = 0.714V}$$

Test A

2

13) cont.

We now start the problem:

(a)

$$\underline{I_x} = \frac{8 - V_A}{6} = \frac{8 - 7.14}{6} = \underline{0.143 \text{ A}}$$

(b)

$$P_{\text{sup}} = \frac{5I_x}{5I_x} (I_A)$$

$$I_A = -(I_x + 2) = -2.143 \text{ A}$$

check:

$$I_A = \frac{V_B - V_A}{3} = \frac{0.714 - 7.14}{3} = -2.14 \text{ A check}$$

$$P_{\text{sup}} = \frac{5I_x}{5I_x} = (5 \times 0.143)(-2.143) = -1.53 \text{ W}$$

$$(c) P_{\text{sup}} = \frac{V_A \times 2}{2A} = 7.14 \times 2 = 14.28 \text{ W}$$

$$(d) P_{\text{sup}} = \frac{8V}{8V} \times I_x = 1.14 \text{ W}$$

$$\Sigma \text{ supplied} = (1.14 - 1.53 + 14.28) \text{ W} = 13.89 \text{ W}$$

$$(e) P_{\text{abs}} = \frac{I_x^2 \times 6}{6\Omega} = (0.143)^2 \times 6 = 0.123 \text{ W}$$

$$(f) P_{\text{abs}} = \frac{I_A^2 \times 3}{3\Omega} = (2.143)^2 \times 3 = 13.77 \text{ W}$$

$$\Sigma \text{ Absorber} = 13.89 \text{ W check}$$

Test A

3

(3) cont

Using the dependent source as $3I_x$ rather than $5I_x$, leads to $V_A = 7V$, $V_B = 0.5V$ (for sure)

(a)

$$I_x = \frac{8 - V_A}{6} = \frac{1}{6} A = 0.167 A$$

(b)

$$P_{sup} = (3I_x) I_A$$

where $I_A = -(I_x + 2) = -\frac{13}{6} = -2.167 A$

check

$$I_A = \frac{V_B - V_A}{3} = \frac{-6.5}{3} = -2.167 A$$

$$P_{sup} = 3 \times \left(\frac{1}{6}\right) (-2.167) = -1.084 W$$

(c)

$$P_{sup} = V_A \times 2 = 14 W$$

(d)

$$P_{sup} = 8 \times I_x = 8 \times \frac{1}{6} = 1.333 W$$

$$\Sigma \text{ supplied} = (1.333 + 14 - 1.084) = \underline{14.25 W}$$

(e)

$$P_{abs} = I_x^2 \times 6 = \left(\frac{1}{6}\right)^2 \times 6 = 0.1667 W$$

(f)

$$P_{abs} = I_A^2 \times 3 = (2.167)^2 \times 3 = 14.088 W$$


$$\Sigma \text{ absorbed} = (14.088 + 0.1667) = 14.25 W$$

check

Test A

(4) You are given the circuit of Figure 4. Use nodal analysis for this problem.

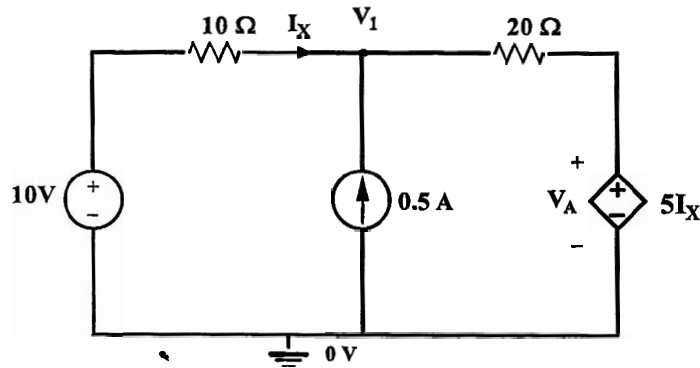- (a) Determine V_1 .
- (b) Determine V_A .



At V_1

$$20 \left(\frac{V_1 - 10}{10} + \frac{V_1 - V_A}{20} - 0.5 = 0 \right)$$

$$2V_1 - 20 + V_1 - V_A - 10 = 0$$

$$\boxed{3V_1 - V_A = 30}$$

Constraint

$$V_A - 5I_X = 0$$

where

$$I_X = \frac{10 - V_1}{10}$$

so

$$V_A - \frac{5(10 - V_1)}{10} = 0$$

$$10V_A - 50 + 5V_1$$

$$\boxed{5V_1 + 10V_A = 50}$$

Test A
(4) cont.

2


$$\begin{bmatrix} 3 & -1 \\ 5 & 10 \end{bmatrix} \begin{bmatrix} V_1 \\ V_A \end{bmatrix} = \begin{bmatrix} 30 \\ 50 \end{bmatrix}$$

$$V_1 = 10 \text{ V} \quad V_A = 0 \text{ V}$$


(a) $V_1 = 10 \text{ V}$

(b) $V_A = 0 \text{ V}$

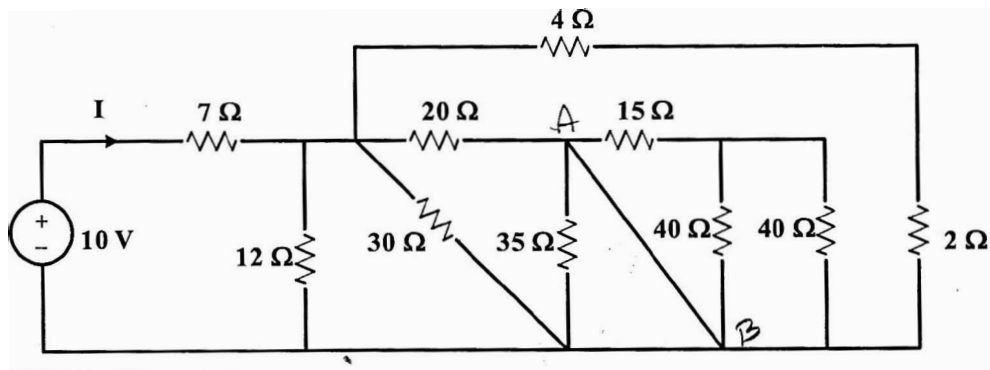
- (5) You are given the circuit shown in Figure 5. Determine the current I . Do not use mesh analysis in your solution.



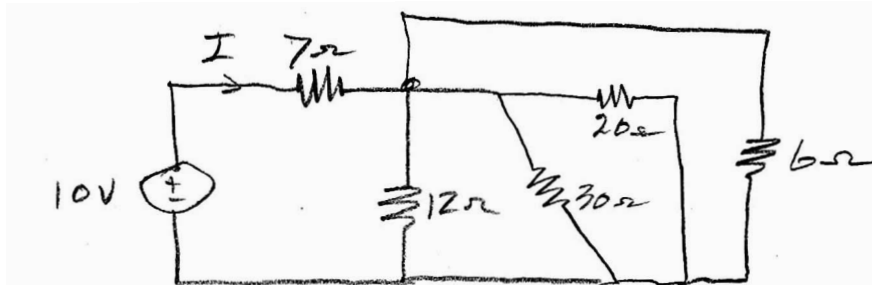The short from A to B causes the circuit to become as follows



Which becomes;

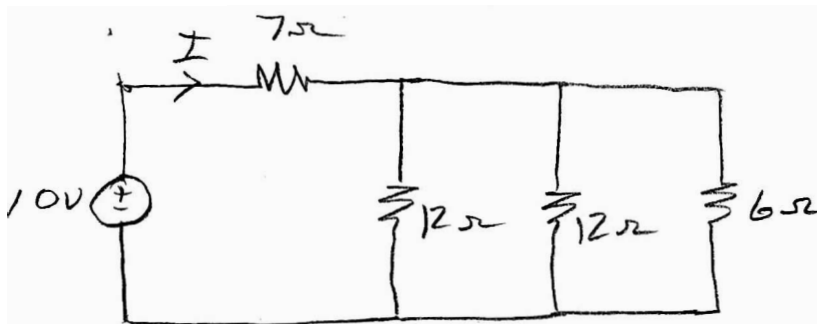

Giving
$$I = \frac{10}{10} = 1A$$