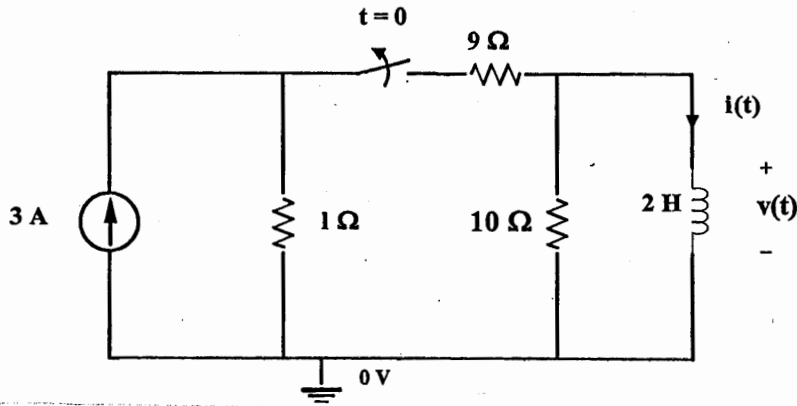



ECE 300  
Spring Semester, 2008  
Test #3

wlg: Test B : Section II: 8:10 AM

- (1) The switch in the circuit of Figure 1 has been closed for a very long time and is opened at  $t = 0$ .
- Find the voltage  $v(t)$ .
  - At what time (in milliseconds) will  $v(t)$  equal to 50% of the initial value of  $v(0^+)$ ?




1a) FOR  $t < 0$

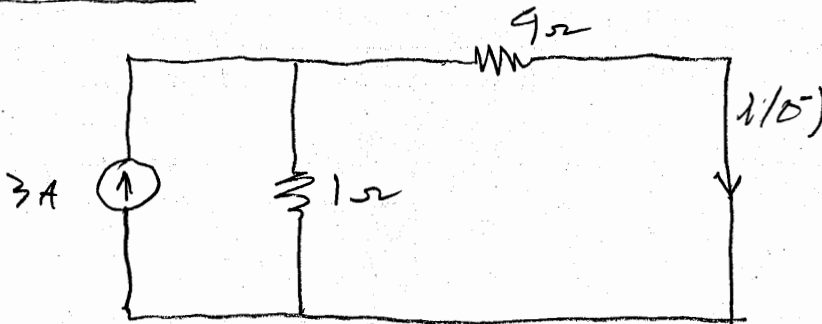

$$i(0^-) = \frac{3 \times 1}{10} = 0.3 \text{ A}$$

$$i(0^+) = i(0^-) = 0.3 \text{ A} \quad (1)$$

$t > 0$

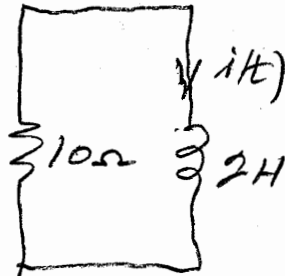

## Test B

$$i(0) = 0$$

$$\tau = \frac{L}{R} = \frac{2}{10} = 0.2$$

$$i(t) = i(0) + [i(0^+) - i(0)] e^{-\frac{t}{\tau}}$$

$$i(t) = 0.3 e^{-5t} \text{ A (A)} \quad \left. \begin{array}{l} \text{One} \\ \text{could} \\ \text{solve} \\ \text{directly} \\ \text{for} \\ v(t). \end{array} \right\}$$

$$v(t) = L \frac{di}{dt} = 2 \left[ -0.3 \times 5 e^{-5t} \right]$$

$$v(t) = -3 e^{-5t} \text{ V}$$

$$\text{OR } v(t) = -iR = -i \times 10 = -3 e^{-5t} \text{ V}$$

(8)

$$v(0^+) = -3$$

$$50\% v(0^+) = -1.5$$

$$-1.5 = -3 e^{-5t}$$

$$0.5 = e^{-5t}$$

$$\ln 0.5 = -5t / \ln e = -5t$$


$$5t = 0.693$$

$$t = 0.139 \text{ sec}$$

$$t = 139 \text{ msec}$$

# Test B

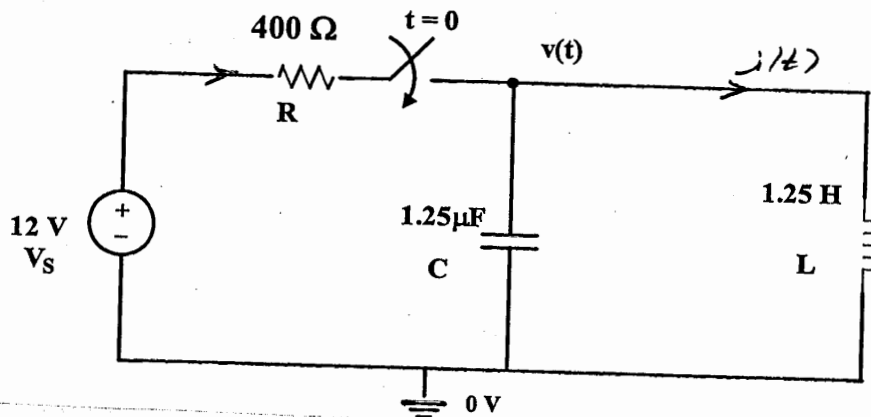- (2) There is no energy stored in the circuit of Figure 2 when the switch is closed at  $t = 0$ . Find  $v(t)$  for  $t \geq 0$ .



For  $t < 0$

$$v(0^-) = 0 \quad \therefore v(0^+) = 0 \quad (1)$$

$$i(0^+) = 0$$

For  $t > 0$

$$\frac{v - V_s}{R} + C \frac{dv}{dt} + \frac{1}{L} \int_0^t v dt + i(0^+) = 0 \quad (2)$$

Take the  $\frac{d}{dt}$  of (2)

$$\frac{1}{R} \frac{dv}{dt} + C \frac{d^2v}{dt^2} + \frac{v}{L} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0 \quad (3)$$

Char. Eq

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \quad (4)$$

With numbers

$$s^2 + 2,000 s + 640,000 = 0 \quad (5)$$

Test B (cont)

Roots of char. eq.

$$(s+400)(s+1600)$$

$$v(t) = A_1 e^{-400t} + A_2 e^{-1600t} \quad (6)$$

$$v(0^+) = 0$$

$$0 = (A_1 e^{-400t} + A_2 e^{-1600t}) \Big|_{t=0}$$

$$\boxed{0 = A_1 + A_2}$$

From (2) at  $t=0^+$

$$C \frac{dv(0^+)}{dt} = \frac{V_s}{R} - \frac{v(0^+)}{R} - i(0^+) \quad \begin{matrix} \nearrow \text{from (1)} \\ \nearrow 0 \end{matrix}$$

$$\frac{dv(0^+)}{dt} = 24,000$$

Take  $\frac{d[\dots]}{dt}$  of (6)

$$\frac{dv(t)}{dt} = -400 A_1 e^{-400t} - 1600 A_2 e^{-1600t} \quad (7)$$

Evaluate (7) at  $t=0^+$


$$\frac{dv(0^+)}{dt} = 24,000 = -400 A_1 - 1600 A_2$$

$$\text{or } 60 = -A_1 - 4A_2$$

$$\begin{bmatrix} 1 & 1 \\ -1 & -4 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 60 \end{bmatrix} \quad \begin{matrix} A_1 = 20 \\ A_2 = -20 \end{matrix}$$

$$\boxed{v(t) = (20 e^{-400t} - 20 e^{-1600t}) \text{ u(t)} \text{ V}}$$

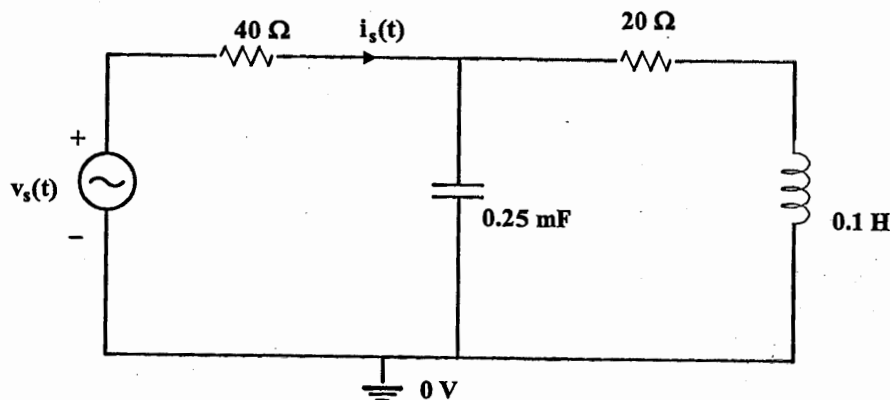- (3) The circuit in Figure 3 is in steady state.  $v_s = 60\sin(200t + 40^\circ)$  V.
- Determine the steady state current  $i_s(t)$  using a cosine reference.
  - Draw a phasor diagram showing  $V_s$  and  $I_s$ .
  - Does  $V_s$  lead  $I_s$  or  $I_s$  lead  $V_s$  and give the angle?



$V_s = 60\sin(200t + 40^\circ)$  V take to cosine reference


$$V_s = 60\cos(200t - 50^\circ)$$

$$\hat{V}_s = 60 \angle -50^\circ$$

$$0.1\text{H} \rightarrow j\omega L \rightarrow j200 \times 0.1 \rightarrow j20 \Omega$$

$$0.25\text{C} \rightarrow \frac{j}{\omega C} \rightarrow \frac{-j}{200 \times 0.25 \times 10^{-3}} \rightarrow -j20$$

(a) Phasor circuit

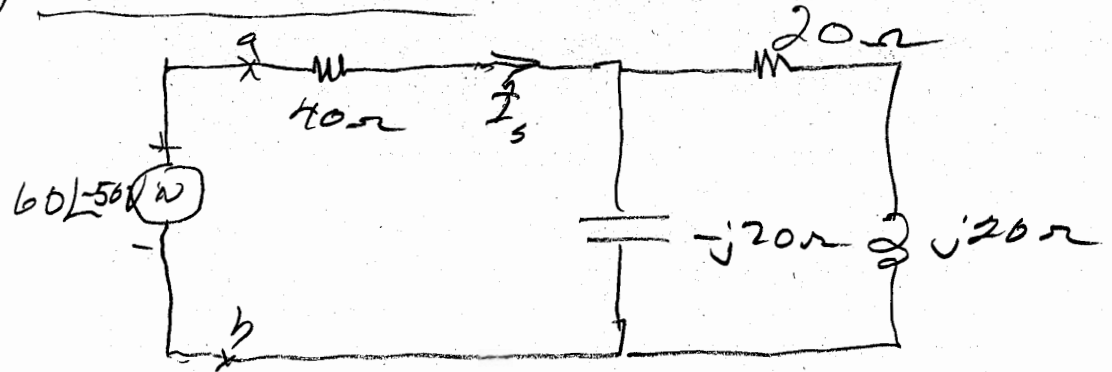

$$Z_{ab} = 40 + \frac{(20 + j20) \parallel (-j20)}{20 + j20 - j20}$$

(3) cont.


(2)

$$Z_{ab} = 63.25 \angle -18.4^\circ \Omega$$

$$\vec{I}_s = \frac{60 \angle -50^\circ}{63.25 \angle -18.4^\circ} = 0.95 \angle -31.6^\circ \text{ A}$$


$$i_s(t) = 0.95 \cos(200t - 31.6^\circ) \text{ A}$$

(b)

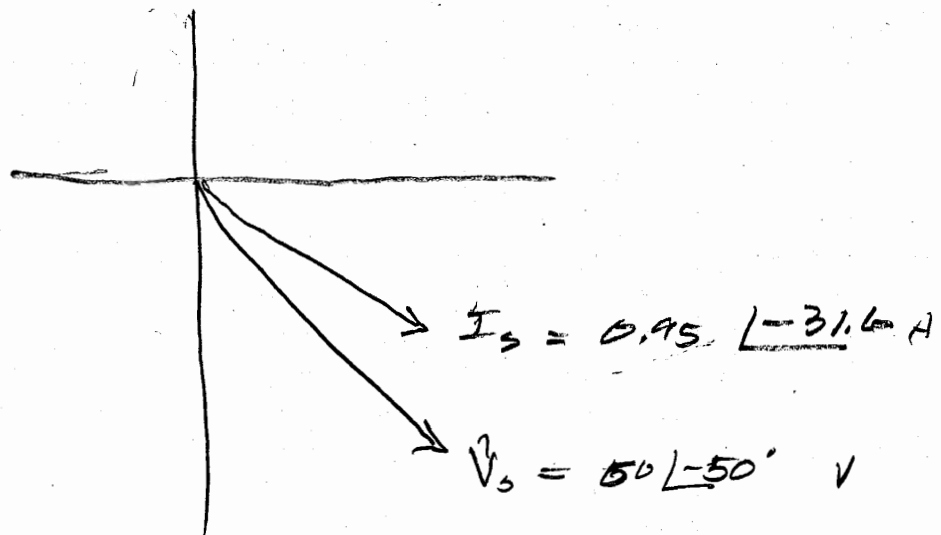

(c)  $\vec{I}_s$  lags  $\vec{V}_s$  by  $50 - 31.6 = 18.4^\circ$

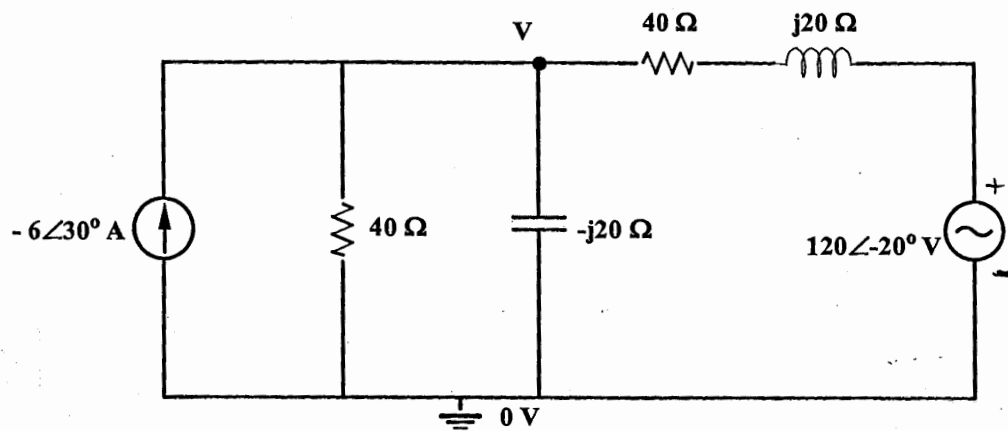(4) Use nodal analysis to find the phasor voltage  $V$  in Figure 4.



At  $\hat{V}$

$$\frac{\hat{V} - 120 \angle -20^\circ}{40 + j20} - \frac{j\hat{V}}{20} + \frac{\hat{V}}{40} = -6 \angle 30^\circ$$

$$(0.02 - j0.01)\hat{V} + 2.68 \angle 133.4^\circ$$

$$+ j0.05\hat{V} + 0.025\hat{V} = -6 \angle 30^\circ$$

$$(0.045 + j0.04)\hat{V} = -2.68 \angle 133.4^\circ - 6 \angle 30^\circ$$

$$\hat{V} = 99.3 \angle -165.8^\circ \text{ V}$$

