

wlg Practice: No turn-in

Name green
 Print (last, first)

- (1) You are given the ideal transformer of Figure 1. (a) Find I_1 . Ans $I_1 = 3.07\angle 39.81^\circ \text{ A}$.
 (b) Find V_o . Ans $V_o = 3.07\angle 39.81^\circ \text{ V}$.

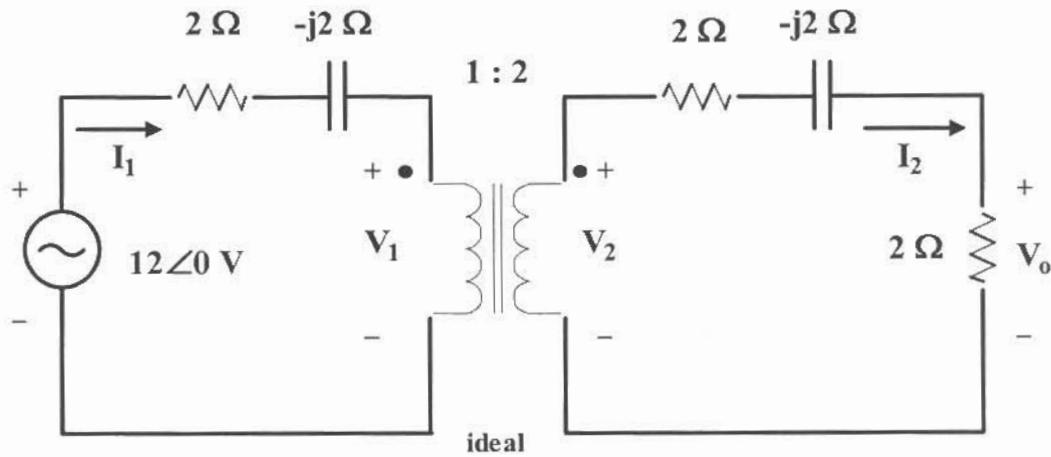


Figure 1: Circuit for problem 1.

- (2) Find I_o and Z_{ab} in the linear transformer of Figure 2. Ans: $I_o = 2.2\angle -4.88^\circ \text{ A}$; $Z_{ab} = 1.5085\angle 17.9^\circ \Omega$

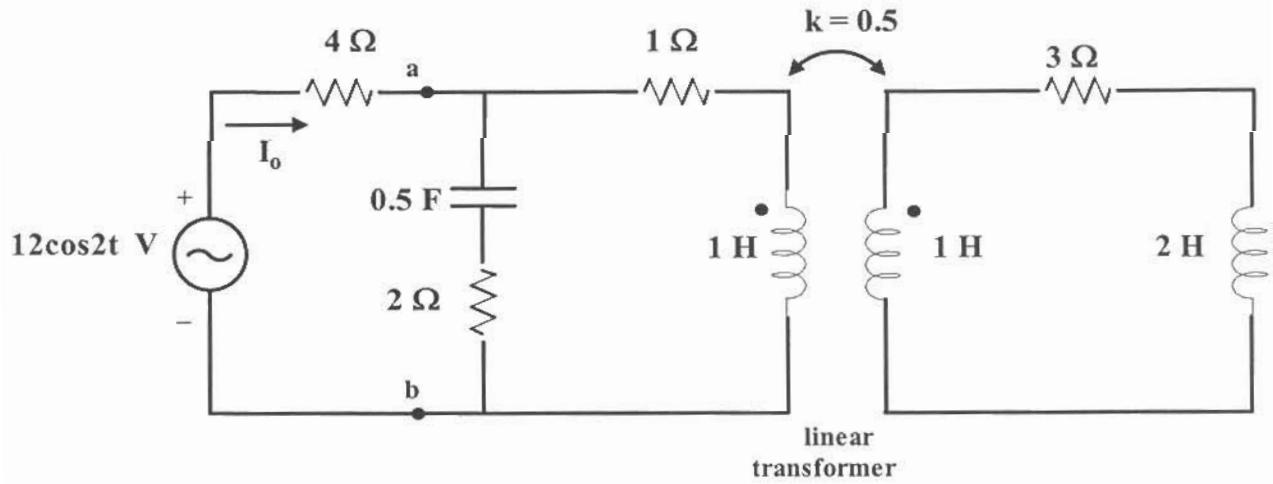


Figure 2: Circuit for problem 2.

- (3) Determine the input impedance looking into terminals a-b of the linear transformer circuit shown in Figure 3. Ans: $Z_{ab} = 0.1989 - j9.7 \Omega$

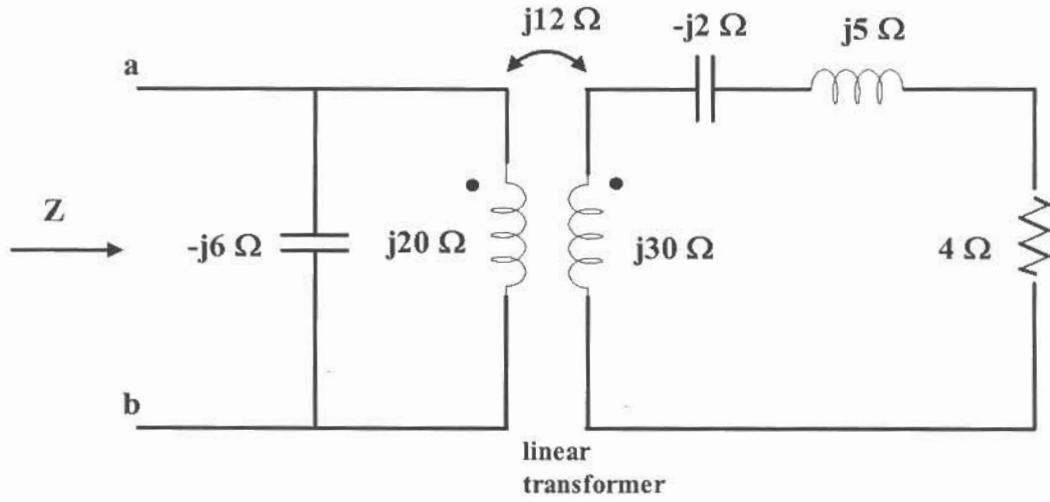


Figure 3: Circuit for problem 3.

- (4) (a) Find I_1 and I_2 in the ideal transformer of Figure 4. Ans: $I_1 = 1.07\angle 5.88^\circ A$, $I_2 = 0.536\angle 185.9^\circ A$
 (b) Switch one of the dots in the circuit of Figure 4. Find I_1 and I_2 again. Ans: $I_1 = 0.625\angle 25^\circ A$, $I_2 = 0.313\angle 25 A$.

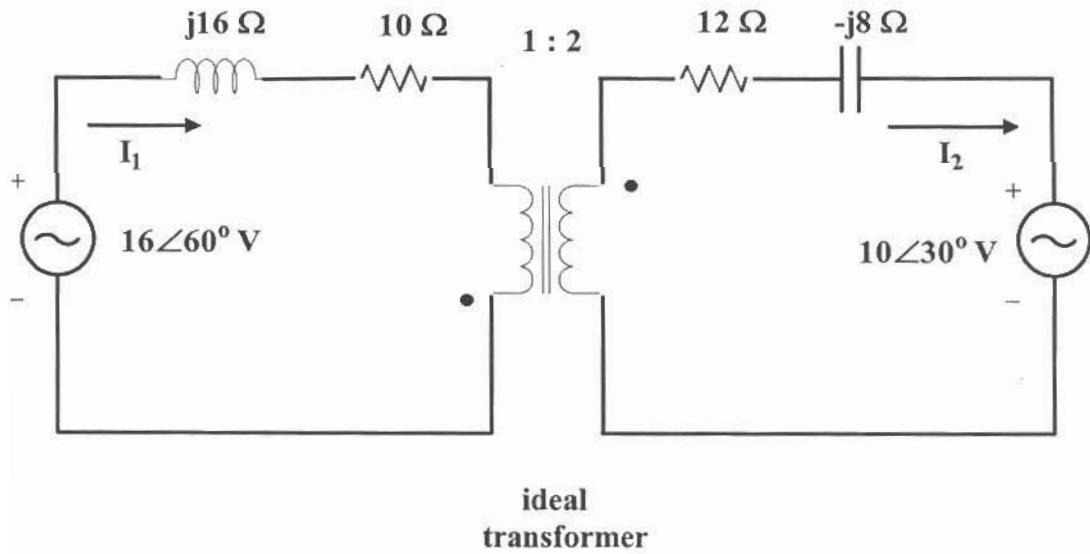


Figure 4: Circuit for problem 4.

- (5) A transformer is used to match an amplifier with an $8\ \Omega$ speaker load as shown in Figure 5. The Thevenin equivalent of the amplifier is $V_{Th} = 10\ V$, $Z_{Th} = 128\ \Omega$.

(a) Find the required turns ratio for the maximum energy power transfer to the speaker.

Ans: $n = 0.25$

(b) Determine the primary and secondary currents. $I_1 = 39.06\ mA$, $I_2 = 4xI_1$

(c) Calculate the primary and secondary voltages. $V_1 = 5\ V$, $V_2 = 1.25\ V$


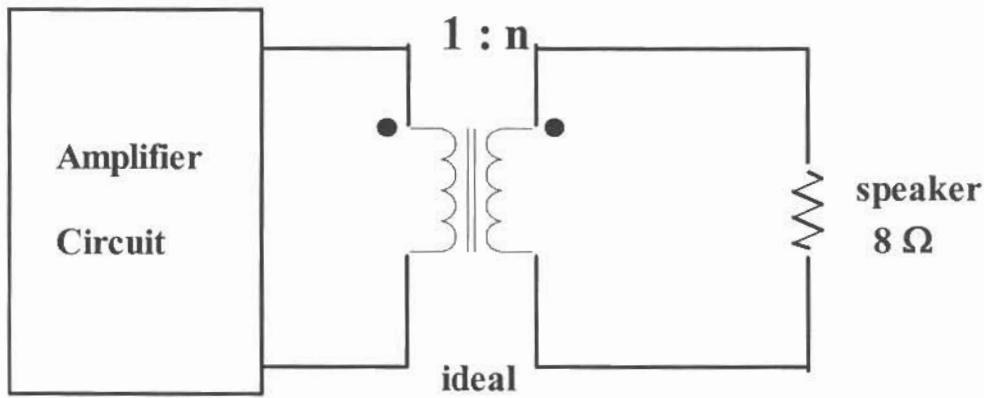



Figure 5: Diagram for problem 5.

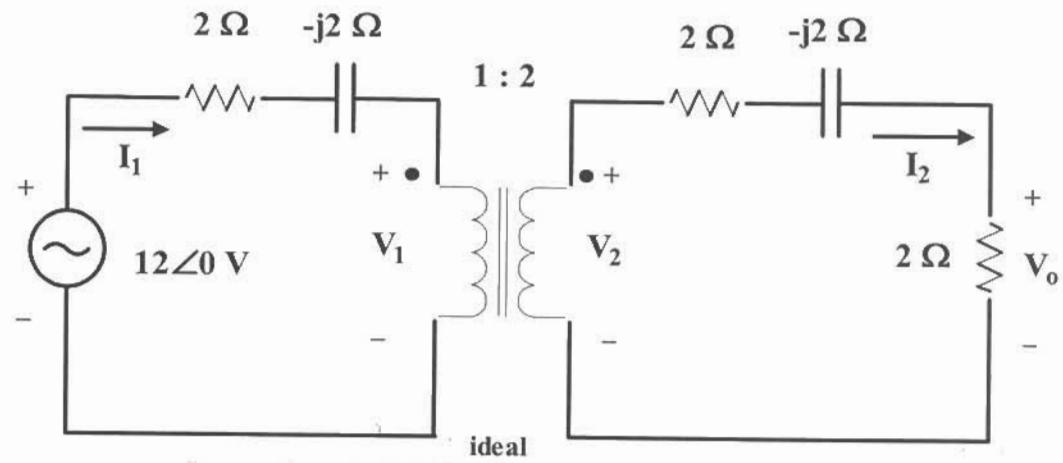- (1) You are given the ideal transformer of Figure 1. (a) Find I_1 . Ans $I_1 = 3.07 \angle 39.81^\circ$ A.
 (b) Find V_o . Ans $V_o = 3.07 \angle 39.81$ V.



Reflect secondary to primary

$$\frac{4-j2}{2^2} = (1-j0.5) \Omega$$

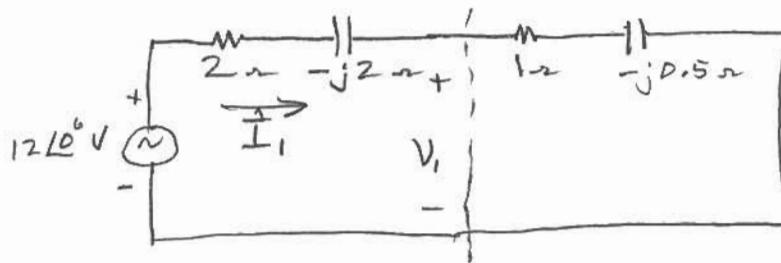

$$-12\angle 0^\circ + (3-j2.5)I_1 = 0$$


$$\hat{I}_1 = \frac{12\angle 0^\circ}{3-j2.5} = 3.07 \angle 39.8^\circ \text{ A}$$

$$\hat{I}_2 = \frac{\hat{I}_1}{2}$$

$$\hat{V}_o = 2 \times \hat{I}_2 = 2 \times \frac{\hat{I}_1}{2}$$

$$\hat{V}_o = 3.07 \angle 39.8^\circ \text{ V}$$

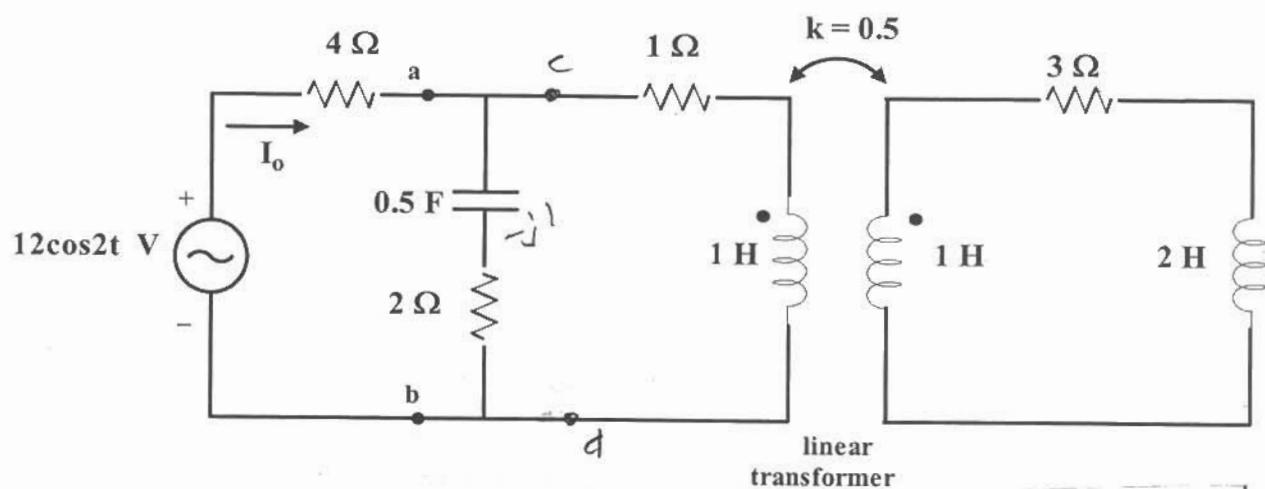- (2) Find I_o and Z_{ab} in the linear transformer of Figure 2. Ans: $I_o = 2.2 \angle -4.88^\circ A$; $Z_{ab} = 1.5085 \angle 17.9^\circ \Omega$



The impedance seen looking to the right of c-d is

$$Z_{cd} = 1+j2 \frac{\omega^2 m^2}{R_2 + Z_L + j\omega L_2}$$

$$Z_L = j\omega 2 = j2 \times 2 = j4$$

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

$$M = 0.5 \sqrt{1 \times 1} = 0.5 H$$

$$Z_{cd} = 1+j2 + \frac{j^2 \times (0.5)^2}{3 + j4 + j2} = ((1+j2) + \frac{1}{(3+j6)})$$


$$Z_{cd} = 2.15 \angle 60.3^\circ \Omega$$

$$Z_{ab} = (2-j)(2.15 \angle 60.3^\circ) / ((2.15 \angle 60.3^\circ) + (2-j))$$

$$Z_{ab} = 1.509 \angle 17.9^\circ \Omega$$

$$I_o = \frac{12 \angle 0^\circ}{4 + 1.509 \angle 17.9^\circ} = 2.2 \angle -4.88^\circ A$$

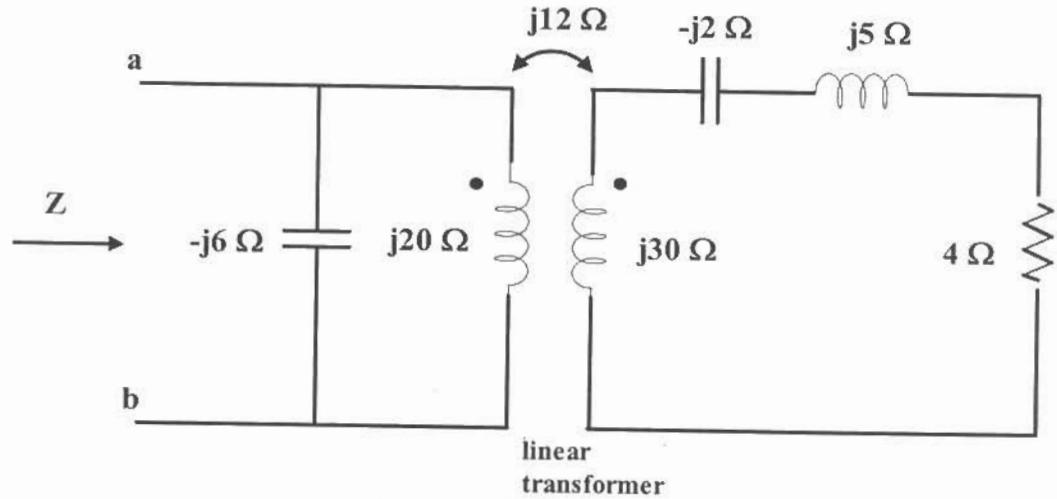- (3) Determine the input impedance looking into terminals a-b of the linear transformer circuit shown in Figure 3. Ans: $Z_{ab} = 0.1989 - j9.7 \Omega$



$$Z = -j6 \parallel Z_0$$

where


$$Z_0 = j20 + \frac{(w_m)^2}{j30 - j2 + j5 + 4} \quad j\omega_m = j12 \quad w_m = 12$$

$$Z_0 = ((j20) + \frac{144}{(4 + j33)}) = 15.71 \angle 88.1^\circ \Omega$$


$$\bar{Z} = (6 \angle -90^\circ) (15.71 \angle 88.1^\circ) / ((6 \angle -90^\circ) + (15.71 \angle 88.1^\circ))$$

$$\boxed{\bar{Z} = (0.1987 - j9.7) \Omega}$$

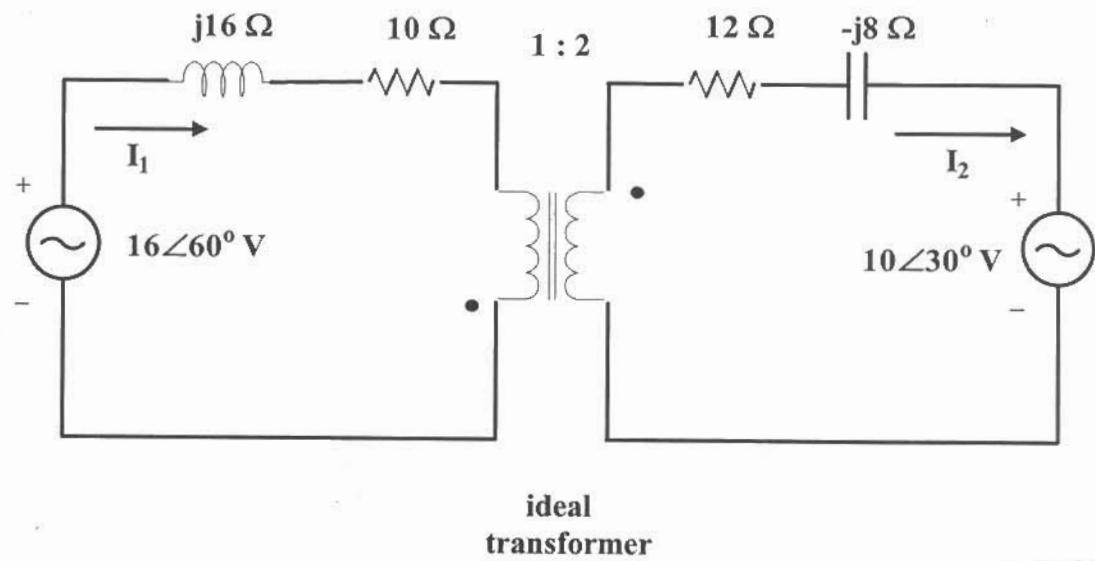- (4) (a) Find I_1 and I_2 in the ideal transformer of Figure 4. Ans: $I_1 = 1.07 \angle 5.88^\circ$ A, $I_2 = 0.536 \angle 185.9^\circ$ A
 (b) Switch one of the dots in the circuit of Figure 4. Find I_1 and I_2 again. Ans: $I_1 = 0.576 \angle -17.1^\circ$ A, $I_2 = 0.288 \angle -17.1$ A.



The secondary reflected to the primary:

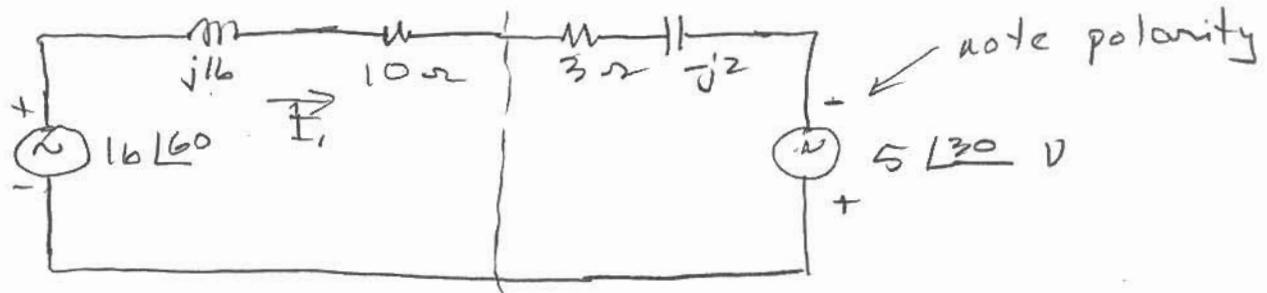

$$\frac{12-j8}{4} = 3-j2 \quad \frac{10\angle 30^\circ}{2} = 5\angle 30^\circ$$

$$I_1 = \frac{(16\angle 60^\circ) + (5\angle 30^\circ)}{(13 + j14)} = 1.07 \angle 5.88^\circ \text{ A}$$


$$I_2 = -\frac{I_1}{n} = -\frac{1.07 \angle 5.88^\circ}{2} = 0.535 \angle 185.9^\circ \text{ A}$$

$$I_2 = 0.535 \angle 185.9^\circ \text{ A}$$

(4) Continue

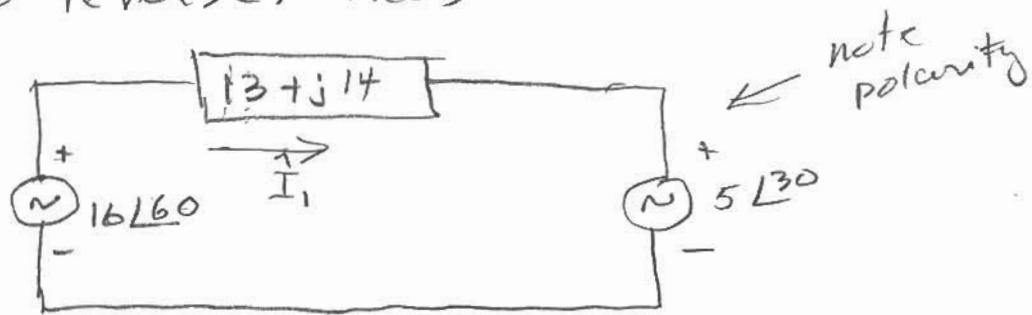(2)

changing one of the dots
causes the polarity of the secondary
to reverse. Thus



$$I_1 = \frac{((16 L 60) + (-5 L 30))}{(13 + j 14)}$$

$$I_1 = 0.625 L 25^\circ \text{ A}$$

$$I_2 = + \frac{I_1}{n} \approx \frac{I_1}{2}$$

$$I_2 = 0.283 L 25^\circ \text{ A}$$

- (5) A transformer is used to match an amplifier with an $8\ \Omega$ speaker load as shown in Figure 5. The Thevenin equivalent of the amplifier is $V_{Th} = 10\text{ V}$, $Z_{Th} = 128\ \Omega$.

(a) Find the required turns ratio for the maximum energy power transfer to the speaker.

$$\text{Ans: } n = 0.25$$

(b) Determine the primary and secondary currents. $I_1 = 39.06\text{ mA}$, $I_2 = 4 \times I_1$

(c) Calculate the primary and secondary voltages. $V_1 = 5\text{ V}$, $V_2 = 1.25\text{ V}$


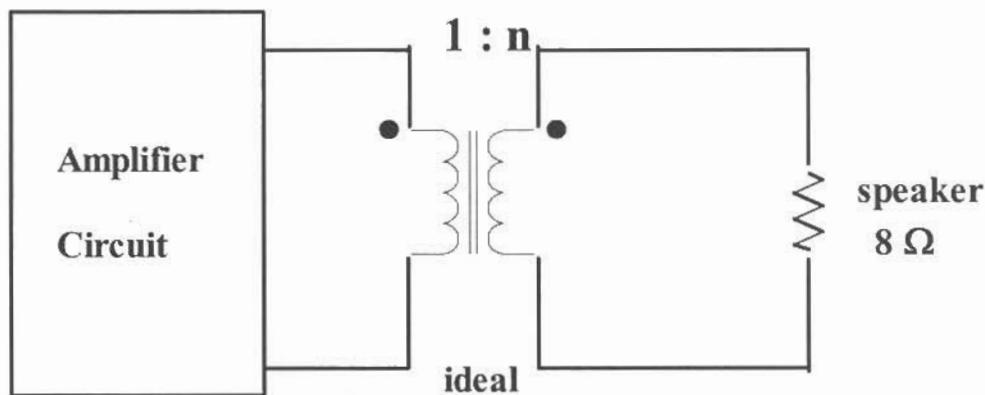


Figure 5: Diagram for problem 5.

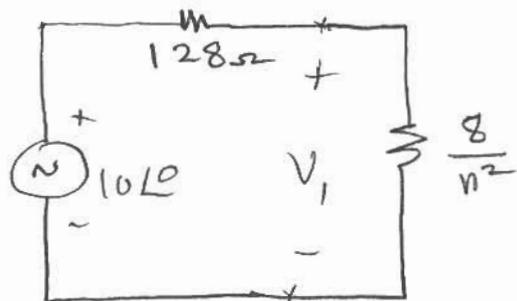

(a) For maximum power transfer, we want

$$\frac{8}{n^2} = 128 \quad n^2 = \frac{8}{128} \quad n = \sqrt{\frac{8}{128}}$$

$$n = 0.25$$

$$(b) I_1 = \frac{10\text{ V}}{2 \times 128} = 39.06\text{ mA}; I_2 = 4 \times I_1$$

$$(c) V_1 = 5\text{ V} \quad (\text{Voltage division})$$

$$V_2 = nV_1 = 0.25 \times 5 = 1.25\text{ V}$$