

Desk copy

ECE 301
Fall Semester, 2006
HW Set #12

Due: November 30, 2006
wlg

Name wlg
Print(last, first)

circle: 2:10 section 3:40 section

Use Engineering Paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 15 points.

- (1) You are given the configuration shown in Figure 1(a). The input voltage is 2 volts. You want to design an op amp circuit so that the output voltage is 10 volts. There are two purposed circuit layouts that you are to use. These are described in Figures 1(b) and 1(c). Your assignment here is to complete the task.

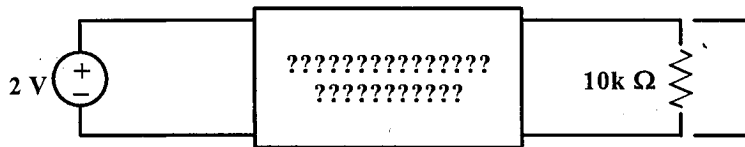


Figure 1(a): Basic layout for problem 1.

- (a) Use the following configuration to achieve the requirements stated above. Give your values of R_1 , R_2 , R_3 , and R_4 . Give the development of your work that leads to your final answer.


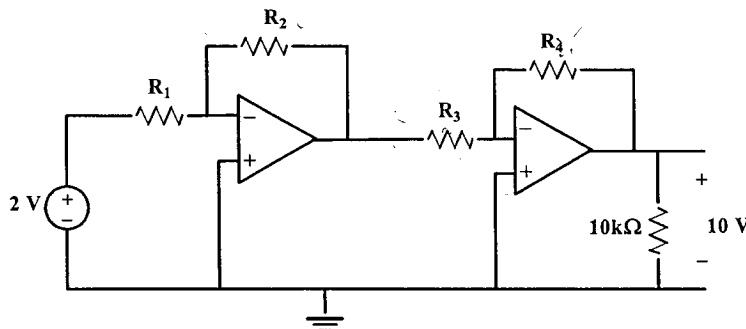


Figure 1(b): Purposed circuit for satisfying design specs.

CONTINUED ON NEXT PAGE

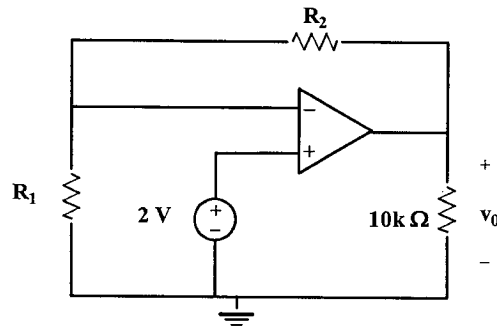- (b) Use the following configuration to achieve the requirements stated above. Give your values of R_1 and R_2 . Again, show the development of your work that leads to your final answer.



$$V_0 = 2 \left(1 + \frac{R_2}{R_1} \right)$$

Figure 1(c): Purposed circuit for satisfying design specs.

- (2) Find i_o in the op amp circuit of Figure 2. Ans: $i_o = 0.12 \text{ mA}$.

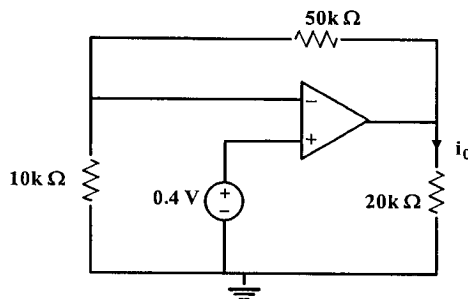


Figure 2: Circuit for problem 2.

- (3) You are given the op amp circuit of Figure 3. Find v_o/v_{in} . Ans: R_2/R_1

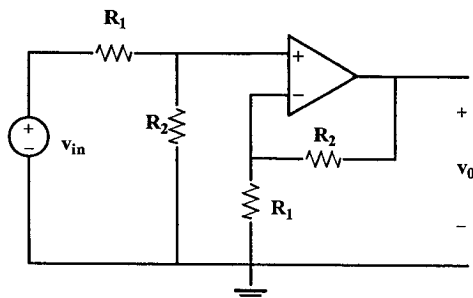


Figure 3: Circuit for problem 3.

(4) For the op amp configuration of Figure 4, find v_0/v_{in} . Ans: $-R_{FB}/R_A$

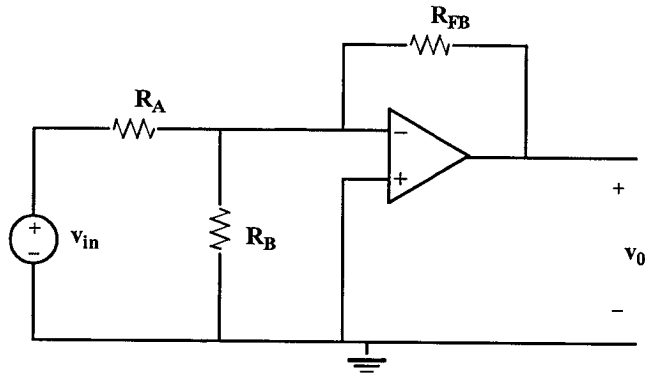


Figure 4: Circuit for problem 4.

(5) Find the output voltage v_0 in terms of the input voltage v_{in} for the op amp circuit of Figure 5.
Ans: $v_0 = -6v_{in}$

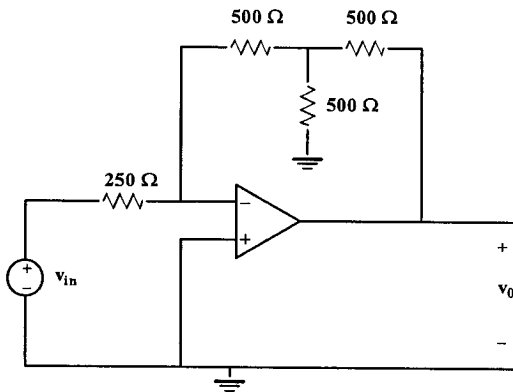


Figure 5: Circuit for problem 5.

(6) You are given the op amp circuit of Figure 6. Show that $v_0 = -(2/3)v_S$.


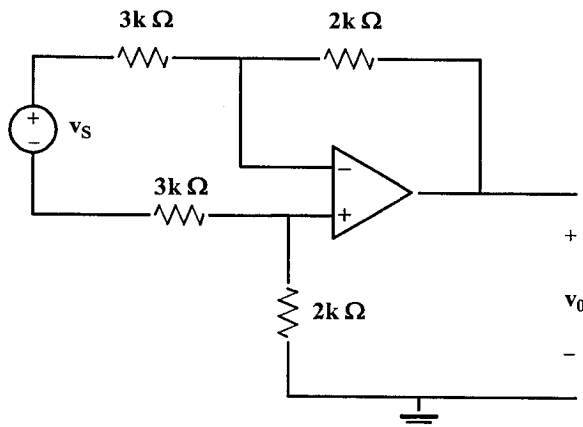


Figure 6: Circuit for problem 6.

wlg

H.W. #12
ECE 301
Fall term '06

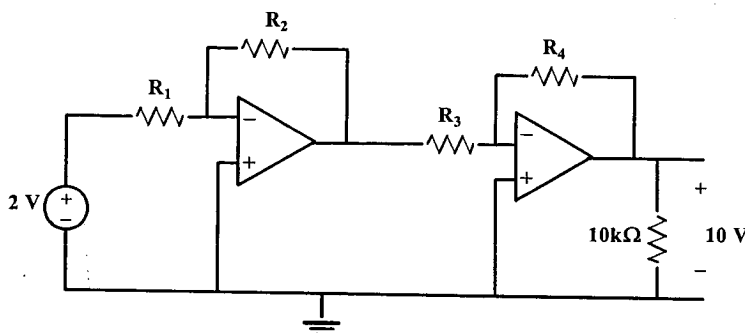
- (1) Want an op amp design that will give 10V out for 2V in. Input +, output positive.



(a)

With the above configuration, make $R_2 = 10k$, $R_1 = 2k$; you get a gain of 5. Then make $R_4 = R_3$, say $2k$ each to change the sign back to +.

(b)

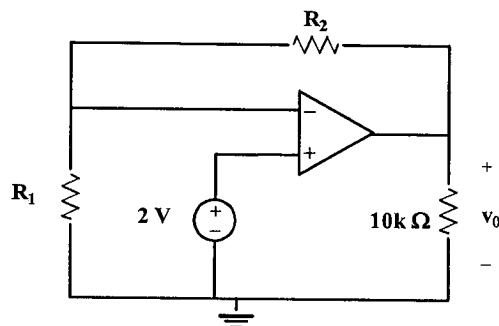


For the above configuration we have shown

$$V_0 = \left(1 + \frac{R_2}{R_1}\right) 2 \quad \text{to get 10V out}$$

make $\frac{R_2}{R_1} = 4$, say $R_2 = 8k\Omega$, $R_1 = 2k\Omega$

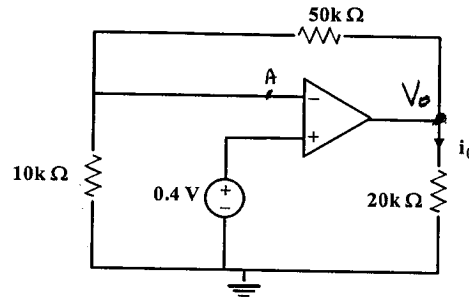(2) Find i_o in the op amp circuit of Figure 2. Ans: $i_o = 0.12 \text{ mA}$.



At "A" we write the node equation

$$\frac{0.4}{10k} + \frac{.4 - V_o}{50k} = 0$$

OR

$$2 + .4 - V_o = 0$$


$$V_o = 2.4 \text{ V}$$

Now,

$$i_o = \frac{V_o}{20k} = \frac{2.4}{20k}$$

$$i_o = 0.12 \text{ mA}$$

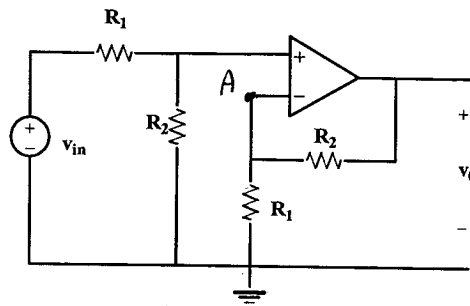(3) You are given the op amp circuit of Figure 3. Find v_o/v_{in} . Ans: R_2/R_1



The voltage at "A" is

$$V_A = \frac{V_{in} \times R_2}{R_1 + R_2} \quad (1)$$

Also, the voltage at "A" is


$$V_A = \frac{V_o \times R_1}{R_1 + R_2} \quad (2)$$

Equate (1) to (2)

$$\frac{V_o \times R_1}{R_1 + R_2} = \frac{V_{in} R_2}{R_1 + R_2}$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{R_2}{R_1}}$$

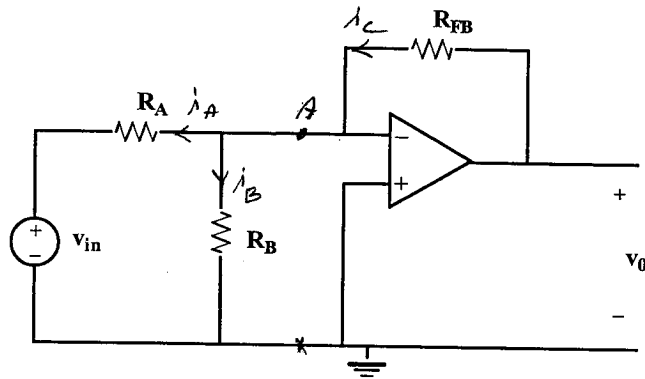(4) For the op amp configuration of Figure 4, find v_o/v_{in} . Ans: $-R_{FB}/R_A$



$$i_C = i_B + i_A$$

but $i_B = 0$ because the voltage at "A" = 0


so,

$$\frac{v_o}{R_{FB}} = \frac{-v_{in}}{R_A}$$

$$\frac{v_o}{v_{in}} = -\frac{R_{FB}}{R_A}$$

(5) Find the output voltage v_0 in terms of the input voltage v_{in} for the op amp circuit of Figure 5.

Ans: $v_0 = -6v_{in}$

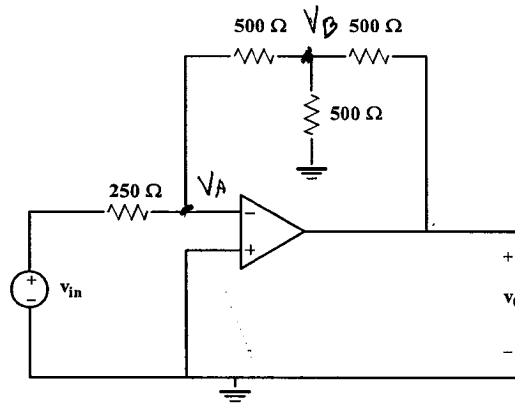

At V_B

$$\frac{V_B}{500} + \frac{V_B - v_0}{500} + \frac{V_B - 0}{500} = 0 \quad (V_A = 0)$$

70

$$V_B + V_B - v_0 + V_B = 0$$

$$v_0 = 3 V_B \quad (1)$$

At V_A


$$\frac{0 - v_{in}}{250} + \frac{0 - V_B}{500} = 0$$

$$-2v_{in} = V_B \quad (2)$$

Substitute (2) into (1)

$$v_0 = -6v_{in}$$

(6)

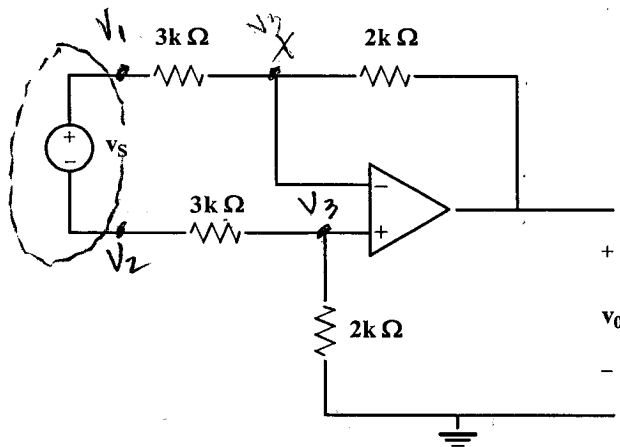(6) You are given the op amp circuit of Figure 6. Show that $v_0 = -(2/3)v_s$.

At the supernode:

$$\frac{V_1 - V_3}{3k} + \frac{V_2 - V_3}{3k} = 0$$

$$\text{OR } V_1 + V_2 - 2V_3 = 0 \quad (1)$$

At V_3

$$\frac{V_3 - V_2}{3k} + \frac{V_3}{2k} = 0$$

OR

$$2V_3 - 2V_2 + 3V_3 = 0$$

$$\boxed{-2V_2 + 5V_3 = 0} \quad (2)$$

At V_x

$$\frac{V_3 - V_1}{3k} + \frac{V_3 - v_0}{2k} = 0$$

OR

$$2V_3 - 2V_1 + 3V_3 - 3v_0 = 0$$

$$\boxed{-2V_1 + 5V_3 - 3v_0 = 0} \quad (3)$$

16) continued

constraint Equation

$$V_2 + V_3 - V_1 = 0$$

or
$$\boxed{V_1 - V_2 = V_3} \quad (4)$$

From (1), (2), (3), (4)

$$\begin{bmatrix} V_1 & 1 & -3 & 0 \\ 0 & -2 & 5 & 0 \\ -2 & 0 & 5 & -3 \\ 1 & -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ V_3 \end{bmatrix}$$

Since we only have one input entry,
Let $V_3 = 1$. Solve simultaneous
equations

$$\boxed{V_0 = -\frac{2}{3} V_3}$$

Just for the exercise of it, and
the fun of doing it, solve using
the symbolic tool kit functions
of MATLAB

(6) continued

$$\text{Let } V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_0 \end{bmatrix}$$

$$V = \begin{bmatrix} 1 & 1 & -3 & 0 \\ 0 & -2 & 5 & 0 \\ -2 & 0 & 5 & -3 \\ 1 & -1 & 0 & 0 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 0 \\ 0 \\ V_s \end{bmatrix} = A * B$$

$$A = \text{sym}([1 \ 1 \ -3 \ 0; 0 \ -2 \ 5 \ 0; -2 \ 0 \ 5 \ -3; 1 \ -1 \ 0 \ 0])$$

$$B = \text{sym}([0; 0; 0; V_s])$$

$$V = \text{symml}(\text{inv}(A), B)$$

The results are shown on the following pages

```
% writing a program to illustrate the symbolic
% solution of equations. W. Green Nov 26, 2006
% call the program symbol_A.m

% Solving the equation;
% V = [V1; V2; V3; Vo] = inv(A)*B
% where

% A = [1, 1, -3, 0;0, -2, 5, 0; -2, 0, 5, -3; 1, -1, 0, 0]
% B = [0;0;0;Vs]

A = sym('[1, 1, -3, 0;0, -2, 5, 0; -2, 0, 5, -3; 1, -1, 0, 0]')
B = sym('[0;0;0;Vs]')

V = symmul(inv(A),B)

% V = [V1; V2; V3; V4] = [V(1); V(2); V(3); V(4)]

V1 = V(1)
V2 = V(2)
V3 = V(3)
Vo = V(4)
```

```
>> symbol_A
```

```
A =
```

```
[ 1, 1, -3, 0]
[ 0, -2, 5, 0]
[-2, 0, 5, -3]
[ 1, -1, 0, 0]
```

```
B =
```

```
[ 0]
[ 0]
[ 0]
[ Vs]
```

```
V =
```

```
[ -1/4*Vs]
[ -5/4*Vs]
[ -1/2*Vs]
[ -2/3*Vs]
```

```
V1 =
```

```
-1/4*Vs
```

```
V2 =
```

```
-5/4*Vs
```

```
V3 =
```

```
-1/2*Vs
```

```
Vo =
```

```
-2/3*Vs
```

```
>>
```