


wlg

ECE 301
Fall Semester
HW #1 Solutions

(1)

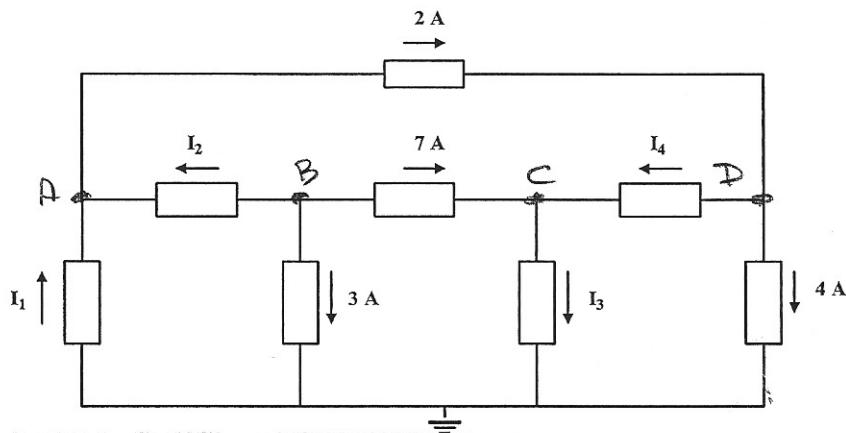- (1) For the circuit shown in Figure 1, find the currents I_1 , I_2 , I_3 , and I_4 .

Answers: $I_1 = 12\text{A}$, $I_3 = 5\text{ A}$ (Answers for I_2 and I_4 on your own)



At D:

$$I_4 + 4 - 2 = 0$$

$$\boxed{I_4 = -2\text{ A}}$$

At C:

$$I_3 = 7 + I_4 = 7 - 2 = 5\text{ A}$$

$$\boxed{I_3 = 5\text{ A}}$$

At B

$$I_2 = -3 - 7 = -10\text{ A}$$


$$\boxed{I_2 = -10\text{ A}}$$

At A

$$I_1 = 2 - I_2$$

$$\boxed{I_1 = 12\text{ A}}$$

(2)

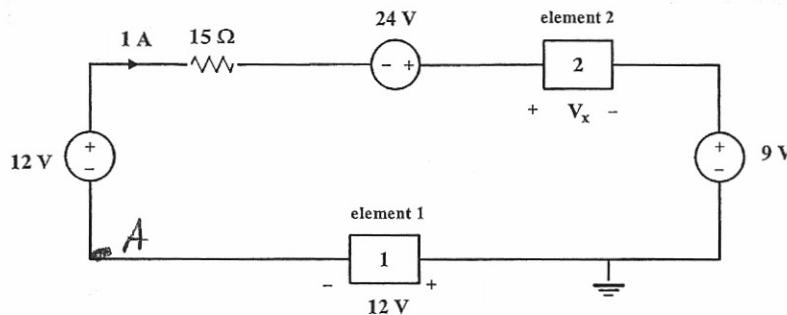

Find V_x

using KVL, starting at A, going \leftarrow ,

using $\sum \text{drops} = 0$

$$-12 + (1)(15) - 24 + V_x + 9 + 12 = 0$$


$$V_x = 12 - 15 + 24 - 21$$

$$= 36 - 36 = 0$$

$$\boxed{V_x = 0 \text{ V}}$$

(3)

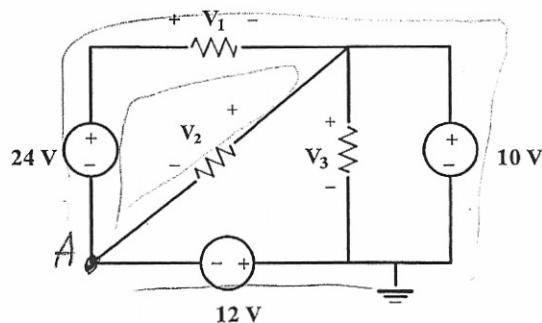- (3) You are given the circuit shown in Figure 3. Find the voltages V_1 , V_2 and V_3 .
Answers on your own.



Starting at A, going cw, use $\sum \text{drops} = 0$

$$-24 + V_1 + 10 + 12 = 0$$

$$V_1 = 24 - 22 = 2 \text{ V}$$

$$\boxed{V_1 = 2 \text{ V}}$$

Start at A, cw, $\sum \text{drops} = 0$

$$-24 + V_1 + V_2 = 0$$


$$V_2 = 24 - V_1 = 24 - 2$$

$$\boxed{V_2 = 22 \text{ V}}$$


By inspection;

$$\boxed{V_3 = 10 \text{ V}}$$

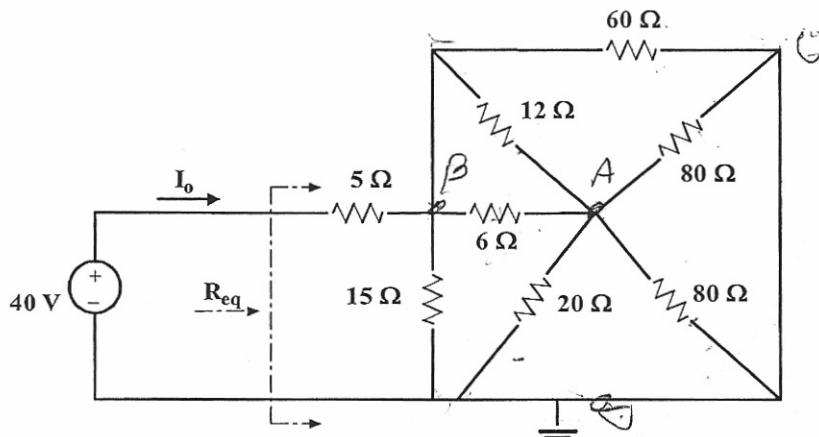
- (4) You are given the circuit shown in Figure 4. Find R_{eq} and I_0 . Ans: $R_{eq} = 12.09 \Omega$, $I_0 = 3.309 A$



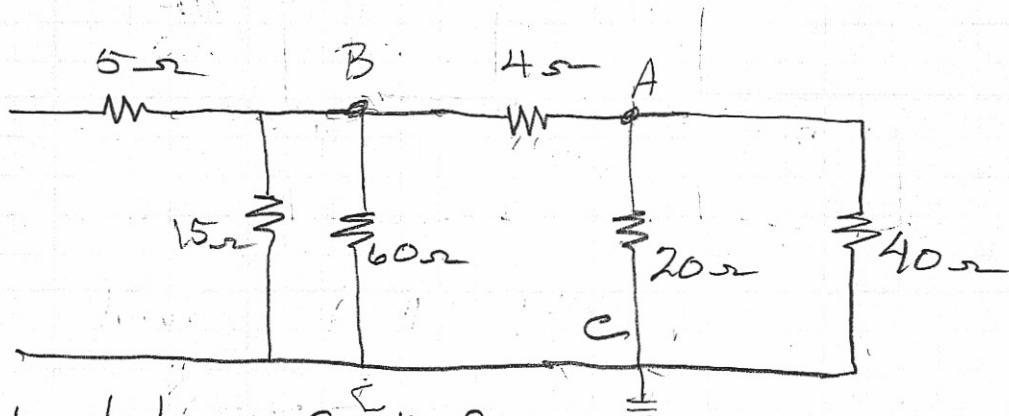
The $6\Omega \neq 12\Omega$ are in parallel. $G \parallel 12 = 4\Omega$
Two 80Ω are in parallel. Redraw



Calculate and redraw

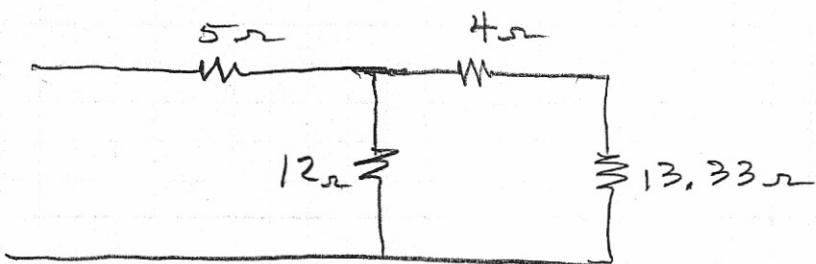

(4) cont.

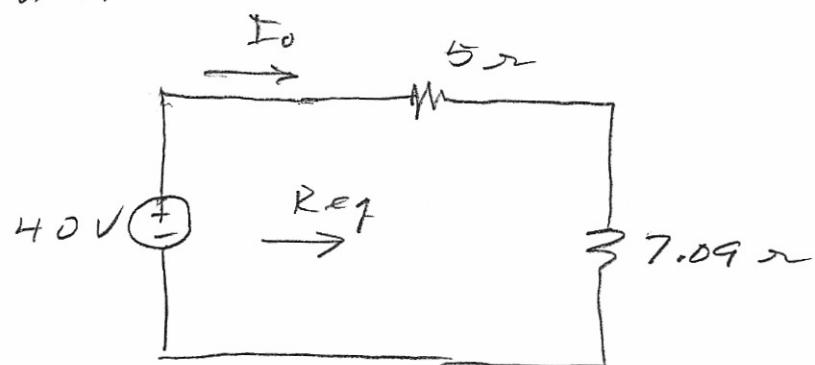

$$R_{\text{eff}} = 5 + 7.09 = 12.09 \Omega$$


$R_{\text{eff}} = 12.09 \Omega$

$$I_0 = \frac{40}{12.09}$$

$I_0 = 3.309 \text{ A}$

(5) Prob 2.16 in text.

use KCL and since V_1 and V_2

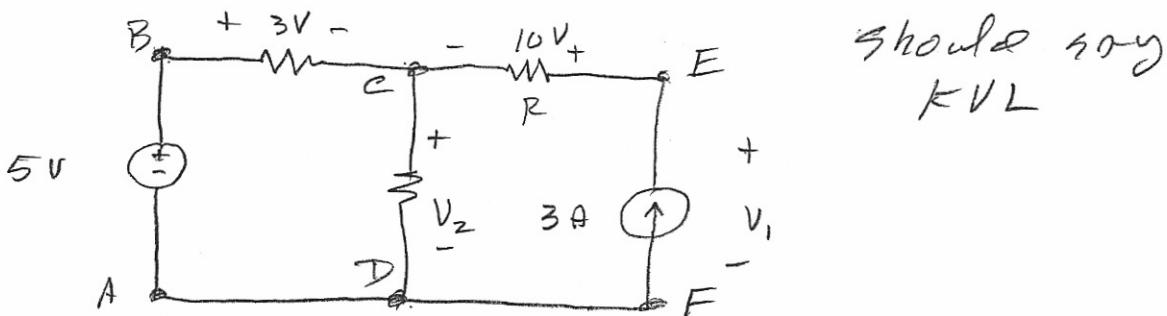

Start at A, go A-B-C-D using $\sum \text{drops} = 0$

$$-5 + 3 + V_2 = 0$$

$$\boxed{V_2 = 2V}$$

Start at D and go D-C-E-F

$$-V_2 - 10 + V_1 = 0$$

$$V_1 = 10 + V_2 = 12V$$

$$\boxed{V_1 = 12V}$$

$$P_{AB} = 3 \times 12 = 36 \text{ W}$$

$$P_{ABC} = 3 \times 10 = 30 \text{ W}$$

$$V_1 = 12 \text{ V}$$

$$V_1 = 10 + V_2 = 10 + 2 = 12 \text{ V}$$


$$0 = V_1 + V_2 - V_2 -$$

Around D-C-E-F we have

$$V_2 = 2 \text{ V}$$

$$-5 + 3 + V_2 = 0$$

Around A-B-C-D we have

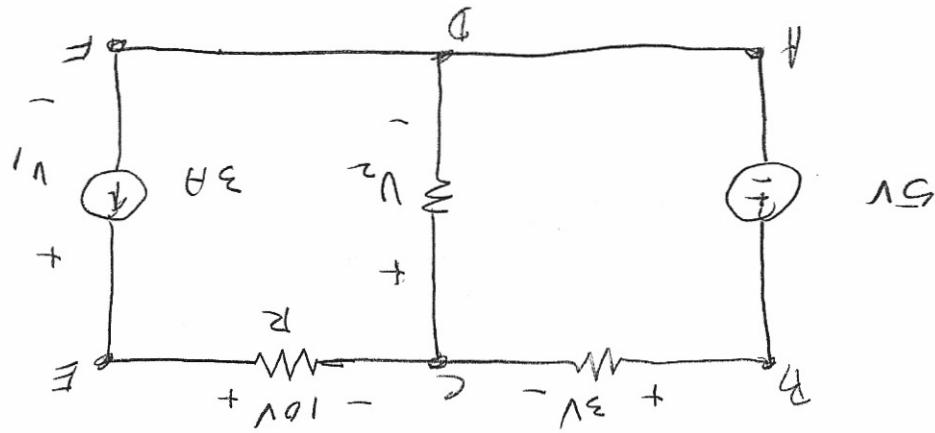

Circuit source

and power delivered by the

the power absorbed by R

For the following circuit find


(b) Power 2.81 first

(7) Prob 2.22 text. For the following ckt;

(a) Find which components are absorbing power.

(b) Is conservation of power satisfied?

Explain

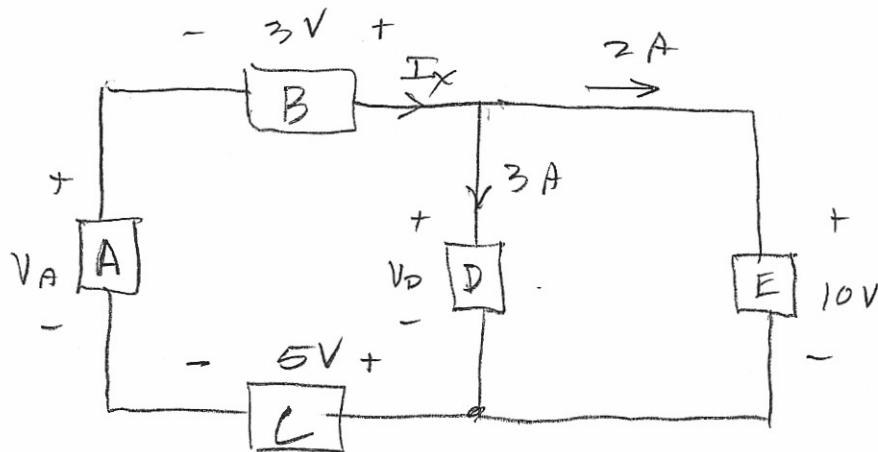

$$I_x = 5A$$

By inspection, $V_D = 10V$

$$-V_A - 3 + 10 + 5 = 0$$

$$V_A = 12V$$

Assume all are absorbing, adjunct

$$\stackrel{A}{=} P_{ABS_A} = 12(-I_x) = -60W$$

$$\stackrel{B}{=} P_{ABS_B} = -3I_x = -15W$$

$$\stackrel{C}{=} P_{ABS_C} = 5 \times I_x = 25W$$

$$\stackrel{D}{=} P_{ABS_D} = V_D \times 3 = 30W$$

(7) cont

$$\sum P_{\text{ABS}} = 10 \times 2 = 20 \text{ W}$$

Elements that absorb power are

C, D, E

Elements Supplying
A and B

Check

$$P_{\text{gap}} = P_{\text{obs}}$$


$$P_{\text{gap}} + 60 \text{ W} + 15 \text{ W} \stackrel{?}{=} 25 \text{ } P_{\text{ABS}} + 30 \text{. } + 20$$

$$75 \text{ W} = 75 \text{ W}$$

Check

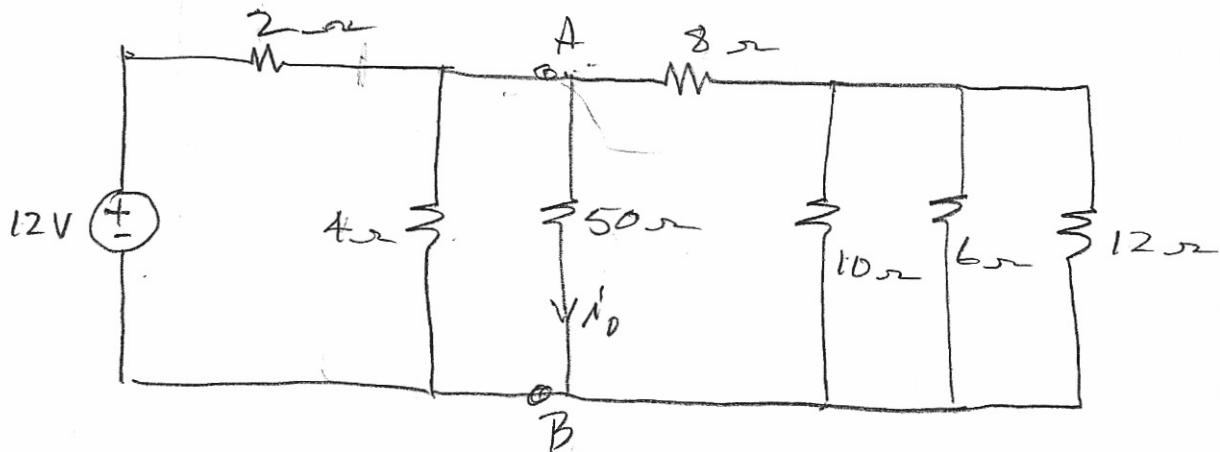18) Prob 2.60

For the following circuit,
find i and resistance seen
by the source



$$8 \Omega + 10 \parallel 11 \parallel 12 = 8 + 4 \parallel 10 = 10.857$$

Then

$$4 \parallel 50 \parallel 10.857 \checkmark \text{ ok}$$

$$\frac{1}{G} = 4^{-1} + 50^{-1} + 10.857^{-1} = .3621 \checkmark \text{ ok}$$

$$\frac{1}{R} = 2.762 \Omega$$

$$R_{eq} = 2 + 2.762 = 4.762 \Omega$$


Want to: Voltage across AB is

$$V_{AB} = \frac{12 \times 2.76}{2 + 2.76} = 6.958$$

$$i_0 = \frac{V_{AB}}{50} = 0.14 \text{ A} = 140 \text{ mA}$$

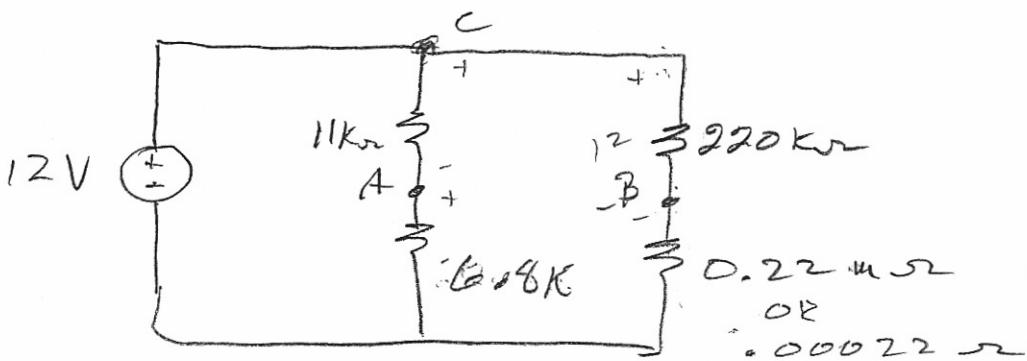(9) Prob 2.67

For the following circuit
determine V_{AB}



$$V_{CA} = \frac{12 \times 11K}{11K + 6.8K} = 7.416 \text{ V}$$

For all practical purposes, $V_{CB} = 12V$
so,


$$V_{AB} + V_{CA} - V_{CB} = 0$$

$$V_{AB} = V_{CB} - V_{CA} = 12 - 7.42$$

$$\boxed{V_{AB} = 4.58 \text{ V}}$$

(10) 2.72 in the text
 Finding r_B (battery resistance)

Assume the following conditions

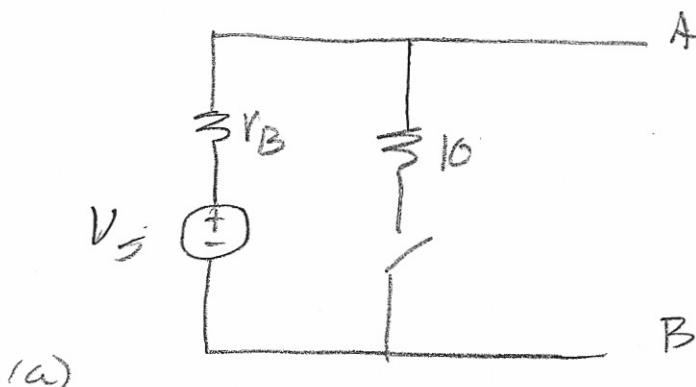


(a)

(i) V_{AB} is 2.28V when the switch is open.

(ii) V_{AB} is 2.27V when the switch is closed.

Find r_B .

From (i) we know $V_s = 2.28$

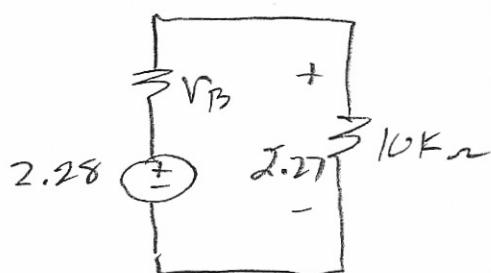

Using Voltage Division

$$2.27 = \frac{2.28 \times 10}{10 + r_B}$$

(10)

$$2.27(10 + r_B) = 2.28 \times 10$$

$$2.27 r_B = (2.28 - 2.27)10$$

$$r_B = \frac{0.1}{2.27}$$

$$r_B = 0.0044 \Omega$$

(11) Year later

$$V_{AB} = 2.2V, \text{ switch open}$$

$$V_{AB} = 0.31V, \text{ switch closed}$$

$$-31 = \frac{2.2 \times 10}{r_B + 10}$$

$$-31(r_B + 10) = 2.2 \times 10$$

$$-31r_B = 2.2 \times 10 - 31 \times 10$$

$$R_B = 60.97 \Omega$$