

Wlyg


ECE 301

HW #3

Desk
Copy

(1) Problem

(a) Find the short circuit current for the following using Nodal.

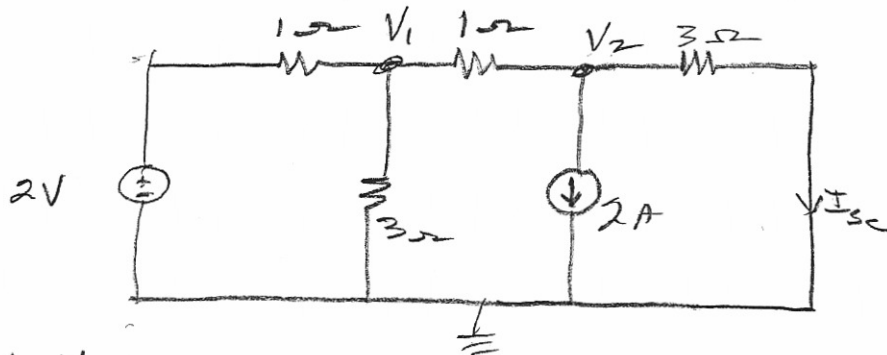At V_1

$$\frac{V_1 - 2}{1} + \frac{V_1}{3} + \frac{V_1 - V_2}{1} = 0$$

$$3V_1 - 6 + V_1 + 3V_1 - 3V_2 = 0$$

$$\boxed{7V_1 - 3V_2 = 6}$$

At V_2

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} = -2$$

$$3V_2 - 3V_1 + V_2 = -6$$

$$\boxed{-3V_1 + 4V_2 = -6}$$

$$\begin{bmatrix} 7 & -3 \\ -3 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -6 \end{bmatrix}$$

$$V_1 = 1.6316 \text{ V}$$


$$V_2 = -1.263 \text{ V}$$

$$I_{sc} = \frac{-1.263}{3} = -0.42 \text{ A}$$

1.263

(1) cont.

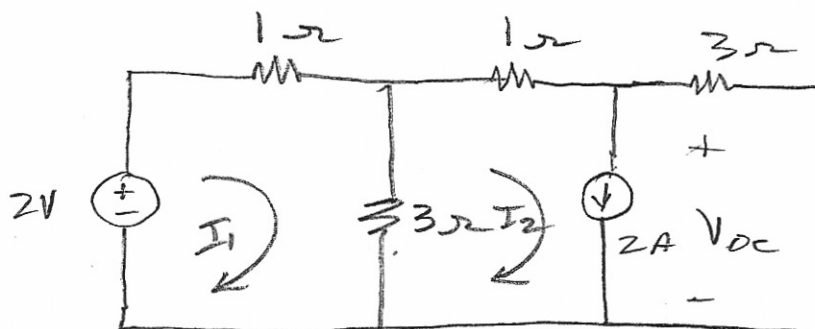(b) Find the open-circuit voltage.
Use mesh analysis



$$4I_1 - 3I_2 = 2$$

$$I_2 = 2 \quad \therefore 4I_1 = 2 + 3I_2$$

$$4I_1 = 2 + 6$$

$$I_1 = 2A$$

$$V_{oc} = -3(I_2 - I_1) + 1 \cdot I_2$$

$$= -3(2 - 2) + 2$$


$$V_{oc} = -2V$$

(c)

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{-2}{-0.42}$$

$$R_{TH} = 4.76 \Omega$$

(2) Consider the following circuit

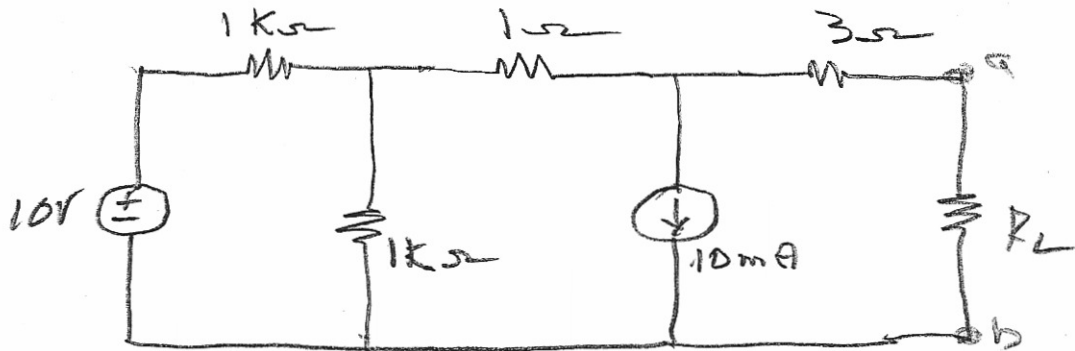


(a) Find the Thevenin equivalent circuit to the left of R_L .

(b) Make $R_L = 300\Omega$ and find V_{ab} using the Thevenin circuit.

(Practically the same as (i).)

(a) Find V_{oc} using nodal

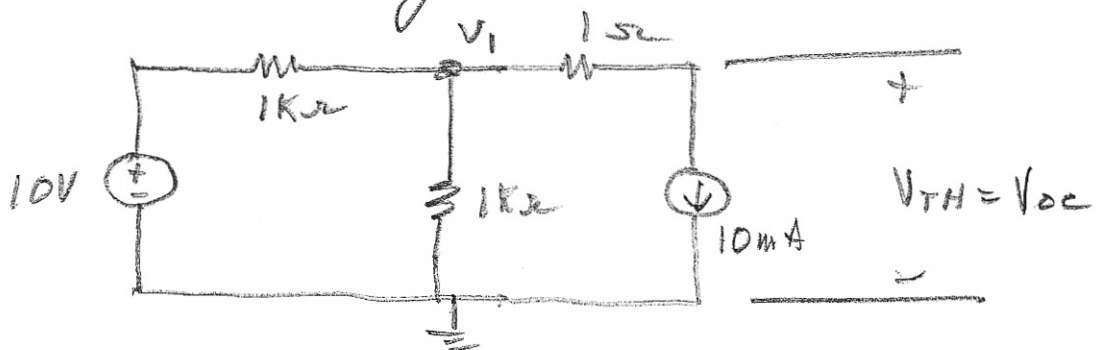

$$\frac{V_1 - 10}{1K} + \frac{V_1}{1K} = -10K^{-1}$$

$$V_1 - 10 + V_1 = -10 \Rightarrow V_1 = 0$$

Apply KVL to the outer loop


$$-V_1 + 10mA \times 1 + V_{oc} = 0$$

$$\therefore \boxed{V_{oc} = -0.01V}$$

(2) cont.


(2)

To find R_{TH} , Disable the sources,

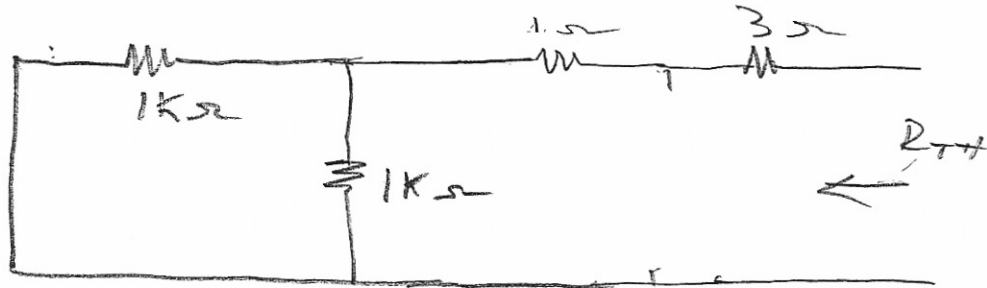

∴ $R_{TH} = 504\Omega$


(b)

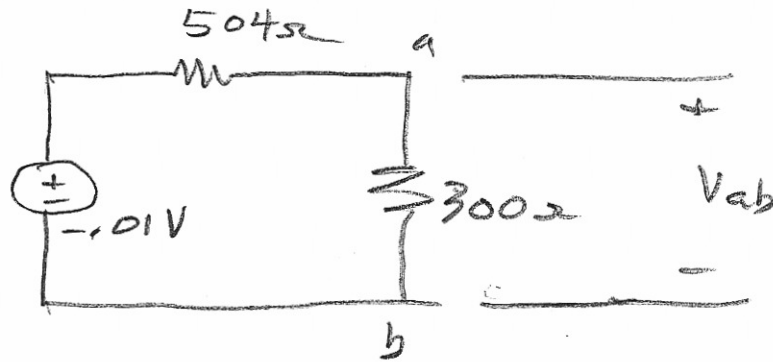


$$V_{ab} = \frac{(-0.01) \times 300}{504 + 300} = -0.00373 V$$

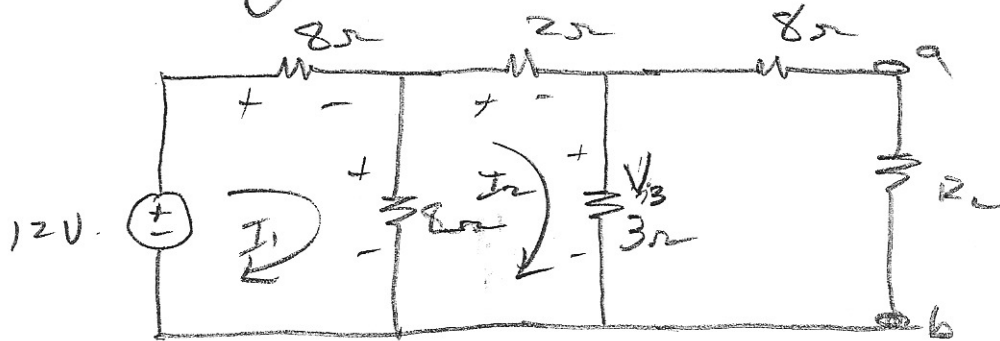(13) P 3.57

Find the Thevenin equivalent of the following circuit.



For R_{TH}

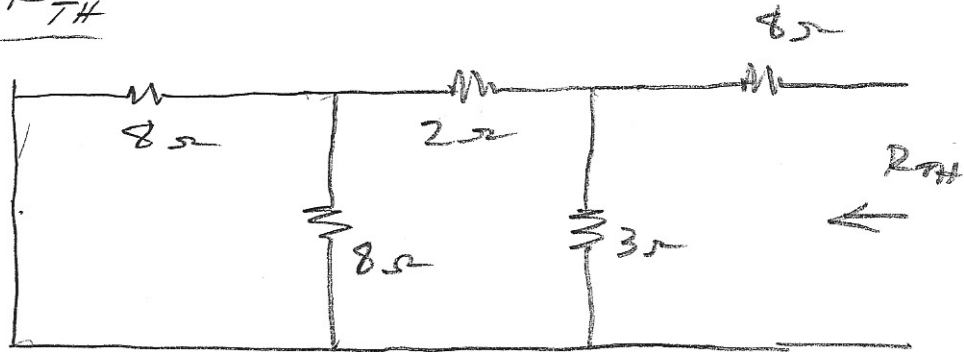

$$R_{TH} = 8 + 3 \parallel 6 = 10 \Omega$$

For V_{TH}

$$8I_1 + 8(I_1 - I_2) = 12$$

$$\boxed{16I_1 - 8I_2 = 12}$$

$$-8(I_1 - I_2) + 2I_2 + 3I_2 = 0$$


$$\boxed{-8I_1 + 13I_2 = 0}$$

(3)

$$\begin{bmatrix} 16 & -8 \\ -8 & 13 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \end{bmatrix}$$

$$I_1 = 1.083 \text{ A} \quad I_2 = 0.667 \text{ A}$$

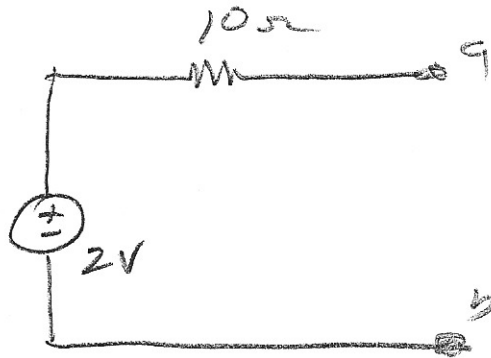
$$V_{TH} = V_{oc} = 3 \times I_2 = 2 \text{ V}$$



THEVENIN CIRCUIT


(4) P 3.66

Given the following circuit

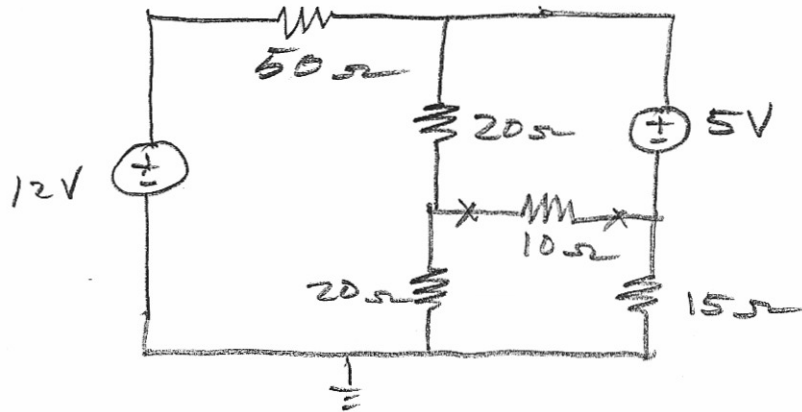

Find R_{TH} , V_{TH} , I_H

Find V_{TH}

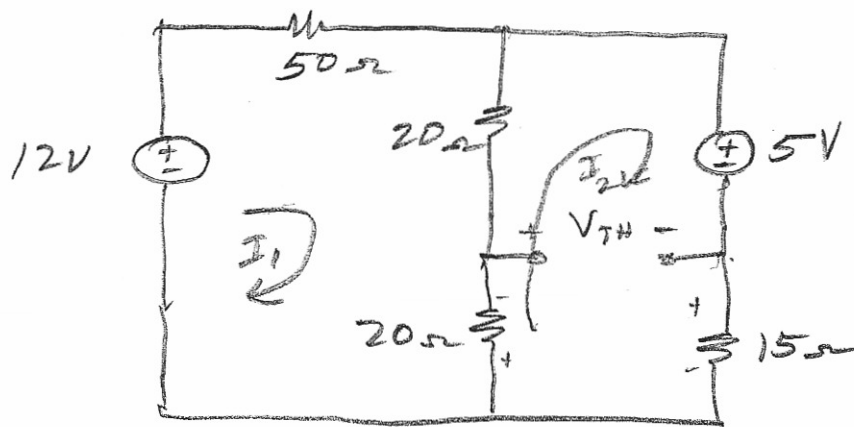

$$\begin{bmatrix} 90 & -40 \\ -40 & 55 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ -5 \end{bmatrix}$$

$$I_1 = 0.137 \text{ A}, \quad I_2 = .00896 \text{ A}$$


$$-V_{TH} + 20(I_1 - I_2) - 15I_2 = 0$$

(4) cont.

$$V_{TH} = 20(-.137 - .00896) - 15 \times .00896$$

$$\boxed{V_{TH} = 2.43 \text{ V}}$$

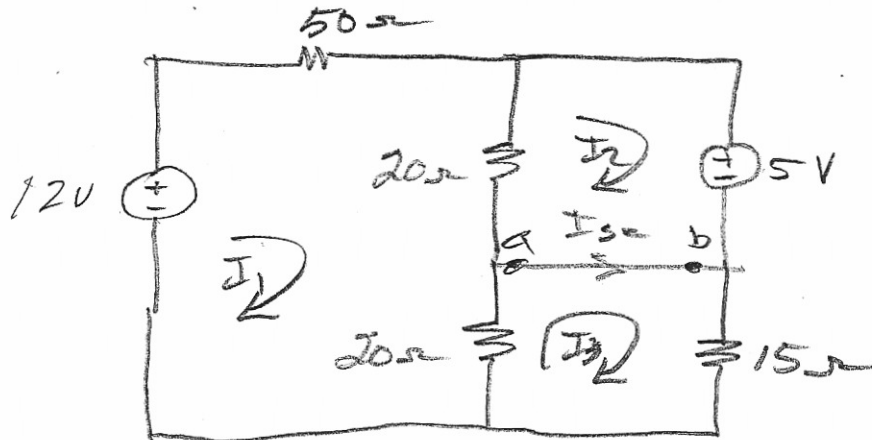To find $I_N = I_{sc}$, analyze the following



$$I_{sc} = I_3 - I_2$$

$$\begin{bmatrix} 90 & -20 & -20 \\ -20 & 20 & 0 \\ -20 & 0 & 35 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \\ -5 \\ 0 \end{bmatrix}$$

$$I_1 = .1195 \text{ A}, \quad I_2 = -0.13049, \quad I_3 = 0.06829$$


$$\therefore I_{sc} = .06829 + 0.13049 = .1988$$

$$I_N = I_{sc} = 198.8 \text{ mA}$$


$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{2.43}{.1988} = 12.22 \Omega$$

(4) cont.


THOVENIN circuit

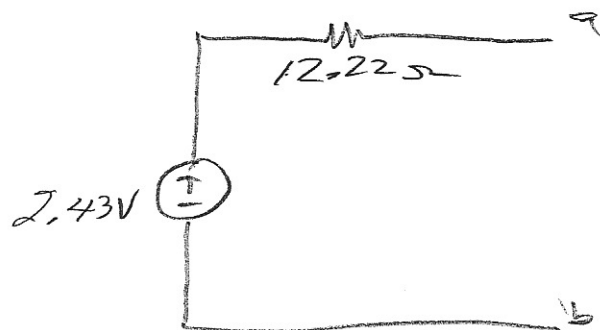


NORTON circuit

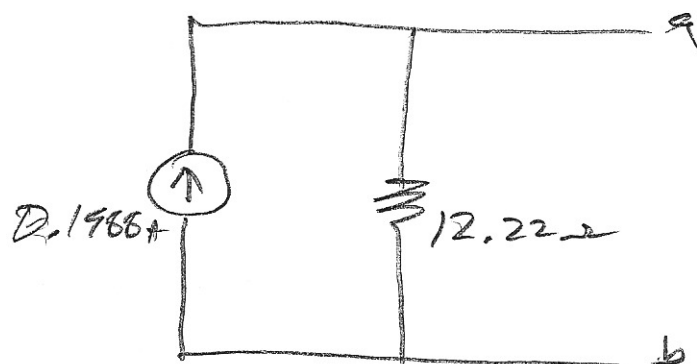


(5) Given the following circuit

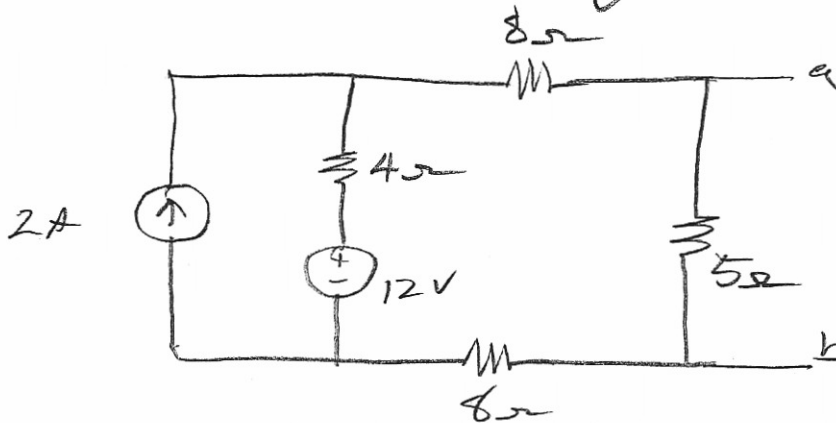

(a) Develop & Draw the Thevenin circuit.

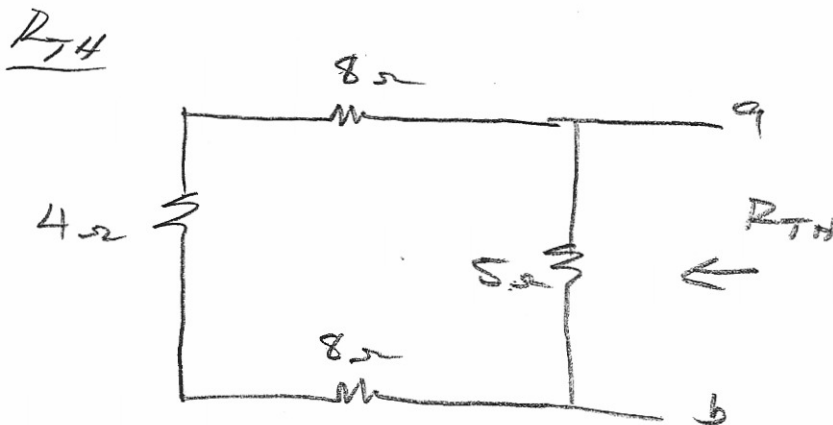

$$R_{TH} = 5 \parallel 20 = 4\Omega$$

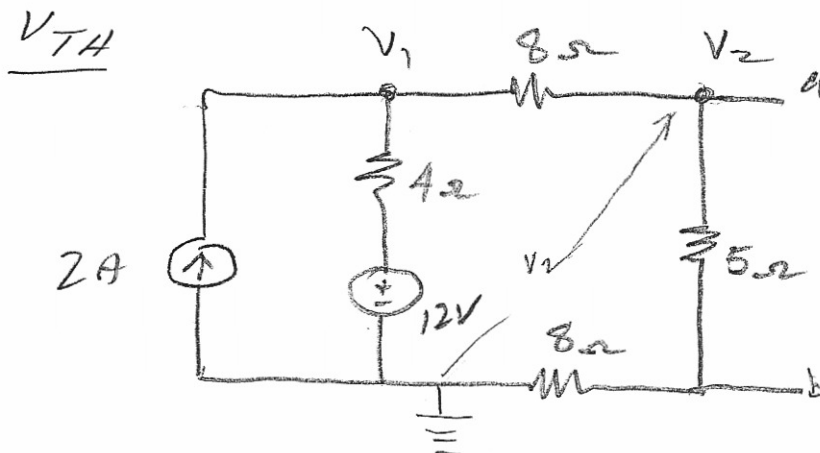

$$V_{TH} = \underline{V_2 \times 5}$$

(5) cont

5.2

At V_1

$$\frac{V_1 - 12}{4} + \frac{V_1 - V_2}{8} = 2$$

$$2V_1 - 24 + V_1 - V_2 = 16$$

$$\boxed{3V_1 - V_2 = 40}$$

At V_2

$$\frac{V_2 - V_1}{8} + \frac{V_2 - 12}{13} = 0$$

$$13V_2 - 13V_1 + 8V_2 = 0 \quad \text{--- (1)}$$

$$-13V_1 + 21V_2 = 0 \quad \text{--- (2)}$$

$$\begin{bmatrix} 3 & -1 \\ -13 & 21 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \end{bmatrix}$$

$$V_1 = 16.8 \text{ V}, \quad V_2 = 10.4$$


$$V_{TH} = V_{OC} = \frac{10.4 \times 5}{5 + 8} = 4$$

$$V_{TH} = 4 \text{ V}$$

(5) cont


5.3

THEVENIN Ckt

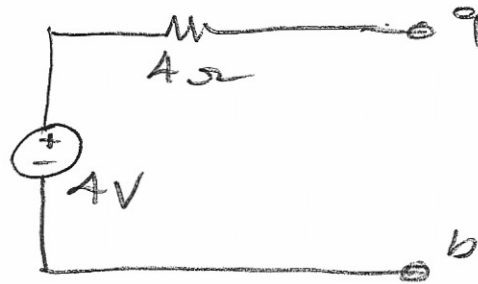

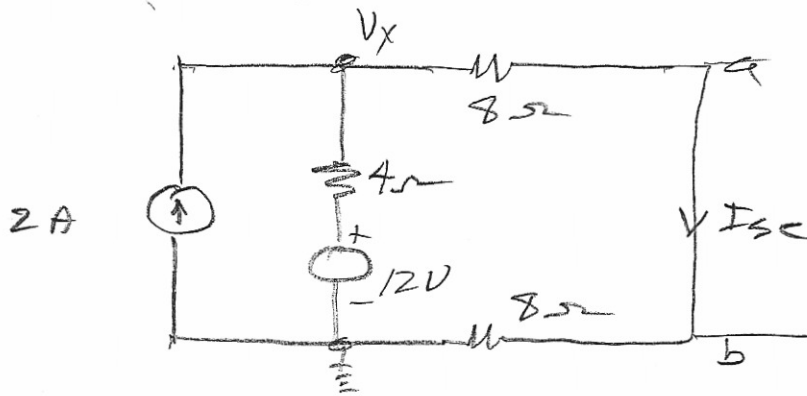(b) Norton

To find $I_{sc} = I_N$. Analyze the following ckt,



$$\frac{V_x - 12}{4} + \frac{V_x}{16} = 2$$

$$4V_x - 48 + V_x = 32$$

$$5V_x = 80$$

$$V_x = 16V$$

$$I_{sc} = \frac{16}{16} = 1A$$

(5) cont.

5.4

The Norton ckt,

