


Wlg

ECE 301

H.W. #4

FALL 2006

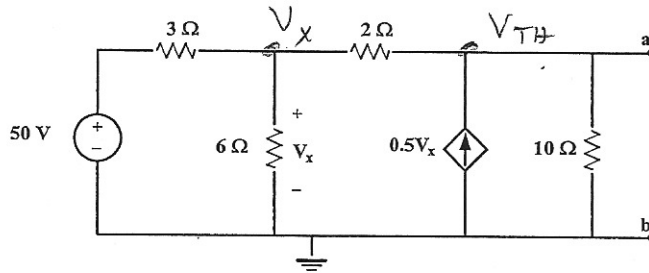- (1) You are given the circuit of Figure 1. Find the Thevenin voltage and Thevenin resistance seen looking into terminals a-b. Ans:  $V_{TH} = 166.67 \text{ V}$ ,  $R_{TH} = 10 \Omega$



Solution for  $V_{TH}$  using Nodal. Node voltages defined above.

At  $V_x$

$$\frac{V_x - 50}{3} + \frac{V_x}{6} + \frac{V_x - V_{TH}}{2} = 0$$

$$2V_x - 100 + V_x + 3V_x - 3V_{TH} = 0$$

$$\boxed{6V_x - 3V_{TH} = 100}$$

At  $V_{TH}$

$$\frac{V_{TH} - V_x}{2} + \frac{V_{TH}}{10} - 0.5V_x = 0$$

$$5V_{TH} - 5V_x + V_{TH} - 5V_x = 0$$

$$\boxed{-10V_x + 6V_{TH} = 0}$$

$$\begin{bmatrix} 6 & -3 \\ -10 & 6 \end{bmatrix} \begin{bmatrix} V_x \\ V_{TH} \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$


$$V_{TH} = 166.67 \text{ V}$$

$$V_x = 100 \text{ V}$$

(1) cont.

1.2

Will work by applying a 1 volt source

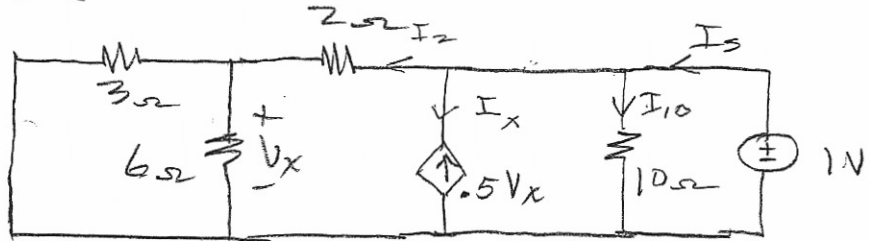

$$R_{TH} = \frac{1}{I_3} ; \text{ Find } I_3$$

$$I_{10} = \frac{1}{10} = 0.1 \text{ A}$$

$$I_3 = 0.1 + I_2 - 0.5V_x$$


$$V_x = \frac{1 \times 2}{2+2} = 0.5 \text{ V}$$

$$I_2 = \frac{1 - V_x}{2} = \frac{0.5}{2} = 0.25$$


$$I_x = -0.5V_x = -0.25$$

$$I_3 = 0.1 + 0.25 - 0.25 = 0.1$$


$$R_{TH} = \frac{1}{0.1} = 10 \Omega$$

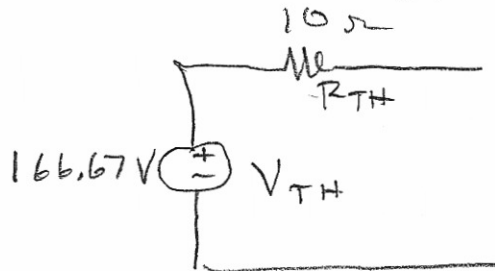

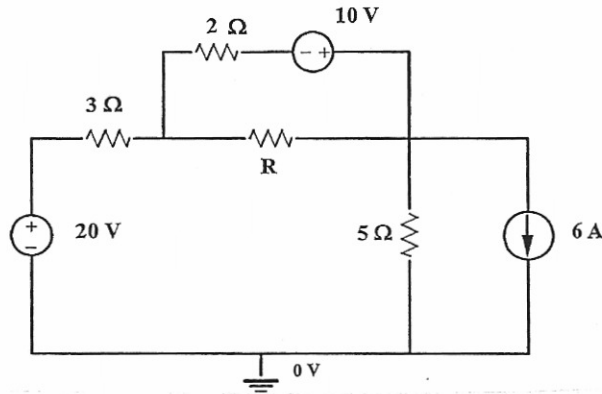- (2) You are given the circuit of Figure 2. Find the maximum power that can be delivered to the resistor R. Answer: 625 mW (Along the way,  $V_{TH} = 2V$ ,  $R_{TH} = 1.6 \Omega$ )




FOR  $R_{TH}$

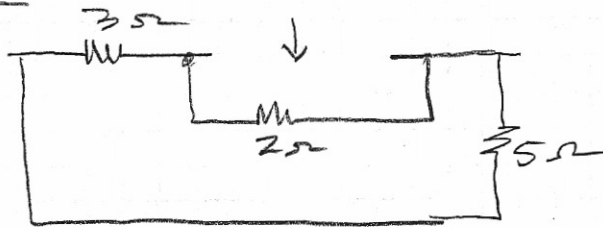

$$R_{TH} = 2 \parallel (3+5) = \frac{2 \times 8}{2+8} = 1.6 \Omega$$

FOR  $V_{TH}$

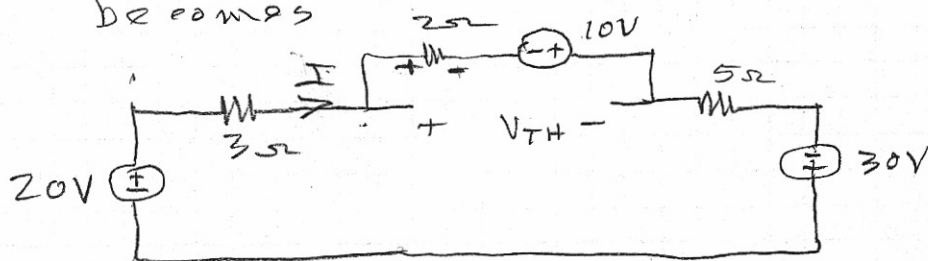Using a source transformation, ext becomes




$$I = -60/10 = 6A$$

$$V_{TH} - 2 \times 6 + 10 = 0$$

$$V_{TH} = 2V$$

(3) You are given the circuit of Figure 3. It is known that  $C_{eq} = 10 \mu F$ .

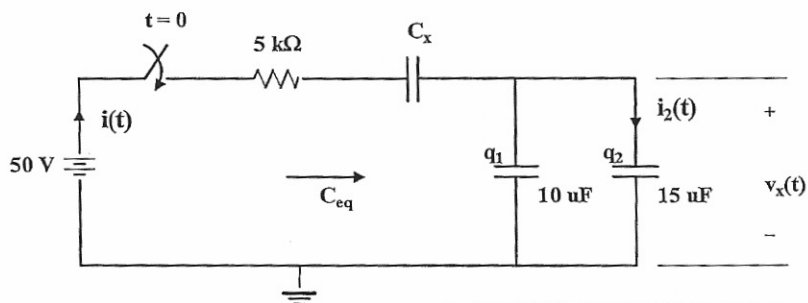- (a) Determine  $q_{eq}$ ,  $q_1$ , and  $q_2$  in steady state. Ans:  $500 \mu C$ ,  $200 \mu C$ ,  $300 \mu C$ ,  $500 \mu C$ .  
 (b) Determine  $V_x$  in steady state. Ans:  $20 V$   
 (c) Determine  $i_2(\infty)$ . On your own  
 (d) Determine  $i(0^+)$ . Explain your answer. Ans:  $10 mA$



(a)  $C_{eq} = 10 \mu F$

$\therefore Q = CV \Rightarrow Q_{eq} = 10 \mu F \times 50$   
 $Q_{eq} = 500 \mu C$

$V_x = \frac{Q_{eq}}{C_{eq}} = \frac{500 \mu C}{25 \mu F} = 20 V$

$Q_1 = 10 \mu F \times 20 V = 200 \mu C$

$Q_1 = 200 \mu C$

$Q_2 = 15 \mu F \times 20 V$

$Q_2 = 300 \mu C$

(b) From the above  $V_x = 20 V$


(c)  $t \rightarrow \infty$ , capacitors look like an open ckt.

$\therefore i_2(\infty) = 0$

(d) initially ( $t=0^+$ ) capacitors look like shorts

$\therefore i(0^+) = \frac{50}{5k} = 10 mA$

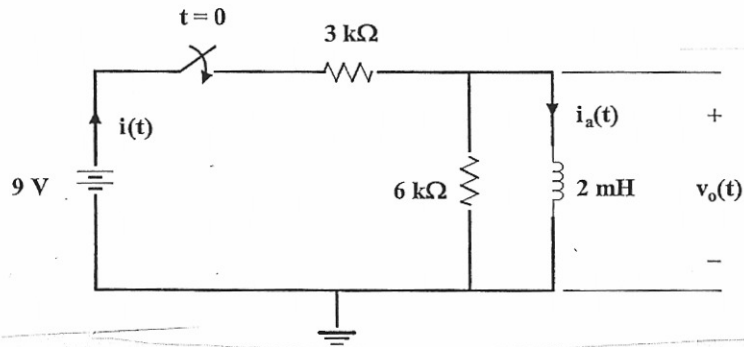- (4) You are given the circuit of Figure 4.
- Find  $v_o(t)$  for  $t = 0^+$ . Ans: 6 V
  - Find  $v_o(\infty)$ . Ans: On your own
  - Find  $i(0^+)$ . 1 mA
  - Find  $i_a(0^+)$ . Ans: On your own
  - Find  $i(\infty)$ . Ans: On your own



(a) initially coil looks like open ckt.

$$\therefore v_o(t) = \frac{9 \times 6k}{6k + 3k} = 6V$$

(b) In steady state, coil looks like short circuit.

$$\therefore v_o(\infty) = 0$$

(c) initially coil looks like an open

$$\therefore i(0^+) = \frac{9}{9k} = 1mA$$

(d) initially coil looks like open  
 $\therefore i_a(0^+) = 0$

(e) with coil as short & as  $t \rightarrow \infty$

$$i(\infty) = \frac{9}{3k}$$

$$i(\infty) = 3mA$$