

Wdy

ECE 301
HW #5
Fall 2006

(1) You are given the circuit of Figure 1.


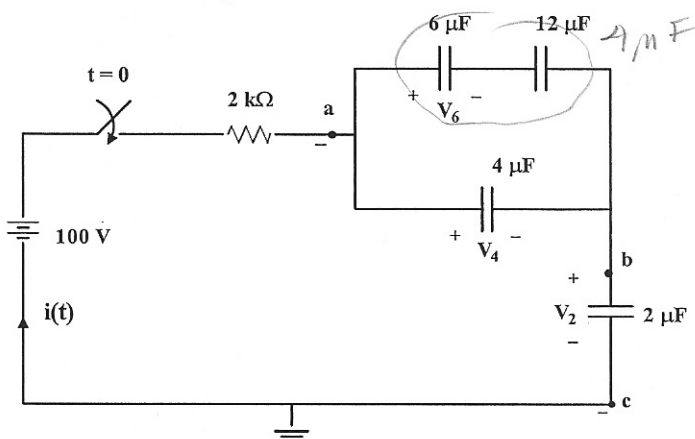


Figure 1: Circuit for problem 1.

- (a) Find the steady state voltages, V_2 , V_4 and V_6 . Ans: 80 V, 20 V and 13.33 V.
- (b) Find the value of $i(\infty)$, that is, the steady state value of $i(t)$. Ans: on your own
- (c) Find the value of $i(0^+)$. Explain your answer. Ans: 50 mA

(a) Circuit Reduces to

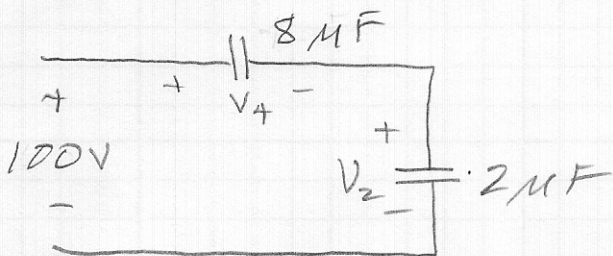

$$V_2 = \frac{100 \times 8 \mu F}{2 \mu F + 8 \mu F} = \underline{\underline{80V}}$$

$$\therefore V_4 = \underline{\underline{20V}}$$

$$V_6 = \frac{20 \times 12 \mu F}{12 \mu F + 6 \mu F} = \underline{\underline{13.33V}}$$

(1) (b) Find $i(\infty)$

circuit looks like open circuit
in steady state. \therefore

$$i(\infty) = 0$$

(c) Find $i(0^+)$,

capacitors look like short ext
at $t = 0^+$

\therefore


$$i(0^+) = \frac{100}{2k} = 50 \text{ mA}$$

(2) For the circuit of Figure 2.

(a) Determine the steady state voltage, v_x . Ans: On your own

(b) Determine $v_x(0^+)$. On your own.

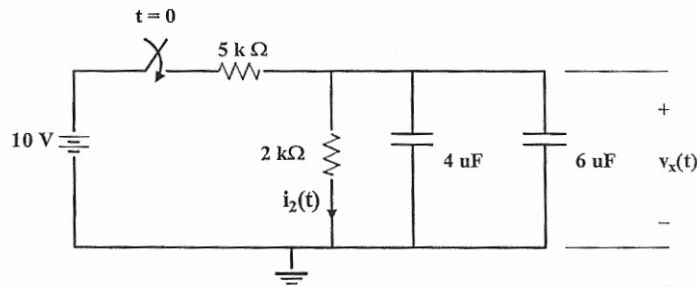(c) Determine $i_2(0^+)$ (explain your answer). Ans: 0



(a) capacitors look like
an open ckt at $t = \infty$

$$\therefore V_x(\infty) = \frac{10 \times 2k}{2k + 5k}$$

$$V_x(\infty) = 2.86 \text{ V}$$

(b) capacitors look like an
short circuit at $t = 0^+$


$$\therefore V_x(0^+) = 0 \text{ V}$$

(c) Since $V_x(0^+) = 0$

$$i_2(0^+) = 0$$

through $2k\Omega$

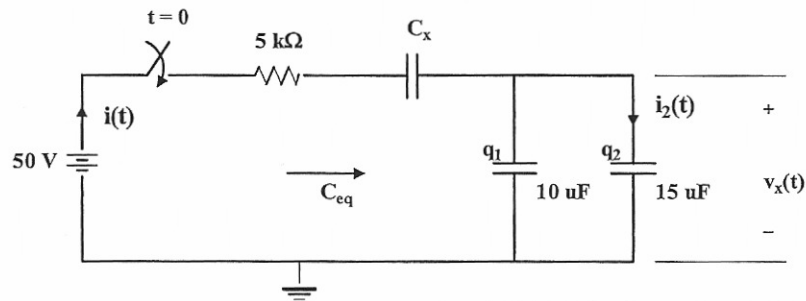- (3) You are given the circuit of Figure 3. It is known that $C_{eq} = 10 \mu F$.
- Determine q_{eq} , q_1 , and q_2 in steady state. Ans: $500 \mu C$, $200 \mu C$, $300 \mu C$, $500 \mu C$.
 - Determine V_x in steady state. Ans: $20 V$
 - Determine $i_2(\infty)$. On your own
 - Determine $i(0^+)$. Explain your answer. Ans: $10 mA$



(a) $C_{eq} = 10 \mu F$

$\therefore Q = CV \Rightarrow Q_{eq} = 10 \mu F \times 50$
 $Q_{eq} = 500 \mu C$

(b) $V_x = \frac{Q_{eq}}{C_{eq}} = \frac{500 \mu C}{25 \mu F} = 20 V$

$Q_1 = 10 \mu F \times 20 V = 200 \mu C$

$Q_1 = 200 \mu C$

$Q_2 = 15 \mu F \times 20 V$

$Q_2 = 300 \mu C$

(b) From the above $V_x = 20 V$


(c) $t \rightarrow \infty$, capacitors look like an open circuit.

$\therefore i_2(\infty) = 0$

(d) initially ($t=0^+$) capacitors look like shorts

$\therefore i(0^+) = \frac{50}{5k} = 10 mA$

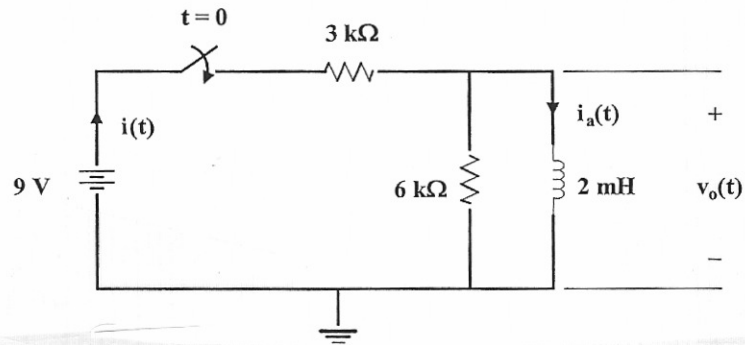- (4) You are given the circuit of Figure 4.
- Find $v_o(t)$ for $t = 0^+$. Ans: 6 V
 - Find $v_o(\infty)$. Ans: On your own
 - Find $i(0^+)$. 1 mA
 - Find $i_a(0^+)$. Ans: On your own
 - Find $i(\infty)$. Ans: On your own



(a) initially coil looks like open ckt.

$$\therefore v_o(t) = \frac{9 \times 6k}{6k + 3k} = 6V$$

(b) in steady state, coil looks like short circuit.

$$\therefore v_o(\infty) = 0$$

(c) initially coil looks like an open

$$\therefore i(0^+) = \frac{9}{9k} = 1mA$$

(d) initially coil looks like open
 $\therefore i_a(0^+) = 0$

(e) with coil as short & as $t \rightarrow \infty$

$$i(\infty) = \frac{9}{3k}$$

$$i(\infty) = 3mA$$