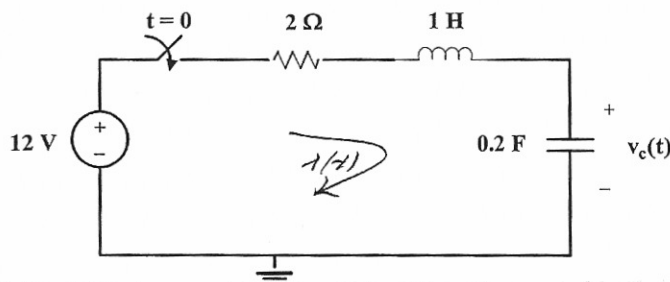


wkg

ECE 301
H.W. #7
Fall 2006

(1) You are given the circuit of Figure 7.1. $v_c(0^-) = 8$ V. Find $v_c(t)$ for $t > 0$.

Ans: $12 - e^{-t}[4\cos 2t + 2\sin 2t]$ V



We write the differential equation for the circuit (use R, L, C and V_s to avoid errors).

$$Ri(t) + L \frac{di}{dt} + v_c(t) = V_s \quad (1.1)$$

$$\text{but } i(t) = C \frac{dv_c}{dt} \quad (1.2)$$

Place (1.2) into (1.1)

$$RC \frac{dv_c}{dt} + LC \frac{d^2v_c}{dt^2} + v_c(t) = V_s$$

AND

$$\frac{d^2v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{v_c}{LC} = \frac{V_s}{LC}$$

Characteristic equation is

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

(4) cont.

Putting in numerical values,

$$s^2 + 2s + 5 = 0$$

$$(s+1+j2)(s+1-j2) = 0$$

The solution will be of the form

$$V_c(t) = V_{ct}(t) + V_{chs}$$

$$V_{chs} = V_s = 12 \quad (\text{by inspection})$$

so

$$V_c(t) = 12 + e^{-t} [A \cos 2t + B \sin 2t] \quad (1.3)$$

Now we know

$$V_c(0^-) = 8 = V_c(0^+)$$


$$i(0^-) = 0 = C \frac{dV_c}{dt} = i(0^+)$$

$$\text{so } \frac{dV_c(0^+)}{dt} = 0$$


Evaluate (1.3) @ $V_c(0^+)$ and $\dot{V}_c(0^+)$
to get two equations and solve for
A & B as follows.

$$V_c(0^+) = 8 = 12 + A \Rightarrow \boxed{A = -4}$$

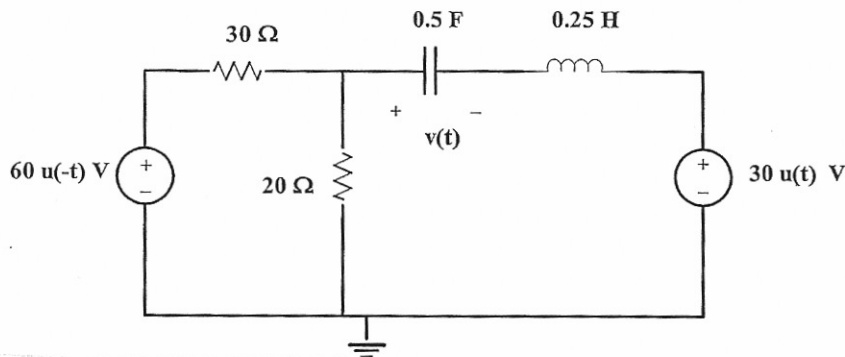(2) You are given the circuit of Figure 7.2. Find $v(t)$ for $t > 0$. Ans $-30 - 0.19e^{-47.83t} + 54.19e^{-0.167t}$ V




For $t < 0$, the circuit is

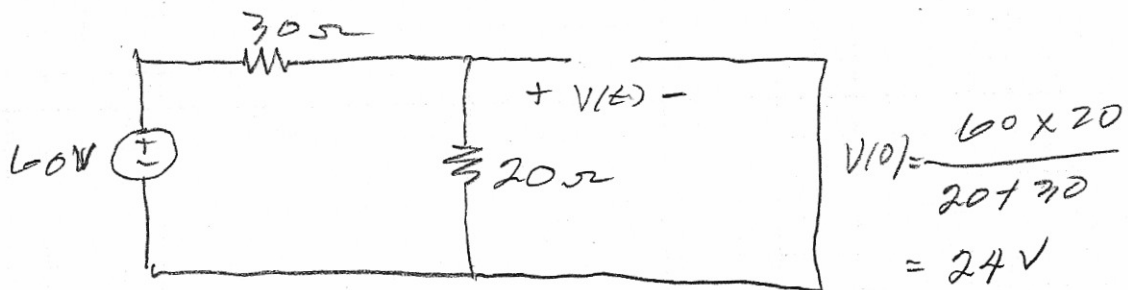

We see that

$$v(0) = 24 \text{ V} = v(0^+)$$

For $t > 0$, the circuit is

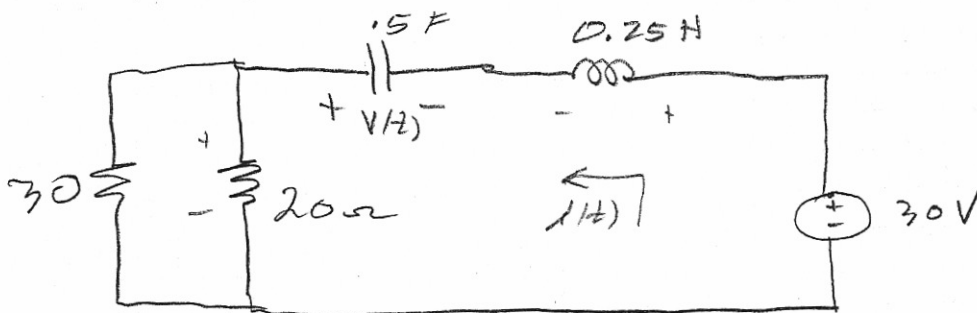

$$-30 + L \frac{di}{dt} - v(t) + R i(t) = 0$$

$$i = -C \frac{dv}{dt} = -0.5 \frac{dv}{dt}$$

$$R_T = 30 \parallel 20 = 12 \Omega$$

(1) cont.

1.3

$$\frac{dv_c}{dt} = e^{-t} [-2(-4)\sin 2t + 2B\cos 2t] - e^{-t} [-4\cos 2t + B\sin 2t] \Big|_{t=0} = 0$$

$$0 = 2B + 4$$

$$B = -2$$

\therefore

$$v_c(t) = 12 - e^{-t} [4\cos 2t + 2\sin 2t]$$

(2) cont.

2.2

Substituting for $i(t)$ gives

$$L C \frac{d^2 V}{dt^2} + R C \frac{dV}{dt} + V = -30$$

$$\frac{dV}{dt} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = -\frac{30}{LC}$$

$$s^2 + 48s + 8 = 0$$

$$(s + .167)(s + 47.83) = 0$$

$$V(t) = -30 + k_1 e^{-0.167t} + k_2 e^{-47.83t}, \quad \checkmark$$

$$\boxed{V(0^+) = 24} \quad i = -C \frac{dV}{dt} = 0 \quad \dot{V}(0^+) = 0$$

$$24 = -30 + k_1 + k_2$$

$$\boxed{k_1 + k_2 = 54}$$

$$\frac{dV}{dt} = -.167 k_1 e^{-.167t} - 47.83 k_2 e^{-47.83t}$$

$$0 = .167 k_1 + 47.83 k_2$$

$$\begin{bmatrix} 1 & 1 \\ .167 & 47.83 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 54 \\ 0 \end{bmatrix}$$

(2) cont.

$$K_1 = 54.19$$

$$K_2 = -0.19$$


∴

$$v(t) = \left(-30 + 54e^{-.167t} - 47.83e^{-.4783t} - 0.19e^{-.4783t} \right) V$$


(3) You are given the circuit of Figure 7.3.

(a) Find $i(t)$ for $t > 0$. Ans: $4 - 0.0655(e^{-0.522t} - e^{-11.98t})$ A

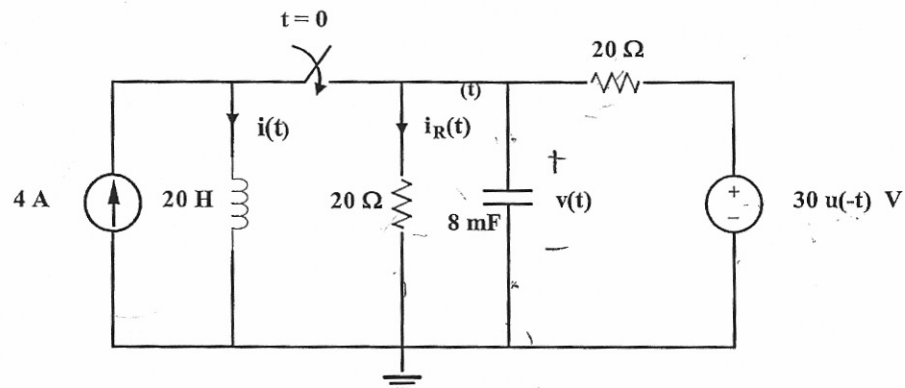(b) Find $i_R(t)$ for $t > 0$. Ans: $0.785e^{-11.98t} - 0.0342e^{-0.522t}$ A




$t < 0$

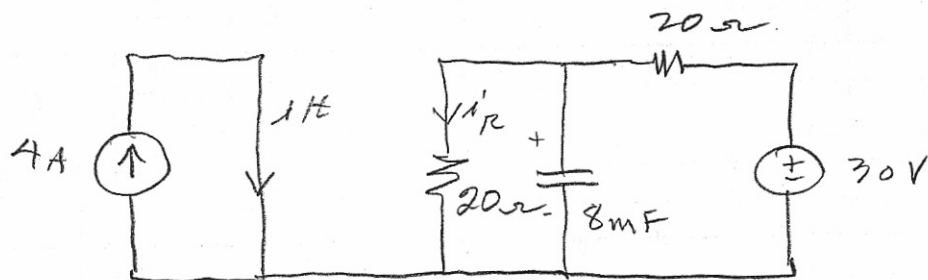

$$i(0^-) = 4A = i(0^+)$$

$$v(0^-) = v(0^+) = 15V$$

$t > 0$

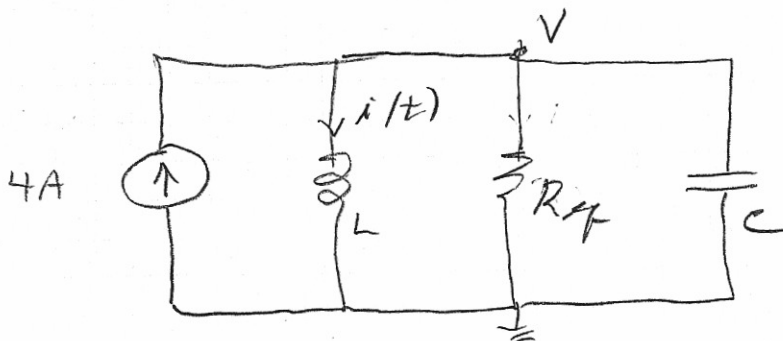

Write a general equation

(3)

$$\frac{V}{R_g} + C \frac{dV}{dt} + i' = I_s$$

$$V = L \frac{di'}{dt}$$

$$\frac{L}{R_g} \frac{di'}{dt} + LC \frac{d^2 i'}{dt^2} + i' = I_s$$

$$\frac{d^2 i'}{dt^2} + \frac{1}{R_g C} \frac{di'}{dt} + \frac{i'}{LC} = \frac{I_s}{LC}$$

$$R_{gC} = 10 \Omega, C = 8 \text{ mF}, L = 20 \text{ H}$$

$$s^2 + \frac{1 \times 10^3}{10 \times 8} s + \frac{1 \times 10^3}{20 \times 8} = 0$$

$$(s^2 + 12.5s + 6.25) = 0$$

$$(s + 0.522)(s + 11.98) = 0$$

so

$$i'(t) = 4 + k_1 e^{-0.522t} + k_2 e^{-11.98t}$$

$$i'(0^+) = 4 = 4 + k_1 + k_2$$

$$k_1 + k_2 = 0$$

$V_{L=0} = L \frac{di'}{dt}$

$$\left. \frac{di'}{dt} \right|_{t=0} = \frac{15}{L} = \frac{15}{20} = 0.75$$

$$0.75 = -0.522 k_1 - 11.98 k_2$$

$$\begin{bmatrix} 1 & 1 \\ -1.522 & -11.98 \end{bmatrix} \begin{bmatrix} K_1 \\ K_2 \end{bmatrix} = \begin{bmatrix} 0 \\ .75 \end{bmatrix}$$

$$K_1 = 0.0655$$

$$K_2 = -0.0655$$

$$i(t) = 4 + 0.0655 \left[e^{-0.522t} - e^{-11.98t} \right] A$$

FOR $i_R(t)$

$$V = L \frac{di}{dt}; \quad i_R = \frac{V}{20} = \frac{L}{20} \frac{di}{dt} \quad L = 20 H$$

$$\begin{aligned} i_R(t) &= \frac{20}{20} \left[-0.522 \times 0.0655 e^{-0.522t} + 0.0655 \times 11.98 e^{-11.98t} \right] \\ &= \left(-0.034 e^{-0.522t} + 0.785 e^{-11.98t} \right) A \end{aligned}$$

OR (turns around)

$$i_R(t) = \left(0.785 e^{-11.98t} - 0.034 e^{-0.522t} \right) A$$