

wk 2

Examples Solving Differential Equations Using The Symbolic Tool Kit of Matlab

Example 1

Given:

$$\frac{dv}{dt} + 5v = 10 \quad v(0) = 0$$

```
>> dsolve('Dv + 5*v = 10', 'v(0) = 0')
```

```
ans =
```

```
2 + 2*exp(-5*t)
```

Example 2

Given:

$$\frac{d^2v}{dt^2} + 8\frac{dv}{dt} + 12v = 5$$

```
>>
```

```
>> dsolve('D2v + 8*Dv + 12*v = 5', 'v(0) = 0', 'Dv(0) = 0')
```

```
ans =
```

```
5/12 - 5/8*exp(-2*t) + 5/24*exp(-6*t)
```

Example 3

```
>>
```

```
>> % The following DE has complex roots
```

```
>>
```

```
>> dsolve('D2v + 4*Dv + 16*v = 0', 'v(0) = 2', 'Dv(0) = 0')
```

```
ans =
```


```
2/3*3^(1/2)*exp(-2*t)*sin(2*3^(1/2)*t) + 2*exp(-2*t)*cos(2*3^(1/2)*t)
```

$$\frac{d^2v}{dt^2} + 4\frac{dv}{dt} + 16v = 0;$$

wlog

Solution for Take Home Exam Problem.

Start with the circuit.

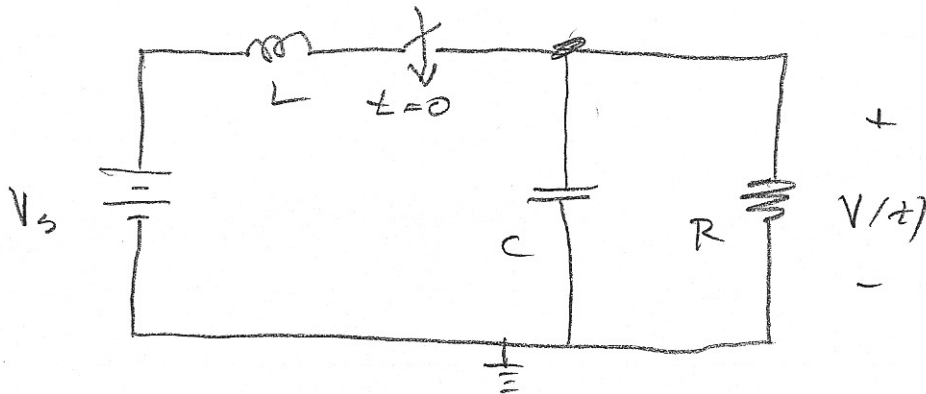

1a)

Use nodal analysis to develop the following equation.

$$C \frac{dV(t)}{dt} + \frac{V(t)}{R} + \frac{1}{L} \int_0^t (V(t) - V_s) dt = 0$$

Take the derivative of the above equation.

$$C \frac{d^2V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{V(t) - V_s}{L} = 0$$

clearing;

$$\boxed{\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V(t)}{LC} = \frac{V_s}{LC}} \quad (1)$$

We know the solution will
be of the form

(2)

$$v(t) = V_{ss} + v_t$$

where $V_{ss} = V_s$

so

$$v(t) = V_s + e^{-\xi \omega_n t} [A \cos \omega_d t + B \sin \omega_d t]$$

where we use the characteristic
equation as

$$s^2 + 2\xi \omega_n s + \omega_n^2 = 0$$

AND roots of

$$s_1, s_2 = -\xi \omega_n \pm j \omega_d$$

$$\omega_d = \omega_n \sqrt{1 - \xi^2}$$

We know $v(t)$ can be expressed
as

$$v(t) = V_s + e^{-\xi \omega_n t} [\sqrt{A^2 + B^2} \cos(\omega_d t + \phi)]$$

We don't know, prior to selecting
 ξ & ω_n , the values of A & B .

As a ball park approximation we
try that 3

$$\sqrt{A^2+B^2} \doteq V_s = 10 \text{ (for here)}$$

We know we want

$$V(t_{ss}) = 10 + e^{-\frac{1}{3} \omega_n t_{ss}} \left[\sqrt{A^2+B^2} \cos(\omega_n t_{ss} + \phi) \right]$$

$$\doteq 10 + e^{-\frac{1}{3} \omega_n t_{ss}} \frac{\sqrt{A^2+B^2}}{10}$$

$$V(t_{ss}) \doteq 10 + e^{-\frac{1}{3} \omega_n t_{ss}} \quad 10 = 10 \pm .01$$

OR we want

$$10 e^{-\frac{1}{3} \omega_n t_{ss}} \leq .01$$

$$t_{ss} = 0.1, \quad \frac{1}{3} = 0.4$$

$$e^{-.04 \omega_n} \leq .001$$

$$-.04 \omega_n / n e \leq \ln .001$$

$$\text{OR } .04 \omega_n > +6.91$$

$$\omega_n \geq 173$$

$$\text{TRY } \omega_n = 175$$

(4)

This gives

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0 \quad (\zeta = 0.4, \omega_n = 175)$$

$$s^2 + 140s + 30625 = 0$$

The differential equation will be

$$\frac{\partial^2 v}{\partial t^2} + 140 \frac{\partial v}{\partial t} + 30625 v(t) = 306250$$

Characteristic equation factors as

$$(s + 70 + j160.4)(s + 70 - j160.4) = 0$$

$$v(t) = 10 + e^{-70t} [A \cos 160t + B \sin 160t]$$

$$v(0^+) = 0;$$

$$\dot{v}(0^+) = 0$$

$$0 = 10 + A \Rightarrow A = -10$$

$$\frac{dv}{dt} = e^{-70t} [-160A \sin 160t + 160B \cos 160t] - 70 e^{-70t} [A \cos 160t + B \sin 160t]$$

$$0 = 160.4B - 70A$$

$$B = \frac{-700}{160.4} = -4.364$$

(5)

$$v(t) = 10 - e^{-70t} [10 \cos 160.4t + 4.364 \sin 160.4t]$$

Now check with symbolic:

```
>>
>>
>> dsolve('D2v + 140*Dv + 30625*v = 306250' , 'v(0) = 0', 'Dv(0) = 0')

ans =

10-10*exp(-70*t)*cos(35*21^(1/2)*t)-20/21*21^(1/2)*exp(-70*t)*sin(35*21^(1/2)*t)
```

```
>>
```

$$10 - 10e^{-70t} \cos 160.4t - 4.364e^{-70t} \sin 160.4t$$

checks,


Now run MATLAB to check response and steady state.

```
% program to verify take home problem
% for ECE 301. Fall Semester, 2006.
% save as: take_home_RLCm.m

t = 0:.001:.15;

v = [10-10*exp(-70*t).*cos(35*21^(1/2)*t)-20/21*21^(1/2)*exp(-70*t).*sin(35*21^(1/2)*t)];
[t;v]'
plot(t,v)
grid
ylabel('v(volts)')
xlabel('t (sec)')
```

16

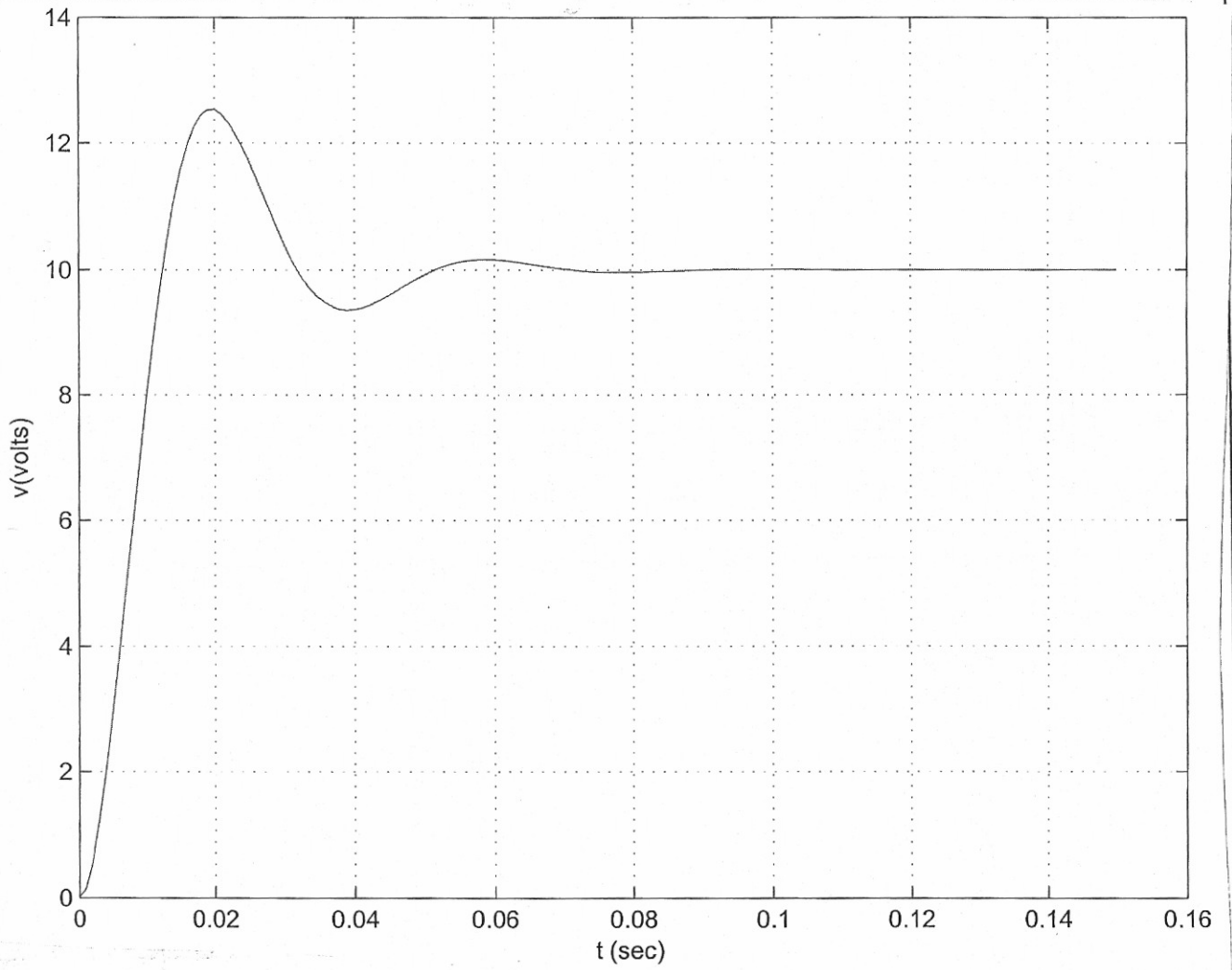

| | |
|--------|---------|
| 0.0950 | 10.0090 |
| 0.0960 | 10.0099 |
| 0.0970 | 10.0104 |
| 0.0980 | 10.0105 |
| 0.0990 | 10.0104 |
| 0.1000 | 10.0099 |
| 0.1010 | 10.0092 |
| 0.1020 | 10.0084 |
| 0.1030 | 10.0074 |
| 0.1040 | 10.0064 |
| 0.1050 | 10.0053 |
| 0.1060 | 10.0042 |

(7)

Now find R, L, C .

$$\text{Use } C = 100 \mu\text{F}$$

$$\frac{1}{LC} = 30625$$

$$L = \frac{1}{30625C} = \frac{10,000}{30625}$$

$$L = 0.327 \text{ H}$$

$$\frac{1}{RC} = 140$$

$$R = \frac{1}{140C} = \frac{10,000}{140}$$

$$R = 71.4 \Omega$$

$$0.327 \text{ H} < L < 4 \text{ H}$$

$$\frac{100000}{30625} = 7.26$$