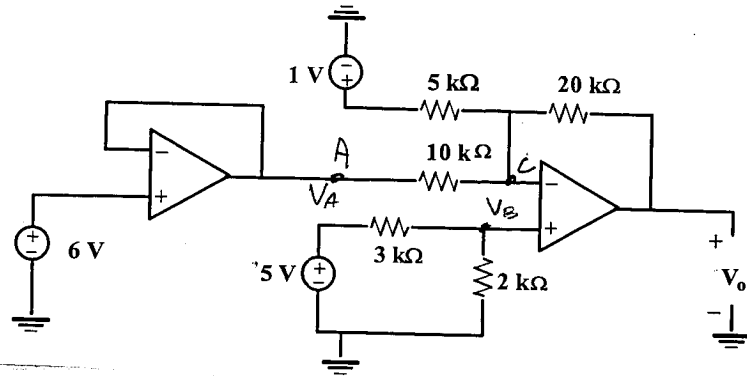


Test #3

ECE 301
Test #4 B

(1) Find the output voltage, V_o , for the op amp circuit shown in Figure 1.



At "A"; $V_A = 6V$

At V_B

$$V_B = \frac{5 \times 2k}{2k + 3k} = 2V$$

At "C"

$$\frac{V_B - 6}{10k} + \frac{V_B - 1}{5k} + \frac{V_B - V_o}{20k} = 0$$

$$2(2-6) + 4(2-1) + 2 - V_o = 0$$


$$-8 + 4 + 2 - V_o = 0$$

$$V_o = -2V$$


turn in

(2) You are given the ideal transformer shown in Figure 2.

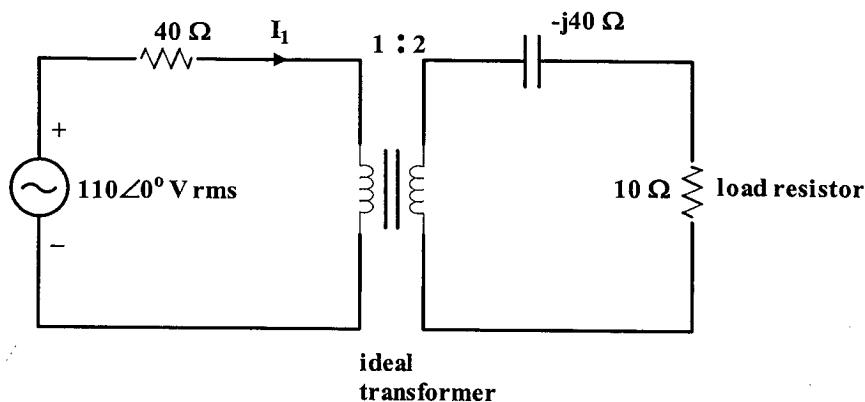- (a) Find the phasor current I_1 .
- (b) Find the power dissipated in the 10Ω load resistor.



Reflect the secondary to the primary.

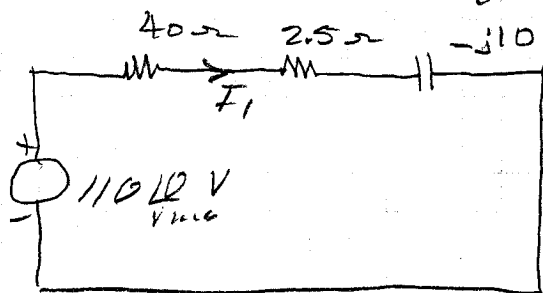

(a)

$$I_1 = \frac{110}{42.5 - j10} = 2.52 \angle 13.24^\circ \text{ A rms}$$

(b)


$$\left| \frac{I_1}{I_2} \right| = \frac{N_2}{N_1} = 2$$

$$|I_2| = \frac{|I_1|}{2} = \frac{2.52}{2} = 1.26 \text{ A rms}$$

$$P_{10} = |I_2|^2 \cdot 10 = (1.26)^2 \times 10$$

$$P_{10} = 15.88 \text{ W}$$

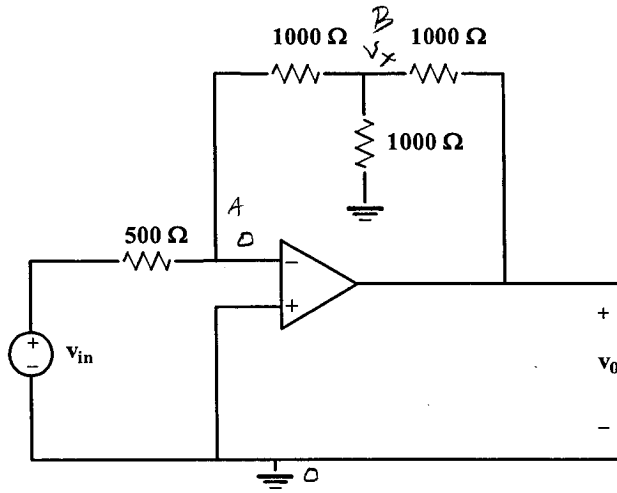(3) Find the output voltage v_0 in terms of the input voltage v_{in} for the op amp circuit of Figure 3.



At A

$$\frac{0 - v_{in}}{500} + \frac{0 - v_x}{1000} = 0$$

$$-2v_{in} = v_x = 0$$

$$\underline{v_x = -2v_{in}}$$


At B

$$\frac{v_x - 0}{1000} + \frac{v_x}{1000} + \frac{v_x - v_0}{1000} = 0$$

$$v_0 = 3v_x$$

$$\boxed{v_0 = -6v_{in}}$$

Counter Example #3-

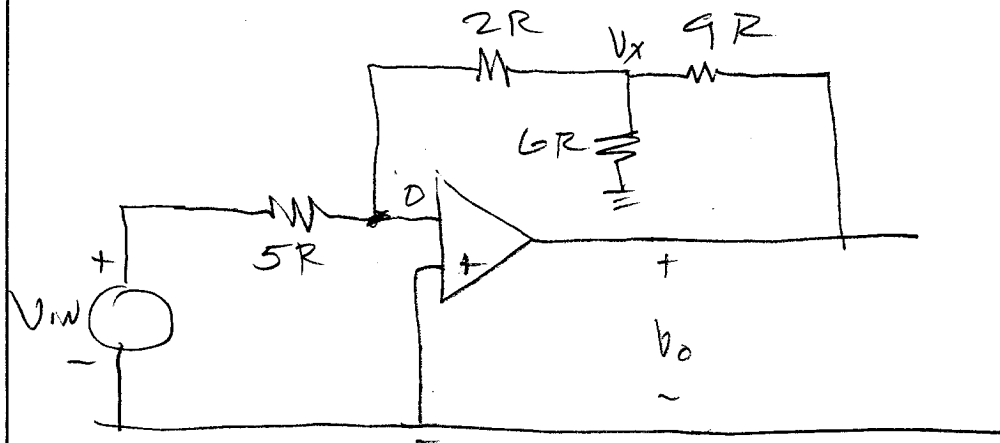

$$-\frac{V_{in}}{5R} + \frac{-V_x}{2R} = 0 \quad \left(\frac{V_x}{2} = -\frac{V_{in}}{5} \right)$$

$$\left(V_x = -\frac{2}{5} V_{in} \right)$$

$$\frac{V_x}{2R} + \frac{V_x}{6R} + \frac{V_x - V_o}{9R} = 0$$

$$54 \left(\frac{V_x}{2R} + \frac{V_x}{6R} + \frac{V_x}{9R} = \frac{V_o}{9R} \right)$$

$$27V_x + 9V_x + 6V_x = 6V_o$$

$$42V_x = 6V_o$$

$$V_o = \frac{42}{6} \left(-\frac{2}{5} \right) V_{in} = -\frac{84}{30} V_{in} = -\frac{14}{5} V_{in}$$


Other way

$$-\frac{V_{in}}{5R} + \frac{-V_o}{17R} = 0$$

$$V_o = -\frac{17}{5} V_{in}$$

Does not agree

Counter Example #3

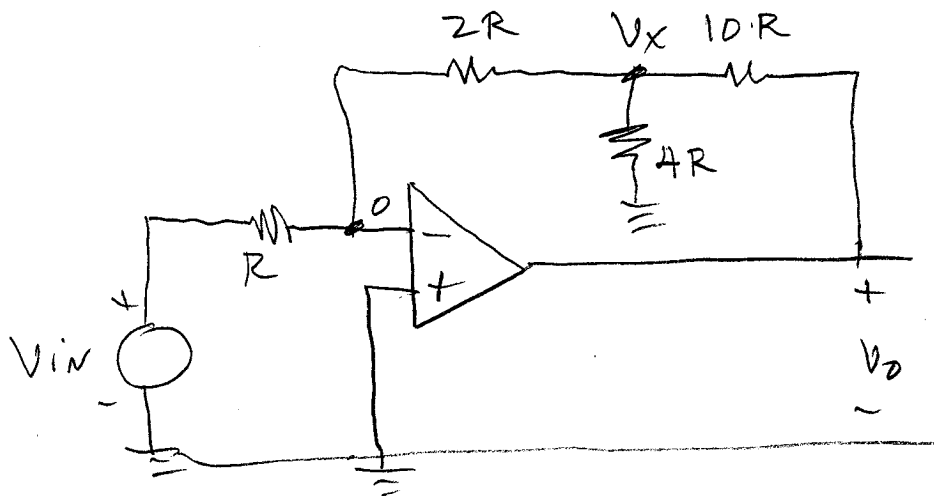

$$-\frac{V_{in}}{R} + \frac{(-V_x)}{2R} = 0$$

$$-2V_{in} - V_x = 0$$

$$\underline{V_x = -2V_{in}}$$

At V_x

$$20 \left(\frac{V_x - 0}{2R} + \frac{V_x}{4R} + \frac{V_x - V_o}{10R} \right) = 0$$

$$10V_x + 5V_x + 2V_x - 2V_o = 0$$

$$2V_o = 17V_x = 17(-2V_{in})$$

$$\boxed{V_o = -17V_{in}}$$

$$-\frac{V_{in}}{R} - \frac{V_o}{16R} = 0$$



$$V_{in} = -\frac{V_o}{16}$$

$$\boxed{V_o = -16V_{in}}$$

Does not agree

B

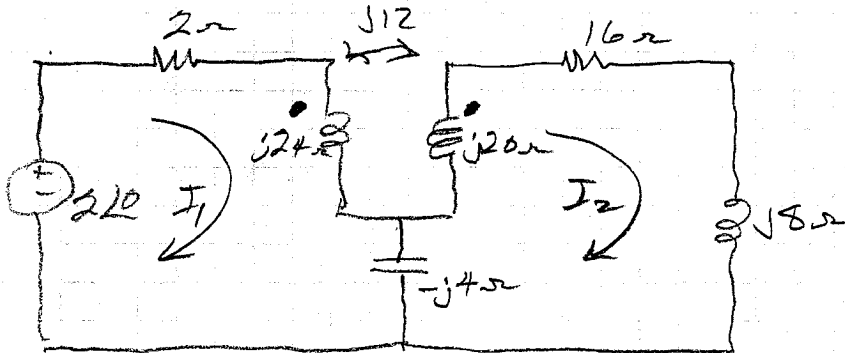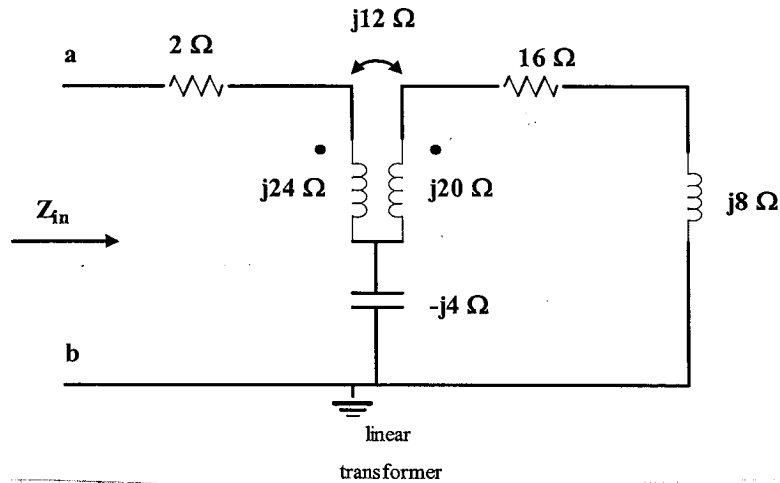(4) You are given the linear transformer circuit shown in Figure 4. Find the input impedance Z_{in} of the circuit.



$$(2 + j24 - j4)I_1 + j4I_2 - j12I_2 = 2 \angle 0^\circ$$

$$(2 + j20)I_1 - j8I_2 = 2 \angle 0^\circ$$

$$(-j4 + j20 + 16 + j8)I_2 + j4I_1 - j12I_1 = 0$$


$$-j8I_1 + (16 + j24)I_2 = 0$$

$$I_1 = 0.1085 \angle -80^\circ$$

$$Z_{in} = \frac{2 \angle 0^\circ}{0.1085 \angle -80^\circ}$$

$$Z_{in} = 18.43 \angle 80^\circ \Omega = (3.2 + j18.15) \Omega$$

(4) This is a tedious and really unnecessary way to work the problem, but I will. One should use reflected impedance for the answers required (I_1 & $|I_2|$) it does not matter how I assume dots. I will use the following.

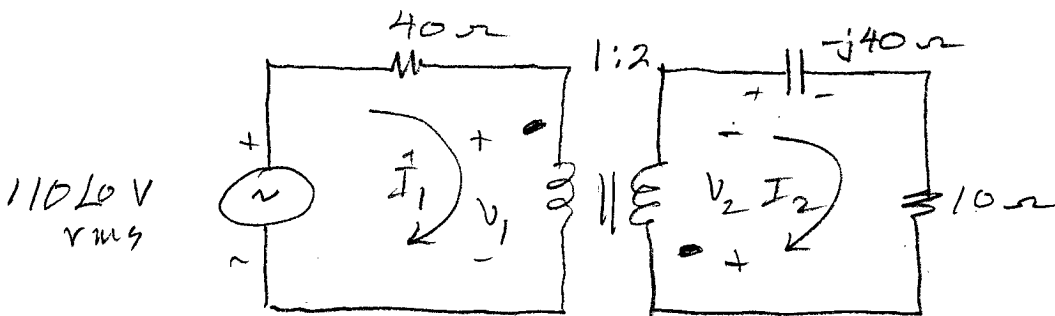

mesh 1

$$V_1 + 40I_1 = 110\angle 0$$

or

$$40I_1 + 0I_2 + V_1 + 0V_2 = 110\angle 0$$

mesh 2

$$(10 - j40)I_2 + V_2 = 0$$

or

$$0I_1 + (10 - j40)I_2 + 0V_1 + V_2 = 0$$

$$\frac{V_2}{V_1} = 2$$

or

$$0I_1 + 0I_2 + 2V_1 - V_2 = 0$$

$$\frac{I_1}{I_2} = -2$$

or

$$I_1 + 2I_2 + 0V_1 + 0V_2 = 0$$

(A) or

3

$$\begin{bmatrix} 40 & 0 & 1 & 0 \\ 0 & 10 \angle -40^\circ & 0 & 1 \\ 0 & 0 & 2 & -1 \\ 1 & 2 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 110 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Need I_1 & I_2

$$I_1 = 2.52 \angle 13.2^\circ \text{ A rms}$$

$$I_2 = 1.26 \angle -166.7^\circ \text{ A rms}$$

(b)

$$P_{10} = |I_2|^2 \times 10 = (1.26)^2 \times 10$$

$$P_{10} = 15.88 \text{ W}$$

Real average power always has zero phase angle.