

wlg

ECE 301
RC & RL Circuits

Lesson 10

9/28/06

In considering the RC and RL circuit we assume a single structure at first and add more complexity later. There are two divisions we make.

A. The RC & RL circuit with no external forcing function. (Initial condition only)

B. The RC & RL circuit with a forcing function. (Can also include an initial condition).

A. Consider the circuit below.

Be Kind

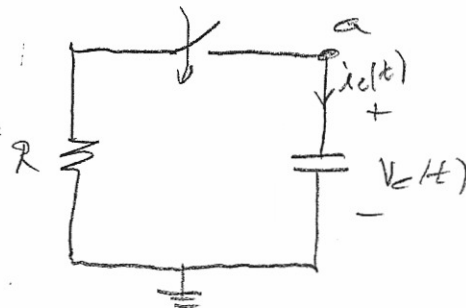


Figure 10: RC circuit without a forcing function.

We assume $V_C(0^-) = V_0$. We know $V_C(0^+) = V_C(0^-)$.

Writing a nodal equation at "a" gives

$$\frac{V_C(t)}{R} + C \frac{dV_C}{dt} = 0 \quad (10.1)$$

or

$$\frac{dV_C}{dt} + \frac{V_C(t)}{RC} = 0 \quad (10.2)$$

We can also put the equation in the form

10.2

$$RC \frac{dV_c(t)}{dt} + V_c(t) = 0 \quad (10.3)$$

The solution to (10.1) is of the form

$$V_c(t) = A e^{st} \quad (10.4)$$

where A & s are unknowns. Placing this assumed solution in (10.2) gives

$$\frac{d[Ae^{st}]}{dt} + \frac{Ae^{st}}{RC} = 0$$

OR

$$sAe^{st} + \frac{Ae^{st}}{RC} = 0$$

OR

$$s + \frac{1}{RC} = 0 \quad (10.5)$$

giving

$$s = -\frac{1}{RC} \quad (10.6)$$

Placing (10.6) into (10.4) gives

$$V_c(t) = A e^{-\frac{t}{RC}} \quad (10.7)$$

We now use the initial condition

$$V_c(0^+) = V_0$$

giving

$$V_0 = A e^{-\frac{t}{RC}} \Big|_{t=0} = A$$

And

$$V_c(t) = V_0 e^{-\frac{t}{RC}} \quad (10.8)$$

This is called the natural response of the circuit. A sketch of $V_c(t)$ is shown in Figure 10.2

10.3

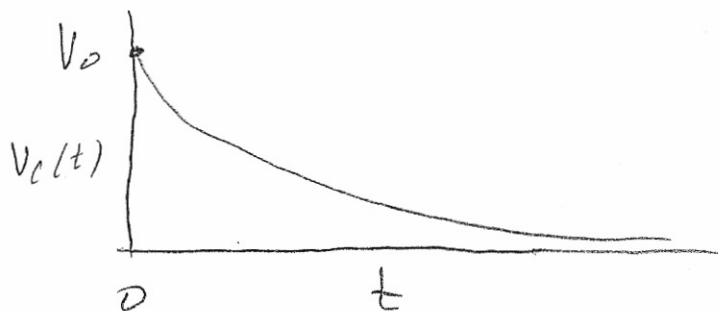


Figure 10.2: Natural Response of RC circuit.

τ is defined as the time constant

$$\tau = \text{time constant} = RC$$

If you find the equation of a line tangent to $V_c(t)$ at $t=0$, the line intersects the t axis at $t = \tau$.

At $t = \tau$

$$V_c(t) = V_0 e^{-\frac{t}{\tau}} \Big|_{t=\tau} = V_0 e^{-1} = .368 V_0 \quad (10.9)$$

So;

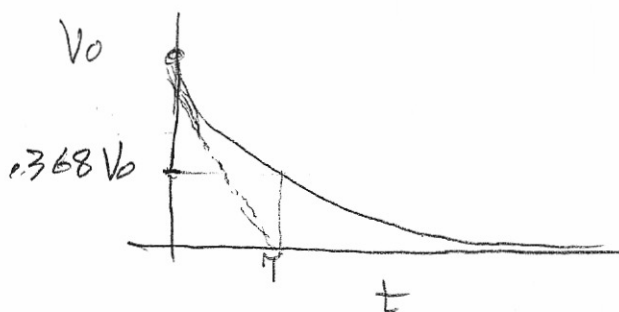


Figure 10.3: Show the time constant, graphically.

A side note;

If we take the Laplace Transform of (10.2) we have

$$\mathcal{L}\left[\frac{dV_c(t)}{dt}\right] + \mathcal{L}\left[\frac{V_c(t)}{RC}\right] = 0 \quad (10.10)$$

$$sV_c(s) - V_c(0^+) + \frac{V_c(s)}{RC} = 0$$

$$\left(s + \frac{1}{RC}\right)V_c(s) = V_0$$

$$V_c(s) = \frac{V_0}{s + \frac{1}{RC}} \quad (10.11)$$

Now

$$\mathcal{L}^{-1}[V_c(s)] = V_c(t) = \mathcal{L}^{-1}\left[\frac{V_0}{s + \frac{1}{RC}}\right]$$

$$\text{So } V_c(t) = V_0 e^{-\frac{t}{RC}} \quad (10.12)$$

If we want $i_c(t)$, we know

$$i_c(t) = C \frac{dV_c}{dt}$$

Now what about the inductor?

consider Figure 10.4

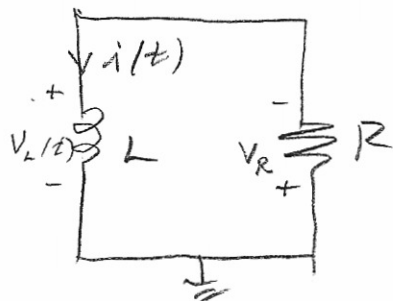


Figure 10.4: The force free RL ckt.

We assume, that by some way or the other, that $i(0^-) = I_0$. Current can't change instantaneously through the inductor

so

$$i(0^+) = i(0^-) = I_0$$

From Figure 4.4;

$$V_L + V_R = 0$$

$$L \frac{di}{dt} + Ri = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = 0 \quad (10.12)$$

The solution is

$$i(t) = I_0 e^{-\frac{Rt}{L}} \quad (10.13)$$

We define

$$\tau = \text{time constant} = \frac{L}{R}$$

$$i(t) = I_0 e^{-\frac{t}{\tau}} \quad (10.14)$$

The response is as shown in Figure 10.5

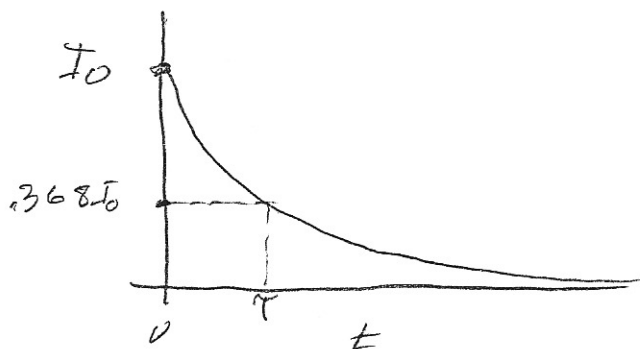


Figure 10.5: Free Response of RL circuit

Let's see how we use this at a little different level.

Example 10.1

For the circuit in Figure 10.6, find $V_0(t)$. Also find the time required for $V_0(t)$ to decay to $\frac{V_0(0^+)}{3}$.

Switch has been closed for a very long time.

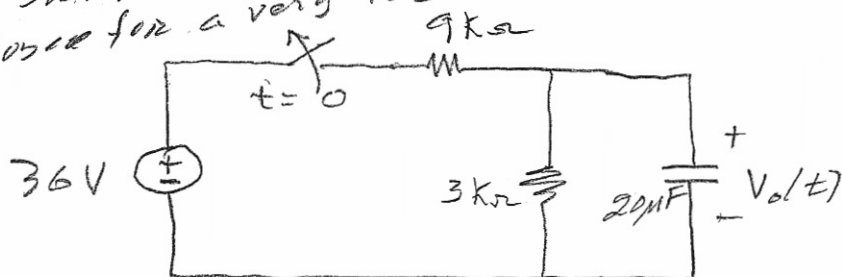


Figure 10.6: Circuit for Example 10.1

Solution:

Since the switch has been closed for a very long time, the capacitor looks like an open circuit for $t = 0^-$. The voltage across the capacitor is given by

$$V_0(0^-) = \frac{36 \times 3k}{3k + 9k} = 9V = V_0$$

We know from previous work

$$V_0(t) = V_0 e^{-\frac{t}{\tau}}$$

$$\tau = RC = 20\mu F \times 3k = 60 \times 10^{-3}$$

$$V_0(t) = 9 e^{-16.67t} \quad u(t)$$

To find the time to reach $\frac{V_0(10^+)}{3}$.

Now $V_0(10^+) = V_0 = 10$

So

$$V_c(t) = 9e^{-16.67t} = \frac{10}{3}$$

$$27e^{-16.67t} = 10$$

$$-16.67t = \ln\left(\frac{10}{27}\right) = -.9933$$

$$t = 59.6 \text{ mSec}$$

##

Example 10.2

Find $i_0(t)$ for $t > 0$ for the circuit of Figure 10.7


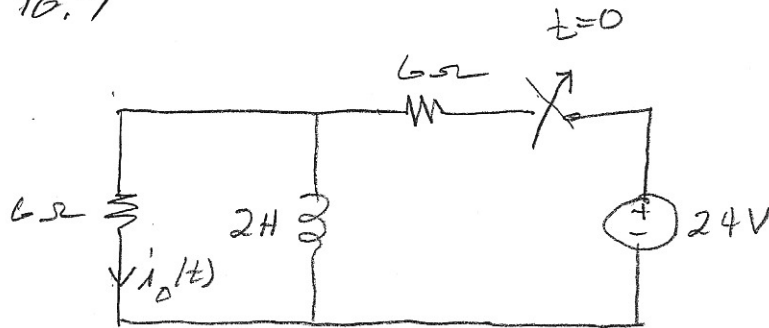



Figure 10.7: Circuit for example 10.2

For $t < 0$, the circuit appears as

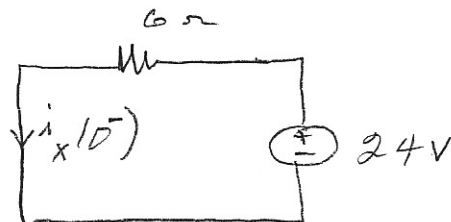

$$i_x(0^-) = \frac{24}{6} = 4 \text{ A}$$

For $t \geq 0$, the circuit is

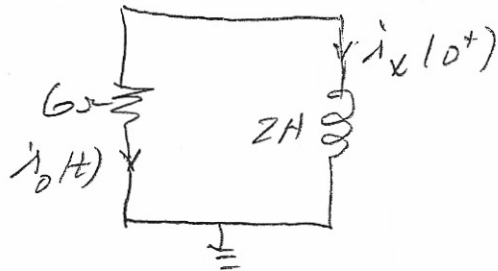

$$i_x(0^+) = i_x(0^-) = 4 \text{ A}$$

We know that the solution for $i_0(t)$ is

$$i_0(t) = I_0 e^{-\frac{Rt}{L}} = I_0 e^{-\frac{t}{\tau}}$$

$$I_0 = -i_x(0^+) = -4 \text{ A}$$

\therefore

$$i_0(t) = -4 e^{-3t} u(t)$$

##

Example 10.3

For the circuit of Figure 10.8, the switch has been closed for a very long time. It is opened at $t=0$. Find $i_2(t)$, $0 \leq t$.


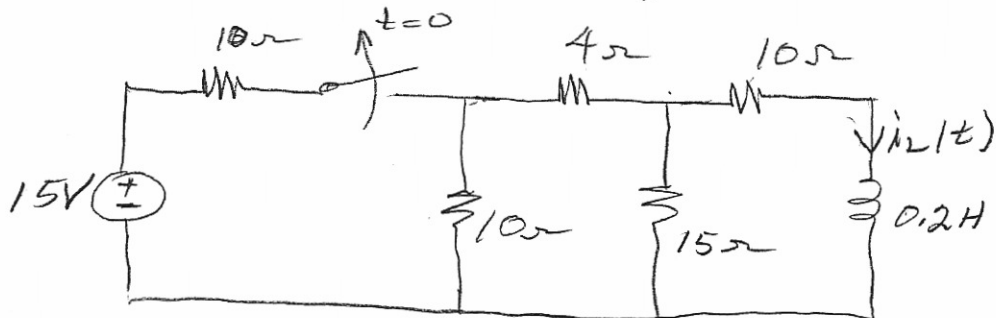



Figure 10.8; Circuit for Example 10.3

At $t = 0^-$ the circuit appears as 10.9

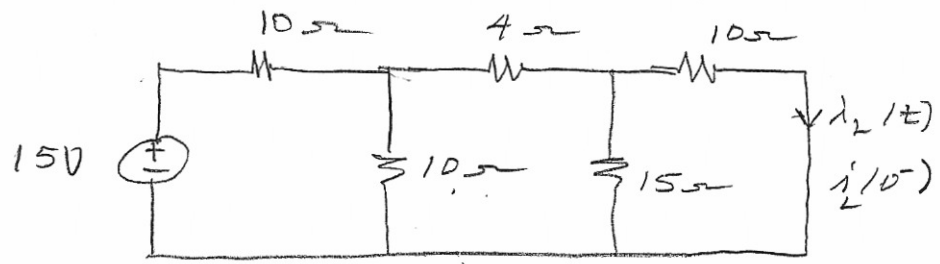


We can find that $i_L(0^-) = 0.3 \text{ A} = i_L(0^+)$.

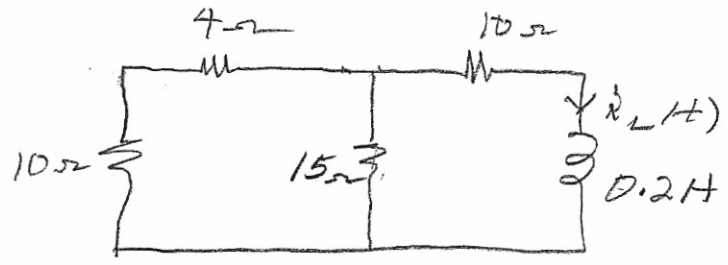
Now for $t = 0^+$ the circuit is as follows.



OR
15 || 14

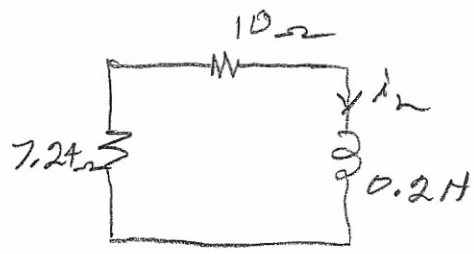

OR

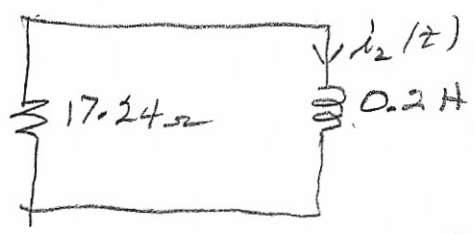

We know $i_L(t) = I_0 e^{-\frac{Rt}{L}}$ $I_0 = i_L(0^+)$

40

$$i_L(t) = 0.3 e^{-86.2t}$$

The Forced RC Circuit:

We consider the circuit shown in Figure 10.9.

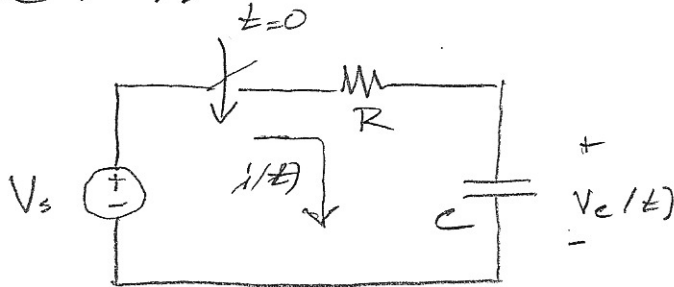


Figure 10.9: The forced RC circuit.

Given:

$$V_c(0^-) = V_0$$

then we know $V_c(0^+) = V_c(0^-) = V_0$

and

$$i(t) = C \frac{dV_c}{dt}$$

We can write KVL for Fig 10.9 as, $t > 0$

$$-V_s + R i(t) + V_c(t) = 0$$

OR

$$RC \frac{dV_c}{dt} + V_c(t) = V_s$$

OR

$$\frac{dV_c}{dt} + \frac{V_c(t)}{RC} = \frac{V_s}{RC} \quad (10.15)$$

We assume

$$V_c(t) = V_N(t) + V_{ss}(t)$$

where $V_N(t)$ = natural response

$V_{ss}(t)$ = steady state response

The natural response comes from

$$\frac{dV_N}{dt} + \frac{V_N(t)}{RC} = 0 \quad (10.16)$$

which has a solution of

$$V_N(t) = A e^{-\frac{t}{RC}} \quad (10.17)$$

The forced response is

$$V_{ss}(t) = K \quad \left(\text{A constant } K \text{ since the right side of 10.15 is a constant} \right)$$

OR

$$\frac{dV_{ss}}{dt} + \frac{V_{ss}}{RC} = \frac{V_s}{RC} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} V_F = K$$

which gives

$$\frac{K}{RC} = \frac{V_s}{RC}$$

$$K = V_s$$

Thus, combining $V_N + V_{ss}$

$$V_C(t) = A e^{-\frac{t}{RC}} + V_s \quad (10.18)$$

We need to evaluate A ;

From the initial condition,

$$V_C(0^+) = V_0$$

From (10.18) we have

$$V_C(0^+) = V_0 = \left[A e^{-\frac{t}{RC}} + V_s \right] \Big|_{t=0^+}$$

$$V_C(0^+) = V_0 = A + V_s$$

$$A = V_0 - V_s = V_c(0^+) - V_s$$

We note from (10.18) that

$$V_c(\infty) = V_s$$

$$A = V_c(0) - V_c(\infty)$$

So we can write (10.18) as

$$\boxed{V_c(t) = V_c(\infty) + (V_c(0^+) - V_c(\infty))e^{-\frac{t}{\tau}}} \quad (10.19)$$

We can also write this as

$$V_c(t) = \underbrace{V_0 e^{-\frac{t}{\tau}}}_{V_{\text{NATURAL}}} + \underbrace{(V_s - V_s e^{-\frac{t}{\tau}})}_{V_{\text{FORCED}}} \quad (10.20)$$

We can re-arrange as

$$V_c(t) = \underbrace{V_s}_{V_{\text{SS}}} + \underbrace{(V_0 - V_s)e^{-\frac{t}{\tau}}}_{V_{\text{TRANSIENT}}} \quad (10.21)$$

We can save ourselves a lot of work if we use the form of (10.19)

We only need to $V_c(\infty)$, $V_c(0^+)$, and τ and we write the solution.

This format works for RC and RL circuits (first order).

EXAMPLE 10.4

You are given the following circuit (circuit of 5.37 in the text).

- (a) Use the step-by-step method (10.19) to find $v_c(t)$,
 (b) Use nodal analysis, find the DE, solve for $v_c(t)$.

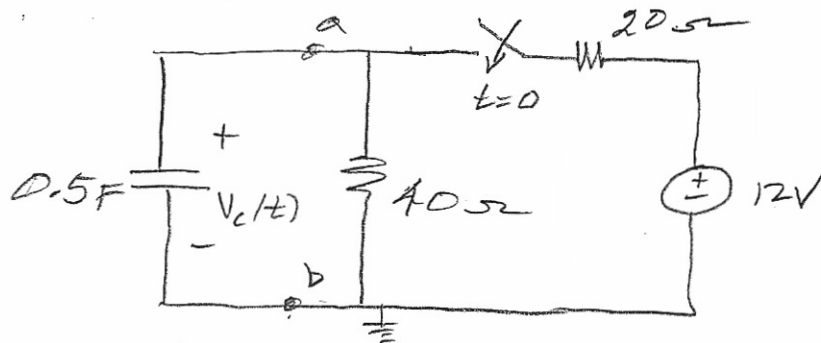


FIGURE 10.10:

$$(a) \quad v_c(\infty) = v_c(\text{SS}) = \frac{12 \times 40}{20 + 40} = 8 \text{ V}$$

$$v_c(0^+) = v_c(0^-) = 0$$

To find R_{eq} look into a-b as if finding R_{TH}


$$R_{\text{eq}} = 20 \parallel 40 = \frac{20 \times 40}{20 + 40} = 13.33 \Omega$$

$$\therefore v_c(t) = v_c(\infty) + [v_c(0^+) - v_c(\infty)] e^{-\frac{t}{R_{\text{eq}}C}}$$

$$v_c(t) = (8 - 8e^{-0.15t}) \text{ u(t)}$$

10.14

1b) By nodal analysis

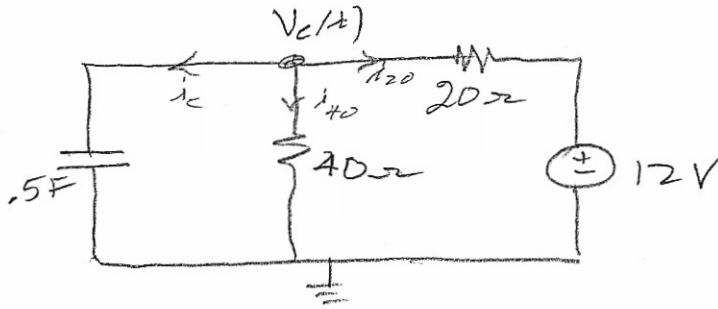

$$C \frac{dV_c}{dt} + \frac{V_c}{40} + \frac{V_c - 12}{20} = 0 \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} C = 0.5$$

$$0.5 \frac{dV_c}{dt} + 0.025 V_c + 0.05 V_c = 0.6$$

$$\frac{dV_c}{dt} + 0.15 V_c = 1.2$$

$$V_N = A e^{-0.15t}$$

$$V_{ss} = \frac{1.2}{0.15} = 8$$


$$V_c(t) = A e^{-0.15t} + 8$$

$$V_c(0^+) = 0$$

$$\therefore V_c(0^+) = [A e^{-0.15t} + 8] \Big|_{t=0^+}$$

$$A = -8$$
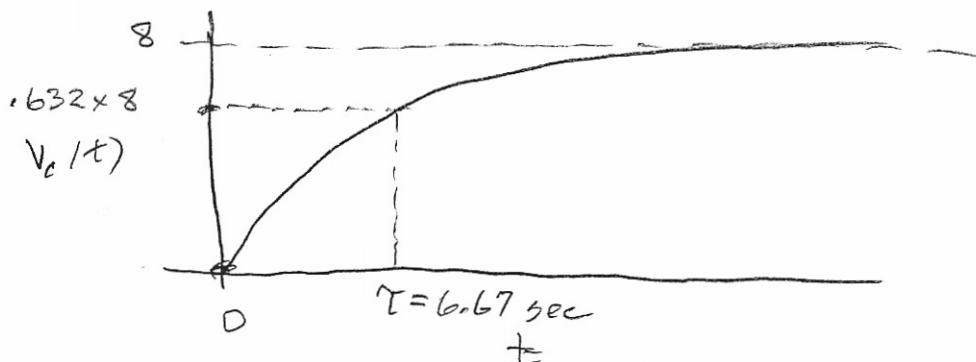
$$\therefore V_c(t) = (8 - 8 e^{-0.15t}) \quad u(t)$$



The RL Forced Circuit:

We are given the following circuit of Figure 10.11.

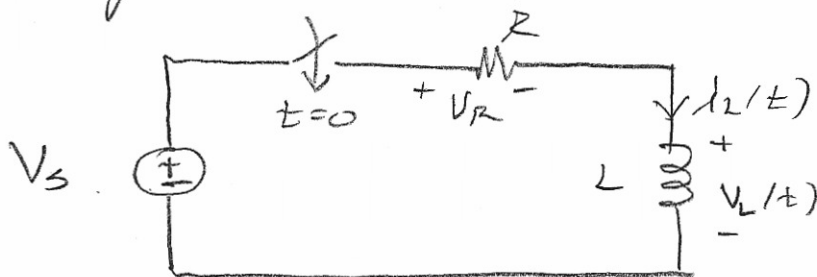


Figure 10.11: The forced RL circuit.

Knowns:

$$i_L(0^-) = I_0$$

$$\therefore i_L(0^+) = I_0$$

$$V_L(t) = L \frac{di_L}{dt}$$

Solution:

K.V.L

$$V_R(t) + V_L(t) = V_s$$

$$L \frac{di_L}{dt} + R i_L(t) = V_s$$

$$\frac{di_L}{dt} + \frac{R}{L} i_L(t) = \frac{V_s}{L}$$

$$\frac{di_L}{dt} + \frac{i_L(t)}{\tau} = \frac{V_s}{L} \quad (10.23)$$

$$\tau = \text{time constant} = \frac{L}{R}$$

Solve using the same reasoning as applied for the forced RC circuit.

$$i_L(t) = i_N(t) + i_{ss}(t) \quad (10.23)$$

$$i_N(t) = A e^{-\frac{t}{\tau}}$$

$$i_{ss} = K \quad (\text{substitute in (10.24)})$$

$$\therefore \frac{K}{\tau} = \frac{V_s}{L}$$

$$K = \frac{\tau V_s}{L} = \frac{L}{R} \frac{V_s}{L} = \frac{V_s}{R}$$

so

$$i_L(t) = A e^{-\frac{t}{\tau}} + \frac{V_s}{R}$$

$$\text{At } t = 0^+, i_L(0^+) = I_0 = i_L(0^+)$$

$$i_L(0^+) = \left[A e^{-\frac{t}{\tau}} + \frac{V_s}{R} \right] \Big|_{t=0^+}$$

$$i_L(0^+) = A + \frac{V_s}{R}$$

$$A = i_L(0^+) - \frac{V_s}{R}$$

$$\text{Now } \frac{V_s}{R} = i_L(ss) = i_L(\infty)$$

$$A = i_L(0^+) - i_L(\infty)$$

$$i_L(t) = i_L(\infty) + (i_L(0^+) - i_L(\infty)) e^{-\frac{t}{\tau}}$$

(10.25)

We see this is the same form as (10.19). We can therefore find

$i_L(\infty) = i_L(ss)$, $i_L(0^+)$, τ and write down the solution.

Example 10.5

10.17

You are given the following circuit. Use step-by-step to find $V_o(t)$. (From Tzwin 7.42)

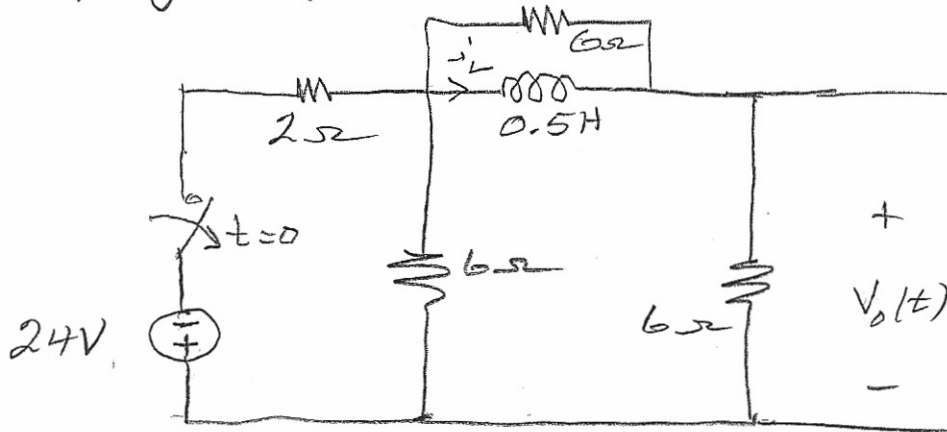


Figure 10.12: Circuit for Example 10.5.

The expression to use is

$$V_o(t) = V_o(\infty) + [V_o(0^+) - V_o(\infty)]e^{-\frac{t}{\tau}}$$

We must determine $V_o(\infty)$, $V_o(0)$, τ

Solution: for $t < 0$

Looking at the circuit, $V_o(\infty) = 0$

For $t < 0$ the circuit is as follows.

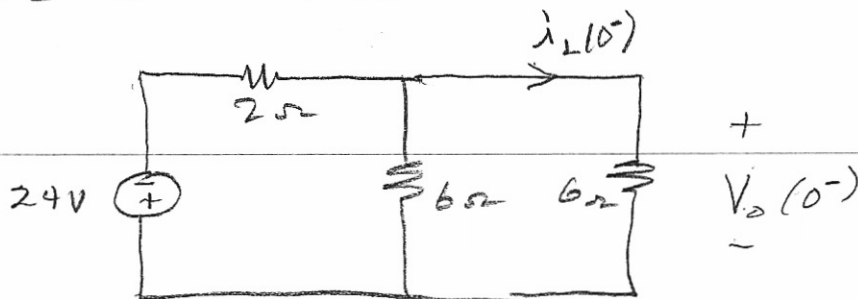


Figure 10.13

We see that

$$V_0(0^-) = \frac{-24 \times 3}{3+2} = -14.4 \text{ V}$$



The problem is, we don't know if this is $V_0(0^+)$. The only thing we know is that $i_L(0^+) = i_L(0^-)$

We see from Figure 10.13 that


$$i_L(0^-) = \frac{V_0(0^-)}{6} = 2.4 \text{ A}$$

$$\therefore i_L(0^+) = 2.4 \text{ A}$$

Now for $t = 0^+$

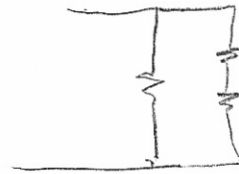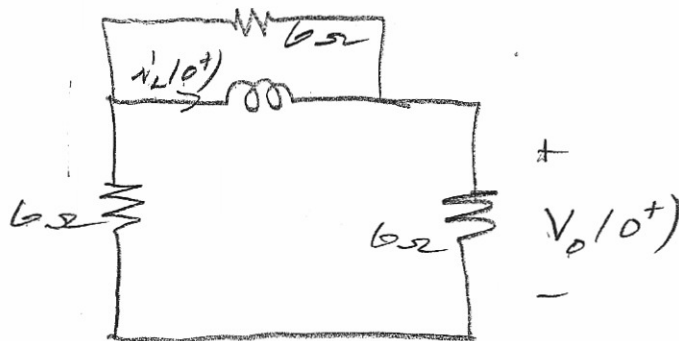

OR

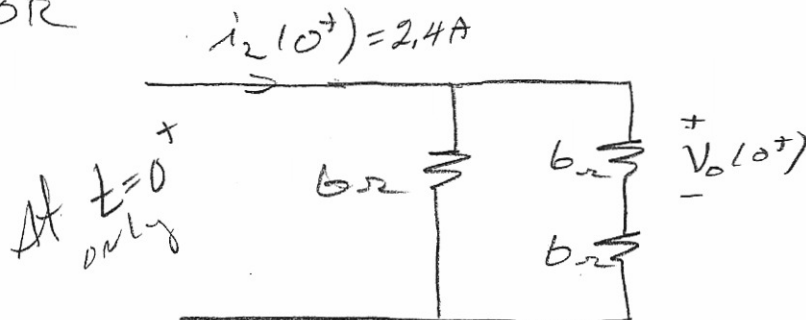

$$V_0(0^+) = \left(\frac{2.4 \times 6}{1.8} \right) \times 6 = 4.8 \text{ V}$$

10.19

It is easy to see that

$$R_{eq} = 6 \parallel 12 = \frac{6 \times 12}{6 + 12}$$

$$R_{eq} = 4 \Omega$$

$$V_o(t) = V_o(0^+) e^{-\frac{R_{eq} t}{L}}$$

$$V_o(t) = 4.8 e^{-8t}$$

pretty tough problem.