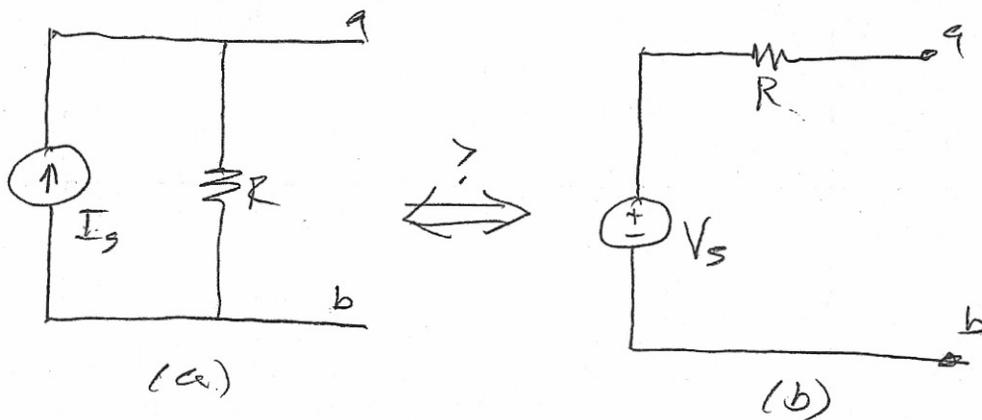


Lecture 6
why

ECE 301 Source Transformation

Source Transformations

Suppose we are given a current source shunted by resistance R and we want to determine if we can transform this to a voltage source in series with a resistor. Also, we want to know if the transformation is reversible, that is,



For the circuits to be equivalent, for each case

(a) the open-circuit voltage must be the same

(b) the short circuit current must be the same.

For the circuit in (a) the open circuit voltage

$$V_{oc1} = I_s R \quad (1)$$

The short circuit current is

$$I_{sc1} = I_s \quad (2)$$

For the circuit on the right the open circuit voltage is

$$V_{oc2} = V_s \quad (3)$$

The short circuit current is

$$I_{sc2} = \frac{V_s}{R} \quad (4)$$

So (1) and (3) must agree.

Thus

$$I_s R = V_s$$

and

(2) and (4) must agree

$$I_{sc1} = I_{sc2}$$


$$I_s = \frac{V_s}{R}$$

How do we use this,



Example (very simple case)

Give the following circuit.
Transform the current source and resistor to a voltage source in series with a resistor

Then find I_x as indicated.

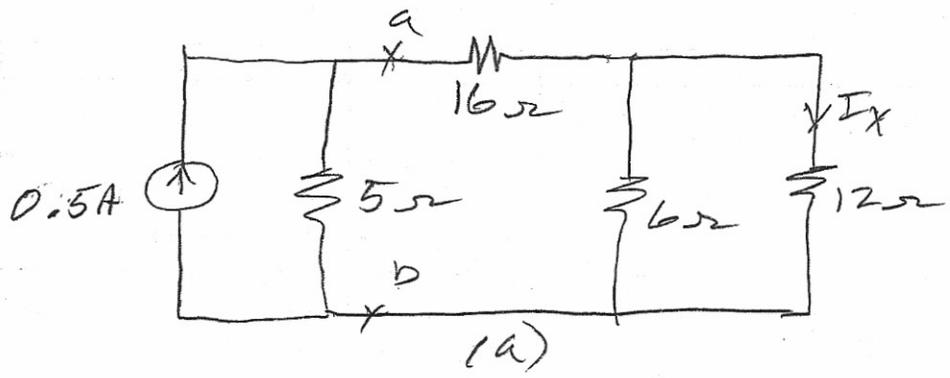

$$V_s = 0.5 \times 5 = 2.5V$$

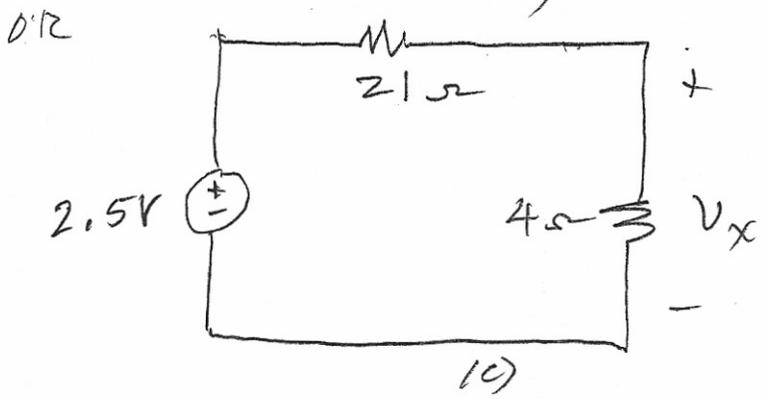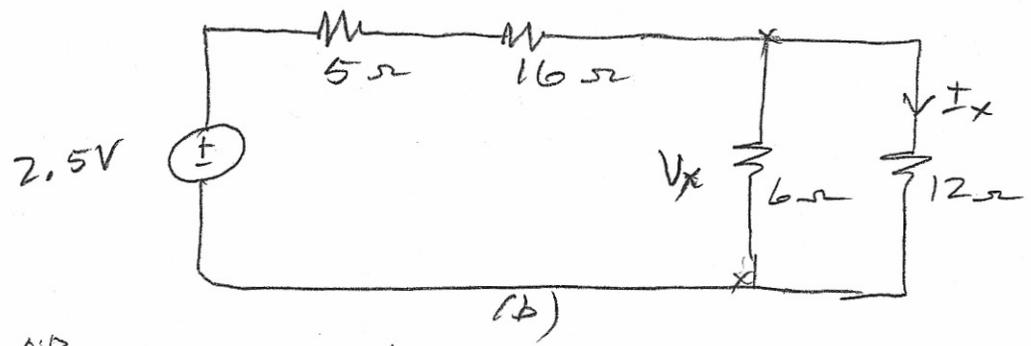

By voltage division,


$$V_x = \frac{2.5 \times 4}{21 + 4} = 0.4 \text{ V}$$

Then

$$I_x = \frac{V_x}{12} = \frac{0.4}{12}$$

$$I_x = 0.0333 \text{ A}$$

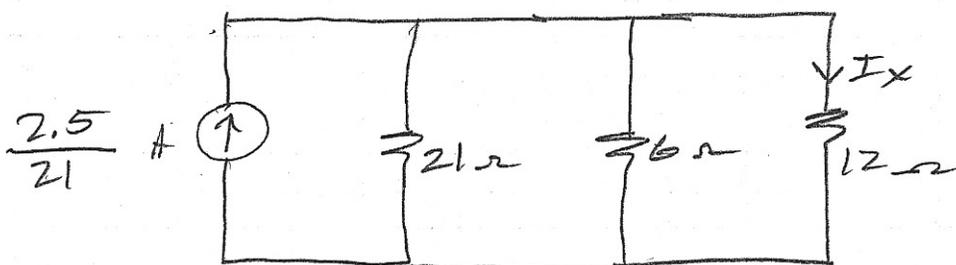You can also transform the circuit in (b) to the following:



$$\frac{1}{R_{\text{eq}}} = \frac{1}{21} + \frac{1}{6} + \frac{1}{12} = 0.0476 + 0.1667 + 0.0833$$

$$\frac{1}{R_{\text{eq}}} = 0.2948 \text{ S}$$





$$I_x = \left(\frac{2.5}{21}\right) \times \frac{R_{\text{eq}}}{12} = \left(\frac{2.5}{21}\right) \times \frac{1}{12 \times 0.2948}$$

$$I_x = 0.033 \text{ A} \quad (\text{rounding})$$

(Not the easiest way)

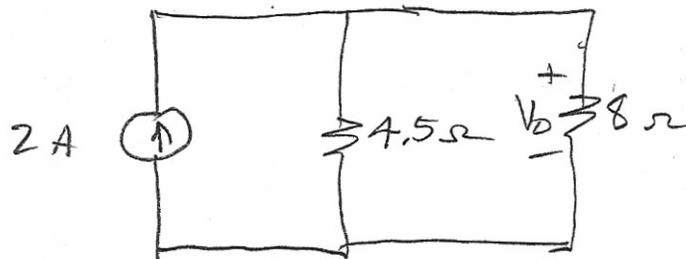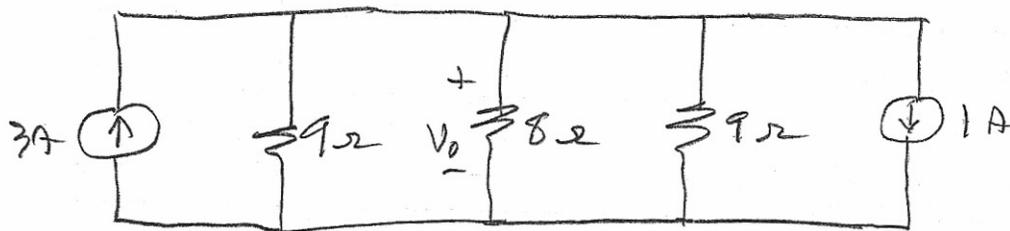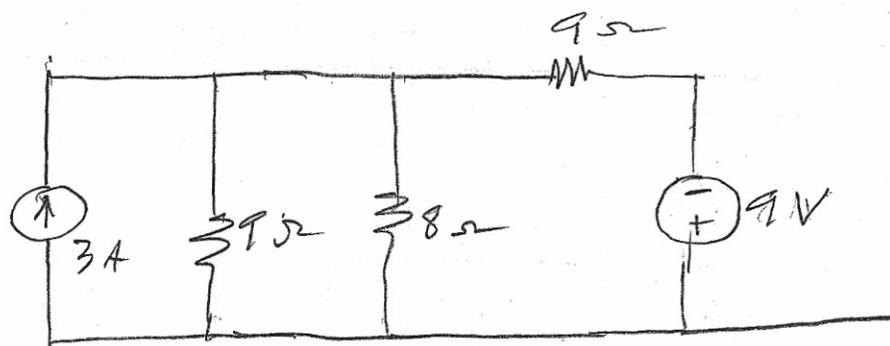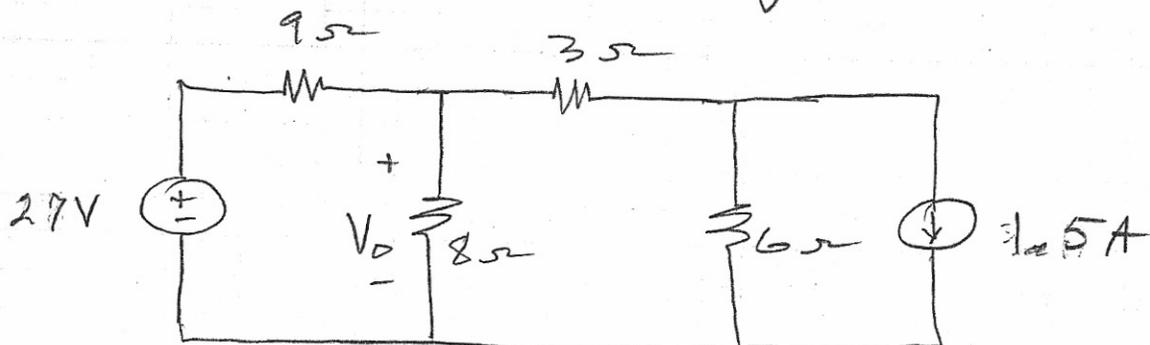Example 2


Use source transformation to find V_0 in the following circuit.



$$V_0 = \left(\frac{2 \times 4.5}{4.5 + 8} \right) 8 = 5.76 \text{ V}$$

Verify by nodal analysis

Example 2 by Nodal Analysis

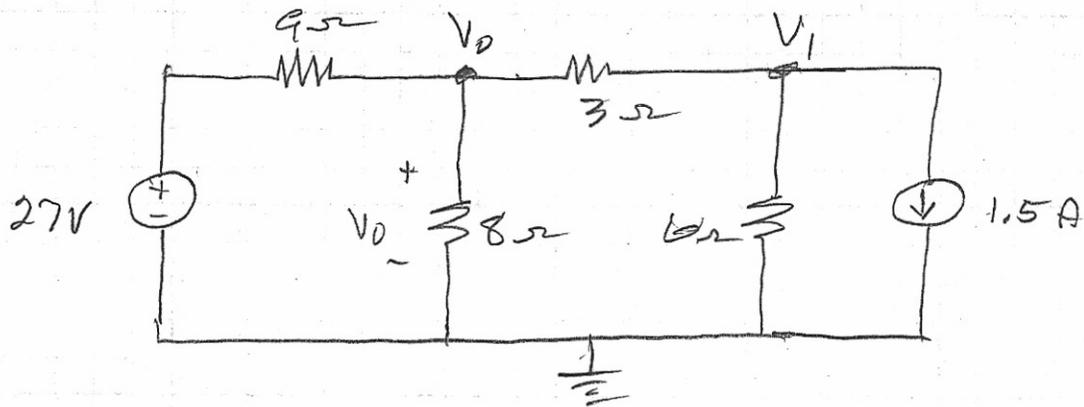

At V_0

$$\frac{V_0 - 27}{9} + \frac{V_0}{8} + \frac{V_0 - V_1}{3} = 0$$

$$0.111V_0 - 3 + 0.125V_0 + 0.333V_0 - 0.333V_1 = 0$$

$$\boxed{0.569V_0 - 0.333V_1 = 3} \quad (1)$$

At V_1

$$\frac{V_1 - V_0}{3} + \frac{V_1}{6} = -1.5$$

$$2V_1 - 2V_0 + V_1 = -9$$

$$\boxed{-2V_0 + 3V_1 = -9} \quad (2)$$

Solving (1) and (2)

$$V_0 = 5.76 \text{ V}, \quad V_1 = 0.844 \text{ V}$$



OK