

Thévenin's Theorem  
Norton's TheoremThevenin's Theorem

Consider the following

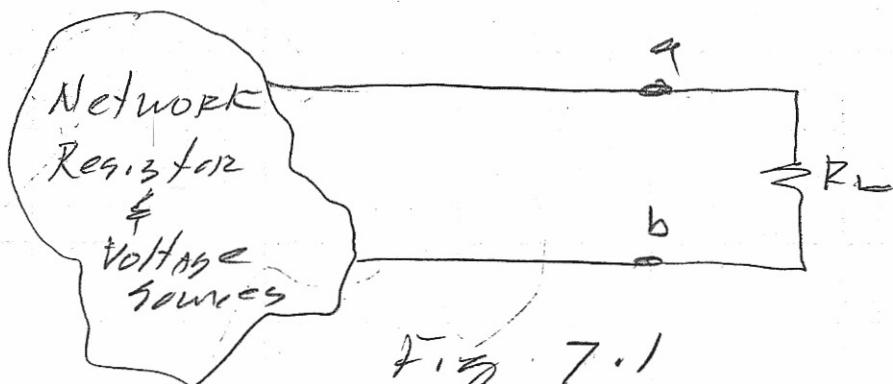


Fig. 7.1

The network inside the "glob" can be very complex - structured in this case by 168 resistors and 27 independent voltage sources.

We would like to replace the network by one that has 1 resistor and 1 source that will deliver the same current and same voltage to  $R_L$ .

The situation is that shown in Figure 7.1

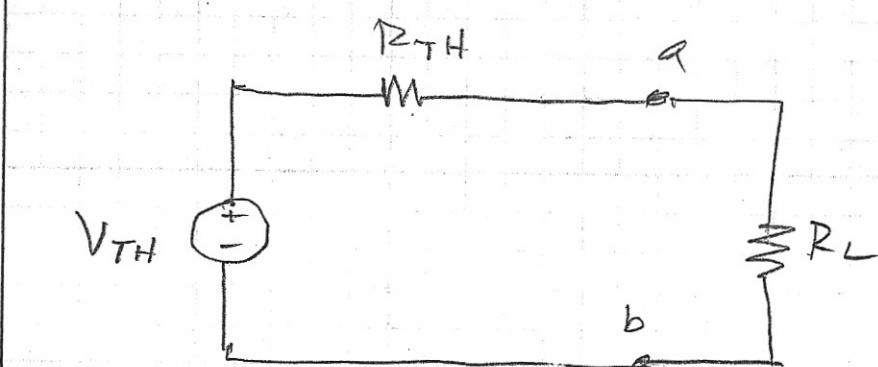


Fig. 7.2

We call  $V_{TH} \rightarrow V_{\text{THEVENIN}}$  and

$R_{TH} \rightarrow R_{\text{THEVENIN}}$

If we remove  $R_L$  from the circuit in Fig 7.1 and de-activate all sources (this means replace all voltage sources with a short) if we then placed an ohmmeter across terminals a-b we would read  $R_{TH}$ .

With  $R_L$  removed, if we place a voltmeter across ab we read the open circuit voltage,

The open circuit voltage is

$V_{TH}$ . Let's see how this works.

Example 7.1

Find the Thvenin equivalent circuit to the left of terminals a-b in the circuit of Figure 7.3

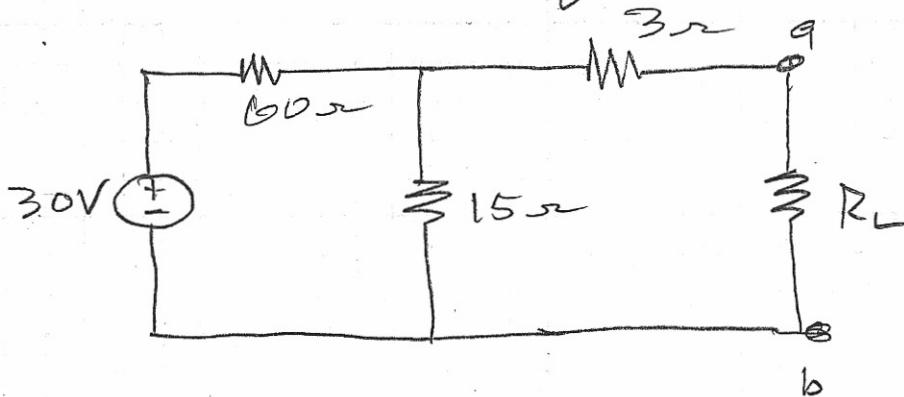


Figure 7.3

Solution

To find  $R_{TH}$ . Deactivate the 30V source. Remove  $R_L$  and determine  $R_{eq}$  below in Figure 7.4



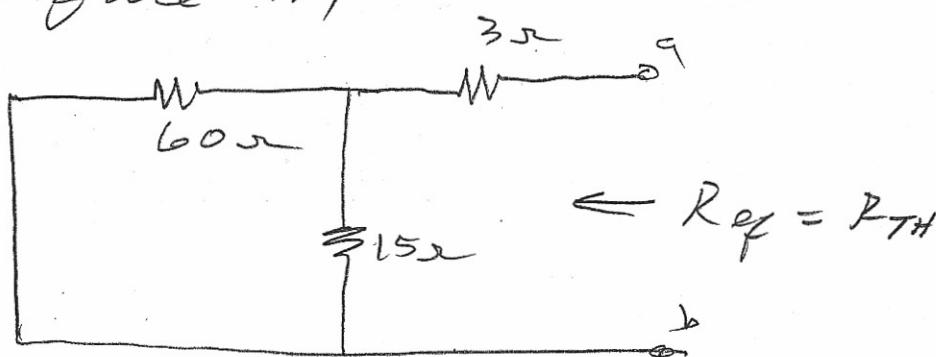


Figure 7.4

becomes

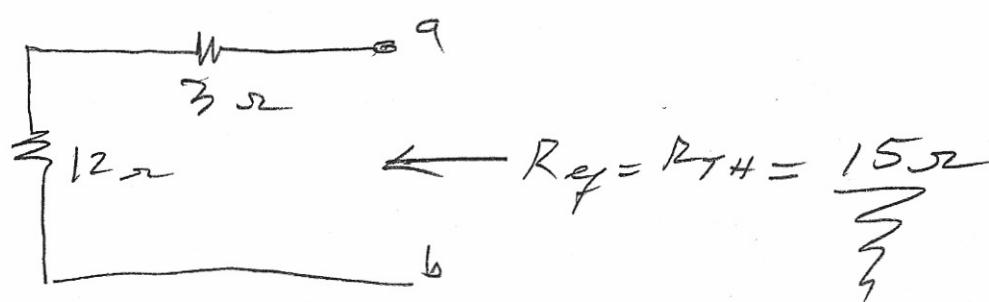

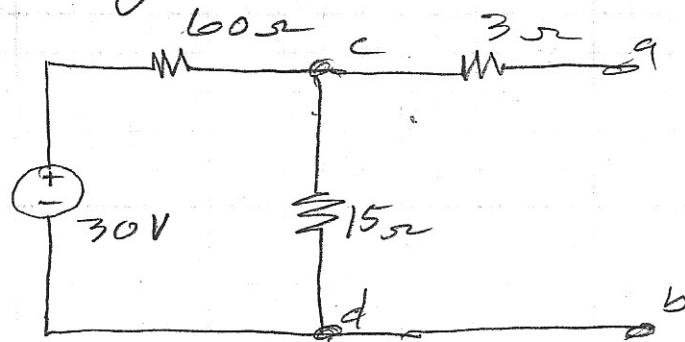To find  $V_{OC} = V_{TH}$  we consider the following circuit.



Since terminals a-b are opened, no current flows through the  $3\Omega$  resistor so there is no voltage drop across this resistor. This means that  $V_{ab} = V_{TH} = V_{cd}$ . We can find  $V_{cd}$  by using the voltage division rule.

$$V_{cd} = V_{TH} = \frac{30 \times 15}{75} = 6V$$

The Thévenin circuit, connected to the load becomes

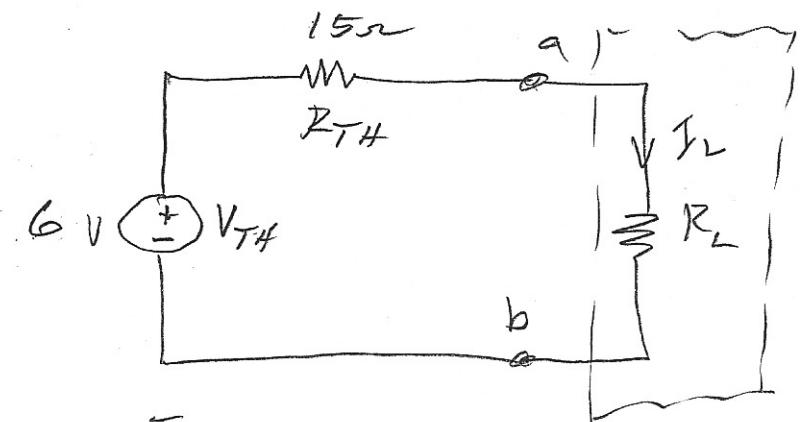


Figure 7.5

We can now find  $I_2$  and  $V_{ab}$  for any  $R_L$ . Furthermore,  $R_L$  could be replaced by another circuit as below.

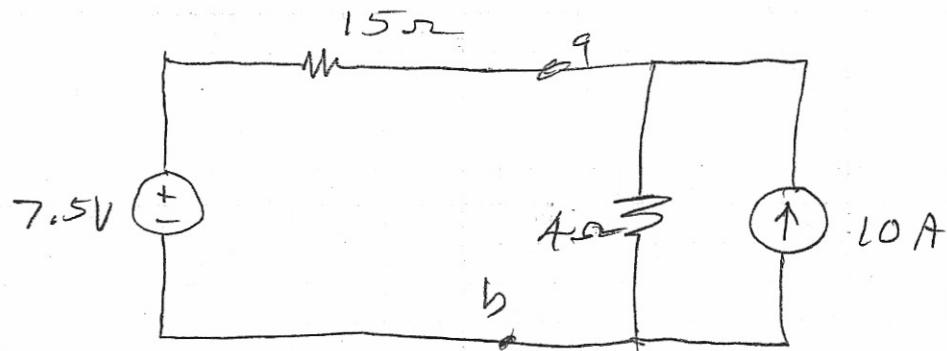


Figure 7.6

Suppose we want to find  $V_{ab}$ .

We can use source transformation to change the circuit as follows


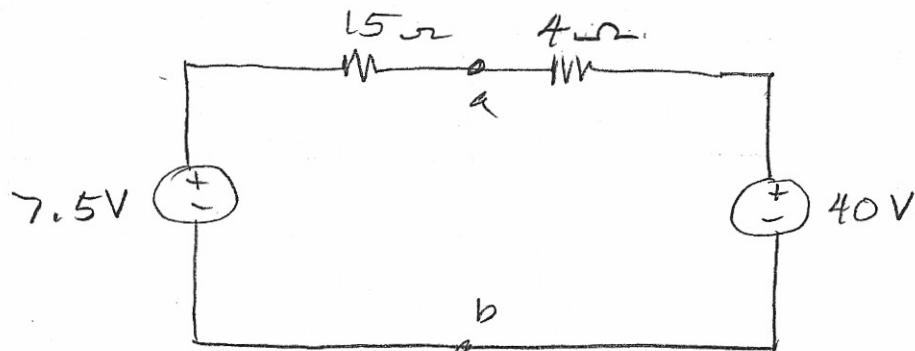


Figure 7.7

Solving this circuit we find,

$$V_{ab} = 33.16 \text{ V}$$

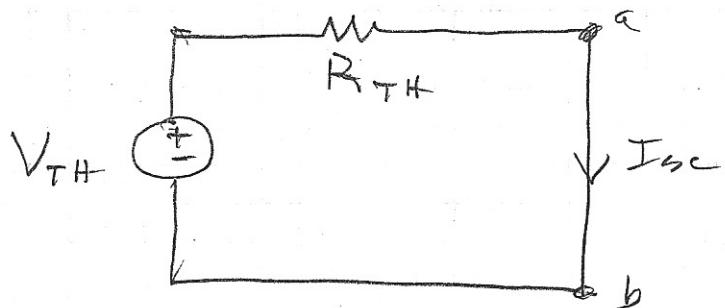(6)  
Reconsider the Thevenin equivalent circuit, with a short across the load




We designate the current in the short as  $I_{SC}$ . We see that

$$I_{SC} = \frac{V_{TH}}{R_{TH}}$$

Now recall that

$$V_{OC} = V_{TH}$$

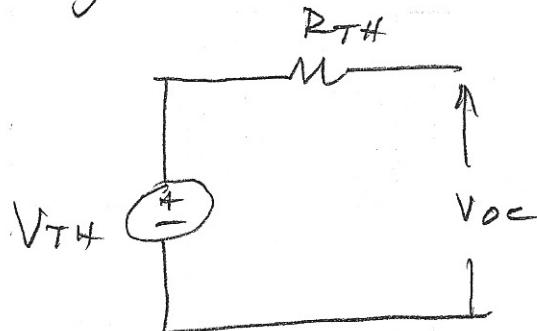which you see from the following circuit.




Therefore,

$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{V_{TH}}{V_{TH}/R_{TH}} = R_{TH}$$



$$\therefore R_{TH} = \frac{V_{OC}}{I_{SC}}$$

This is an alternate way of finding  $R_{TH}$ .

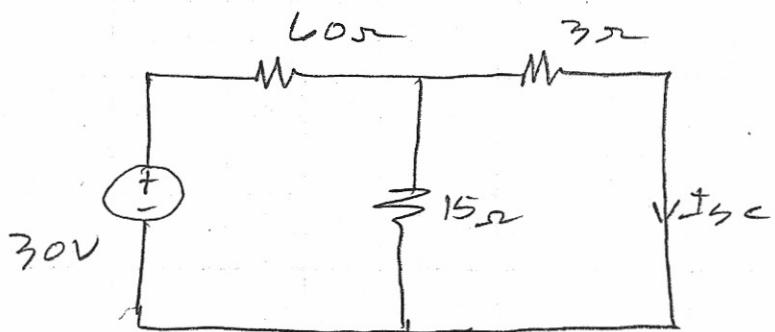Reconsider Example 7.1 and find  $R_{TH}$  by  $\frac{V_{oc}}{I_{sc}}$ . Let us actually find  $I_{sc}$ .



with source transformation,

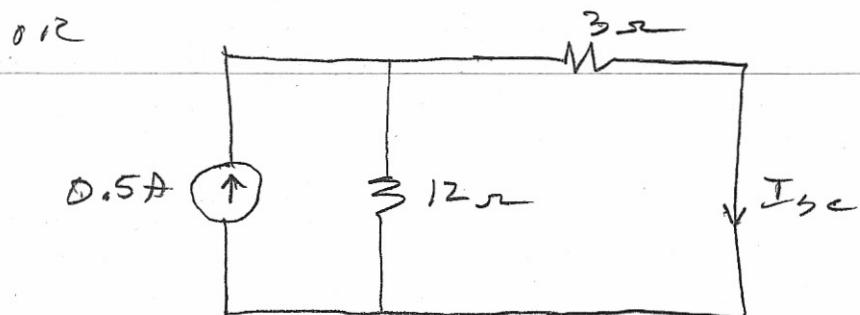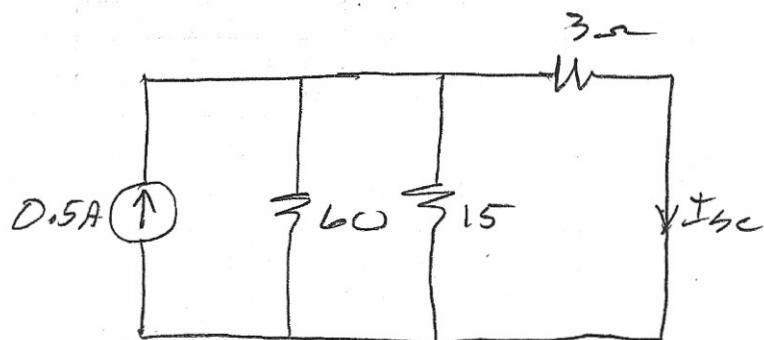

Using current division,

$$I_{sc} = \frac{0.5 \times 12}{12 + 3} = 0.4 \text{ A}$$

We already know that  $V_{OC} = V_{TH} = 16V$

$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{16}{0.4}$$

$$R_{TH} = 15\Omega$$

This agrees with previous work.

### Norton's Theorem

Consider the following:

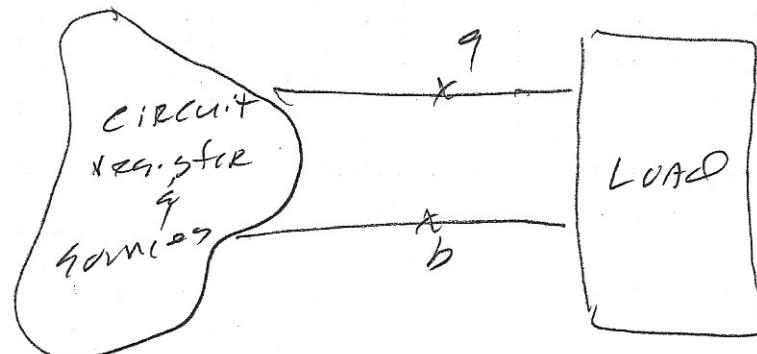


Figure 7.8

Norton's theorem states that for any linear circuit to the left of a-b we can replace by a current source in parallel with a resistor,


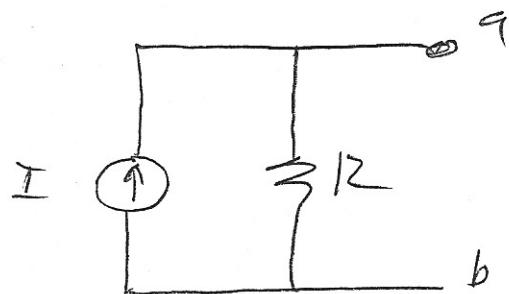


Figure 7.9

The value of  $\underline{R}$  is the resistance seen looking into a-b with all independent sources disabled. We disable current sources by removing them. Let disable voltage sources by replacing them with a short.

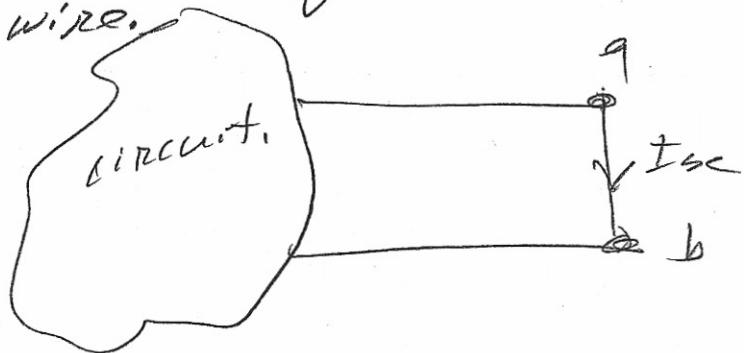The  $I$  in Figure 7.9 is the short circuit current, that is, the current that flows through a wire the load in Figure 7.8 is replaced by this wire.



If you know the Thevenin it you can easily determine the Norton because

$$I_N = \frac{V_{TH}}{R_{TH}}$$

However, we want to also be able to find  $I_{SC}$  by direct calculation from the circuit if for no other

reason it makes us better at circuit analysis. 10

We now consider an example of finding a Norton equivalent circuit.

### Example 7.2

Find the Norton equivalent circuit for the following, to the left of terminals a-b,


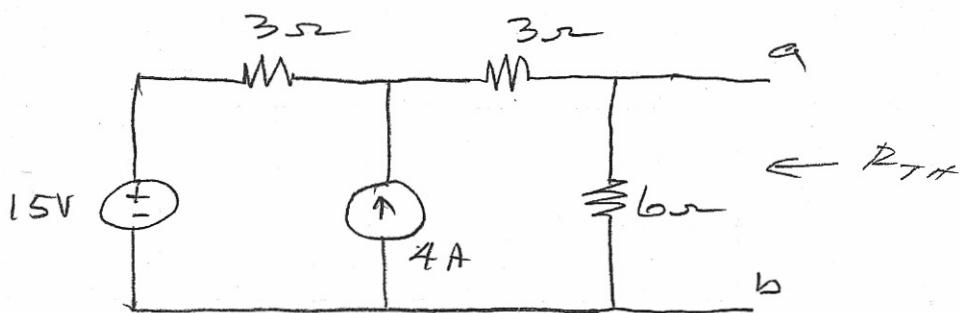


Figure 7.10

To find  $R_{TH}$

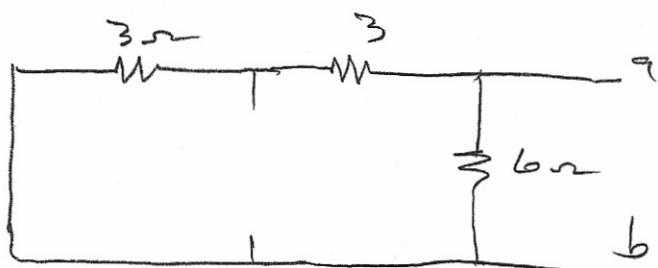

By inspection, practically,

$$R_{TH} = 3\Omega$$

To find the  $I_{sc}$  we analyze the following circuit.

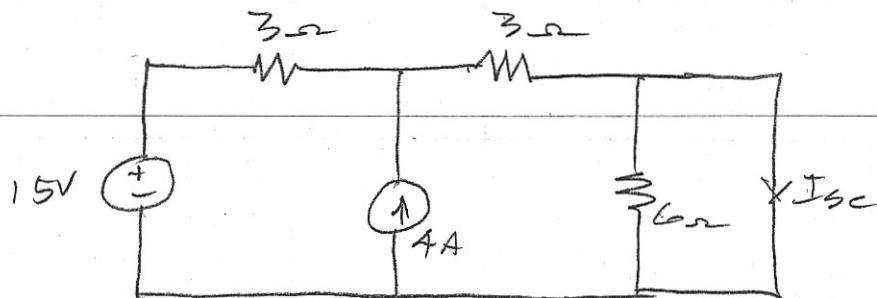


Figure 7.11

Actually, the  $6\Omega$  resistor is shorted so we can change the circuit to that of Figure 7.12

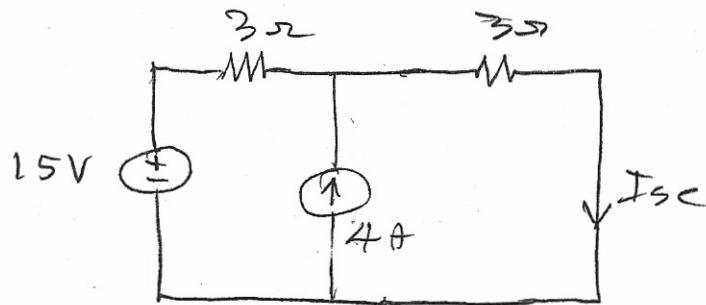


Figure 7.12

We can use nodal analysis, mesh analysis, source transformation to find  $I_{sc}$ . Source transformation is easy to apply here. Then we have

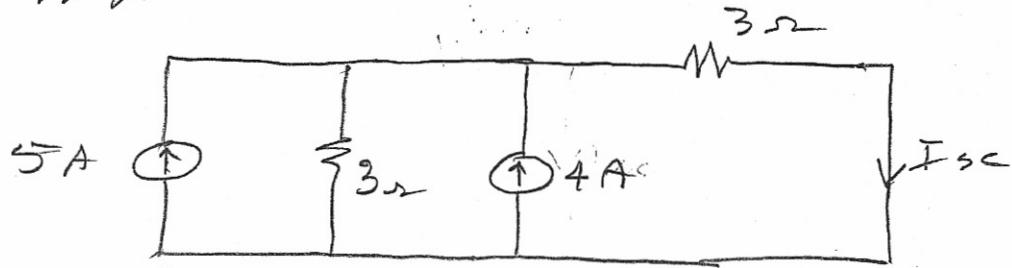


Figure 7.13

Figure 7.13 becomes

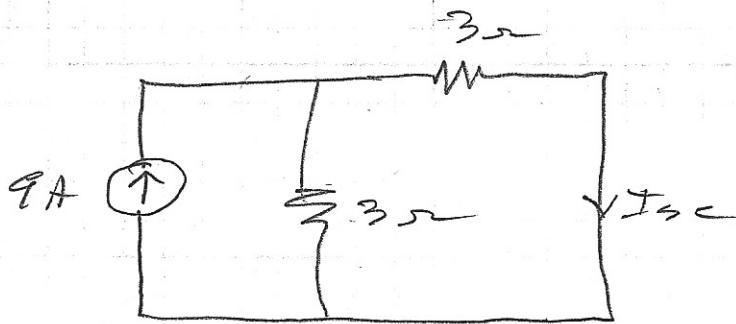


Figure 7.14

$$I_{sc} = \frac{9 \times 3}{3+3} = 4.5A$$

so the Norton circuit is

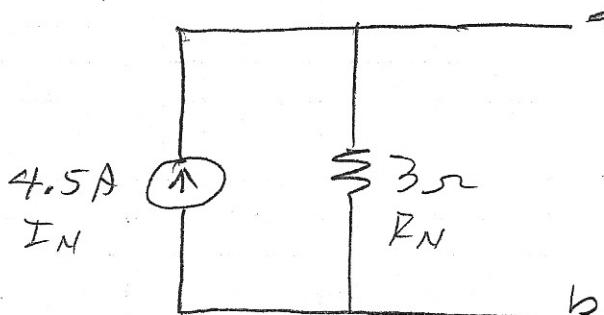


Figure 7.15

Now we can go back to the circuit of Figure 7.10 and find  $V_{TH}$  from the open-circuit voltage, i.e.,  $V_{ab}$ . The answer should be  $I_{sc} \times R_{TH}$  from above, or

$$V_{TH} = 4.5 \times 3 = 13.5V$$

You might want to verify this.

Let's look at another example

### Example 7.3

Find the Thévenin equivalent circuit for the following and draw the Thévenin circuit.

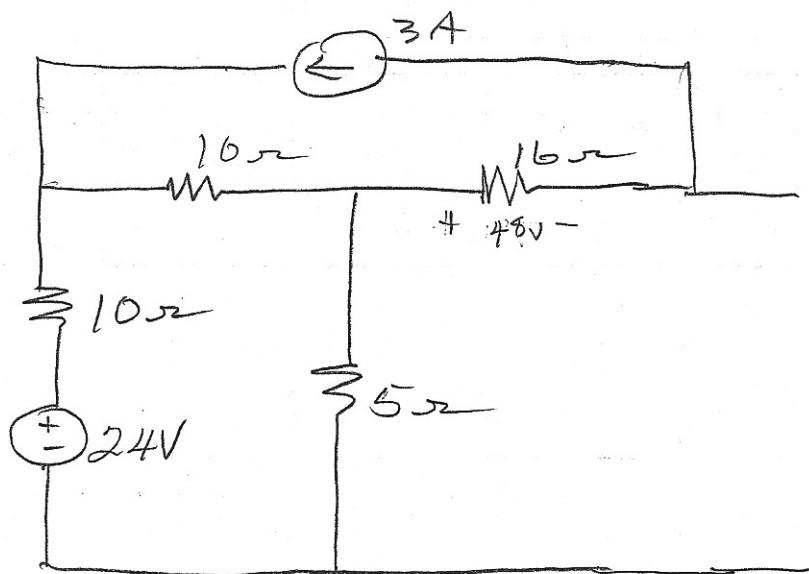


Figure 7.16

We use the following circuit to find  $R_{TH}$ .

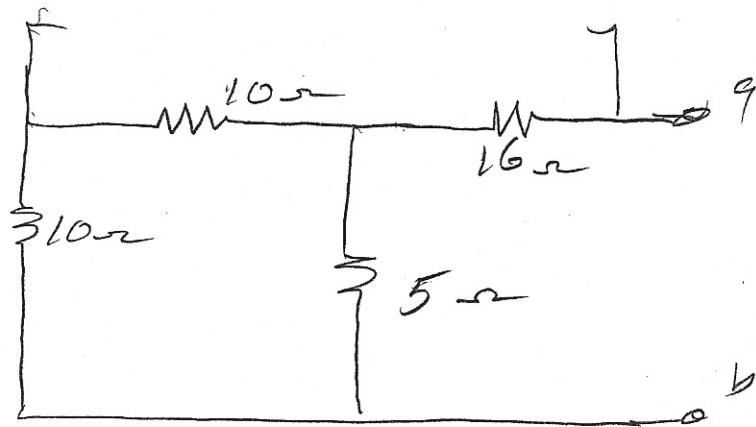


Figure 7.17


so we have

$$R_{TH} = 16 + 5/20$$

$$R_{TH} = 16 + 4$$

$$R_{TH} = 20 \Omega$$

We can use mesh to find  $V_{TH}$

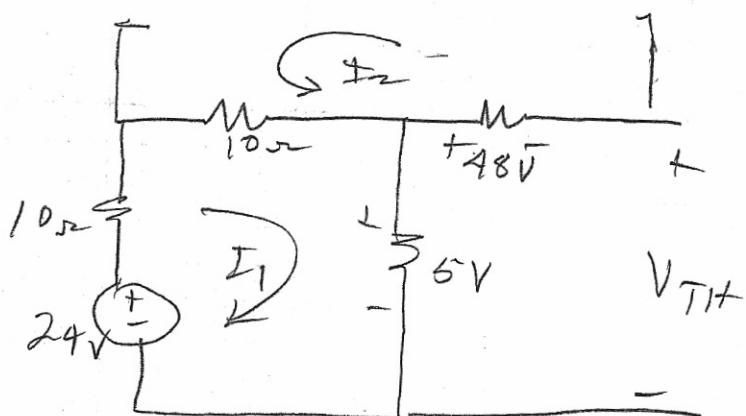

$$-24 + 10I_1 + 10(I_1 + I_2) + 5I_2 = 0$$

$$I_2 = 3A$$

$$-24 + 10I_1 + 10I_1 + 30 + 5I_2 = 0$$

$$25I_1 = -6$$

$$I_1 = I_2 = \frac{-6}{25}$$

$$V_{TH} = -\frac{6}{25} \times 5 - 48 = -49.2V$$

The answer is  $-49.2V$

