

ECE 301
Spring Semester, 2007
Test #1

wlg Test A

Name _____
Print (last, first)

Work the exam on the paper provided. Each problem counts 25%.

- (1) You are given the circuit of Figure 1.
(a) Use mesh analysis to find currents I_1 and I_2 as indicated in the diagram.
(b) How much power is supplied by the 50 V source?
(c) How much power is absorbed by the 10Ω resistor?

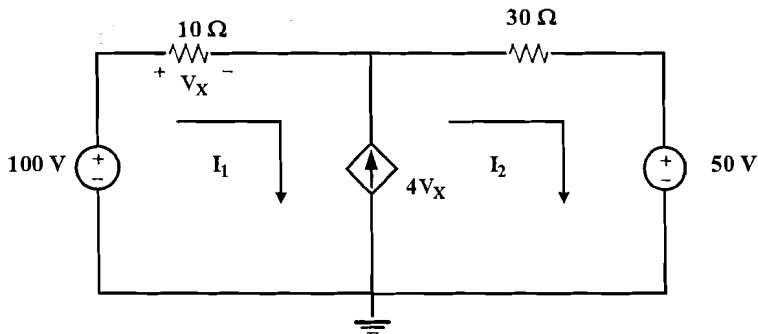


Figure 1: Circuit diagram for problem 1.

(a)

$$-100 + 10I_1 + 30I_2 + 50 = 0$$

$$10I_1 + 30I_2 = 50$$

$$I_2 - I_1 = 4V_x = 4 \times 10I_1$$

$$-41I_1 + I_2 = 0$$

$$\begin{bmatrix} 10 & 30 \\ -41 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \end{bmatrix}$$

$$I_1 = 0.04 \text{ A}$$

$$I_2 = 1.65 \text{ A}$$

[1]

1b)

$$P_{50}^{\text{sup}} = -50 I_2 = -50 (1.65)$$

$$P_{50}^{\text{sup}} = -82.5 \text{ W}$$

1c) $P_{10} = I_1^2 \times 10 = (0.04)^2 \times 10$

$$P_{10} = 0.016 \text{ W}$$

- (2) You are given the circuit of Figure 2.
- Find the Thevenin equivalent circuit looking into terminals a-b.
 - Draw the Thevenin equivalent circuit and determine the current flowing through a $20\ \Omega$ resistor connected between terminals a-b.


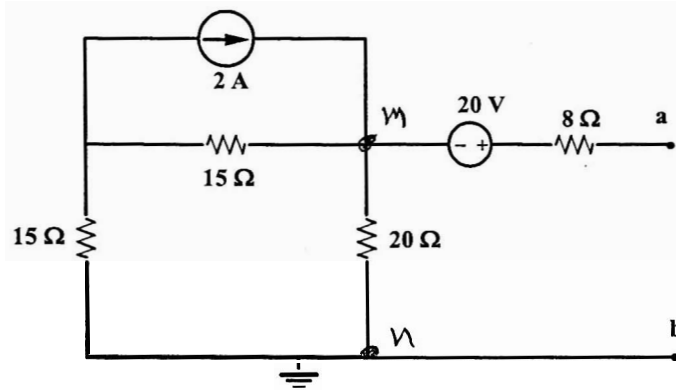


Figure 2: Circuit diagram for problem 2.

Use source transformation:

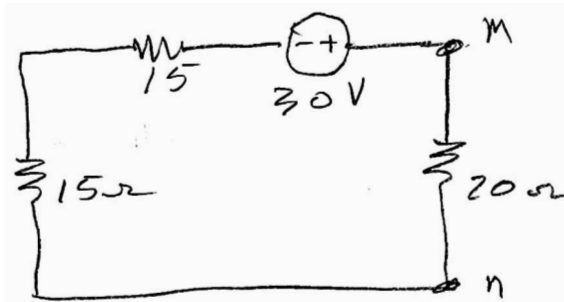


Using voltage division:

$$V_{mn} = \frac{30 \times 20}{20 + 15 + 15} = 12V$$

$$V_{TH} = V_{mn} + 20 = 32V$$

(2) A

FOR R_{TH}

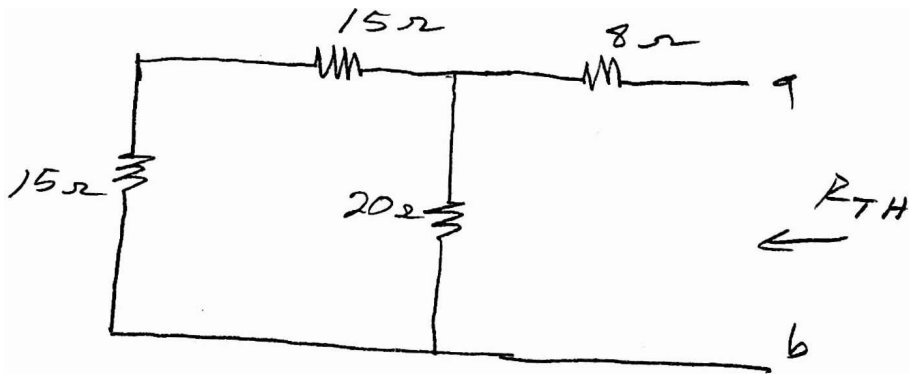


$$R_{TH} = (15 + 15) \parallel 20 + 8$$

$$= \frac{30 \times 20}{30 + 20} + 8$$

$$R_{TH} = 12 + 8 = 20 \Omega$$

(b)

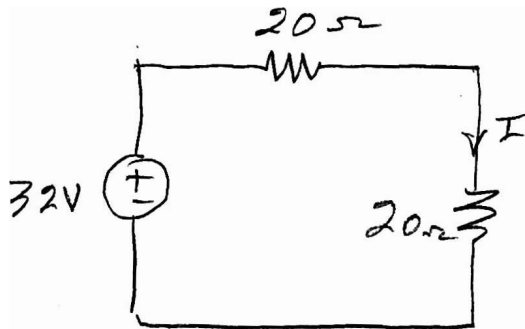

$$I = \frac{32}{40} = 0.8 \text{ A}$$

(3) You are given the circuit of Figure 3.

Determine the value of R_L so that maximum power will be delivered to R_L .


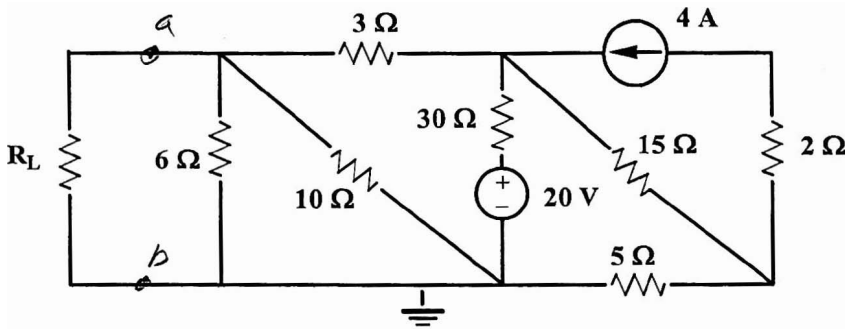


Figure 3: Circuit diagram for problem 3.

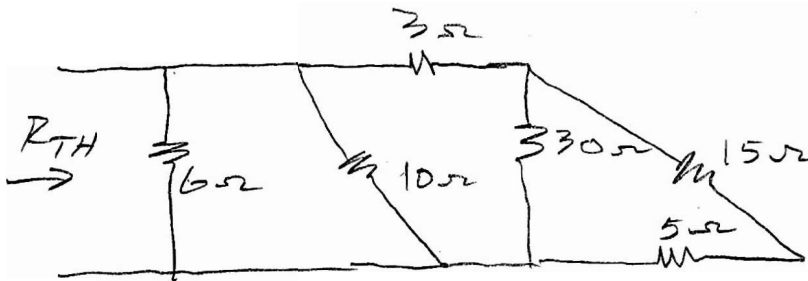The R_L will be the resistance seen looking into terminals a-b.



$$R_{TH} = \left(\left((15 + 5) \parallel 30 + 3 \right) \parallel 10 \right) \parallel 6$$

$$(15 + 5) \parallel 30 = \frac{20 \times 30}{50} = 12 \Omega$$

$$(12 + 3) \parallel 10 = \frac{15 \times 10}{25} = 6 \Omega$$

$$6 \parallel 6 = 3 \Omega$$

40

$R_L = 3 \Omega$

(4) You are given the circuit of Figure 4.

Use nodal analysis to find voltages v_1 and v_2 .

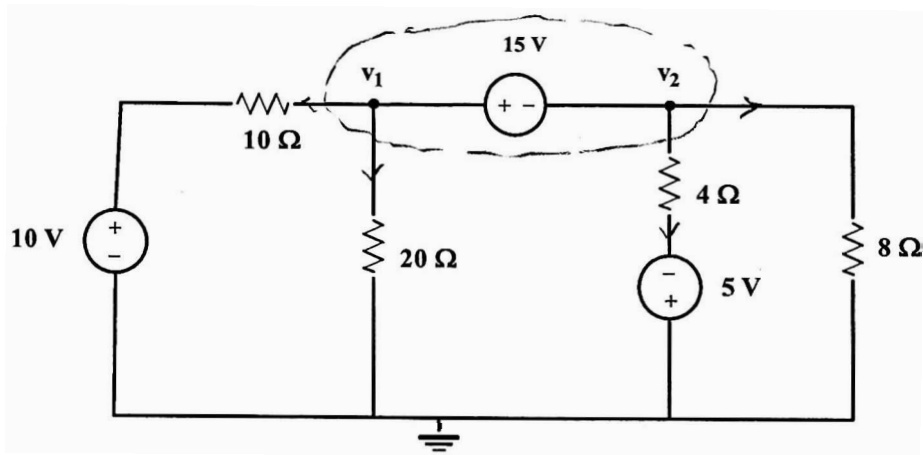


Figure 4: Circuit diagram for problem 4.

We have a supernode.

$$40 \left(\frac{v_1 - 10}{10} + \frac{v_1}{20} + \frac{v_2 + 5}{4} + \frac{v_2}{8} = 0 \right)$$

$$4v_1 - 40 + 2v_1 + 10v_2 + 50 + 5v_2 = 0$$

$$6v_1 + 15v_2 = -10$$

constraint

$$v_1 - 15 - v_2 = 0$$

$$v_1 - v_2 = 15$$

$$\begin{bmatrix} 6 & 15 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -10 \\ 15 \end{bmatrix}$$

$$v_1 = 10.24 \text{ V}$$

$$v_2 = -4.76 \text{ V}$$