

ECE 301
Spring Semester, 2007
Test #1

wlg Test B

Name _____

Print (last, first)

Work the exam on the paper provided. Each problem counts 25%.

(1) You are given the circuit of Figure 1.

Use nodal analysis to find voltages v_1 and v_2 .

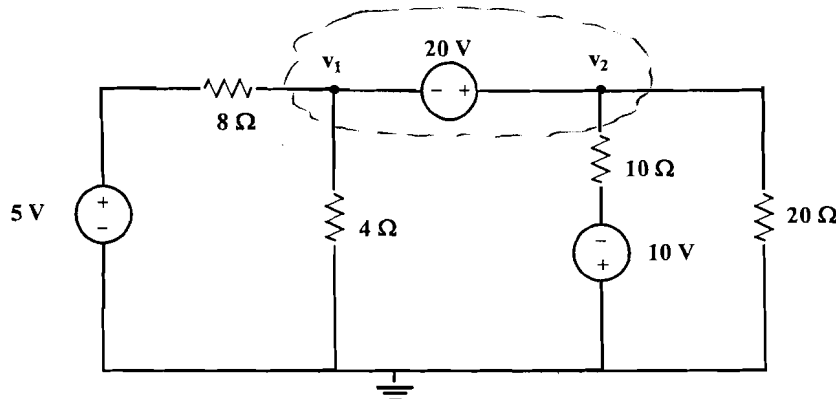


Figure 1: Circuit diagram for problem 1.

We have a super node as indicated

$$40 \left(\frac{v_1 - 5}{8} + \frac{v_1}{4} + \frac{v_2 + 10}{10} + \frac{v_2}{20} = 0 \right)$$

$$5v_1 - 25 + 10v_1 + 4v_2 + 40 + 2v_2 = 0$$

$$15v_1 + 6v_2 = -15$$

constraint

$$v_1 + 20 - v_2 = 0$$

$$v_1 - v_2 = -20$$

$$\begin{bmatrix} 15 & 6 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -15 \\ -20 \end{bmatrix}$$

$$v_1 = -6.43V$$

$$v_2 = 13.57V$$

(2) You are given the circuit of Figure 2.

Determine the value of R_L so that maximum power will be delivered to R_L .


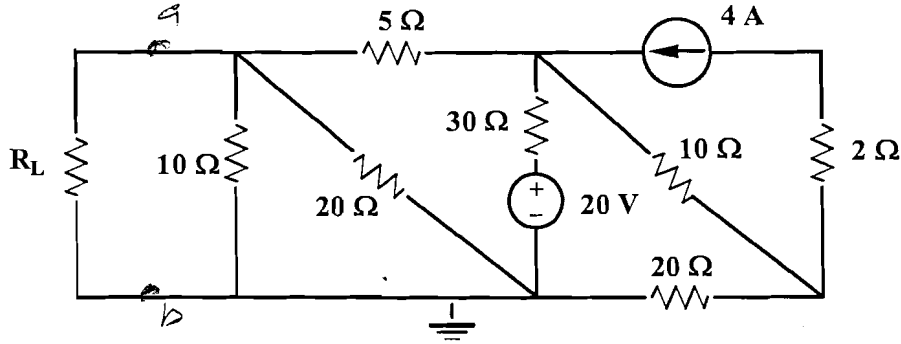


Figure 2: Circuit diagram for problem 2

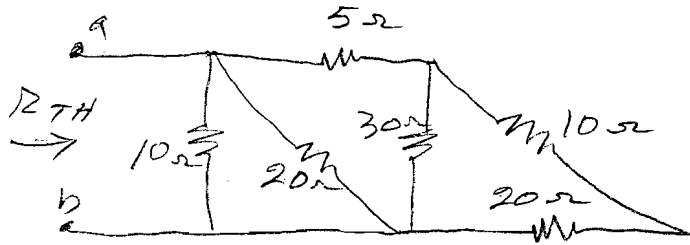To get maximum power transfer, R_L equals the resistance seen looking into terminals a-b.



$$R_{TH} = ((10 + 20) \parallel 30 + 5) \parallel 20 \parallel 10$$

$$(10 + 20) \parallel 30 = \frac{30 \times 30}{60} = 15 \Omega$$

$$(15 + 5) \parallel 20 = \frac{20 \times 20}{20 + 20} = 10 \Omega$$

$$10 \parallel 10 = \frac{10 \times 10}{10 + 10} = 5 \Omega$$

So

$$R_L = 5 \Omega$$

(3) You are given the circuit of Figure 3.

(a) Find the Thevenin equivalent circuit looking into terminals a-b.

(b) Draw the Thevenin equivalent circuit and determine the current flowing through a $20\ \Omega$ resistor connected between terminals a-b.


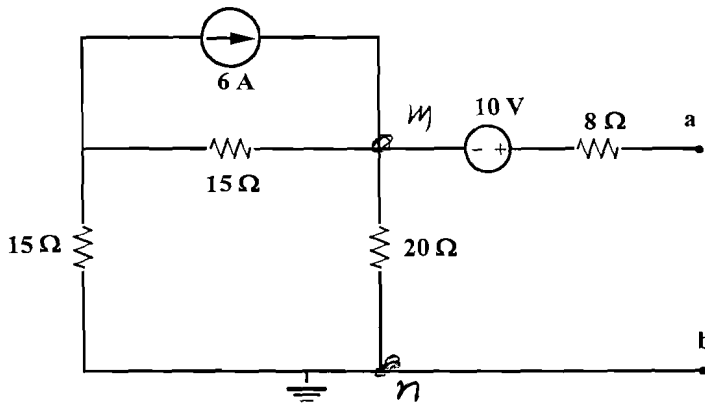


Figure 3: Circuit diagram for problem 2.

use source transformation

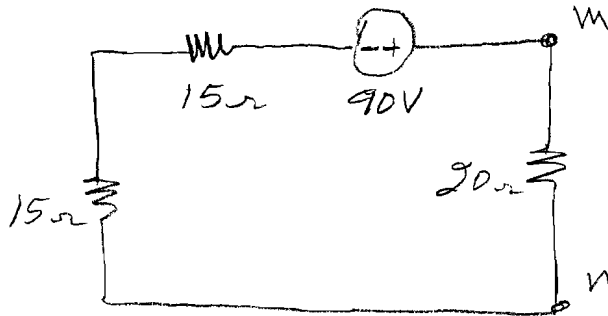


By voltage division

$$V_{mn} = \frac{90 \times 20}{20 + 15 + 15} = 36V$$


$$V_{OC} = V_{TH} = V_{mn} + 10 = 46V$$

3B

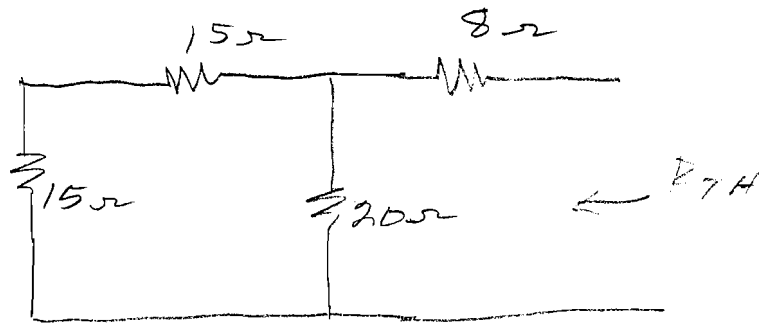FOR R_{TH} 

$$R_{TH} = (15 + 15) \parallel 20 + 8$$

$$R_{TH} = 12 + 8 = 20\Omega$$

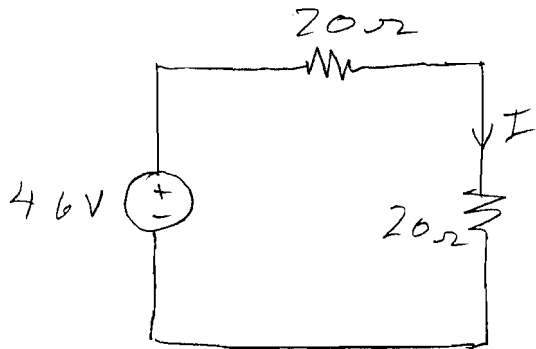

$$I = \frac{46}{40} = 1.15 \text{ A}$$

- (4) You are given the circuit of Figure 4.
- Use mesh analysis to find currents I_1 and I_2 as indicated in the diagram.
 - How much power is supplied by the 50 V source?
 - How much power is absorbed by the 10 Ω resistor?

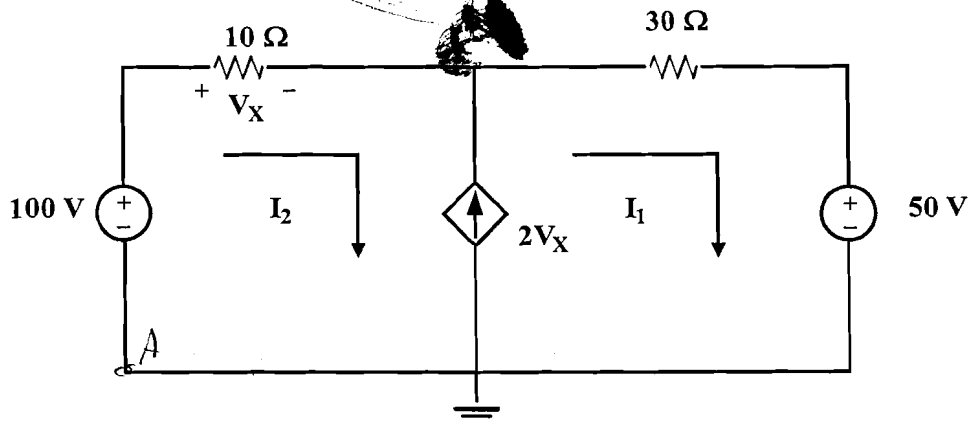


Figure 4: Circuit diagram for problem 1.

1a) We have a super mesh.
 Start at A, go c.w, $\sum \text{drops} = 0$
 $-100 + 10 I_2 + 30 I_1 + 50 = 0$

$$\boxed{30 I_1 + 10 I_2 = 50}$$

constraint

$$I_1 - I_2 = 2V_x = 2 \times 10 I_2$$

$$\boxed{I_1 - 21 I_2 = 0}$$

$$\begin{bmatrix} 30 & 10 \\ 1 & -21 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \end{bmatrix}$$

$$\boxed{I_1 = 1.64 \text{ A}, \quad I_2 = 0.078 \text{ A}}$$

4 B

(b)

$$P = -50 I_1$$

$$P_{sup} = -50 \times 1.64 = -82 \text{ W}$$
₃₀

$$P_{sup} = -82 \text{ W}$$
₃₀

(c) $P_{ABS} = I_2^2 \times 10 = (0.078)^2 \times 10$

₁₀

$$P_{ABS} = 0.0608 \text{ W}$$
₁₀