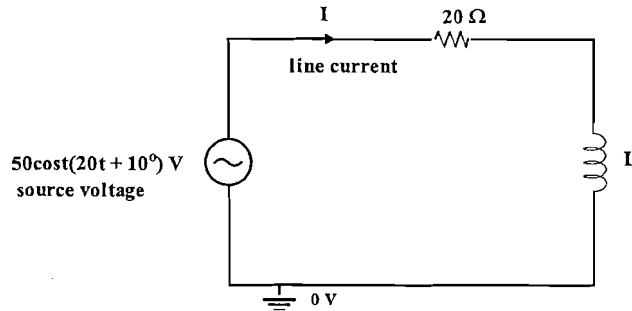


ECE 301
Test 3A
Fall 2007

- (1) You are given the circuit of Figure 1 with the indicated source voltage and line current. The line current is known to be; $I = 1.77 \angle -35^\circ$ A. Determine the approximate value of the inductance L.



$$Z = \frac{\vec{V}}{\vec{I}}$$

where $\vec{V} = 50 \angle 10^\circ$; $\vec{I} = 1.77 \angle -35^\circ$ A

$$Z = \frac{50 \angle 10^\circ}{1.77 \angle -35^\circ} = 28.25 \angle 45^\circ$$


$$Z = R + j\omega L = 20 + j\omega L = 19.99 + j19.99$$

$$\omega L = 19.99$$

$$L = \frac{19.99}{20} \approx 1 \text{ H}$$


3A

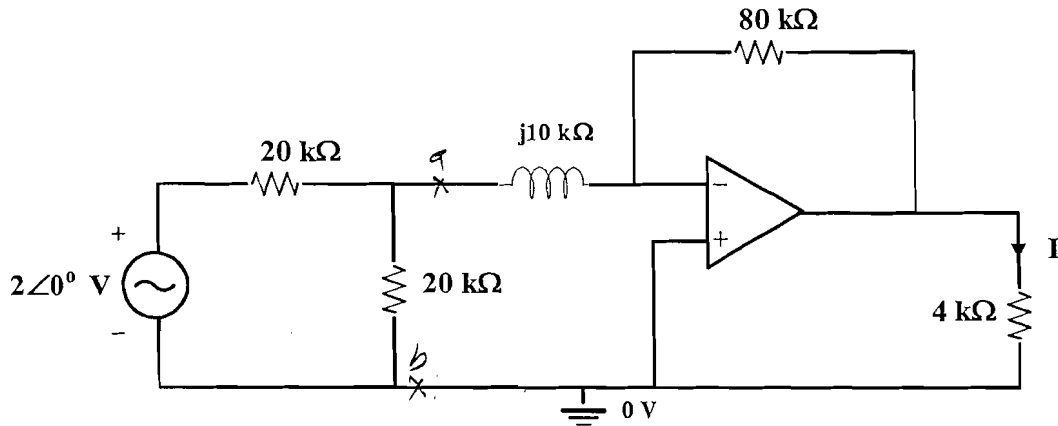- (2) You are given the op-amp circuit of Figure 2. Determine the phasor current I shown in the diagram. Express your answer in polar form.



Thevenin to the left of a-b
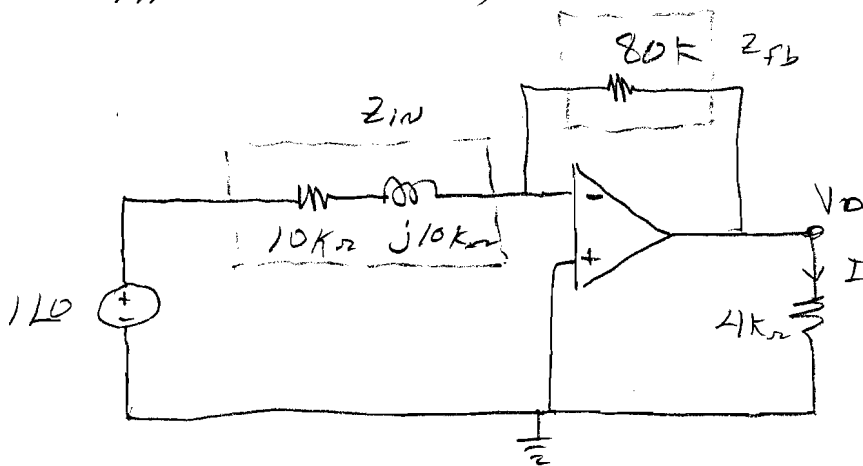
$$V_{TH} = 1 \angle 0 \quad ; \quad R_{TH} = 10 \text{ k}\Omega$$




$$\vec{V}_0 = -1 \angle 0 \times \frac{80 \text{ k}}{10 \text{ k} + j10 \text{ k}} = -\frac{8}{1+j}$$

$$\vec{I} = \frac{\vec{V}_0}{4 \text{ k}} = -\frac{2}{1+j} \text{ mA}$$

$$\vec{I} = 1.414 \angle 135^\circ \text{ mA}$$

3A

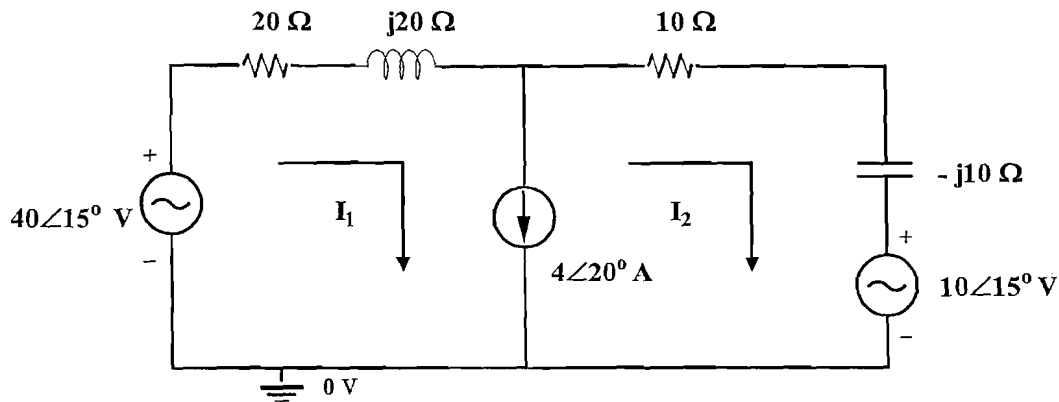- (3) You are given the AC circuit shown in Figure 3. Use mesh analysis to find the mesh currents I_1 and I_2 as indicated in the circuit diagram. Express I_1 and I_2 in polar form.



Around the supermesh:

$$-40\angle 15^\circ + (20 + j20)\hat{I}_1 + (10 - j10)I_2 + 10\angle 15^\circ = 0$$

$$(20 + j20)I_1 + (10 - j10)I_2 = 40\angle 15^\circ - 10\angle 15^\circ$$

$$= 40\angle 15^\circ + 10\angle -165^\circ$$

OR

$$30\angle 15^\circ$$

Constraint

$$I_1 - I_2 = 4\angle 20^\circ$$

$$\begin{bmatrix} (20 + j20) & (10 - j10) \\ 1 & -1 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 30\angle 15^\circ \\ 4\angle 20^\circ \end{bmatrix}$$

$$\hat{I}_1 = 2.59\angle -29.8^\circ \text{ A}$$


$$\hat{I}_2 = 3.06\angle -119.7^\circ \text{ A}$$

(4) You are given the AC circuit shown in Figure 4.

(a) Use nodal analysis to find the node voltages V_1 and V_2 as indicated in the circuit diagram.

Express V_1 and V_2 in polar form.

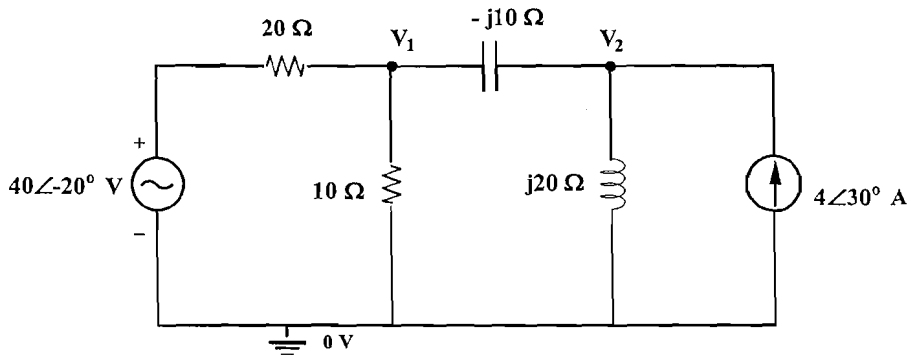(b) Prepare a phasor diagram showing V_1 and V_2 . Which voltage is leading? Explain.



At node V_1

$$\frac{V_1 - 40\angle-20}{20} + \frac{V_1}{10} + \frac{V_1 - V_2}{-j10} = 0$$

$$0.05V_1 + 0.1V_1 + j0.1V_1 - j0.1V_2 = 2\angle-20$$

$$(0.15 + j0.1)V_1 + (0 - j0.1)V_2 = 2\angle-20$$

At node V_2

$$\frac{V_2 - V_1}{-j10} + \frac{V_2}{j20} = 4\angle30$$

$$j0.1V_2 - j0.1V_1 - j0.05V_2 = 4\angle30$$


$$(0 - j0.1)V_1 + (0 + j0.05)V_2 = 4\angle30$$

$$\begin{bmatrix} (0.15 + j0.1) & (0 - j0.1) \\ (0 - j0.1) & (0 + j0.05) \end{bmatrix} \begin{bmatrix} \hat{V}_1 \\ \hat{V}_2 \end{bmatrix} = \begin{bmatrix} 2\angle-20 \\ 4\angle30 \end{bmatrix}$$

$$\hat{V}_1 = 52.2\angle54.3^\circ \text{ V}$$

$$\hat{V}_2 = 102.1\angle8.75^\circ \text{ V}$$

(4) (b)

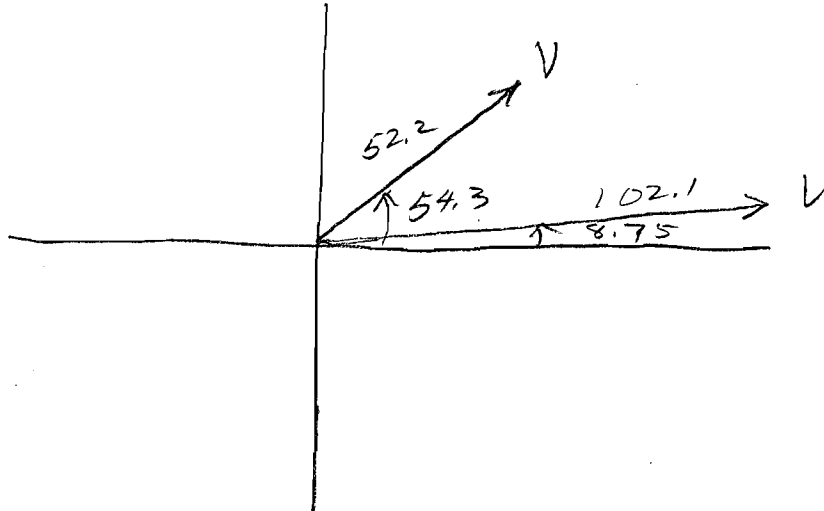


V_1 leads V_2 by $54.3 - 8.75 = 45.6^\circ$
The reason is that angle of V_1 is
greater than the angle of V_2

(5) The load for a certain AC circuit is shown in Figure 5.

(a) Find the impedance of this load, Z , as indicated in the diagram. Express your answer in polar form.

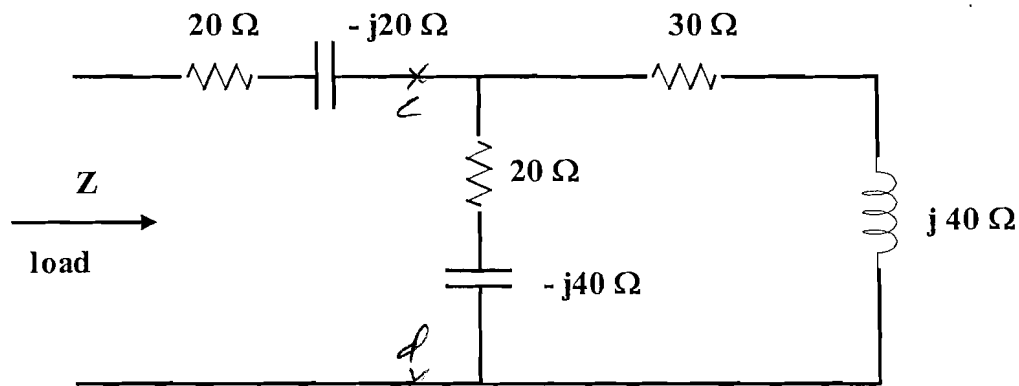(b) Determine whether this is a leading or lagging load. Explain your answer.



1a)

$$Z_{cd} = \frac{(30 + j40)(20 - j40)}{30 + j40 + 20 - j40} = \frac{(30 + j40)(20 - j40)}{50}$$

$$Z = 20 - j20 + Z_{cd}$$

$$Z = 64 - j28\ \Omega$$

$$Z = 69.86 \angle -23.6^\circ\ \Omega$$

1b) lagging load, angle of Z is negative.