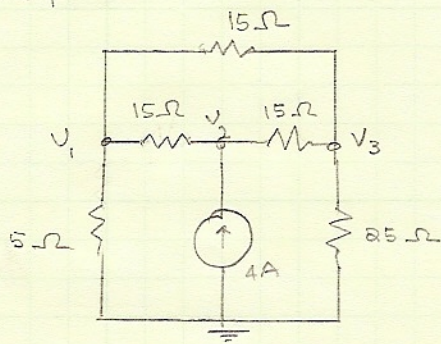


HW #2 Solution

#2.49

Find  $V_1, V_2, V_3$ Solution:

Using nodal analysis

$$\text{Node 1: } \frac{V_1}{5} + \frac{V_1 - V_2}{15} + \frac{V_1 - V_3}{15} = 0$$

$$5V_1 - V_2 - V_3 = 0 \quad \text{--- (1)}$$

$$\text{Node 2: } \frac{V_2 - V_1}{15} + \frac{V_2 - V_3}{15} = 4$$

$$-V_1 + 2V_2 - V_3 = 60 \quad \text{--- (2)}$$


$$\text{Node 3: } \frac{V_3}{25} + \frac{V_3 - V_1}{15} + \frac{V_3 - V_2}{15} = 0$$

$$-5V_1 - 5V_2 + 13V_3 = 0 \quad \text{--- (3)}$$

Solve eqn (1), (2) and (3):

$V_1 = 15 \text{ V}$
$V_2 = 50 \text{ V}$
$V_3 = 25 \text{ V}$

# 2.50.

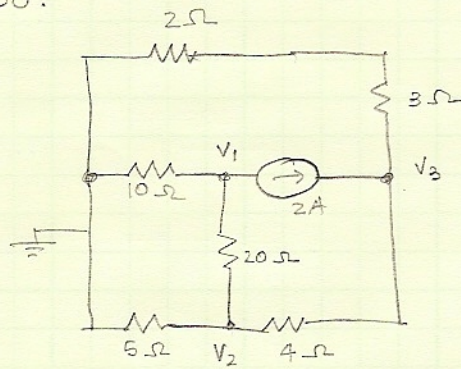FIND  $V_1, V_2, V_3$ .Solution.

Using NODAL ANALYSIS.

$$\text{Node 1 : } \frac{V_1}{10} + \frac{V_1 - V_2}{20} + 2A = 0$$

$$3V_1 - V_2 = -40 \quad \text{--- (1)}$$

$$\text{Node 2 : } \frac{V_2}{5} + \frac{V_2 - V_1}{20} + \frac{V_2 - V_3}{4} = 0$$

$$-V_1 + 10V_2 - 5V_3 = 0 \quad \text{--- (2)}$$


$$\text{Node 3 : } \frac{V_3}{5} + \frac{V_3 - V_2}{4} - 2A = 0$$

$$-5V_2 + 9V_3 = 40 \quad \text{--- (3)}$$


Solving eqns (1), (2) &amp; (3):

$V_1 =$	$-12.90 \text{ V}$
$V_2 =$	$1.29 \text{ V}$
$V_3 =$	$5.16 \text{ V}$

# 2.54

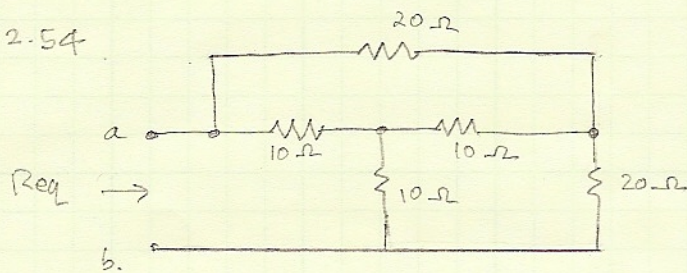FIND  $R_{EQ}$ .ANSWER:

Let's apply 1A across terminal a-b.

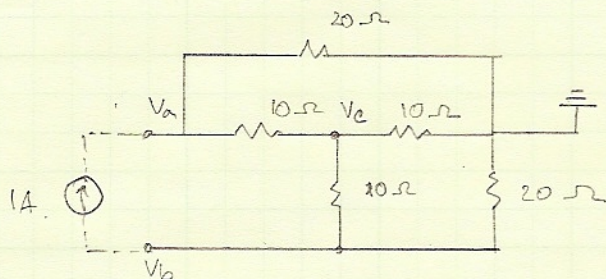

Use Nodal analysis.

$$\text{Node a. } \frac{V_a}{20} + \frac{V_a - V_c}{10} = 1A$$

$$3V_a - 2V_c = 20 \quad \text{--- (1)}$$

$$\text{Node b. } \frac{V_b}{20} + \frac{V_b - V_c}{10} = -1A$$

$$3V_b - 2V_c = -20 \quad \text{--- (2)}$$

$$\text{Node c. } \frac{V_c}{10} + \frac{V_c - V_a}{10} + \frac{V_c - V_b}{10} = 0$$


$$-V_a - V_b + 3V_c = 0 \quad \text{--- (3)}$$

$$\text{Solving for (1), (2), (3): } \begin{aligned} V_a &= 6.667 \text{ V} \\ V_b &= -6.667 \text{ V} \\ V_c &= 0 \text{ V} \end{aligned}$$

$$V_a - V_b = 6.667 - (-6.667) \text{ V} = 13.334 \text{ V}$$

$$\text{Therefore } R_{EQ} = \frac{V_a - V_b}{1A} = \frac{13.334 \text{ V}}{1A} = \underline{\underline{13.334 \Omega = R_{EQ}}}$$

# 2.55.

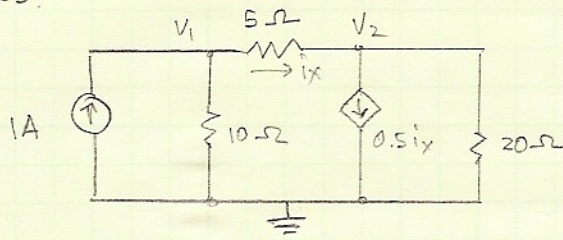FIND  $V_1, V_2, i_x$ .ANSWER:

Use Nodal Analysis.

$$\text{Node 1: } \frac{V_1}{10} + \frac{V_1 - V_2}{5} = 1 \text{ A.}$$

$$3V_1 - 2V_2 = 10 \quad \text{--- (1)}$$

$$\text{Node 2: } \frac{V_2}{20} + \frac{V_2 - V_1}{5} + 0.5i_x = 0$$

$$-4V_1 + 5V_2 + 10i_x = 0 \quad \text{--- (2)}$$


Also,

$$\frac{V_1 - V_2}{5} = i_x \Rightarrow V_1 - V_2 - 5i_x = 0 \quad \text{--- (3)}$$


Solving (1), (2), &amp; (3), we have

$V_1 =$	$6 \text{ V}$
$V_2 =$	$4 \text{ V}$
$i_x =$	$0.4 \text{ A}$

# 2. 58.

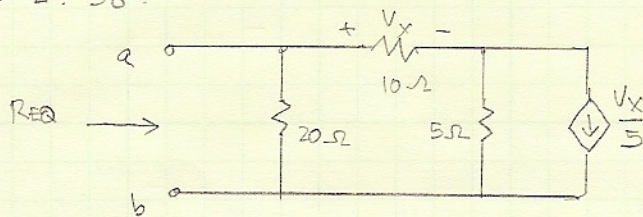Find  $R_{EQ}$ .

Solution

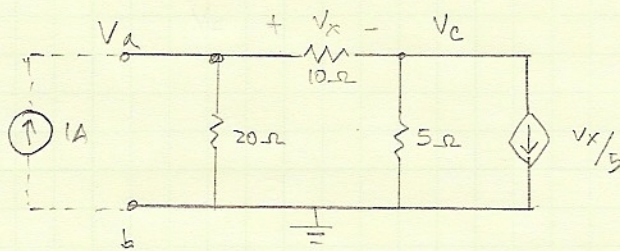Let  $V_b$  be the ground  $\Rightarrow V_b = 0$ .

Node a.  $\frac{V_a}{20} + \frac{V_a - V_c}{10} = 1A.$

$$3V_a - 2V_c = 20 \quad \text{--- (1)}$$

Node c.  $\frac{V_c}{5} + \frac{V_c - V_a}{10} = -\frac{V_x}{5}$

$$-V_a + 3V_c + 2V_x = 0 \quad \text{--- (2)}$$


Also,  $V_a - V_c = V_x \Rightarrow V_a - V_c - V_x = 0 \quad \text{--- (3)}$

Solving for EQNS (1), (2), & (3) :

$$\begin{aligned} V_a &= 4V \\ V_c &= -4V \\ V_x &= 8V \end{aligned}$$

Therefore,  $R_{EQ} = \frac{V_a - V_b}{1A} = \frac{(4 - 0)V}{1A} = \underline{\underline{4\Omega = R_{EQ}}}$

# 2. (a)

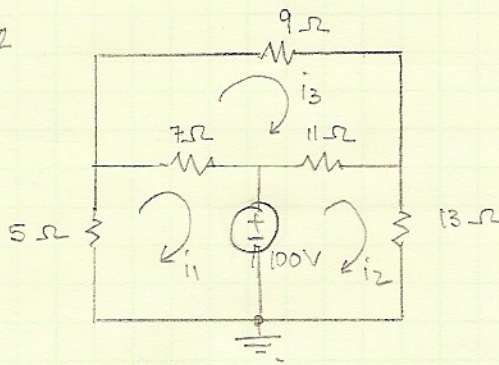FIND  $P_{100V}$ Answer :

$$\text{Loop 1 : } 5i_1 + 7(i_1 - i_3) + 100V = 0.$$

$$12i_1 - 7i_3 = -100 \quad \text{--- (1)}$$

$$\text{Loop 2 : } -100V + 11(i_2 - i_3) + 13i_2 = 0$$

$$24i_2 - 11i_3 = 100 \quad \text{--- (2)}$$

$$\text{Loop 3 : } 7(i_3 - i_1) + 11(i_3 - i_2) + 9i_3 = 0$$

$$-7i_1 - 11i_2 + 27i_3 = 0$$

Solving eqns (1), (2) and (3), we get :

$$i_1 = -8.74A$$

$$i_2 = 3.85A$$

$$i_3 = -0.699A$$


$$\text{Therefore } P_{100} = V(i_2 - i_1)$$

$$= 100V (3.85 - (-8.74))A$$

$$= 1259W$$

$$= \underline{\underline{1.26kW}}$$

# 2.66

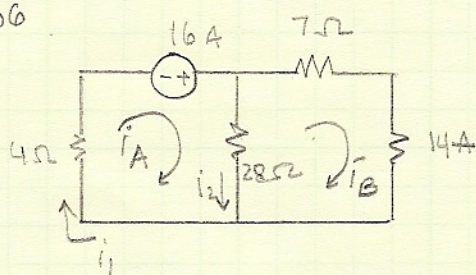FIND  $i_1$  and  $i_2$ ANSWER :

$$\text{Loop A : } 4i_A - 16A + 28(i_A - i_B) = 0$$

$$32i_A - 28i_B = 16 \quad \text{--- ①}$$

$$\text{Loop B : } 28(i_B - i_A) + 7i_B + 14i_B = 0$$

$$-28i_A + 49i_B = 0 \quad \text{--- ②}$$

Solve for EQNS ① AND ② :

$$i_A = 1A$$


$$i_B = 0.571A$$

$$\text{Therefore, } i_1 = i_A = 1A$$

$$i_2 = i_A - i_B = (1 - 0.571)A$$

$$= \underline{\underline{0.429A}}$$

# 2.69

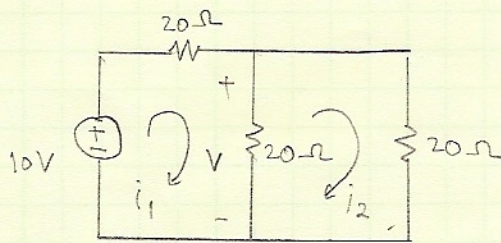FIND V USE mesh  
CURRENT ANALYSIS.ANSWER :

$$\text{Loop 1 : } -10V + 20i_1 + 20(i_1 - i_2) = 0$$

$$40i_1 - 20i_2 = 10 \quad \text{--- (1)}$$

$$\text{Loop 2 : } 20(i_2 - i_1) + 20i_2 = 0$$

$$-20i_1 + 40i_2 = 0 \quad \text{--- (2)}$$

$$\text{Solve eqns (1) and (2) : } \begin{aligned} i_1 &= 0.333 \text{ A} \\ i_2 &= 0.1667 \text{ A} \end{aligned}$$


$$\text{Therefore } V = R_{20}(i_1 - i_2)$$

$$= 20\Omega(0.333 - 0.167) \text{ A}$$

$$= \underline{\underline{3.33 \text{ V}}}$$



# 2.70.

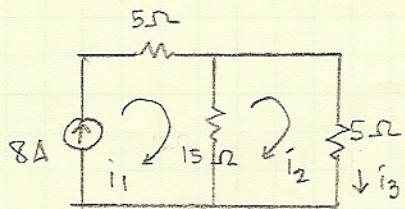FIND  $i_3$  using mesh ANALYSISANSWER

$$\text{Loop 1: } i_1 = 8A$$

$$\begin{aligned} \text{Loop 2: } 15(i_2 - i_1) + 5i_2 &= 0 \\ -15i_1 + 20i_2 &= 0 \end{aligned}$$


$$\text{and } i_1 = 8A \rightarrow -15(8) + 20i_2 = 0$$

$$20i_2 = 120 A$$

$$i_2 = 6A$$

Therefore  $i_3 = i_2 = 6A$ .

# 2. XX

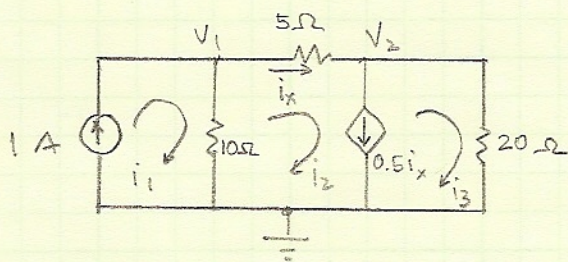FIND  $i_x$  using mesh analysis

$$i_x = i_2$$

ANSWER.From loop 1, we know  $i_1 = 1A$  — ①

Supermesh 2 and 3:

$$10(i_2 - i_1) + 5i_2 + 20i_3 = 0.$$

$$-10i_1 + 15i_2 + 20i_3 = 0. \quad \text{--- ②}$$

Constraint

$$i_2 - i_3 = 0.5i_x$$

$$i_x = i_2 \Rightarrow i_2 - i_3 = 0.5i_2$$

$$0.5i_2 - i_3 = 0 \quad \text{--- ③}$$

Solving for eqns ①, ②, and ③:

$$i_1 = 1A$$

$$i_2 = 0.4A$$

$$i_3 = 0.2A$$

Therefore,  $i_x = i_2 = 0.4A$