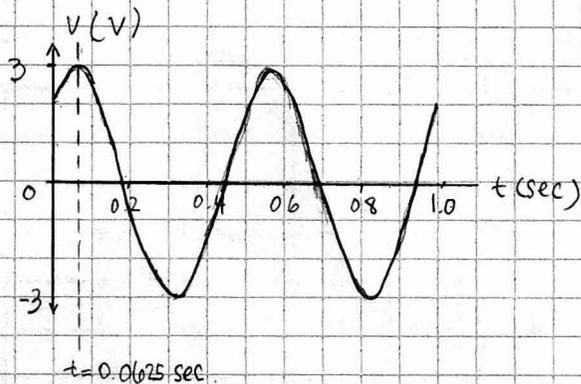


#5.26



Write the sinusoid in the form $V_m \cos(\omega t + \theta)$
 Determine the phasor $\frac{1}{\sqrt{2}}$ RMS value of $v(t)$

ANS

$$V_m = 3$$

$$T = 0.5 \text{ s}$$

$$\rightarrow f = \frac{1}{T} = 2 \text{ Hz}$$

$$\rightarrow \omega = 2\pi f = 4\pi \text{ rad/sec}$$

$$\theta = (-360^\circ) \frac{t_{\max}}{T} = (-360^\circ) \frac{0.0625}{0.5}$$

$$= -45^\circ$$


$$\therefore \underline{\underline{v(t) = 3 \cos(4\pi t - 45^\circ)}}$$

Phasor :

$$\underline{\underline{V = 3 \angle -45^\circ}}$$

$$V_{\text{RMS}} = \frac{3}{\sqrt{2}} = \underline{\underline{2.121 \text{ V}}}$$

5.53

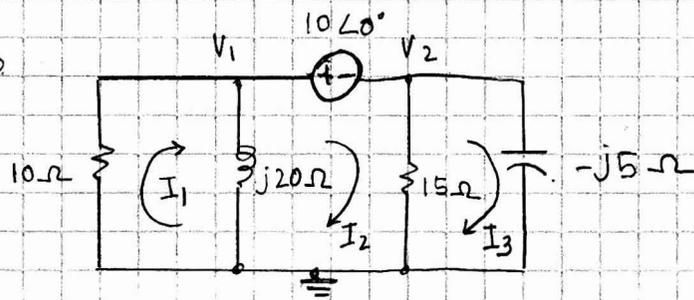

Use nodal Analysis.

At Supernode :
$$\frac{V_1}{10} + \frac{V_1}{j20} + \frac{V_2}{15} + \frac{V_2}{-j5} = 0$$

$$V_1 \left(\frac{1}{10} + \frac{1}{j20} \right) + V_2 \left(\frac{1}{15} + \frac{1}{-j5} \right) = 0 \quad \text{--- ①}$$

Constraint : $V_1 - V_2 = 10 \angle 0^\circ \quad \text{--- ②}$

Solving eqns ① & ② we have

$$V_1 = 9.402 \angle 29.58^\circ \text{ V}$$

$$V_2 = 4.986 \angle 111.45^\circ \text{ V}$$

5.59 Same problem as in P5.53, but using nodal analysis

Mesh 1 : $10I_1 + j20(I_1 - I_2) = 0$
 $(10 + j20)I_1 - j20I_2 = 0 \quad \text{--- ①}$

Mesh 2 : $j20(I_2 - I_1) + 15(I_2 - I_3) + 10 = 0$
 $-j20I_1 + (15 + j20)I_2 - 15I_3 = -10 \quad \text{--- ②}$

Mesh 3 : $15(I_3 - I_2) - j15I_3 = 0$
 $-15I_2 + (15 - j15)I_3 = 0 \quad \text{--- ③}$


Solve eqn ① & ② & ③ we have.

$$I_1 = 0.940 \angle -150.4^\circ \text{ A}$$

$$I_2 = 1.051 \angle -177^\circ \text{ A}$$

$$I_3 = 0.997 \angle -158.55^\circ \text{ A}$$

5.54

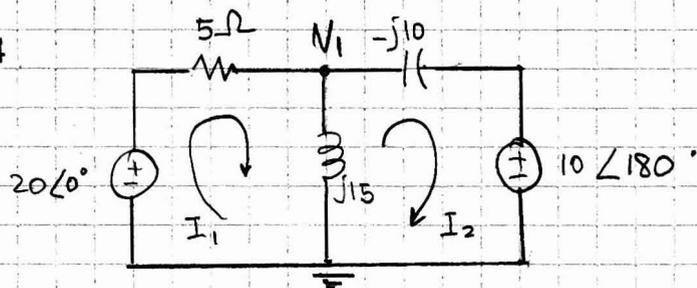

Solve the node voltage using nodal analysis

At node V_1 :

$$\frac{V_1 - 20\angle 0^\circ}{5\Omega} + \frac{V_1}{j15} + \frac{V_1 - 10\angle 180^\circ}{-j10} = 0$$

$$V_1 \left(\frac{1}{5} + \frac{1}{j15} - \frac{1}{j10} \right) = \frac{20\angle 0^\circ}{5} - \frac{10\angle 180^\circ}{j10}$$

$$\underline{\underline{V_1 = 20.33 \angle -23.5^\circ \text{ V}}}$$

5.57. Same problem as # 5.54 using mesh analysis to find currents

Mesh 1:

$$-20\angle 0^\circ + 5I_1 + j15(I_1 - I_2) = 0$$

$$(5 + j15)I_1 - j15I_2 = 20\angle 0^\circ \quad \text{--- (1)}$$

Mesh 2:

$$j15(I_2 - I_1) - j10I_2 + 10\angle 180^\circ = 0$$


$$-j15I_1 + j5I_2 = -10\angle 180^\circ \quad \text{--- (2)}$$

Solving (1) & (2), we have

$$I_1 = 1.064 \angle 80.54^\circ \text{ A}$$

$$\underline{\underline{I_2 = 2.977 \angle 74.2^\circ \text{ A}}}$$

5.55

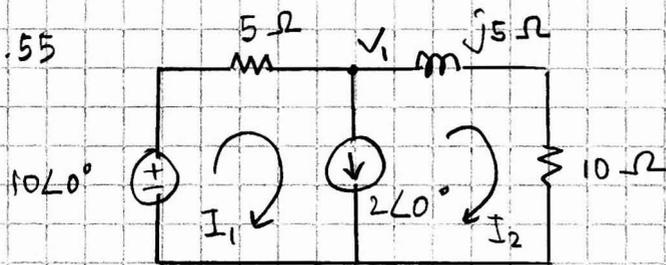

Solve V_1 using nodal analysis

$$\frac{V_1 - 10}{5} + 2\angle 0^\circ + \frac{V_1}{10 + j5} = 0$$

$$V_1 \left(\frac{1}{5} + \frac{1}{10 + j5} \right) = -2\angle 0^\circ + 2$$
$$= 0$$

$$\underline{\underline{V_1 = 0V}}$$

5.58 Solve the mesh current for problem 5.55

$$\text{Mesh 1 \& 2: } -10\angle 0^\circ + 5I_1 + (10 + j5)I_2 = 0$$


$$5I_1 + (10 + j5)I_2 = 10\angle 0^\circ \quad \text{--- (1)}$$

$$\text{Constraint: } I_1 - I_2 = 2\angle 0^\circ \quad \text{--- (2)}$$

Solving eqn (1) & (2) we have


$$\underline{\underline{I_1 = 2\angle 0^\circ A}}$$
$$\underline{\underline{I_2 = 0A}}$$

589

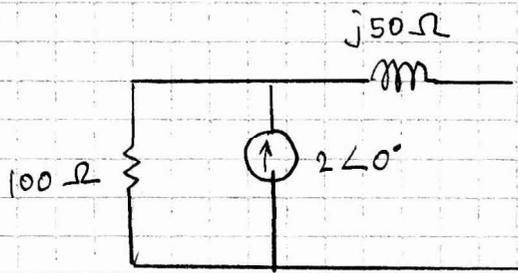

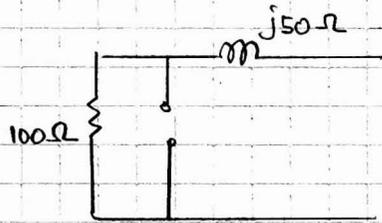(a) Find thevenin & norton equivalent ckt


To find thevenin impedance, we remove the current source.



$$Z_{TH} = (100 + j50) \Omega$$

$$= 111.8 \angle 26.6^\circ$$

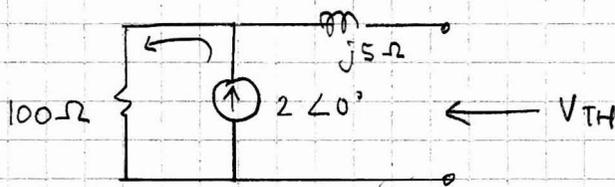To find thevenin voltage, we put the current source back.




but there is no current flows through $j5 \Omega$ due to open ckt, and there is zero voltage across $j5 \Omega$. Current from the current source only flows to 100Ω .

The Thevenin voltage $V_{TH} = V_{OC} = V_{100} = (2 \angle 0^\circ)(100)$

$$= 200 \angle 0^\circ \text{ V}$$

Norton current $I_N = \frac{V_{TH}}{Z_{TH}} = \frac{200 \angle 0^\circ}{(100 + j50)} = 1.789 \angle -26.57^\circ$

Thevenin eqn ckt:

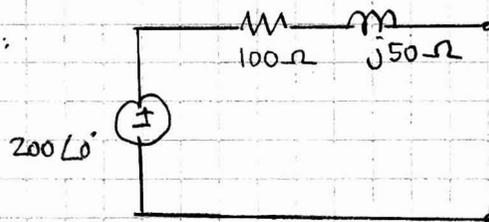

Norton eqn ckt:

