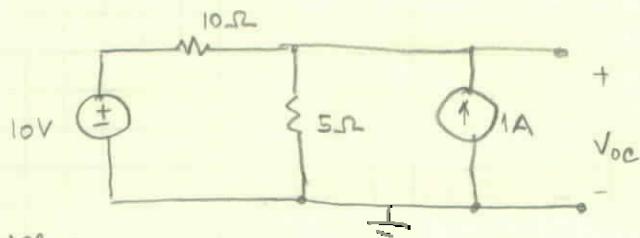


HW #3
SOLUTION


P. 2.75.

FIND THEVENIN & NORTON
EQUIVALENT CIRCUITANSWER :

- Open circuit solution:


(i) USE nodal analysis to solve for the open-ckt voltage.

$$\frac{V_{oc} - 10}{10} + \frac{V_{oc}}{5} = 1 \Rightarrow V_{oc} = \underline{\underline{6.667 \text{ Volts}}}$$

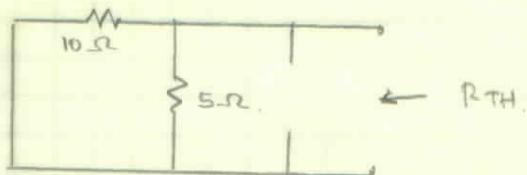
(ii) To find R_{TH} , we turn off all the sources.

Therefore, $R_{TH} = 5 // 10 = \frac{5 \times 10}{15} = 3.333 \Omega$

∴ The Thevenin Equivalent ckt:

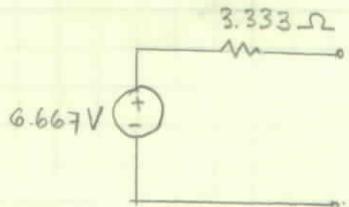

o short circuit solution

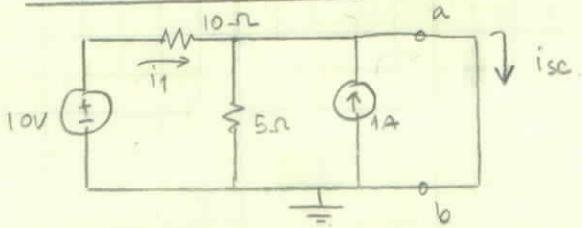


$$(a) \frac{Va - 10}{10} + \frac{Va}{5} + isc - 1A = 0 \quad \text{but } Va = Vb = 0$$

$$\frac{-10}{10} + isc - 1A = 0$$

$$\underline{isc = 2A = IN}$$


FROM the OPEN circuit solution, $R_{TH} = 3.333\Omega$

∴ The NORTON equiv. ckt.

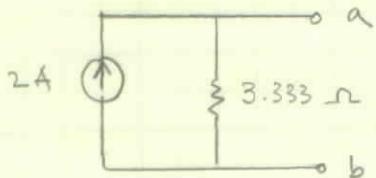

Also, we verify that $isc = IN = \frac{V_{TH}}{R_{TH}} = 2A$.

P2.78

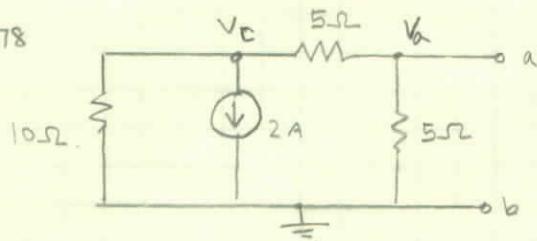

Find the Thevenin or Norton Equivalent ckt.

ANSWER

• the OPEN circuit solution

(i) Using Nodal analysis w/ V_b as the reference node.

$$\frac{V_a}{5} + \frac{V_a - V_c}{5} = 0$$

$$2V_a - V_c = 0 \quad \text{--- (1)}$$


$$\frac{V_c}{10} + 2 + \frac{V_c - V_a}{5} = 0.$$

$$-2V_a + 3V_c = -20 \quad \text{--- (2)}$$

Solving EQUATIONS (1) AND (2), we get $V_a = -5V$
 $V_c = -10V$


thus, $V_{TH} = V_{ab} = -5V$

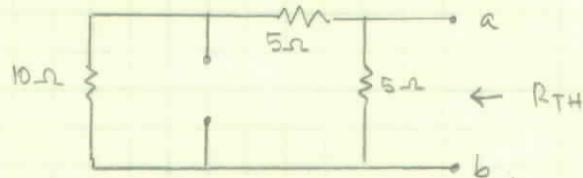(ii). to find the R_{TH} , we turn off the sources.




$$R_{TH} = (10+5)\parallel 5 = 15\parallel 5 = \frac{15 \times 5}{15+5} = \frac{75}{20} = 3.75\Omega$$

Therefore, the Thevenin equiv. ckt

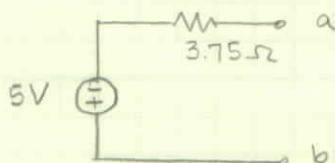

o. the short circuit soln.

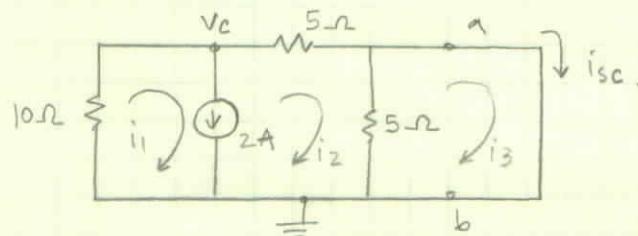

(i) SUPERmesh 1 and 2:

W Constraint

$$i_1 - i_2 = 2A \quad \text{--- (2)}$$

$$10i_1 + 5i_2 + 5(i_2 - i_3) = 0$$

$$10i_1 + 10i_2 - 5i_3 = 0 \quad \text{--- (1)}$$

Mesh 3: $5(i_3 - i_2) = 0$


$$5i_2 - 5i_3 = 0 \quad \text{--- (3)}$$

Solve For eqn. (1), (2) and (3), we get $i_1 = 0.667 A$

$$i_2 = -1.333 A$$


$$i_3 = -1.333 A = i_{sc} = I_N$$

Therefore, the Norton equiv. ckt:

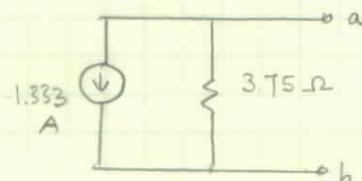

We verify that $i_{sc} = I_N = -1.333 A = \frac{-5V}{3.75\Omega} = \frac{V_{TH}}{R_{TH}}$

P.2.T9

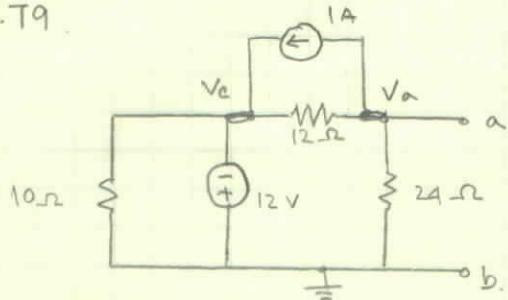

- a. Find the Thévenin & Norton equivalent ckt.
 b. What does the $10\ \Omega$ -Resistor have on the equiv. ckt? Explain your answer.

(a) o the open-circuit solution.


(i) Use nodal analysis w/ V_b as the ref. Node:

$$\frac{V_a}{24} + \frac{V_a - V_c}{12} + 1 = 0$$

$$3V_a - 2V_c = -24 \quad \text{---(1)}$$


but $V_c = -12V$, therefore

$$\begin{aligned} 3V_a + 24 &= -24 \\ 3V_a &= -48 \\ V_a &= -16V = V_{TH} \end{aligned}$$

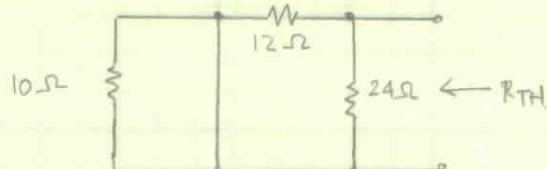
(ii) TURN all SOURCES off to find R_{TH} .

$$\begin{aligned} R_{TH} &= 12 // 24 \\ &= \frac{12 \times 24}{12 + 24} = 8\ \Omega = R_{TH} \end{aligned}$$

Therefore, the Thévenin equivalent ckt:

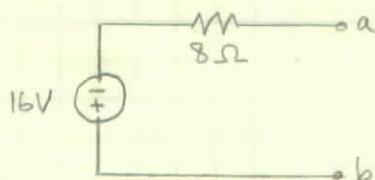

- The short-circuit solution

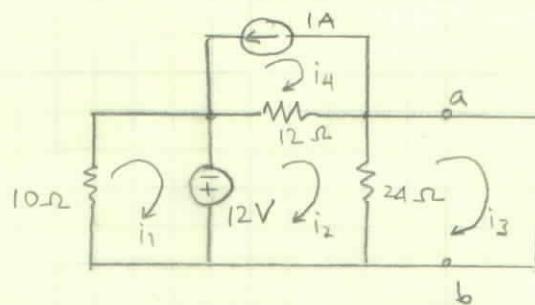

(i) Using mesh analysis:

mesh 1:

$$10i_1 - 12V = 0$$

$$10i_1 = 12$$

$$i_1 = 1.2A$$

mesh 2:

$$12V + 12(i_2 - i_4) + 24(i_2 - i_3) = 0, i_4 = -1A$$

$$12i_2 + 12 + 24i_2 - 24i_3 = -12$$

$$36i_2 - 24i_3 = -24 \quad \text{--- } \textcircled{1}$$


mesh 3:

$$24(i_3 - i_2) = 0$$

$$i_2 = i_3 \quad \text{--- } \textcircled{2}$$

Solving for $\textcircled{1}$ and $\textcircled{2}$, we get $i_3 = i_{sc} = I_N = \underline{\underline{-2A}}$.


Therefore, the Norton equiv. circuit.

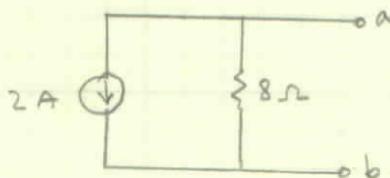

This verify that $i_{sc} = I_N = -2A = -\frac{16V}{8\Omega} = \frac{V_{TH}}{R_{TH}}$.

(b) The 10Ω resistor has no effect on the equiv. ckt because the voltage across the $12V$ source is independent of the resistor value.

P 2.83.

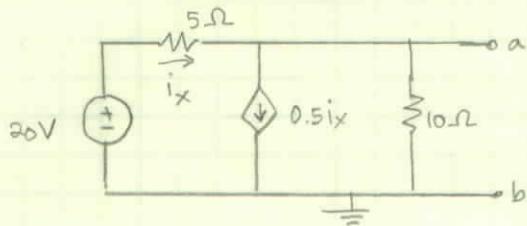

Find Thévenin & Norton Equiv. ckt.

ANSWER(i) Use nodal analysis w/ V_b as Ref. Node.

$$\frac{Va}{10} + \frac{Va-20}{5} + 0.5ix = 0, \text{ but } ix = \frac{20-Va}{5}$$


$$\frac{Va}{10} + \frac{Va-20}{5} + \frac{20-Va}{10} = 0 \quad \times 10$$

$$2Va - 20 = 0$$

$$2Va = 20$$

$$Va = \underline{\underline{10 \text{ V}}} = V_{DC} = V_{TH}$$


(ii) For the short circuit condition:

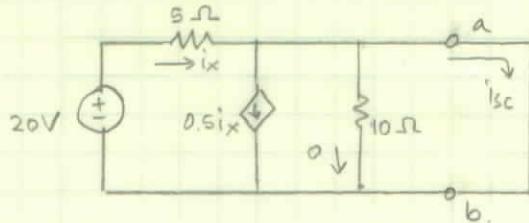


$$ix = \frac{20 \text{ V}}{5\Omega} = 4 \text{ A} \rightarrow Isc = ix - 0.5ix \\ = 0.5ix \\ = \underline{\underline{2 \text{ A}}}$$

$$\text{Therefore, } R_{Th} = \frac{V_{DC}}{Isc} = \frac{10 \text{ V}}{2 \text{ A}} = \underline{\underline{5 \Omega}}$$


The Thévenin equiv. ckt

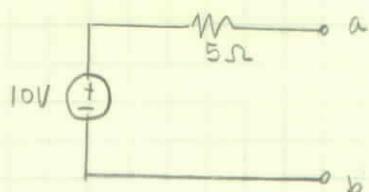

The Norton equiv. ckt

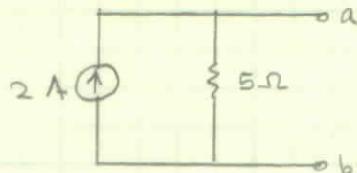


P 2.85.

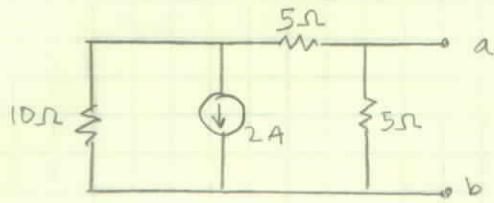

FIND the max. power that can be delivered to a RESISTIVE LOAD by the circuit.

ANSWER

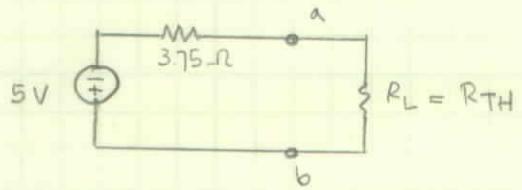From P 2.78 we got the Thevenin equiv. circuit :




$$V_L' = V_{TH} \frac{R_{TH}}{2R_{TH}} = \frac{\sqrt{V_{TH}}}{2}$$


Then, the maximum power is obtained for a Load Resistance EQUAL to R_{TH} .

$$P_{max} = \frac{V^2}{R} = \frac{(V_{TH}/2)^2}{R_{TH}} = \frac{(5/2)^2}{3.75} = \underline{\underline{1.667 \text{ W}}}$$

P 2.89

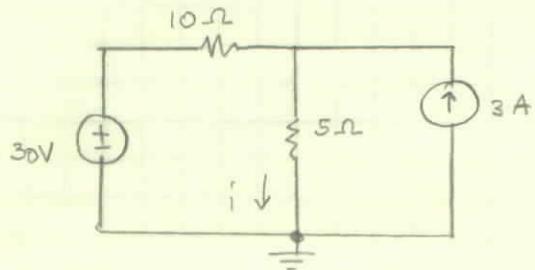
Find i using superposition principle.

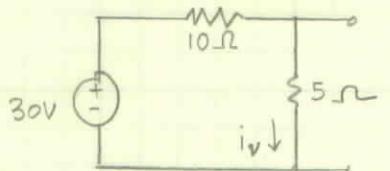(i) turn off the current source, leave the 30V on.



$$i_v = \frac{30V}{(10+5)\Omega} = 2A$$

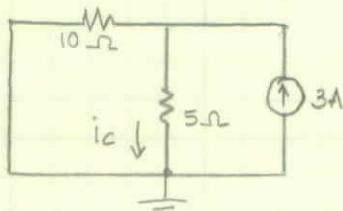(ii) turn off the voltage source, leave the 3A source on.



$$i_c = \frac{10}{10+5} (3A) \\ = 2A$$

Therefore, $i = i_v + i_c$
 $= (2+2)A$
 $= 4A$