

A Prelude

• Complex Numbers

- Euler's identity

$$e^{jx} = \cos x + j \sin x$$

$$\operatorname{Re}[e^{jx}] = \cos x$$


$$\operatorname{Im}[e^{jx}] = \sin x$$

- rectangular form

$$a + jb$$

on a calculator; (a, b)

graphic plot

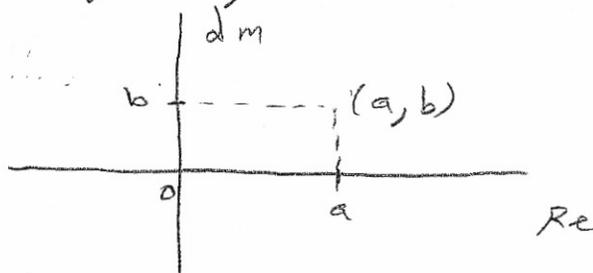


- polar form

$$M \angle \theta$$

on a calculator; $(M \angle \theta)$

graphic plot

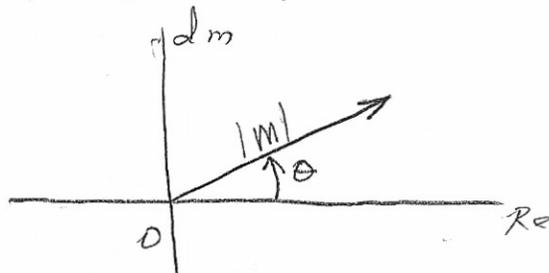

- relationship between rectangular and polar

$$a + jb = \sqrt{a^2 + b^2} \angle \tan^{-1}(b/a)$$

- the exponential form

$$e^{j\theta} \triangleq 1 \angle \theta$$

by
definition

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$|e^{j\theta}| = |\cos \theta + j \sin \theta|$$
$$= \sqrt{\cos^2 \theta + \sin^2 \theta}$$

$$|e^{j\theta}| = 1$$

* of note;

$$e^{j(\omega t + \psi)} = e^{j\omega t} \cdot e^{j\psi}$$

$$\text{Re} [e^{j(\omega t + \psi)}] = \cos(\omega t + \psi)$$

* of Note

$$e^{j90} = \cos 90 + j \sin 90 = j$$

$$e^{j90} = 1 \angle 90 = j$$

* of Note

$$j^2 = j \cdot j = 1 \angle 90^\circ \cdot 1 \angle 90^\circ = 1 \angle 180^\circ = -1$$

$$j^2 = -1$$

Also,

$$j^3 = j^2 \cdot j = -j = 1 \angle -90^\circ$$

$$j^4 = j^2 \cdot j^2 = (-1)(-1) = 1$$

- Calculator Exercises

Note; You need a TI 86, 89 vintage

Perform

$$(20 + j30) * (6 + j25)$$

Express in rectangular and polar form

On the calculator (set to rectangular)

$$(20, 30) * (6, 25) \text{ enter}$$

Ans: $-630 + j680$ rectangular

$926.98 \angle 132.8$ polar

Perform

$$\frac{320 \angle 65}{6 + j8}$$

On the calculator

$$(320 \angle 65) \div (6, 8) \text{ enter}$$

Ans: $31.3 + j6.58$ rectangular

$32 \angle 11.87^\circ$ polar

- converting cosine, sine functions

Suppose you have

<u>given</u>	<u>want</u>
--------------	-------------

$\cos(30^\circ)$	$\sin(?)$
------------------	-----------


$\sin(-60^\circ)$	$\cos(?)$
-------------------	-----------

$\sin(\omega t + 60^\circ)$	$\cos(\omega t + ?)$
-----------------------------	----------------------

If you go back to basic trig relationships you can perform the above operations.


However, there is a simple technique for doing this, as presented below.

Express the quadrant axis as below

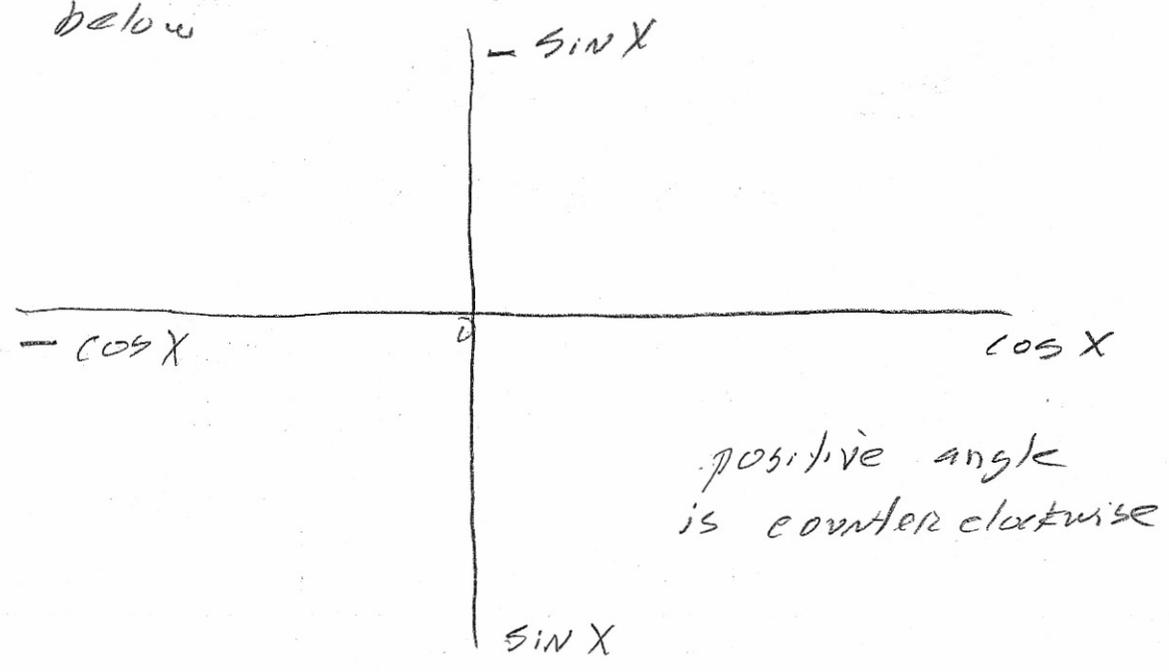

GIVEN

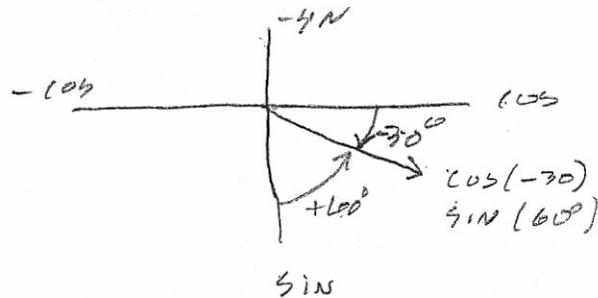
$$\cos(-30^\circ) \xrightarrow{?} \sin(?)$$



$$\therefore \cos(-30^\circ) = \sin(60^\circ)$$

GIVEN
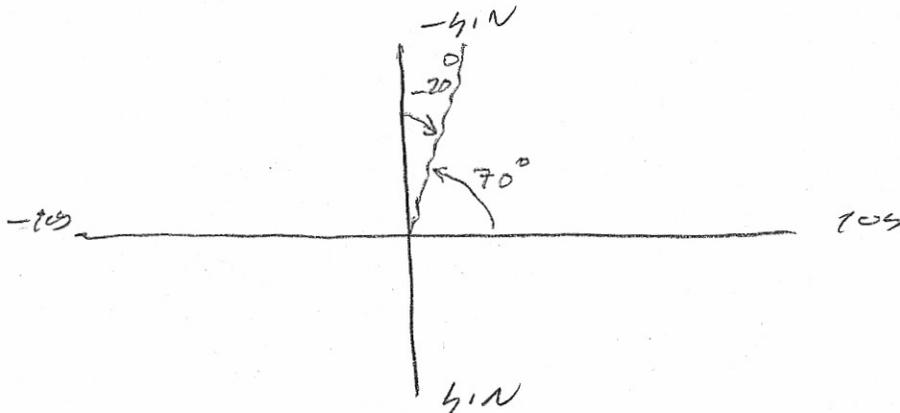
$$-4 \sin(\omega t - 20^\circ) \xrightarrow{\text{convert to cosine form}}$$



$$-4 \sin(\omega t - 20^\circ) = 4 \cos(\omega t + 70^\circ)$$

We need to know how to do the above when dealing with AC voltage and current sources expressed in the time domain.


PHASORS - AND BACKGROUND:

These notes give a very abbreviated background on the theory (analysis) of circuits with sinusoidal sources.

In AC circuits we are nearly always interested in the steady state solution.

Illustrating

Given

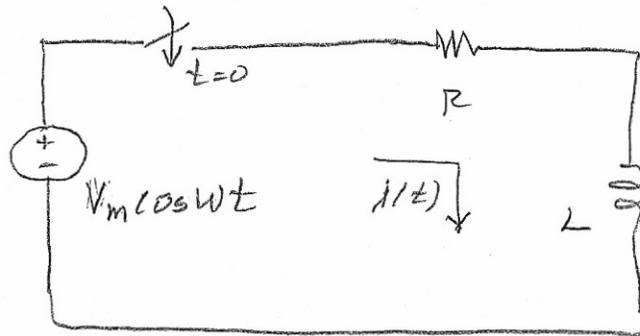

Solve for $i(t)$

$$Ri(t) + L \frac{di}{dt} = V_m \cos \omega t$$

$$\frac{di}{dt} + \frac{R}{L} i(t) = \frac{V_m}{L} \cos \omega t \quad (A)$$

change the source to $\frac{V_m}{L} e^{j\omega t}$

find $\hat{i}(t)$, Take $\text{Re}[\hat{i}(t)]$ to

get the answer to (A)

$$\frac{d\hat{i}}{dt} + \frac{R}{L} \hat{i}(t) = \frac{V_m}{L} e^{j\omega t}$$

$$\hat{i} = \hat{i}_t + \hat{i}_{ss}$$

\hat{i}_{ss} Assume

$$\hat{i}_{ss} = k e^{j\omega t}$$

$$\frac{d}{dt} [k e^{j\omega t}] + \frac{R}{L} k e^{j\omega t} = \frac{V_m}{2} e^{j\omega t}$$

$$k j\omega e^{j\omega t} + \frac{R}{L} k e^{j\omega t} = \frac{V_m}{2} e^{j\omega t}$$

$$k = \frac{V_m / L}{\frac{R}{L} + j\omega} = \frac{V_m}{R + j\omega L}$$

$$\hat{i}_{ss} = \left[\frac{V_m}{R + j\omega L} \right] e^{j\omega t} \quad (B)$$

$$\hat{i}_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} e^{-j\theta} e^{j\omega t}$$

$$\hat{i}_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} e^{j(\omega t - \theta)} \quad \theta = \tan^{-1} \frac{\omega L}{R}$$


We want the real part of this

$$i_{ss} = \text{Re}[\hat{i}_{ss}] = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t - \theta)$$

$$i_t = k e^{-\frac{R}{L} t}$$

$$i(t) = k e^{-\frac{R}{L} t} + \frac{V_m \cos(\omega t - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

+ TRANSIENT part
steady state part

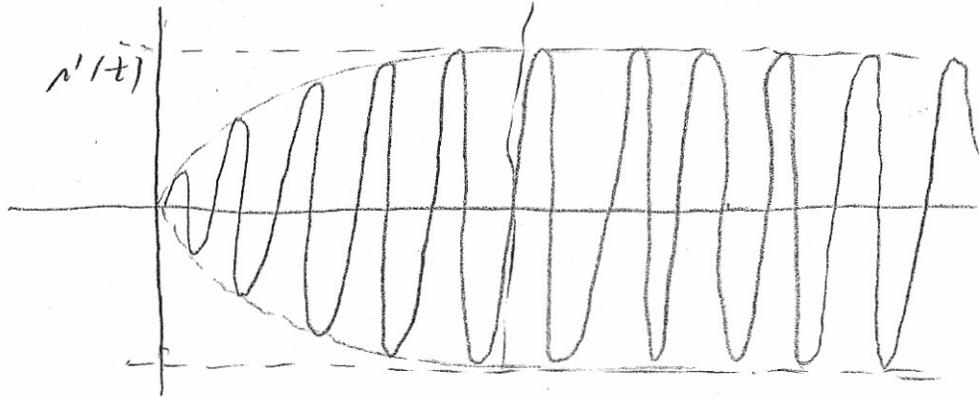

→ steady state

In AC circuits we are mainly interested in the steady state. It turns out there is not a need to express as a differential equation. We express things in phasor form and basically use all the theorems and techniques we learned for dc circuits.

So what is a phasor?


$$\text{Let } v(t) = V_m \cos(\omega t + \theta)$$

then

$$v(t) = \text{Re} [V_m e^{j(\omega t + \theta)}]$$

$$= \text{Re} [V_m \cdot e^{j\theta} \cdot e^{j\omega t}]$$
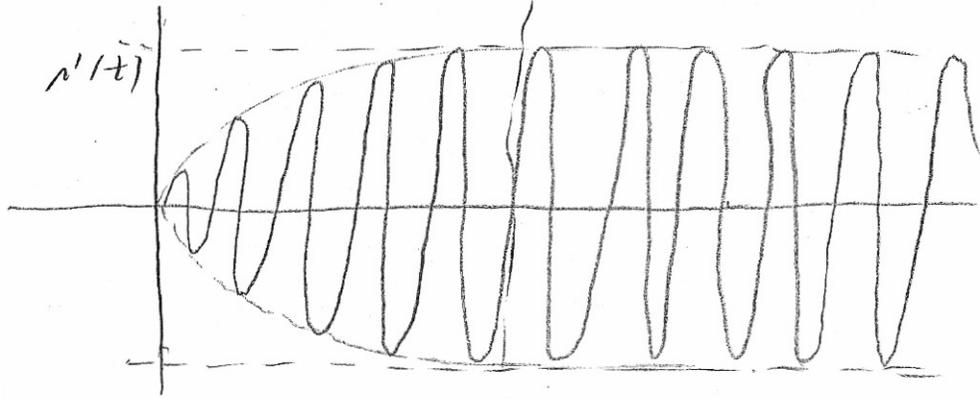
$$v(t) = \text{Re} [\hat{V} e^{j\omega t}]$$



→ steady state

In AC circuits we are mainly interested in the steady state. It turns out there is not a need to express as a differential equation. We express things in phasor form and basically use all the theorems and techniques we learned for dc circuits.

So, what is a phasor?

$$\text{Let } v(t) = V_m \cos(\omega t + \theta)$$

then

$$v(t) = \text{Re} [V_m e^{j(\omega t + \theta)}]$$

$$= \text{Re} [V_m \cdot e^{j\theta} \cdot e^{j\omega t}]$$

$$v(t) = \text{Re} [\hat{V} e^{j\omega t}]$$


We define

\hat{V} as a phasor


$$\hat{V} = V_m e^{j\theta} = V_m \angle \theta$$

\hat{V} is not a vector. It does not obey the rules of vector analysis (product, cross product)

\hat{V} is a number at an angle

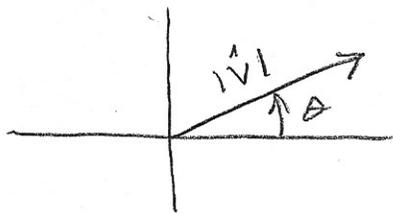

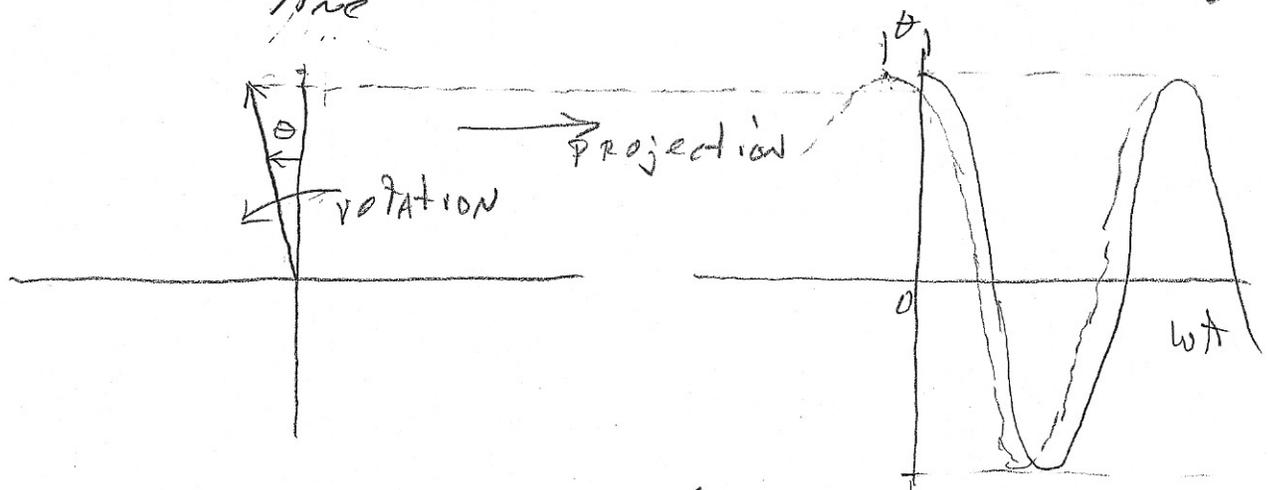The sinor $[\hat{V} e^{j\omega t}]$ is a rotating line



Illustrating A sinor

Going from Phasor To Time Domain

PHASOR

Time Domain


$$V_m \angle \theta$$



$$V_m \cos(\omega t + \theta)$$

A PHASOR DIAGRAM
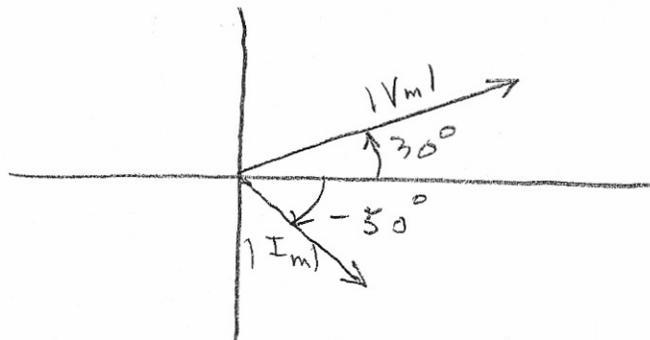
$$\vec{V} = V_m \angle 30^\circ, \quad \vec{I} = I_m \angle -50^\circ$$



Notes: Voltage & current must have a different scale.

We will use the above in AC circuit analysis.

We now turn our attention to formulating the AC circuit as a phasor problem.

Phasor Relations of Circuit Elements

11

The resistor

Assume

$$v(t) = i(t) R$$

$$i(t) = I_m \cos(\omega t + \theta_R)$$

$$\hat{I} = I_m \angle \theta_R$$



$$= I_m \cos(\omega t + \theta_R) R$$

$$= \text{Re} [I_m R e^{j\theta_R} \cdot e^{j\omega t}]$$


$$= \text{Re} [\hat{V} e^{j\omega t}]$$

$$\hat{V} = I_m \angle \theta_R R = \hat{I} R$$

AC Ohm's Law for a resistor

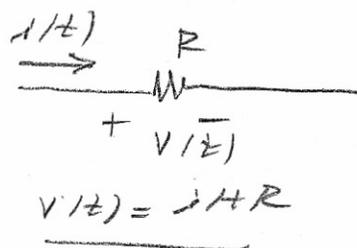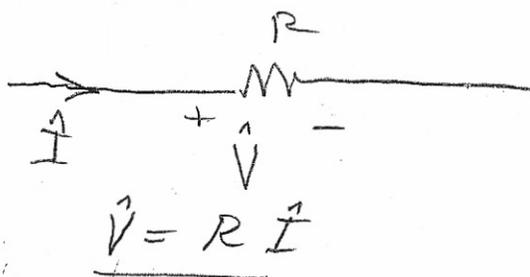

The Inductor

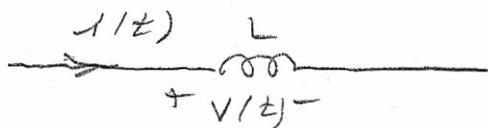

$$v(t) = L \frac{di}{dt}$$

Assume

$$i(t) = I_m \cos(\omega t + \theta_L) \quad \hat{I} = I_m \angle \theta_L$$

$$v(t) = -\omega L I_m \sin(\omega t + \theta_L)$$

$$v(t) = -\omega L I_m \sin(\omega t + \theta_L)$$

$$= \omega L I_m \cos(\omega t + 90^\circ + \theta_L)$$

$$v(t) = \operatorname{Re} \left[\omega L I_m e^{j(\omega t + 90^\circ + \theta_L)} \right]$$

$$= \operatorname{Re} \left[\omega L I_m e^{j\theta_L} \cdot e^{j90^\circ} \cdot e^{j\omega t} \right]$$


$$= \operatorname{Re} \left[\hat{V} e^{j\omega t} \right]$$

$$\hat{V} = \omega L I_m \underline{\angle \theta_L} \cdot j$$

$$\hat{V} = j\omega L I_m \underline{\angle \theta_L}$$

$$\hat{V} = j\omega L \hat{I}$$

AC Ohm's Law for an inductor

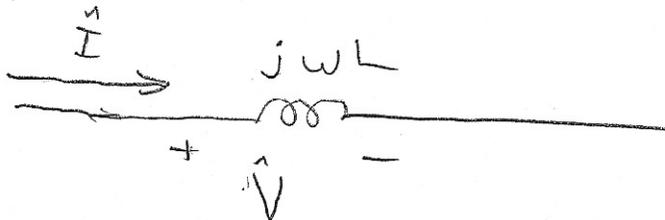

The diagram shows a horizontal wire representing an inductor. Above the wire, an arrow labeled \hat{I} points to the right. Below the wire, a plus sign is on the left and a minus sign is on the right, with a voltage \hat{V} indicated between them. A resistor symbol is drawn above the wire, with $j\omega L$ written above it.

$$\underline{\hat{V} = j\omega L \hat{I}}$$

The Capacitor

$$\text{Let } v_c(t) = V_m \cos(\omega t + \theta_c)$$

$$\hat{V}_c = V_m \underline{\angle \theta_c}$$

Now recall


$$i(t) = C \frac{dv_c}{dt}$$

$$\begin{aligned}
 i(t) &= -\omega C V_m \sin(\omega t + \theta_c) \\
 &= \omega C V_m \cos(\omega t + 90^\circ + \theta_c) \\
 &= \operatorname{Re}[\omega C V_m e^{j90^\circ} \cdot e^{j\theta_c} \cdot e^{j\omega t}]
 \end{aligned}$$

$$\hat{I} = j\omega C V_m \angle \theta_c = j\omega C \hat{V}$$


$$\hat{V} = \left[\frac{1}{j\omega C} \right] \times \hat{I}$$

Ohm's Law
for the
capacitor

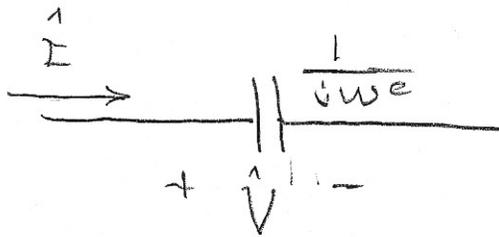


Impedance and Admittance


We have developed the following:

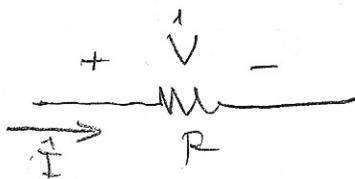

$$\frac{\hat{V}}{\hat{I}} = R$$

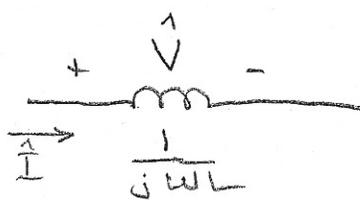

$$\frac{\hat{V}}{\hat{I}} = j\omega L$$

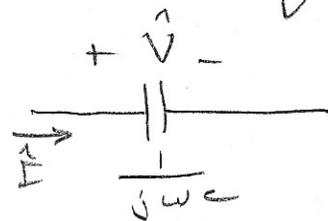

$$\frac{\hat{V}}{\hat{I}} = \frac{1}{j\omega C}$$

In a more general sense

we say


$$\frac{\hat{V}}{\hat{I}} = \hat{Z}$$

where \hat{Z} is impedance, (units of Ohms)

$$\hat{Z} = R + jX$$


resistance
(ohms)

reactance
(ohms)

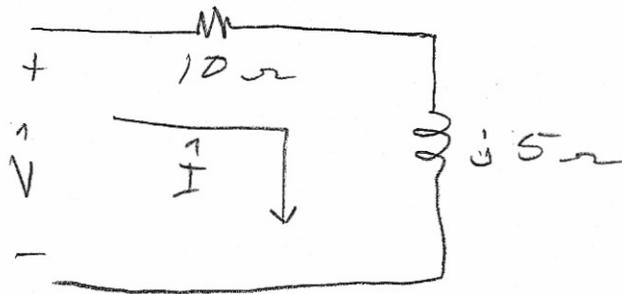

$$\hat{V} = (10 + j5) \hat{I}$$

$$\hat{Z} = (10 + j5) \text{ ohms}$$

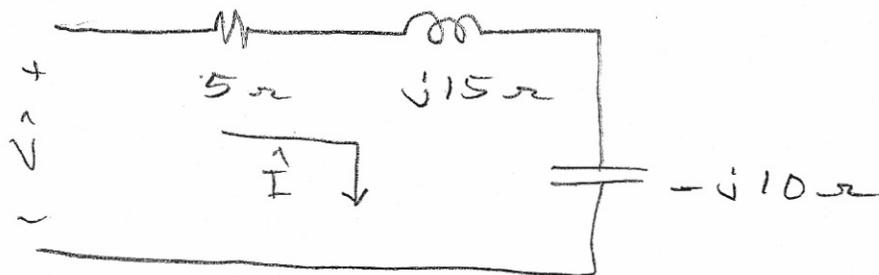

$$\hat{V} = (5 + j15 - j10) \hat{I} = (5 + j5) \hat{I}$$

$$\hat{Z} = (5 + j5) \Omega$$

We define admittance as

$$\hat{Y} = \frac{1}{\hat{Z}} = G + jB \quad (S)$$

conductance
susceptance
(S)
(S)


$Y \rightarrow$ Admittance (siemen, S)

$G \rightarrow$ conductance (siemen, S)


$B \rightarrow$ susceptance (siemen, S)

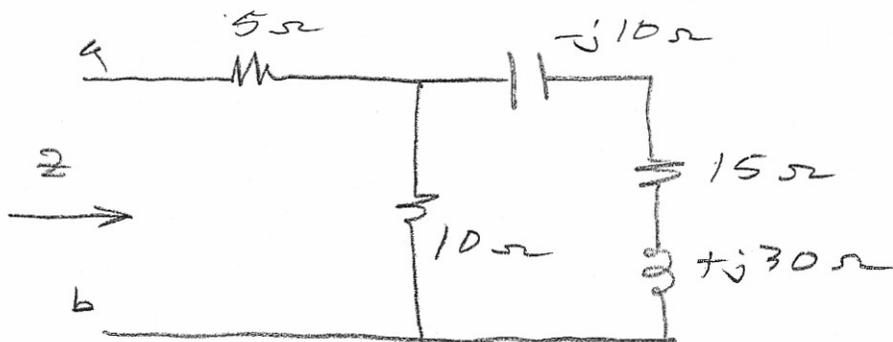Example 1

Find the impedance seen looking into terminals a-b




This becomes

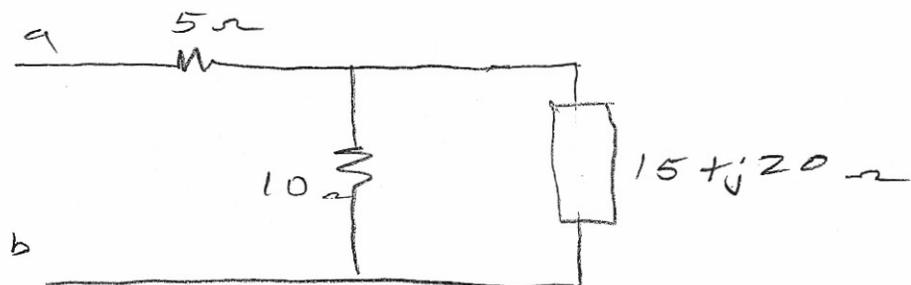

$$\begin{aligned}
 Z &= 5 + 10 \parallel (15 + j20) \\
 &= 5 + \frac{10 \times (15 + j20)}{10 + 15 + j20} \\
 &= 5 + 7.56 + j1.95 \, \Omega \\
 &= 12.56 + j1.95 \, \Omega \\
 \hat{Z} &= 12.74 \angle 8.8^\circ \, \Omega
 \end{aligned}$$

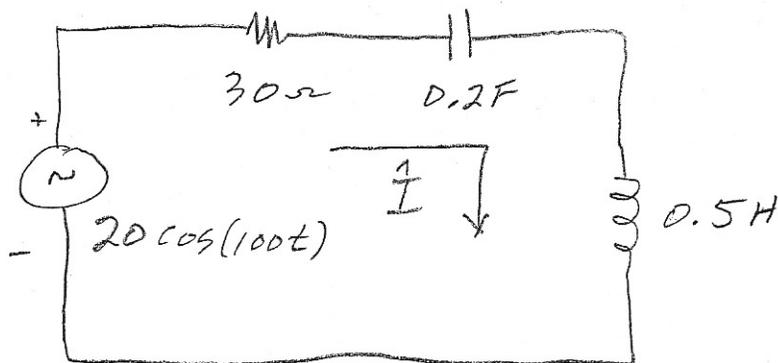From this point it is an easy step to move to solution of A.C. Circuits. We do this in the next lesson. Think about the following.



Find the phasor current \hat{I} .