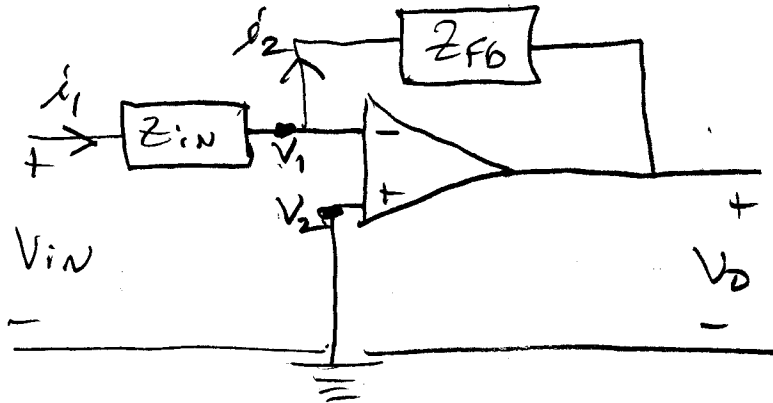


Active Filters

We consider active filters from the standpoint of using op-amps. As a quick review we recall the following:

Inverting Op-Amp




Assumptions

$$\begin{aligned}
 V_1 &= V_2 \\
 R_i &= \infty \\
 R_o &= 0 \\
 i_1 &= -i_2
 \end{aligned}$$

$$\frac{V_{in}}{Z_{in}} = -\frac{V_o}{Z_{fb}} \Rightarrow \boxed{\frac{V_o}{V_{in}} = -\frac{Z_{fb}}{Z_{in}}}$$

Non-Inverting Op-Amp

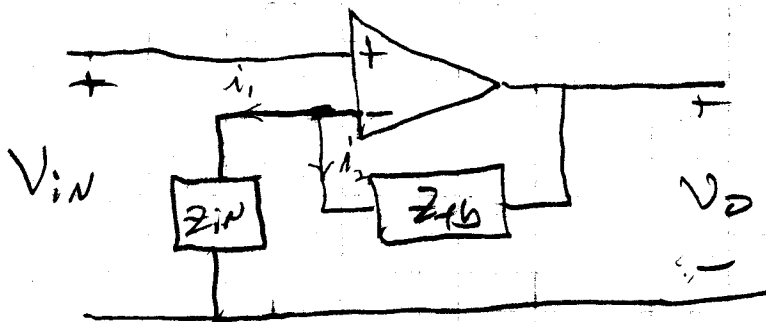

$$i_1 + i_2 = 0$$

$$i_1 = \frac{V_{in}}{Z_{in}}$$


$$i_2 = \frac{V_{in} - V_o}{Z_{fb}}$$

So,
$$\frac{V_{in} - V_o}{Z_{fb}} = -\frac{V_{in}}{Z_{in}} \Rightarrow V_{in} \left[\frac{Z_{in} + Z_{fb}}{Z_{in}Z_{fb}} \right] = \frac{V_o}{Z_{fb}}$$

$$\boxed{\frac{V_o}{V_{in}} = \left[1 + \frac{Z_{fb}}{Z_{in}} \right]}$$

First Order Low Pass Filter

Consider the following circuit.

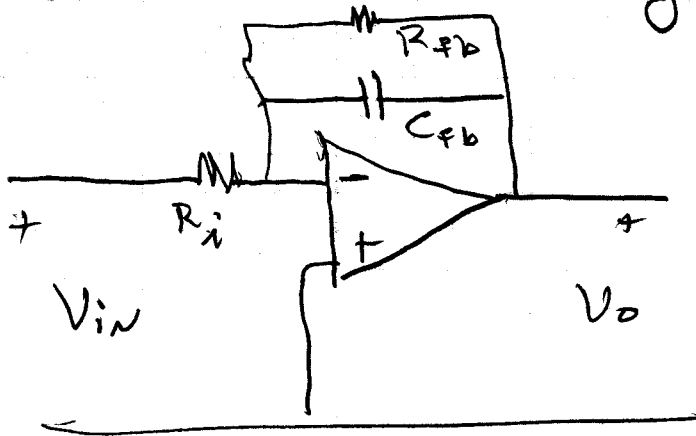

$$Z_{fb} = R_{fb} \parallel \frac{1}{sC_{fb}} = \frac{R_{fb}}{sC_{fb}} = \frac{R_{fb}}{R_{fb} + \frac{1}{sC_{fb}}} = \frac{R_{fb}}{1 + sR_{fb}C_{fb}}$$

$$\frac{V_o}{V_{in}} = \frac{Z_{fb}}{Z_{in}} = \frac{R_{fb}}{R_i [1 + sR_{fb}C_{fb}]} \Big|_{s=j\omega} = \frac{R_{fb}}{R_i} \left(\frac{1}{1 + j\omega R_{fb}C_{fb}} \right)$$

This is a low pass filter.

The -3dB breakpoint is at

$$\omega = \frac{1}{R_{fb}C_{fb}}$$


This filter has a dc gain of

$\frac{R_{fb}}{R_i}$ which could have an

absolute value > 1 (if $R_{fb} > R_i$).

First Order High Pass Filter:

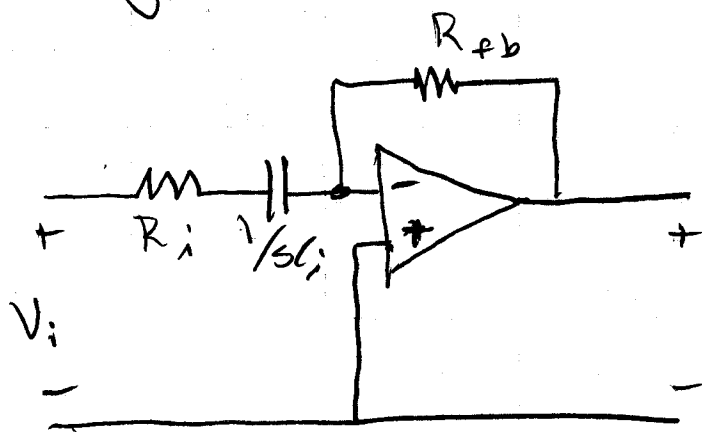As shown below, the following op-amp configuration.




$$\frac{V_o(s)}{V_i(s)} = - \left[\frac{R_{fb}}{R_i + \frac{1}{sC_i}} \right] = \frac{-sR_{fb}C_i}{1 + sR_iC_i}$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = - \left[\frac{j\omega R_{fb}C_i}{1 + j\omega R_iC_i} \right]$$


The dc gain of this filter is zero.

Bode shape

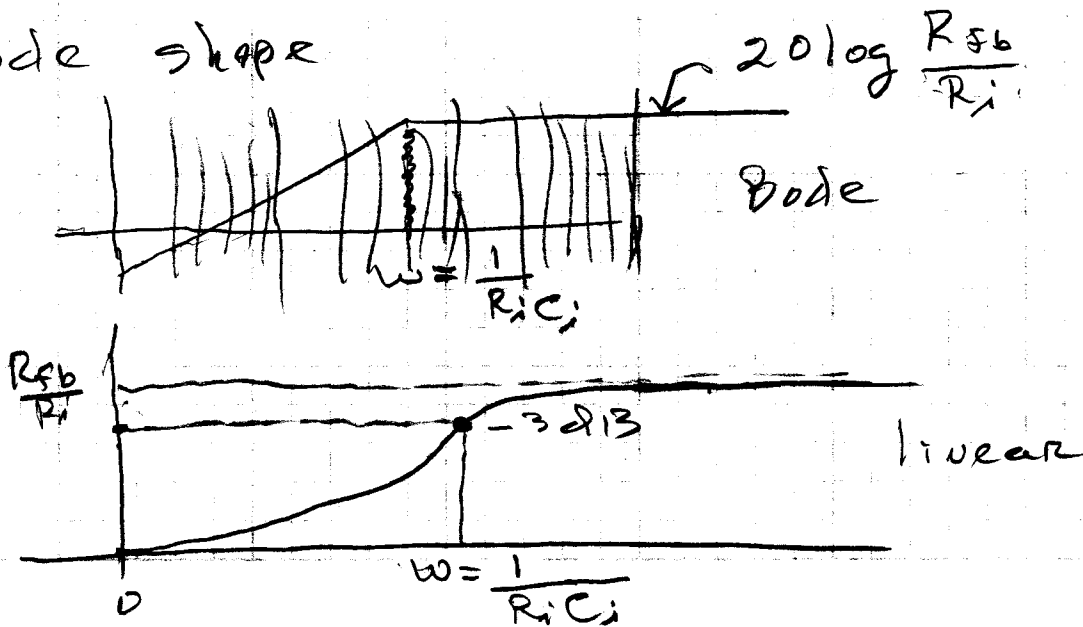


Bandpass Filter

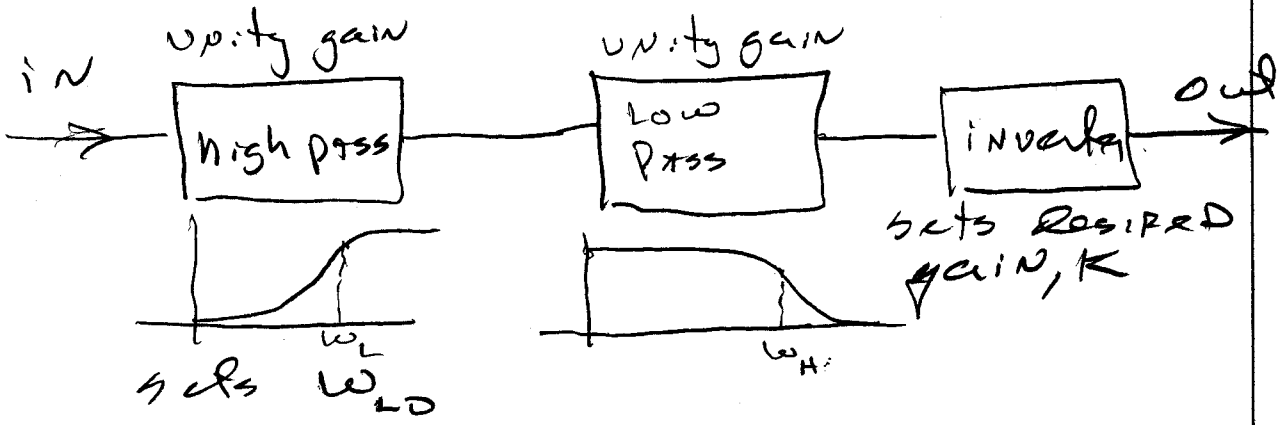An easy way to understand a method for designing a bandpass filter is to think of it as follows,



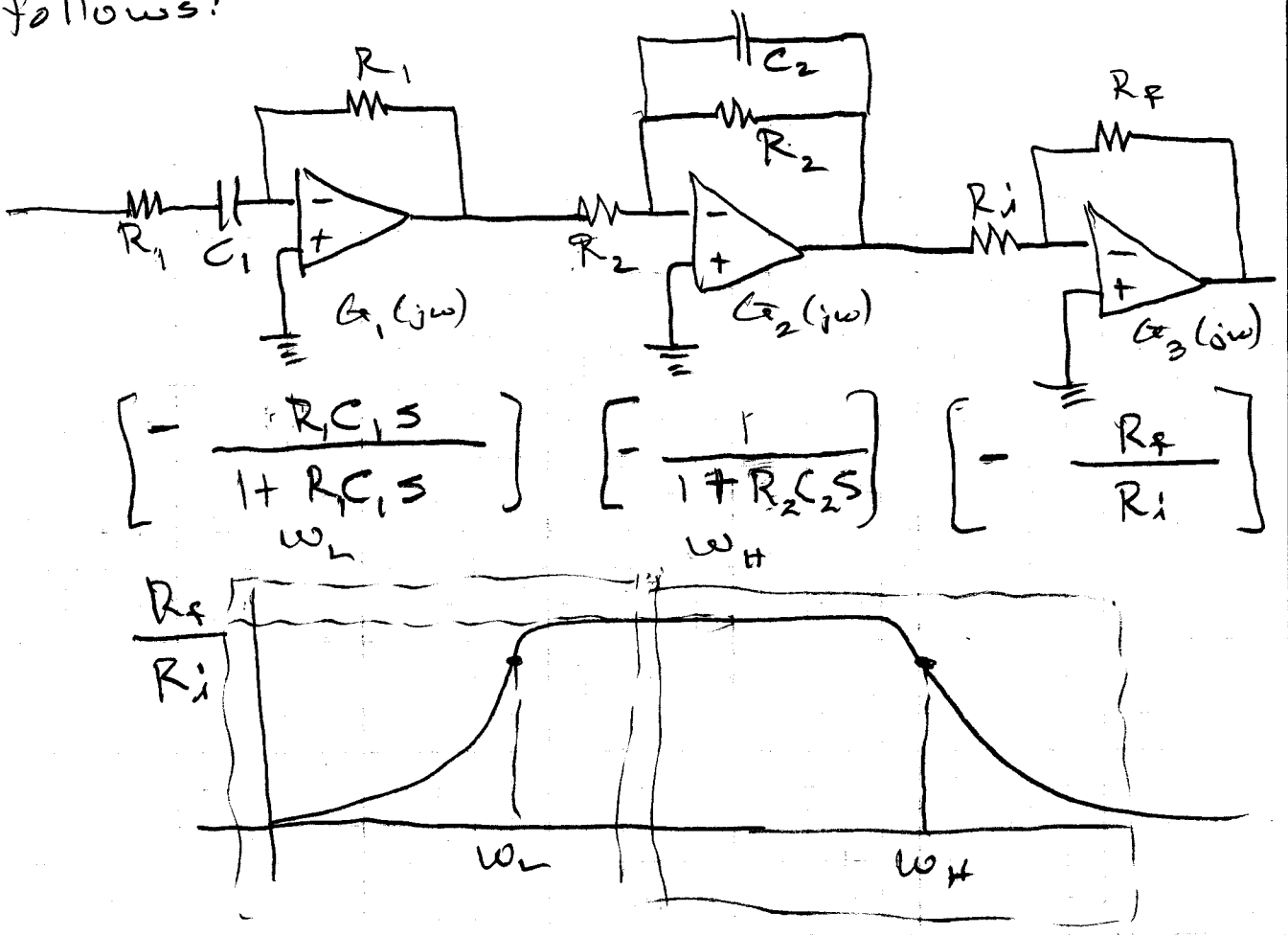This diagram can be constructed as follows:



CONTINUED:

FOR THIS PREVIOUS DESIGN WE KNOW

$$\omega_H = \frac{1}{R_2 C_2} \quad \omega_L = \frac{1}{R_1 C_1}$$

The center frequency, ω_0 , is related to ω_1 and ω_2 as for the series resonant circuit:

$$\omega_0 = \sqrt{\omega_L \omega_H}$$

and

$$B = \omega_H - \omega_L$$

and

$$Q = \frac{\omega_0}{B}$$

we can set the amplification mid frequency gain:

We have $G_c(j\omega) = G_{c1}(j\omega) G_{c2}(j\omega) G_{c3}(j\omega)$

So,

$$G_c(j\omega) = \frac{(-j\omega/\omega_L) \left(\frac{R_f}{R_i}\right)}{(1+j\omega/\omega_L)(1+j\omega/\omega_H)} = \frac{(-j\omega\omega_H) \left(\frac{R_f}{R_i}\right)}{(\omega_L + j\omega)(\omega_H + j\omega)}$$



$$G_c(j\omega) = \frac{-j\omega\omega_H \left(\frac{R_f}{R_i}\right)}{(\omega_L\omega_H + j\omega(\omega_L + \omega_H) - \omega^2)}$$

At the center frequency, $\omega = \omega_0 = \sqrt{\omega_L\omega_H}$

$$G_c(j\omega_0) = \frac{R_f}{R_i} \frac{\omega_H}{\omega_L + \omega_H} = A_{\text{desired}}$$

What do you want the filter gain at ω_0 to be? This is $= A$. Then solve for $\frac{R_f}{R_i}$

BANDSTOP Filter

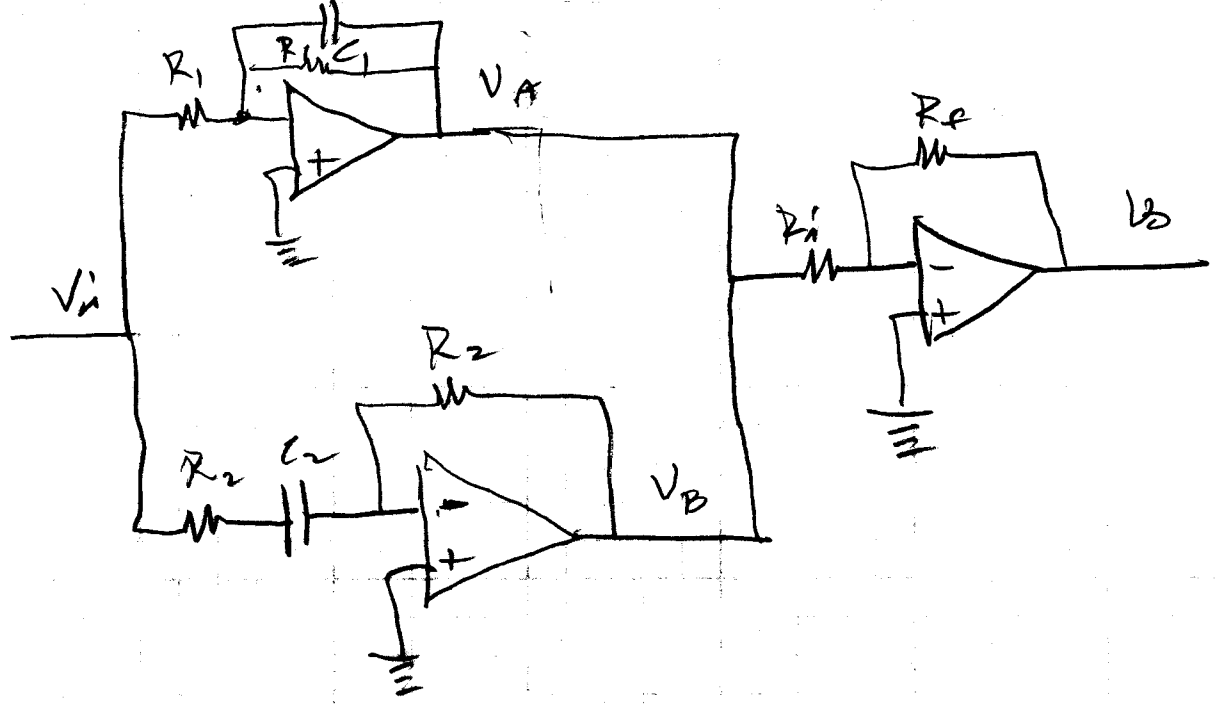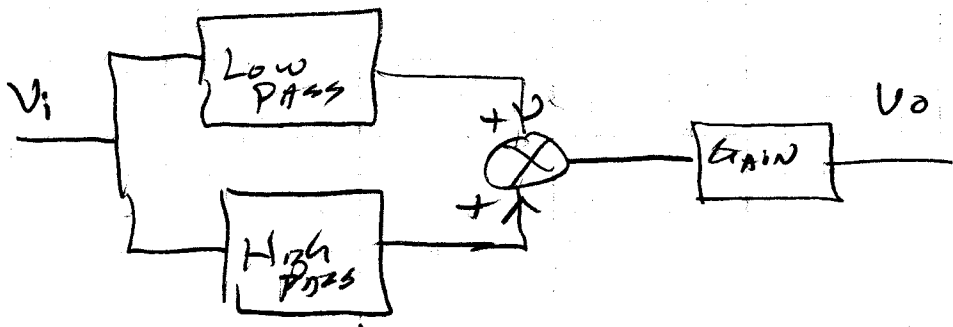

$$\begin{aligned}
 H(s) &= \left[\frac{1}{1 + sR_1C_1} + \frac{sR_2C_2}{1 + sR_2C_2} \right] \frac{R_f}{R_i} \\
 &= \left[\frac{1}{1 + s/\omega_1} + \frac{s/\omega_2}{1 + s/\omega_2} \right] \frac{R_f}{R_i} + \dots \\
 &= \left[\frac{1 + s/\omega_2 + s/\omega_2 + s^2/\omega_1\omega_2}{(1 + s/\omega_1)(1 + s/\omega_2)} \right] \frac{R_f}{R_i} \\
 &= \left[\frac{1 + 2s/\omega_2 + s^2/\omega_1\omega_2}{1 + s(1/\omega_1 + 1/\omega_2) + s^2/\omega_1\omega_2} \right] \frac{R_f}{R_i}
 \end{aligned}$$

$$\text{Let } s \rightarrow j\omega$$

P.7

$$H(j\omega) = \frac{R_f}{R_i} \left[\frac{1 + j2\omega \left(\frac{1}{\omega_2}\right) + (j\omega)^2 / \omega_1 \omega_2}{1 + j\omega \left(\frac{1}{\omega_1} + \frac{1}{\omega_2}\right) + (j\omega)^2 / \omega_1 \omega_2} \right]$$

$$H(0) = \frac{R_f}{R_i}$$

$$H(\infty) = \frac{R_f}{R_i}$$

$$H(j\omega_0) = \frac{R_f \left(1 + j2\omega_0 / \omega_2 - \omega_0^2 / \omega_1 \omega_2 \right)}{R_i \left(1 + j\omega_0 \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) - \omega_0^2 / \omega_1 \omega_2 \right)}$$


$$\omega_0^2 = \omega_1 \omega_2$$

$$\begin{aligned} H(j\omega_0) &= \frac{R_f}{R_i} \left[\frac{j2\omega_0 / \omega_2}{j\omega_0 \left[\frac{1}{\omega_1} + \frac{1}{\omega_2} \right]} \right] \\ &= \frac{R_f}{R_i} \left[\frac{2}{\omega_2 \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right)} \right] \end{aligned}$$

$$H(j\omega_0) = \frac{R_f}{R_i} \left[\frac{2\omega_1}{\omega_1 + \omega_2} \right]$$

get $\frac{R_f}{R_i}$ as you want $H(j\omega_0)$

14.53

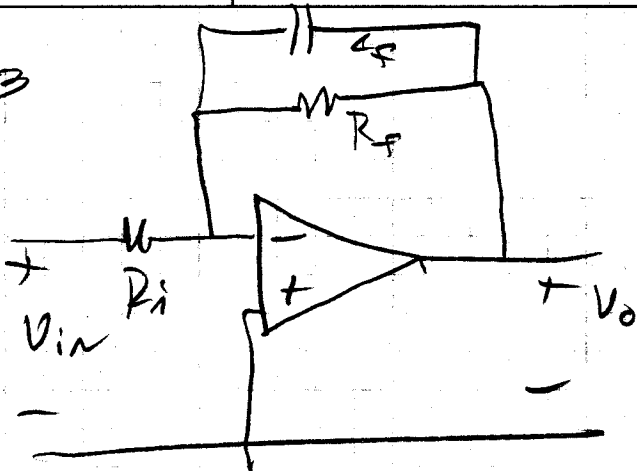

$$\frac{V_o}{V_{in}} = \frac{-R_f / sC_f}{R_i (R_f + 1/sC_f)}$$


$$\frac{V_o}{V_{in}} = -\frac{R_f}{R_i} \times \frac{1}{1 + sR_fC_f}$$

$$\frac{R_f}{R_i} = 0.5$$

$$\omega_c = \frac{1}{R_f C_f}$$

$$f_c = \frac{1}{2\pi R_f C_f}$$

Pr. 48

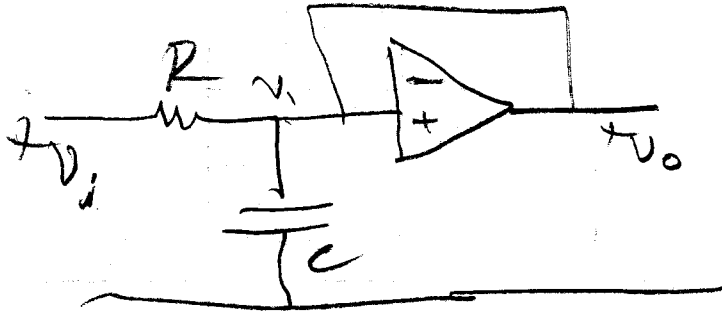


$$V_i = \frac{(1/sC) V_i}{R + 1/sC} = \frac{V_i}{1 + sRC}$$

$$V_i = V_o$$

$$\frac{V_o}{V_i} = \frac{1}{1 + sRC}$$

Pr. 49

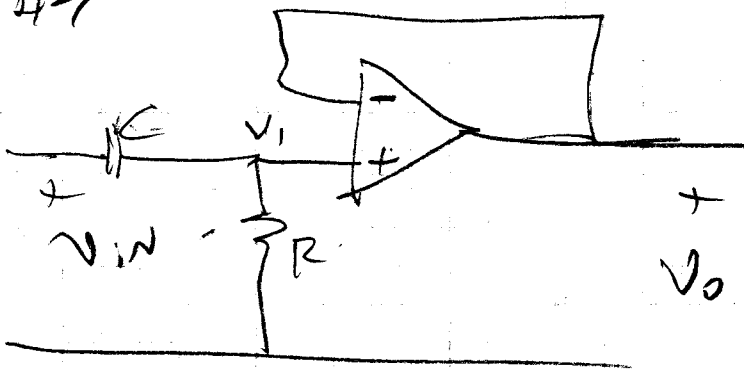

Low pass


$$\frac{V_i}{V_{in}} = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC}$$

$$V_i = V_o$$

$$\frac{V_o}{V_{in}} = \frac{sRC}{1 + sRC}$$

High pass

14.51

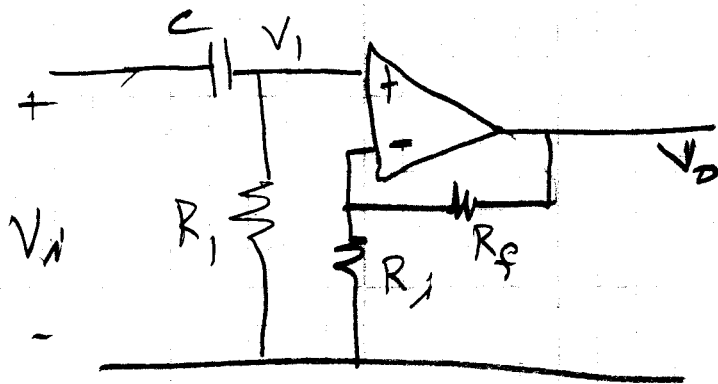

$$V_i = \frac{R_i}{R_i + \frac{1}{sC}} = \frac{sR_i C V_i}{1 + sR_i C}$$

$$V_i = V_o \times \frac{R_i}{R_i + R_f}$$

$$V_o \left[\frac{R_i}{R_i + R_f} \right] = \frac{sR_i C V_i}{1 + sR_i C}$$

$$\frac{V_o}{V_i} = \left[1 + \frac{R_f}{R_i} \right] \left[\frac{sR_i C}{1 + sR_i C} \right]$$