

wlg


ECE 202

3 Examples

Feb 20, 2002

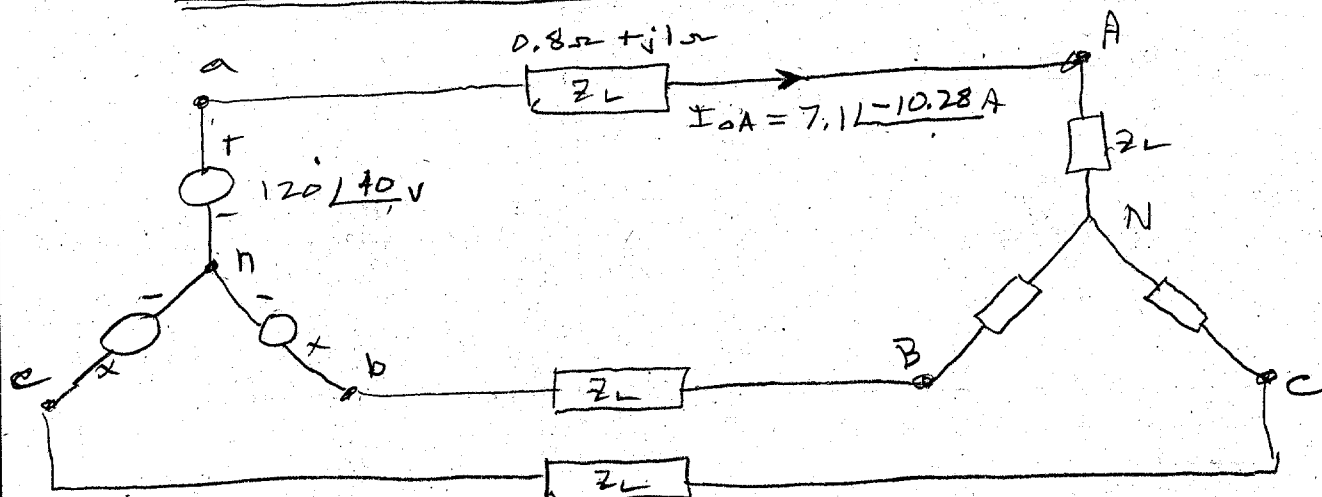10.71

Given a wye-wye system. (balanced)  
Draw the system (1)



Find: The load impedance  
Method 1

$$120\angle 40 = (0.8 + j1)(7.1\angle -10.28) + Z_L(7.1\angle -10.28)$$

$$Z_L = \frac{((120\angle 40) - (0.8 + j1)(7.1\angle -10.28))}{(7.1\angle -10.28)}$$

$$Z_L = 15.62\angle 50.19 = (10 + j12) \text{ ohms}$$

Method 2

$$Z_T = \frac{120\angle 40}{7.1\angle -10.28} = 10.8 + j13$$



$$Z_L = Z_T - Z_e = 10.8 + j13 - 0.8 - j1$$

$$Z_L = (10 + j12) \Omega$$

10.29

Balanced

(2)

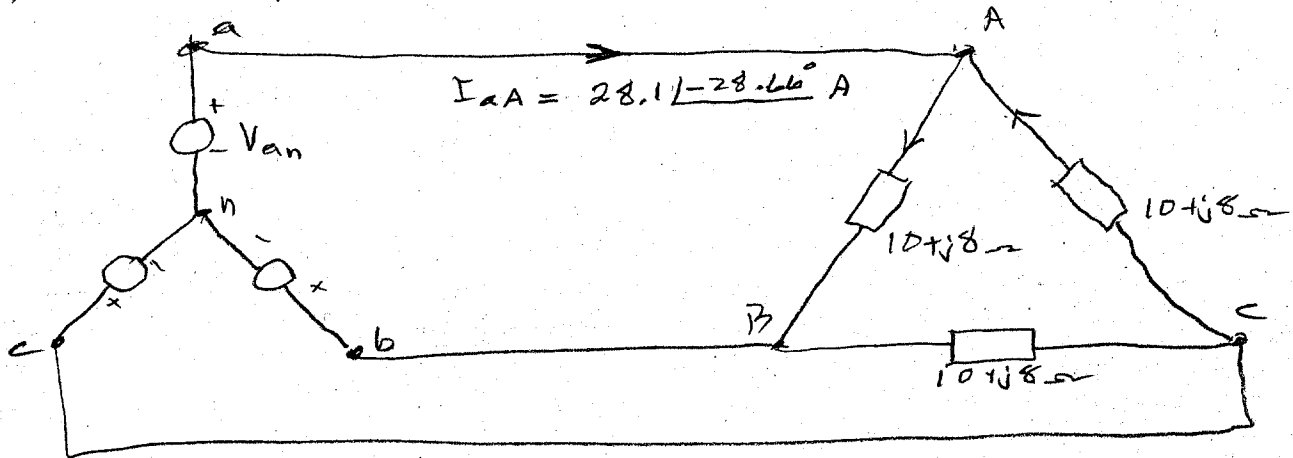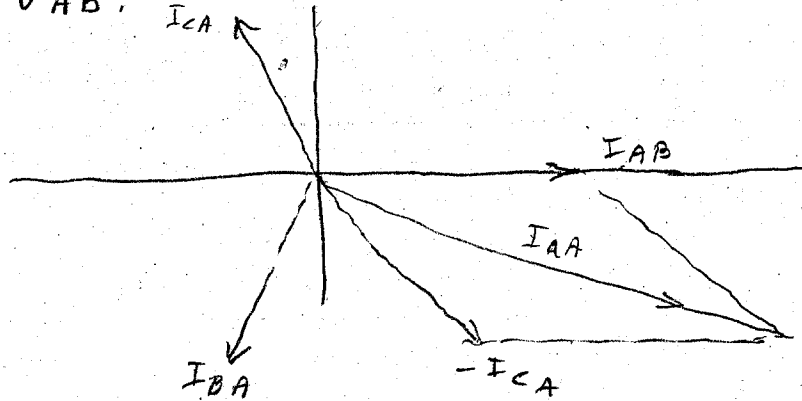Find  $V_{AB}$ ;  $I_{CA}$ 

$$I_{aA} = I_{AB} - I_{CA} = \sqrt{3} I_{AB} \angle -30^\circ$$

$$I_{AB} = \frac{I_{aA}}{\sqrt{3} \angle -30^\circ} = \frac{(28.11 \angle -28.66^\circ)}{\sqrt{3} \angle -30^\circ}$$

$$I_{AB} = 16.22 \angle 1.34^\circ \text{ A}$$


$$V_{AB} = Z_L I_{AB} = (10 + j8)(16.22 \angle 1.34^\circ)$$

$$V_{AB} = 207.7 \angle 40^\circ \text{ V}_{rms}$$

10.37

Balanced

3A

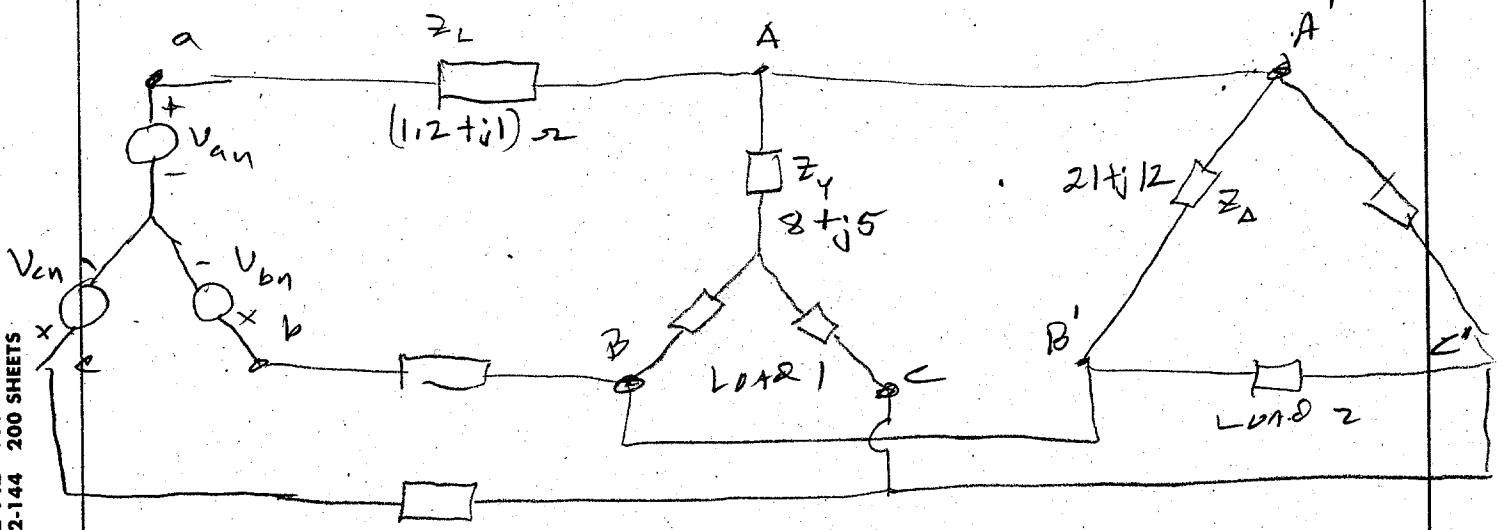

22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS




Given:  $V_{ab} = 208 \angle 60^\circ \text{ V}$

Find the phase currents to the wye load.


Approach: Put the system in a wye source, wye load 1, wye load 2
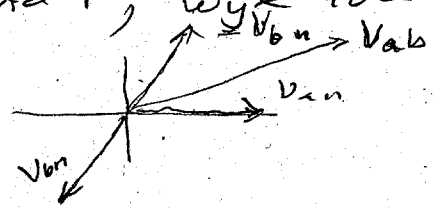
$$V_{an} = \frac{V_{ab} \angle -30^\circ}{\sqrt{3}}$$



$$V_{an} = 120 \angle 30^\circ$$
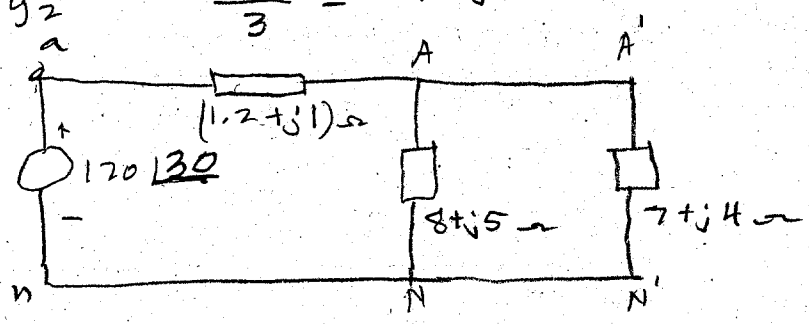
$$Z_{y2} = \frac{Z_{\Delta}}{3} = 7 + j4$$



$$Z_{\text{eff}} = \frac{(8 + j5)(7 + j4)}{15 + j4} = 4.35 \angle 30.79^\circ \Omega$$

10.37 cont.

$$I_{AA} = \frac{(120 \angle 30^\circ)}{((1.2 + j1) + (4.35 \angle 30.79^\circ))}$$

$$I_{AA} = 20.35 \angle -3.17^\circ \text{ A}$$

Use current splitting

$$I_{AN} = \frac{I_{AA} \times (7 + j4)}{15 + j9} = \frac{(20.35 \angle -3.17^\circ)(7 + j4)}{15 + j9}$$

$$I_{AN} = 9.38 \angle -4.4^\circ \text{ A rms}$$

$$I_{BN} = 9.38 \angle -124.4^\circ \text{ A rms}$$

$$I_{CN} = 9.38 \angle 115.6^\circ \text{ A rms}$$

How would you get the currents in the  $\Delta$  load impedances?


$$\text{Find } V_{AB} = I_{BB} Z_2 + V_{ab} - I_{AA} Z_2$$

$$\text{then } I_{A'A'} = \frac{V_{AB}}{Z_A}$$

wlg


10.41 Balanced

4A

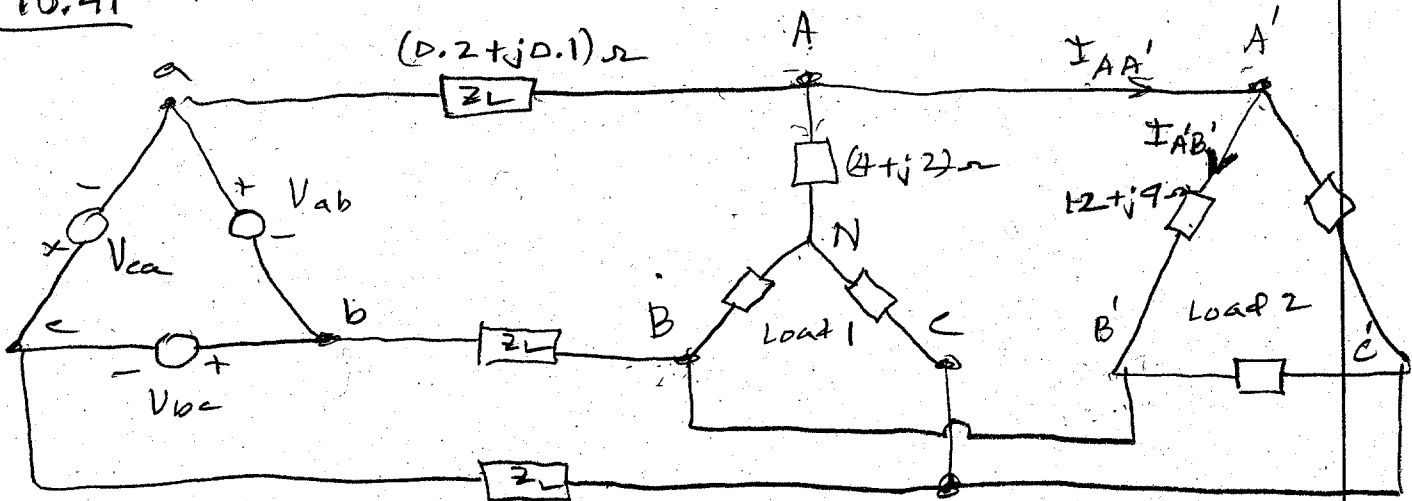

Given:  $I_{A'B'} = 16 \angle 45^\circ$  Arms

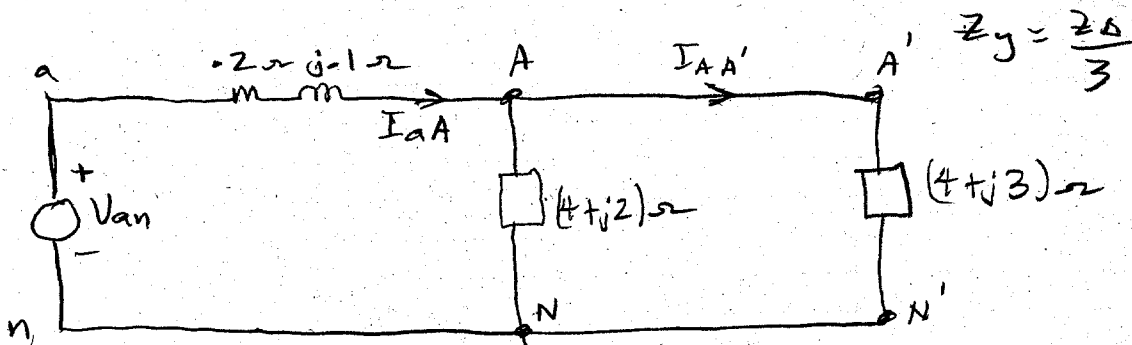Required: Find the phase voltages of the source:  $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$ .



$$I_{AA'} = \sqrt{3} I_{A'B'} \angle -30^\circ = 16\sqrt{3} \angle 15^\circ \text{ A}$$

with current splitting;

$$(16\sqrt{3} \angle 15^\circ) = \frac{I_{aA} \times (4 + j2)}{(8 + j5)}$$

$$I_{aA} = 58.46 \angle 20.4^\circ \text{ A}$$

22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



10.41 cont

$$\bullet V_{an} = (0.2 + j0.1)(58.46 \angle 20.4^\circ) + (16\sqrt{3}/15)(4 + j3)$$

$$V_{an} = 151.6 \angle 51.5^\circ$$

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ$$

$$V_{ab} = (\sqrt{3} \times 151.6 \angle 51.5^\circ \angle 30^\circ)$$

$$V_{ab} = 262.6 \angle 81.5^\circ \text{ V}$$

$$V_{bc} = V_{ab} \angle -120^\circ \text{ V}$$

$$V_{ca} = V_{ab} \angle 120^\circ \text{ OR } V_{ab} \angle -240^\circ \text{ V}$$