

Superposition:

A concept applied to linear systems:

Example, not from circuits:

$$\frac{d^2y(t)}{dt^2} + 6 \frac{dy(t)}{dt} + 8y(t) = At + Be^{-j\omega t}$$


$y_1(t) = y_1(t) \rightarrow$ solution for At

$y_2(t) = y_2(t) \rightarrow$ solution for $Be^{-j\omega t}$

$y(t) = y_1(t) + y_2(t) \rightarrow$ solution for $At + Be^{-j\omega t}$

System must be linear & time invariant

Illustration for a simple circuit

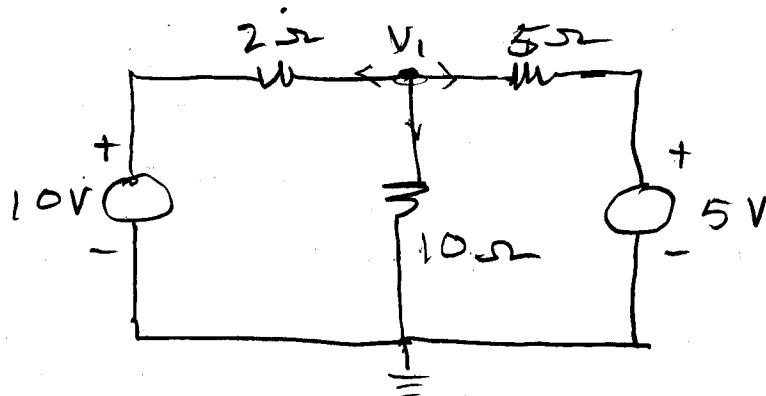

Find V_1 using superposition;

First find the total solution by node analysis.

$$\frac{V_1 - 10}{2} + \frac{V_1}{10} + \frac{V_1 - 5}{5} = 0$$


$$5V_1 - 50 + V_1 + 2V_1 - 10 = 0$$

$$8V_1 = 60$$

$$V_1 = 7.5 \text{ V}$$

with 10V present

8-2

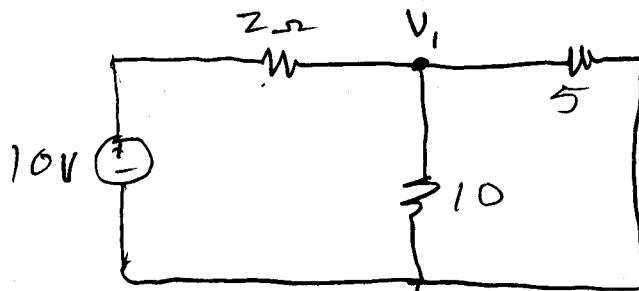


$$\frac{\dot{V}_1 - 10}{2} + \frac{\dot{V}_1}{10} + \frac{\dot{V}_1}{5} = 0$$

$$5\dot{V}_1 - 50 + \dot{V}_1 + 2\dot{V}_1 = 0$$

$$8\dot{V}_1 = 50 \rightarrow \dot{V}_1 = \frac{50}{8}$$

with 5V present

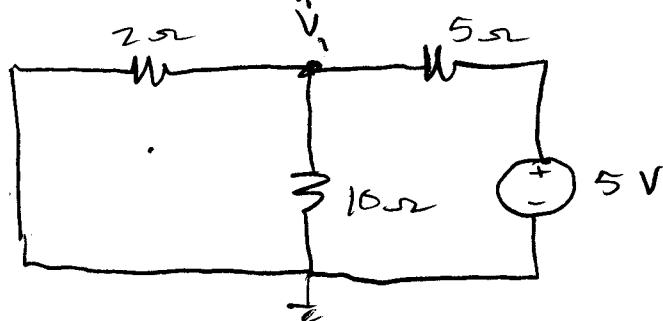

$$\frac{\dot{V}_1}{2} + \frac{\dot{V}_1}{10} + \frac{\dot{V}_1 - 5}{5} = 0$$

$$5\dot{V}_1 + \dot{V}_1 + 2\dot{V}_1 - 10 = 0$$

$$8\dot{V}_1 = 10$$


$$\dot{V}_1 = \frac{10}{8}$$

$$V_1 = \dot{V}_1 + \hat{V}_1 = \frac{50}{8} + \frac{10}{8} = \frac{60}{8} = 7.5V$$

checks

would apply also to

8-3

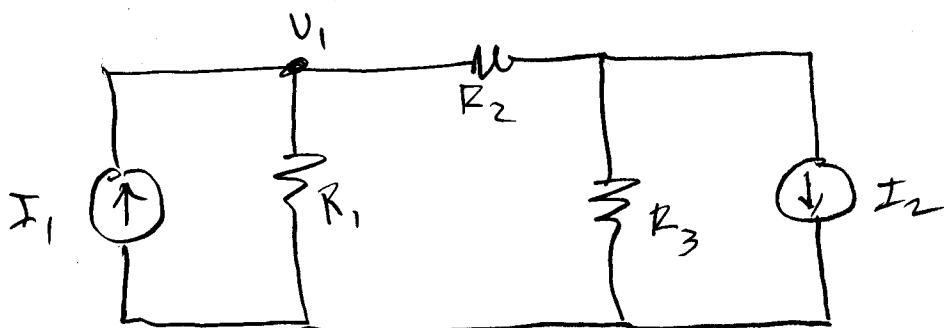


Active I_1 , get V_1 ; I_2 opened

Active I_2 , get V_1 ; I_1 opened

~~II~~


Thevenin's Theorem

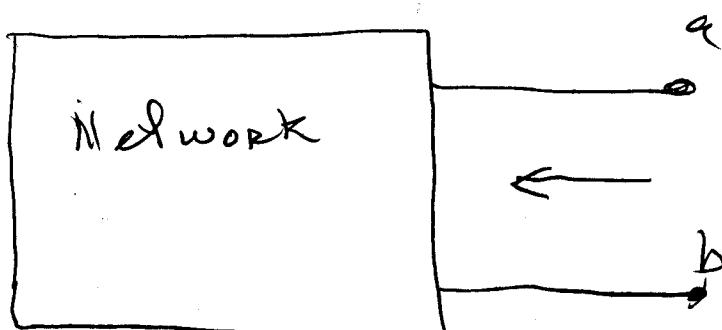Given a network, in the box. We allow independent & dependent sources. We focus on independent sources.



Suppose we have only resistors and sources (voltage and/or current sources).

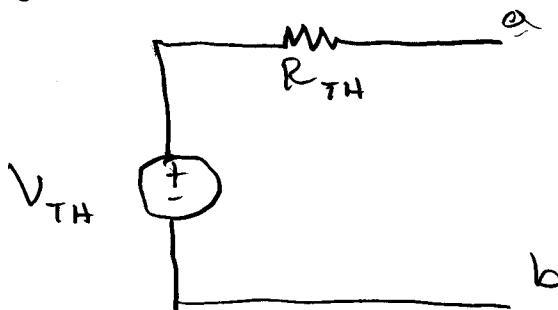If you think about this for a "bit", you will reconcile that this network can be replaced by:




After all, if you placed a voltmeter across a-b you would read a voltage: This is the "open-circuit" voltage.

$$\therefore V_{TH} = V_{ab} \text{ (open-circ)}$$

Similarly, if we disable all sources and place an ohmmeter across a-b (opened to the right) we read R_{TH} . R_{TH} = Resistance at a-b with all sources disabled.

You can also say the following

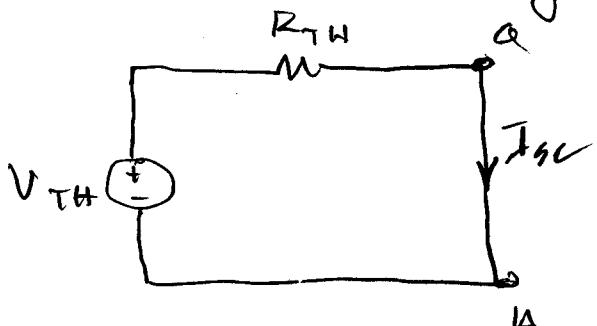


$$R_{TH} = \frac{V_{TH}}{I_{sc}}$$

4-5


We illustrate this with an example.

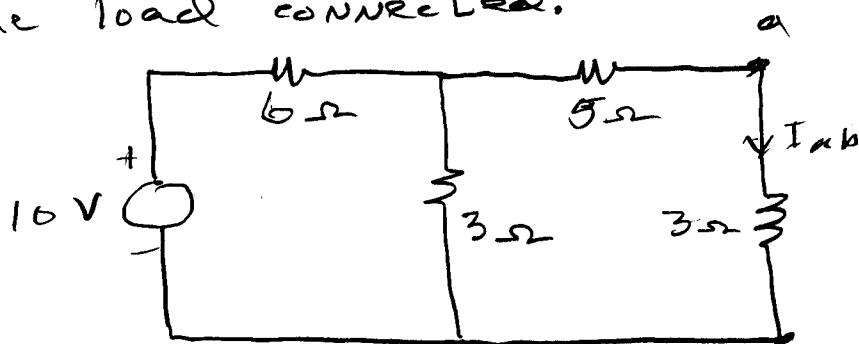Example 1

Find the Thévenin equivalent circuit to the left of a-b and then find V_{ab} with the load connected. Also find I_{ab} with the load connected.



Remove the load. Find V_{os} .

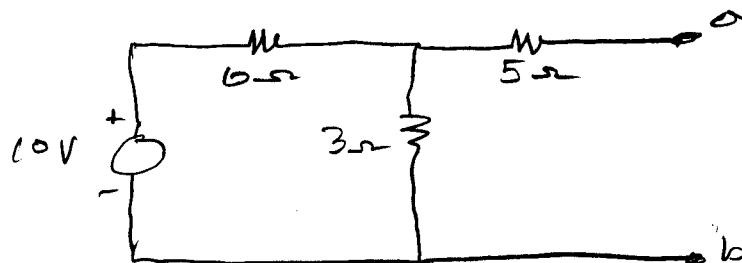


$$V_{ab} = V_{os} = V_{TH} = \frac{10 \times 3}{9} = \frac{30}{9} = \frac{10}{3} V$$

(No current flows through the 5Ω resistor so the voltage across the 5Ω resistor is zero.)


$$\therefore V_{TH} = \frac{10}{3}$$

For R_{TH}

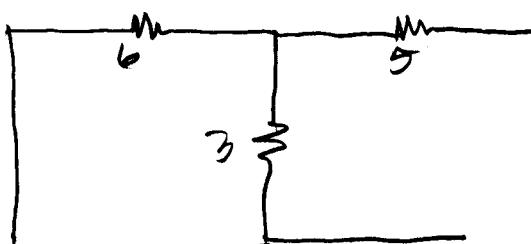

$$\Rightarrow 5 + 3\parallel 6 = 7 \Omega$$


8-16

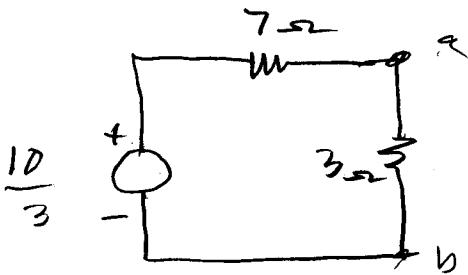

$$V_{ab} = \frac{\left(\frac{10}{3}\right) \times 3}{7+3} = 1V$$

$$I_{ab} = \frac{10/3}{10} = \frac{1}{3}A$$

Suppose we work this by Node analysis:

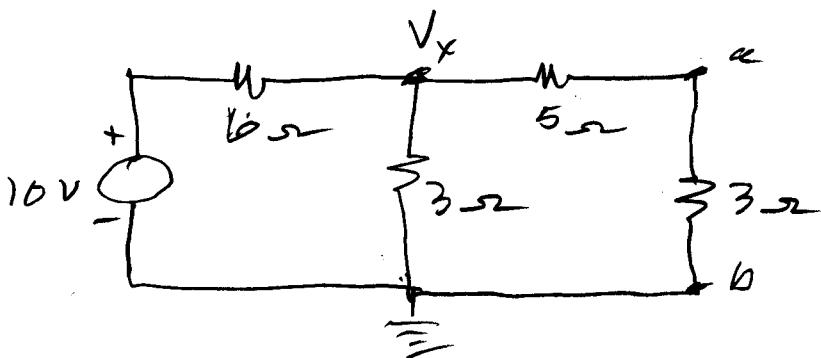

$$\frac{V_x - 10}{6} + \frac{V_x}{3} + \frac{V_x}{8} = 0$$

$$4V_x - 40 + 8V_x + 3V_x = 0$$

$$15V_x = 40$$

$$V_x = \frac{40}{15} = \frac{8}{3}V$$


$$I_{ab} = \frac{8/3}{8} = \frac{1}{3}A$$

$$V_{ab} = 3 \times I_{ab} = 3 \times \frac{1}{3} = 1V$$

Check with Thevenin solution.

Now suppose, for verification, we want to find I_{th} . Then determine

$$R_{th} = \frac{V_{th}}{I_{th}}$$

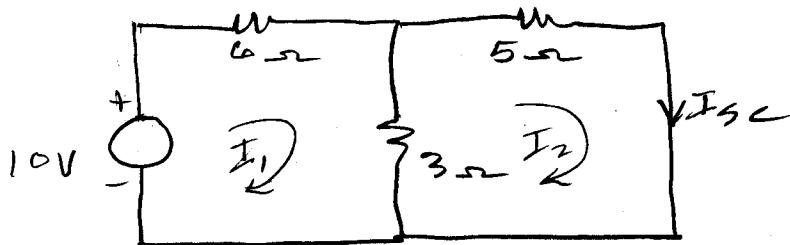

$$9I_1 - 3I_2 = 10$$

$$-3I_1 + 8I_2 = 0$$

$$\therefore I_2 = 0.47619 = \frac{10}{21} = Isc$$



$$R_{TH} = \frac{V_{DS}}{I_{SC}} = \frac{10/3}{10/21} = \frac{21}{3} = 7 \Omega$$

check

Also, we can place a voltage or current source at the output with all independent sources deactivated and find

$$R_{TH} = \frac{V_x}{I_x}$$

For this example

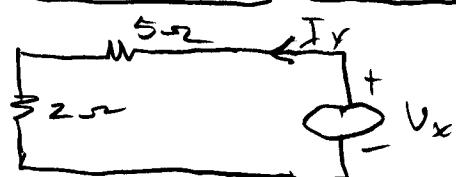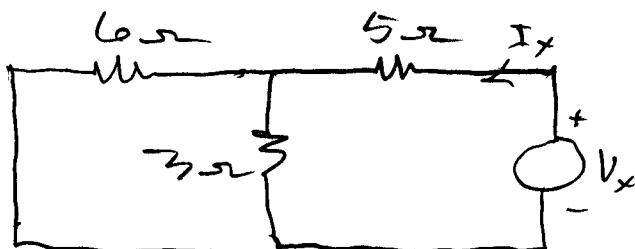

$$V_x = 7I_x$$

$$\frac{V_x}{I_x} = R_{TH} = 7 \Omega$$