

Solving AC Circuit Problems

This lesson is dedicated to solving AC circuit problems.

Example 13.1

For the circuit shown in Figure 13.1, solve for \bar{V}_R , \bar{V}_C and \bar{V}_L . Prepare the phasor diagram for the above phasor voltages. Finally, write the time domain equation for the steady state current in the circuit.

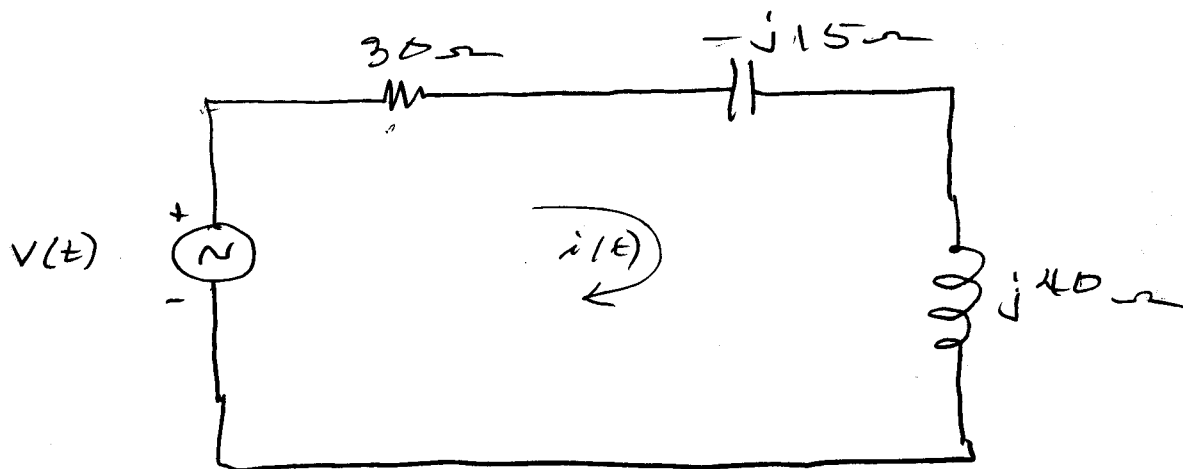


Figure 13.1: Circuit for Example 13.1

becomes

$$V(t) = 150 \sin(377t + 120^\circ) \text{ V}$$

$$V(t) = 150 \cos(377t + 30^\circ) \text{ V}$$

$$\bar{V} = 150 \angle 30^\circ \text{ V}$$

We can write;

$$\bar{I} = \frac{150 \angle 30^\circ}{30 - j15 + j40} = 3.84 \angle -9.8^\circ \text{ A} \quad \text{Eq 13.1}$$

Now calculate the voltages:

$$\bar{V}_R = 30 \times \bar{I} = 115.2 \angle -9.8^\circ \text{ V}$$

$$\bar{V}_C = (15 \angle -90^\circ)(3.84 \angle -9.8^\circ) = 57.6 \angle -99.8^\circ \text{ V}$$

$$\bar{V}_L = (40 \angle 90^\circ)(3.84 \angle -9.8^\circ) = 153.6 \angle 80.2^\circ \text{ V}$$

By KVL;

$$\bar{V} = \bar{V}_R + \bar{V}_C + \bar{V}_L \quad \text{Eq 13.2}$$

Putting in the above values gives,

$$150 \angle 30^\circ = 115.2 \angle -9.8^\circ + 57.6 \angle -99.8^\circ + 153.6 \angle 80.2^\circ$$

According to my calculator, the right hand side of the above equation is; $149.957 \angle 30^\circ \text{ V}$.

This is a good check since we have rounded numbers along the way.

What the phasor diagram shows is that $\bar{V}_R + \bar{V}_C + \bar{V}_L$ will be equal to \bar{V} . We now show this, roughly.

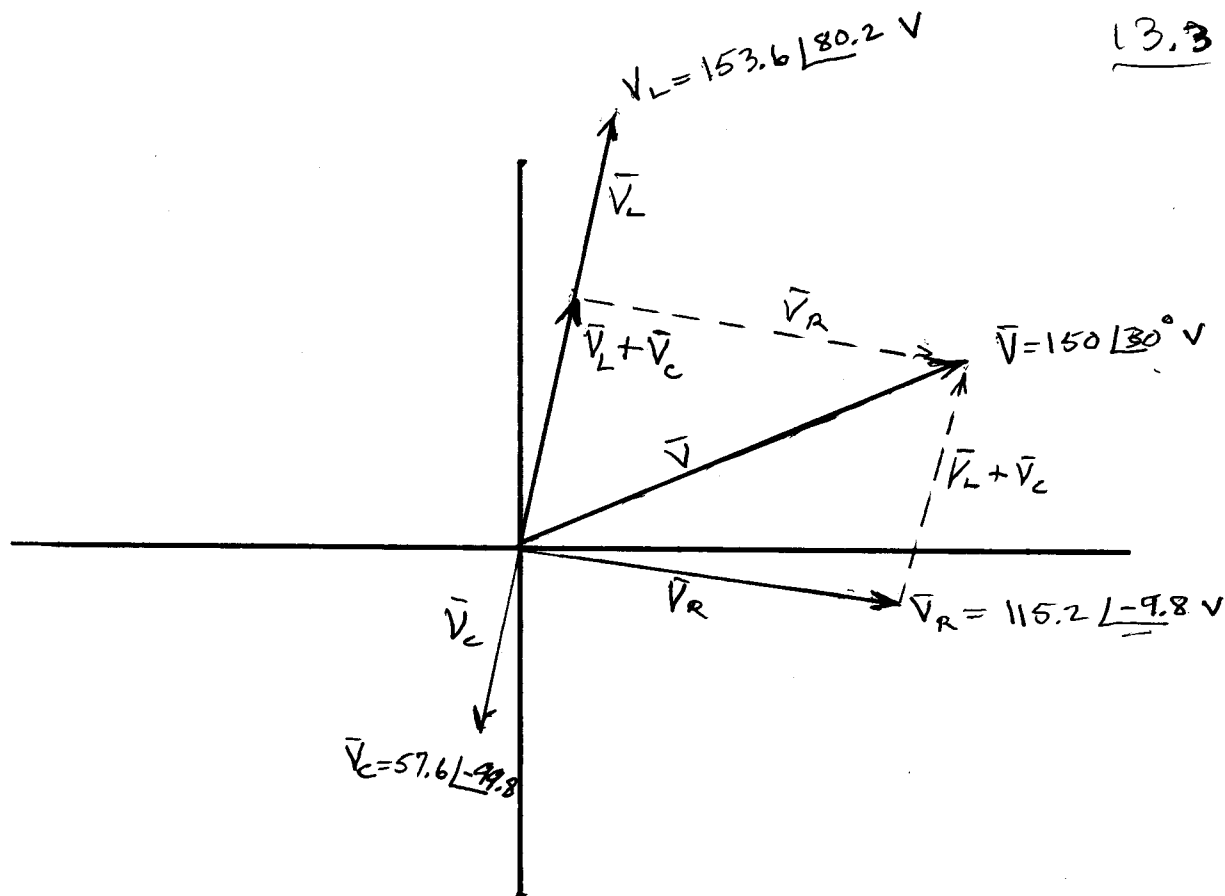


Figure 13.2; Phasor diagram of voltages for Example 13.1

We note the following:

- V_L and V_C are in opposite directions. This will always happen (+j for inductor, -j for capacitor)
- The graphical sum of $\vec{V}_R + \vec{V}_L + \vec{V}_C = \vec{V}$. Verification of KVL.

Finally, in the time domain, $i(t)$ is

$$i(t) = 3.84 \cos(377t - 9.8) \text{ A} \quad \text{Eq 13.3}$$

Example 13.2

Find the mesh currents \bar{I}_1 and \bar{I}_2 in the following circuit.

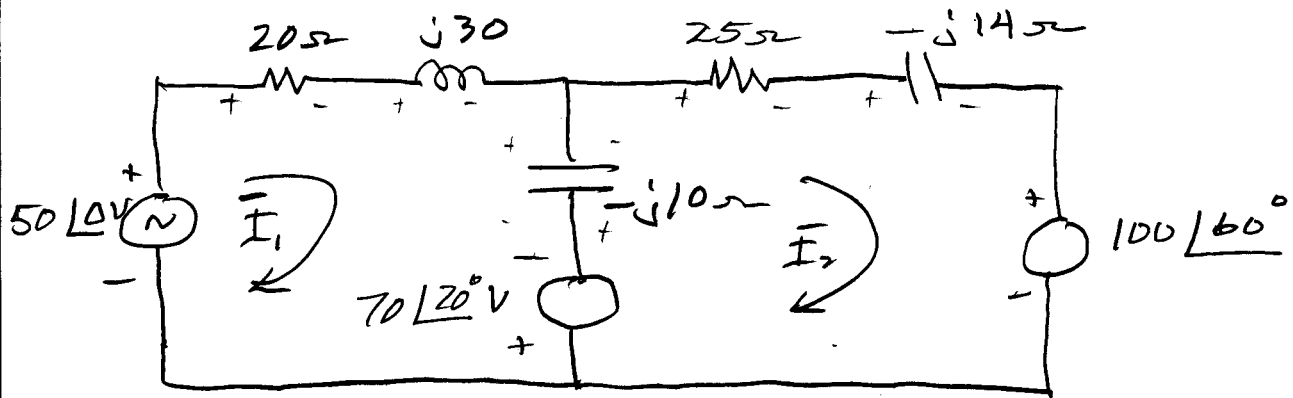


Figure 13.3: Circuit for Example 13.2.

This is about as tough as an AC circuit problems get to be.

We write the following two mesh equations, using $\sum v_{ises} = 0$.

$$50\angle 0 - (20 + j30)\bar{I}_1 - (-j10)(\bar{I}_1 - \bar{I}_2) + 70\angle 20^\circ = 0$$

Simplifying gives

$$(20 + j20)\bar{I}_1 + (j10)\bar{I}_2 = 50\angle 0 + 70\angle 20^\circ \quad \text{Eq 13.4}$$

Around mesh 2 we have

$$-70\angle 20^\circ - (\bar{I}_2 - \bar{I}_1)(-j10) - (25 - j14)\bar{I}_2 - 100\angle 60^\circ = 0$$

$$\text{OR } +j10\bar{I}_1 + (25 - j10 - j14)\bar{I}_2 = -70\angle 20^\circ - 100\angle 60^\circ \quad \text{Eq 13.5}$$

Eq's 13.4 & 13.5 can be put in 13.5
the form

$$(20 + j20)I_1 + j10I_2 = 118.23 \angle 11.7^\circ$$

$$j10I_1 + (25 - j24)I_2 = 160 \angle -136.3^\circ$$

OR

$$\begin{bmatrix} 20 + j20 & j10 \\ j10 & 25 - j24 \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix} = \begin{bmatrix} 118.23 \angle 11.7 \\ 160 \angle -136.3 \end{bmatrix}$$

From this we find;

$$\bar{I}_1 = 2.385 \angle -24.45^\circ \text{ A}$$

$$\bar{I}_2 = 5.26 \angle -89.7^\circ \text{ A}$$

If we want to express these
currents in the time domain
we have

$$i_1(t) = 2.385 \cos(\omega t - 24.45) \text{ A}$$

$$i_2(t) = 5.26 \cos(\omega t - 89.7) \text{ A}$$

We would need to know ω if
we wanted to plot the above
equations as time functions.

Example 13.3-

We make this a 3 mesh problem and write the equations by inspection. Given the circuit in Figure 13.4. Assume $\omega = 377 \text{ rad/sec}$.

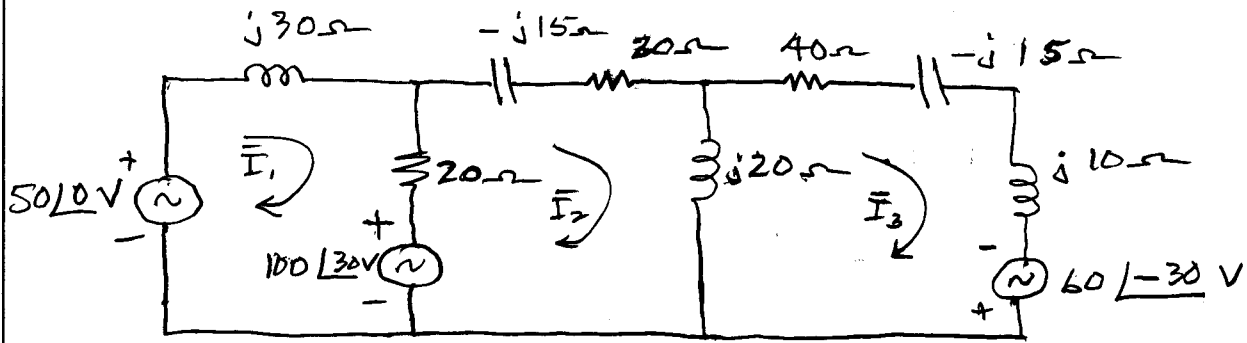


Figure 13.4: Circuit for Example 13.2.

The equations of this circuit are of the form;

$$\begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} \sum V_1 \\ \sum V_2 \\ \sum V_3 \end{bmatrix} \quad \text{Eq 13.6}$$

$\sum V_1 =$ sum of the rises around mesh 1

$\sum V_2 =$ sum of the rises around mesh 2

$\sum V_3 =$ sum of the rises around mesh 3

For this case:

$$\sum V_1 = 50\angle 0 - 100\angle 30 = 61.97\angle -126.2 \text{ V}$$

$$\sum V_2 = 100\angle 30 \text{ V}$$

$$\sum V_3 = 60\angle -30^\circ \text{ V}$$

Z_{11} = impedance of mesh one, common to mesh current \bar{I}_1 ,

$$Z_{11} = 20 + j30 \Omega$$

Z_{12} = impedance shared between mesh one and mesh two. There is a negative sign placed before the impedance if mesh currents \bar{I}_1 and \bar{I}_2 are in opposition. They usually are in opposition if one follows the established method for mesh analysis.

$$Z_{12} = - [20] \Omega$$

Z_{13} = impedance shared between mesh one and mesh three. Again, there is a negative sign placed before the impedance if \bar{I}_1 and \bar{I}_3 are in opposition.

$$Z_{13} = 0$$

Z_{21} = Z_{12} . True for RLC linear circuits. May not be true when we have transformers.

$$Z_{21} = -20 \Omega$$

Z_{22} = impedance of mesh two, common to mesh current \bar{I}_2 .

$$Z_{22} = 20 - j15 + 20 + j20$$

$$\boxed{Z_{22} = (40 + j5) \Omega}$$

Z_{23} = impedance shared between mesh two and mesh three. Again, there is a negative sign placed before the impedance when \bar{I}_2 and \bar{I}_3 are in opposition through this impedance.

$$Z_{23} = -[j20] \Omega$$

Z_{31} = Z_{13} for the same reason as stated for Z_{12} , Z_{21} .

$$\boxed{Z_{31} = 0}$$

Z_{32} = Z_{23} for the reason stated above.

Z_{33} = impedance of mesh three, common to mesh current \bar{I}_3 .

$$Z_{33} = j20 + 40 - j15 + j10$$

$$Z_{33} = (40 + j15) \Omega$$

Substituting into eq 13.6 gives ^{13.9}

$$\begin{bmatrix} 20+j30 & -20 & 0 \\ -20 & 40+j5 & -j20 \\ 0 & -j20 & 40+j15 \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \bar{I}_3 \end{bmatrix} = \begin{bmatrix} 62 \angle -126^\circ \\ 100 \angle 30^\circ \\ 60 \angle -30^\circ \end{bmatrix} \quad \text{Eq 13.7}$$

$\underline{\mathbf{Z}} \qquad \qquad \underline{\mathbf{I}} \qquad \qquad \underline{\mathbf{V}}$

We notice, as expected, that the \mathbf{Z} matrix is symmetrical about the diagonal of the matrix.

The solutions for \bar{I}_1 , \bar{I}_2 , and \bar{I}_3 by hand calculator are:

$$\bar{I}_1 = (-0.586 - j0.522) \text{ A} = 0.785 \angle -138.3^\circ \text{ A}$$

$$\bar{I}_2 = (2.02 + j1.11) \text{ A} = 2.30 \angle 28.8^\circ \text{ A}$$

$$\bar{I}_3 = (0.739 + j0.018) \text{ A} = 0.74 \angle -1.37^\circ \text{ A}$$

The corresponding time domain equations are: (steady state)

$$i_1(t) = 0.785 \cos(377t - 138.3^\circ) \text{ A}$$

$$i_2(t) = 2.3 \cos(377t + 28^\circ) \text{ A}$$

$$i_3(t) = 0.74 \cos(377t - 1.37^\circ) \text{ A}$$

A MATLAB program for solving Eq 13.7 is given below. This type of solution, as opposed to a hand calculator solution, would only be necessary when the number of meshes was greater than five. L13_ex13_3.m

```
% A simple program for solving for mesh currents
% in a three mesh AC circuit. Program: L13_ex13_3.m
% Written by W. Green: October 3, 2002, office PC

Z = [20+j*30  -20  0;  -20  40+j*5  -j*20;  0  -j*20  40+j*15];

V = [-35.27-j*48.54;  86.6+j*50;  51.96-j*30];

% I cannot find a way to express polar form directly in MATLAB
% so I have converted the voltages to rectangular form.  If you
% know how to express polar form, please let me know.

I = inv(Z)*V

% I = [I1; I2; I3]

» L13_ex13_3

I =

-0.5269 - 0.5377i
 2.0431 + 1.0990i
 0.7464 - 0.0083i

»
```

Statements are added to the previous
 PROGRAM in order to plot the currents.
 The modified program is given below
 with the output on the following page.

```
% A simple program for solving for mesh currents
% in a three mesh AC circuit. Program: L13_ex13_3.m
% Written by W. Green: October 3,2002, office PC

Z = [20+j*30 -20 0; -20 40+j*5 -j*20; 0 -j*20 40+j*15];
V = [-35.27-j*48.54; 86.6+j*50; 51.96-j*30];

% I cannot find a way to express polar form directly in MATLAB
% so I have converted the voltages to rectangular form. If you
% know how to express polar form, please let me know.

I = inv(Z)*V

% I = [I1; I2; I3]


% To plot the three currents

t = 0:.0001:.03;

i1 = 0.785*cos(377*t-(138.3/180)*pi);
i2 = 2.3*cos(377*t+(28/180)*pi);
i3 = 0.74*cos(377*t-(1.37/180)*pi);

plot(t,i1,'-',t,i2,'*',t,i3,'--')
ylabel('Current Responses, Amps')
xlabel('time (sec)')
title('Mesh Currents for Example 13.3')
grid
gtext(' _____ i1')
gtext('* * * * * * * * * i2')
gtext('- - - - - - - - - i3')
```

Mesh Currents for Example 13.3

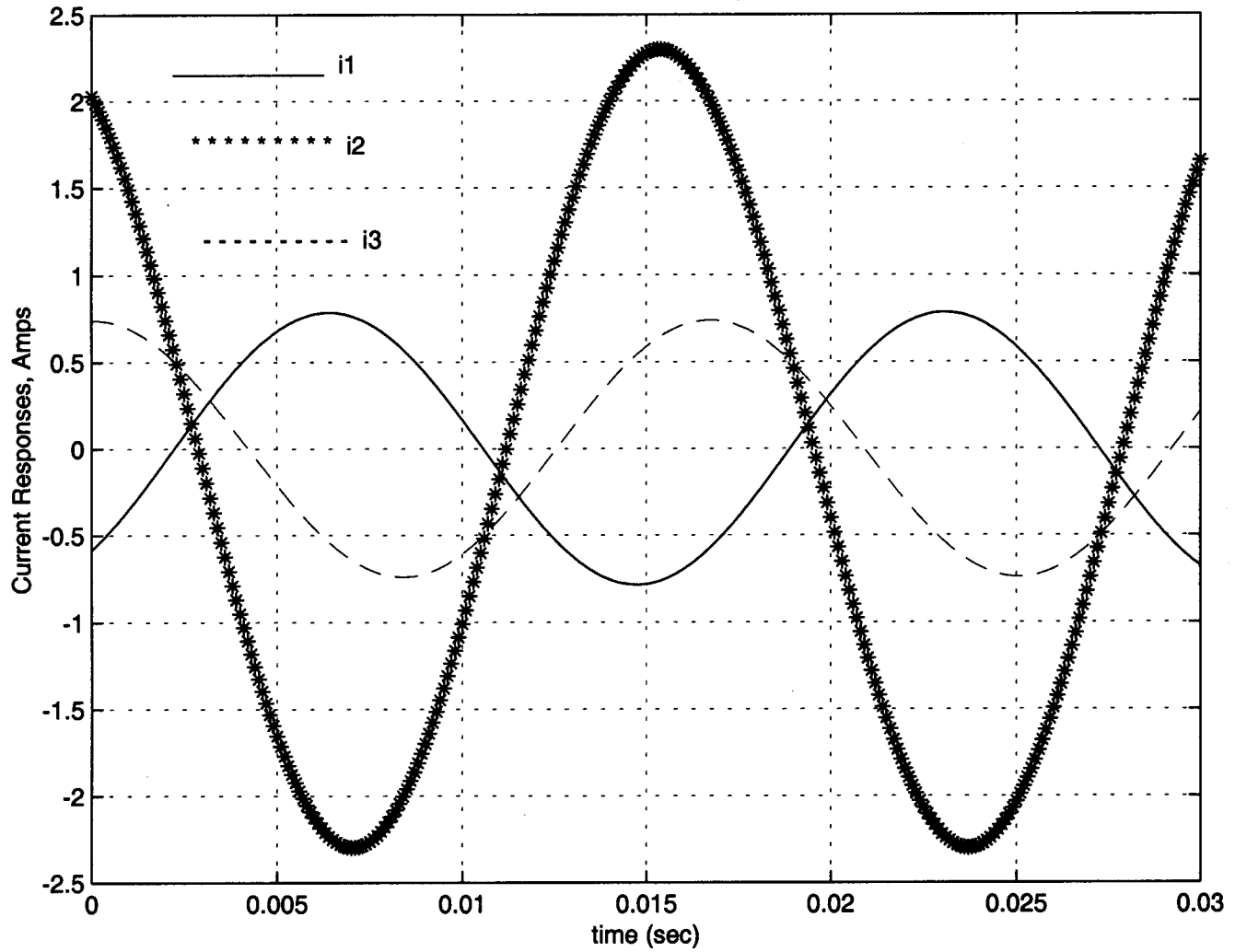

```

% A simple program for solving for mesh currents
% in a three mesh AC circuit. Program: L13_ex13_2.m
% Written by W. Green: October 3,2002, office PC

Z = [20+j*30  -20  0;  -20  40+j*5  -j*20;  0  -j*20  40+j*15];

V = [-35.27-j*48.54; 86.6+j*50; 51.96-j*30];

% I cannot find a way to express polar form directly in MATLAB
% so I have converted the voltages to rectangular form. If you
% know how to express polar form, please let me know.

I = inv(Z)*V

% I = [I1; I2; I3]

% To plot the three currents

t = 0:.0001:.03;

i1 = 0.785*cos(377*t-(138.3/180)*pi);
i2 = 2.3*cos(377*t+(28/180)*pi);
i3 = 0.74*cos(377*t-(1.37/180)*pi);

plot(t,i1,'-',t,i2,'*',t,i3,'--')
ylabel('Current Responses, Amps')
xlabel('time (sec)')
title('Mesh Currents for Example 13.2')
grid
gtext(' _____ i1')
gtext('* * * * * i2')
gtext('- - - - - i3')

```

Mesh Currents for Example 13.2

