

ECE 551


System on Chip Design

State Machine Techniques


Garrett S. Rose
Fall 2018

State Machines

 - Finite state machines (FSM) are key elements in logic design
- A synthesizer can perform *some* state optimization on FSMs to minimize circuit area & delay
- This optimization is often only available if the FSM model fits pre-specified templates




FSM Representation

 


Mealy Machine

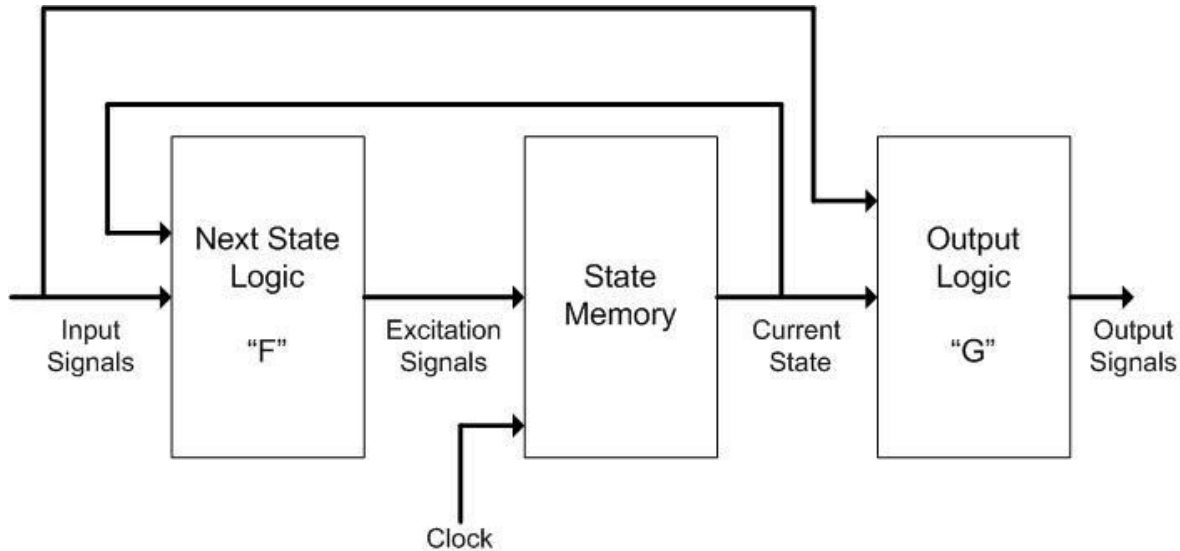- Outputs depend on previous (state) AND present inputs
- Input change causes an immediate output change
 - Asynchronous signals



Moore Machine

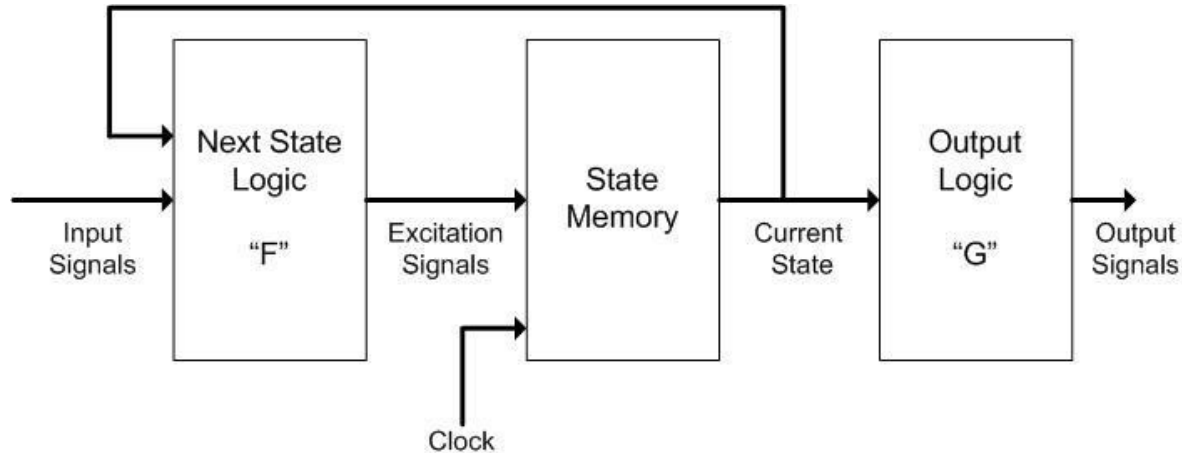- Outputs depend ONLY on previous inputs (i.e. current states)
- Outputs change synchronously with state changes



State Machines in HDL

1. State memory


- Use a `always_ff` procedural block (sensitive to clock) to update the states
- State memory based on “user-enumerated” or “pre-defined” data types
- Synchronous and asynchronous reset options

2. Next state logic “F”

3. Output logic “G”

 Example: Sequence Detector

- Design a machine by hand that takes in a serial bit stream and looks for the pattern “1011”
 - Similar machine useful for detecting malicious network traffic
 - When pattern found, signal called “Found” asserted
 - Must store and recall historic system state
- State diagram
 - If pattern invalidated, restart



State Memory

- Use process that updates “Current_State” with the “Next_State”
- Describe D flip-flop's using **always_ff**
- This will make assignment on the rising edge of CLK


```
always_ff @(posedge CLK) begin  
    if (reset)  
        Current_State <= S0;  
    else  
        Current_State <= Next_State;  
end
```


Procedural Block for Next State Logic

- Use another always block to construct next state logic “F”

```
always_comb
case (Current_State)
  S0: if (In==1'b0) Next_State = S0;
      else Next_State = S1;
  S1: if (In==1'b0) Next_State = S2;
      else Next_State = S0;
  S2: if (In==1'b0) Next_State = S0;
      else Next_State = S3;
  S3: if (In==1'b0) Next_State = S0;
      else Next_State = S0;
endcase
```

 “F” always_comb updates Next_State;
does not update Current_State



Process for Output Logic


- Use a third block to construct output “G”
- Inputs to expressions dictate whether state machine is Mealy or Moore type
- For starters, we'll use combinational logic for G

Mealy Output Logic

- Use a third process to construct output “G”

```
always_comb
case (Current_State)
  S0: if (In==1'b0) Found = 0;
      else if (In==1'b1) Found = 0;
  S1: if (In==1'b0) Found = 0;
      else if (In==1'b1) Found = 0;
  S2: if (In==1'b0) Found = 0;
      else if (In==1'b1) Found = 0;
  S3: if (In==1'b0) Found = 0;
      else if (In==1'b1) Found = 1;
endcase
```

 Executes `always_comb` whenever inputs
In or `Current_State` changes




Moore Output Logic


- Use a third process to construct output “G”

```
always_comb  
  case (Current_State)  
    S0: Found = 0;  
    S1: Found = 0;  
    S2: Found = 0;  
    S3: Found = 1;  
  endcase
```

 Only change in current state
executes & updates output Found



General View of State Machine Logic

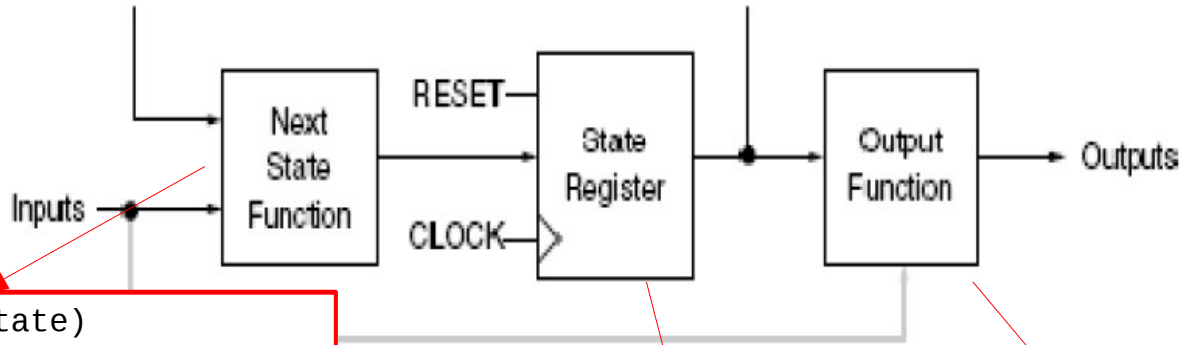

Process 1

```
case (Current_State)
  Idle:
    Next_State = Grab_Data;
  Grab_Data:
    Next_State = Wait_Ack;
  Wait_Ack:
    if (go_pulse==1'b1)
      Next_State = Send_Data;
    else
      Next_State = Abort;
  ...
```


Process 2

```
if (Reset==1'b1)
  Current_State <= Idle;
else
  Current_State <= Next_State;
...
```

Process 3

```
assign Signal_Sending = (Current_State==Send_Data) ? 1'b1 : 1'b0;
assign Machine_Ready = (Current_State==Idle) ? 1'b1 : 1'b0;
```

General View of State Machine Logic

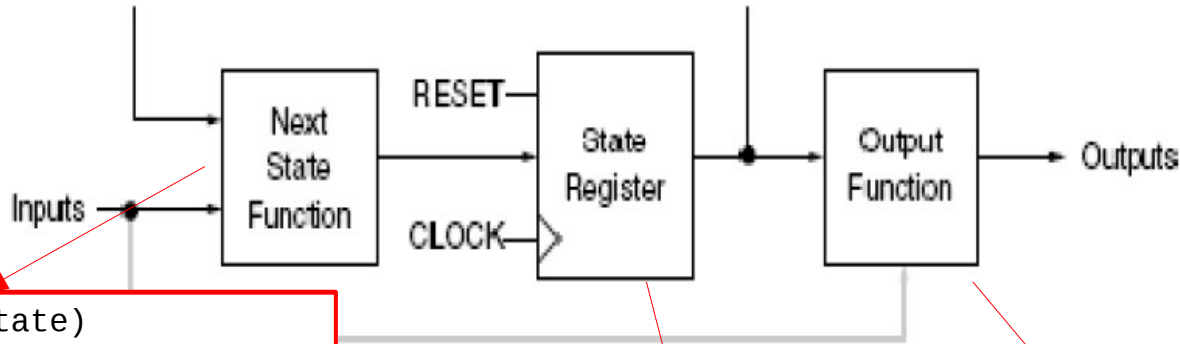

Process 1

```
case (Current_State)
  Idle:
    Next_State = Grab_Data;
  Grab_Data:
    Next_State = Wait_Ack;
  Wait_Ack:
    if (go_pulse==1'b1)
      Next_State = Send_Data;
    else
      Next_State = Abort;
  ...
```

Process 2

```
if (Reset==1'b1)
  Current_State <= Idle;
else
  Current_State <= Next_State;
...
```

Process 3


```
assign Signal_Sending = (Current_State==Send_Data) ? 1'b1 : 1'b0;
assign Machine_Ready = (Current_State==Idle) ? 1'b1 : 1'b0;
```

May not need in own
process, depends
on complexity

Combining Procedural Blocks

- Can combine output decoding into always block for exactly same behavior
- Can combine register and state decoding into one procedural block for same behavior (example to come)
- Can combine all into one synchronous always block for slightly modified behavior

Remember: Smart Battery Charger

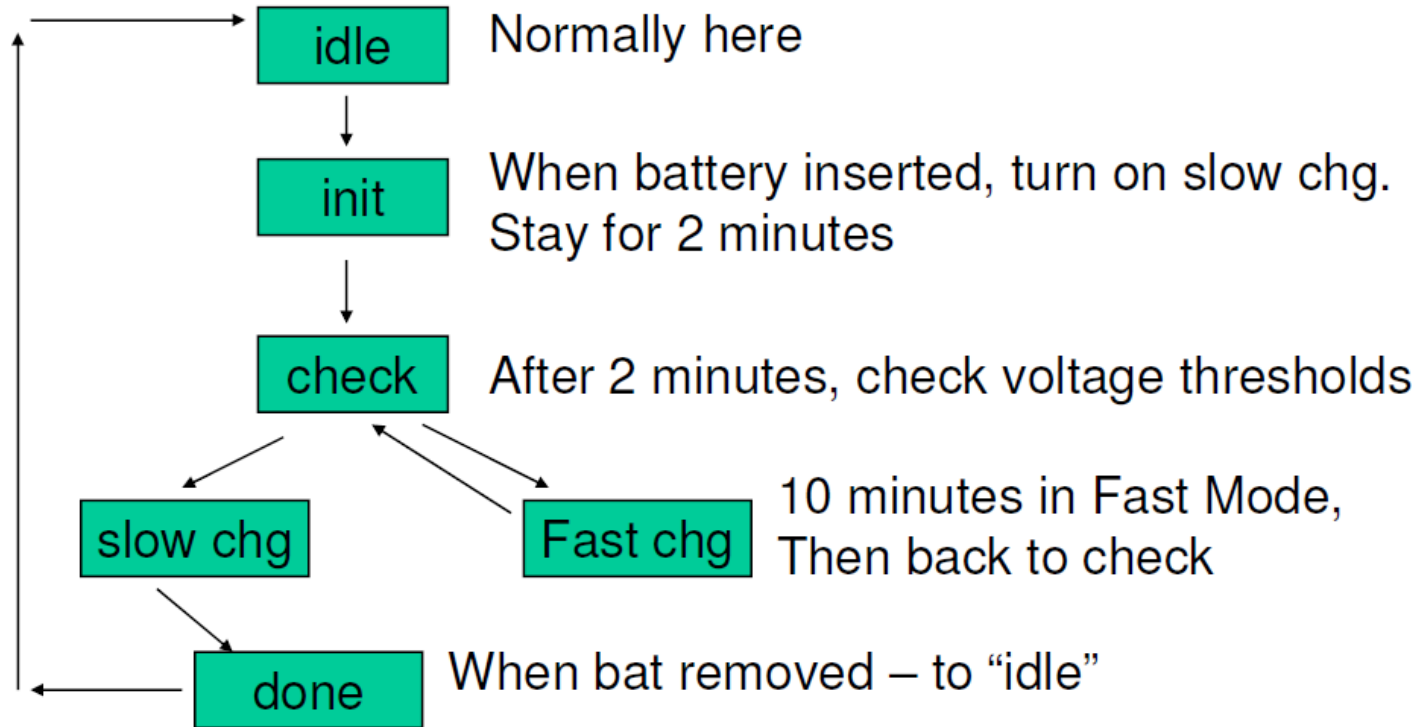

Combining Processes Example

```
always_ff @(CLK, Reset)
  if (Reset==1'b1)
    CurState <= Idle;
  else
    case (CurState)
      Idle:
        if (batt_attached==1'b1)
          CurState <= Init;
      Init:
        if (timer >= two_min)
          CurState <= Check;
      Check:
        if (high_thresh==1'b1)
          CurState <= FastChg;
        else
          CurState <= SlowChg;
      FastChg:
        if (timer >= ten_min)
          CurState <= Check;
      SlowChg:
        if (charge_thresh == 1'b1)
          CurState <= DoneChg;
      DoneChg:
        if (batt_attached==1'b0)
          CurState <= Idle;
    endcase
```

Process After Combination

```
always_ff @(CLK, Reset) begin
  if (Reset==1'b1)
    CurState <= Idle;
  else
    case (CurState)
      Idle:
        if (batt_attached==1'b1)
          CurState <= Init;
        reset_timer <= 1'b1;
      Init:
        if (timer >= two_min)
          CurState <= Check;
        source_low <= 1'b1;
      check:
    ...
```

- Outputs now registered (assigned within clocked always block)
- *Flops made for each output*
 - May be expensive
 - Synchronizes outputs
- Extra flexibility available for setting outputs low and high
- Care should be taken to specify these signals, recognizing when they actually take affect

State Encoding

```
enum {red, yellow, green, fl_yellow, f_red, turn_arrow}  
    Current_State, Next_State;
```

- Sequential states: encodes the states as binary numbers:
 - 000, 001, 010, 011, 100, 101
 - Is this the only way to encode?
- Some encoding options:
 - One-hot encoding
 - Compact encoding
 - Gray encoding
 - Others listed in Xilinx user guides

One-Hot Encoding

- Ensures that individual state register is dedicated to one state
--Only one flip-flop is active, or hot, at any one time
- Very appropriate with most FPGA targets where a large number of flip-flops are available
- Good alternative when optimizing for speed low power dissipation

```
enum {red, yellow, green, fl_yellow, f_red, turn_arrow}  
      Current_State, Next_State;
```

- 100000, 010000, 001000, 000100, 000010, 000001

Compact Encoding

- Option minimizes the number of state variables and flip-flops
 - Technique is based on hypercube immersion
- Appropriate when trying to optimize for reduced area

```
enum {red, yellow, green, fl_yellow, f_red, turn_arrow}  
Current_State, Next_State;
```


- 000, 001, 010, 011, 100, 101

Gray Encoding

- Guarantee that only one state variable switches between two consecutive states
- Appropriate for controllers exhibiting long paths without branching
- Minimizes hazards and glitches
- Very good results can be obtained when implementing state register(s) with T or JK flip-flops
- You can explicitly specify your FSM encoding methods for synthesis

Why State Encoding Matters

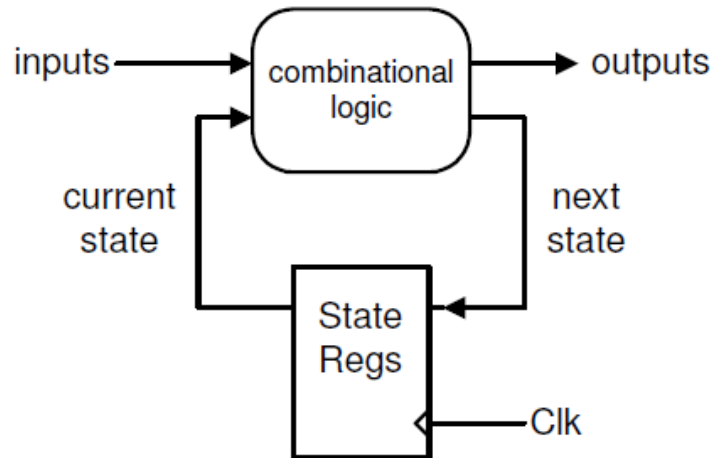- Speed: decoding state variable to determine outputs and next state can be simpler via one-hot, for instance
- State transitions: if combinatorial decode of output with no glitches is desired, encoding makes a difference
- Size: how many flops are required?



Illegal States

- Given our states: (red, yellow, green, fl_yellow, f_red, turn_arrow)
 - 000, 001, 010, 011, 100, 101
- If encoded as above, two illegal states exist
 - Undefined states in the FSM
- What will logic do when those states are encountered?

```
case (Current_State)
  red:      Next_State <= turn_arrow;
  turn_arrow: Next_State <= green;
  green:    Next_State <= yellow;
  ...
```


- It is a mystery...
- Could present security concerns: trigger Hardware Trojans

More on Illegal States

- Consequences of entering illegal state unknown
 - Frequently results in “wedged” machine, doesn't recover
 - System can get stuck once entering illegal state
- Faulty reset circuitry (or none) could lead to power-up into illegal state
 - The initial state would be random!
- Single event upsets in radiation environments can cause a flop to toggle, leaving machine in an illegal state
- Synchronization errors on inputs
 - Setup/hold violations
 - Metastability

More on Illegal States

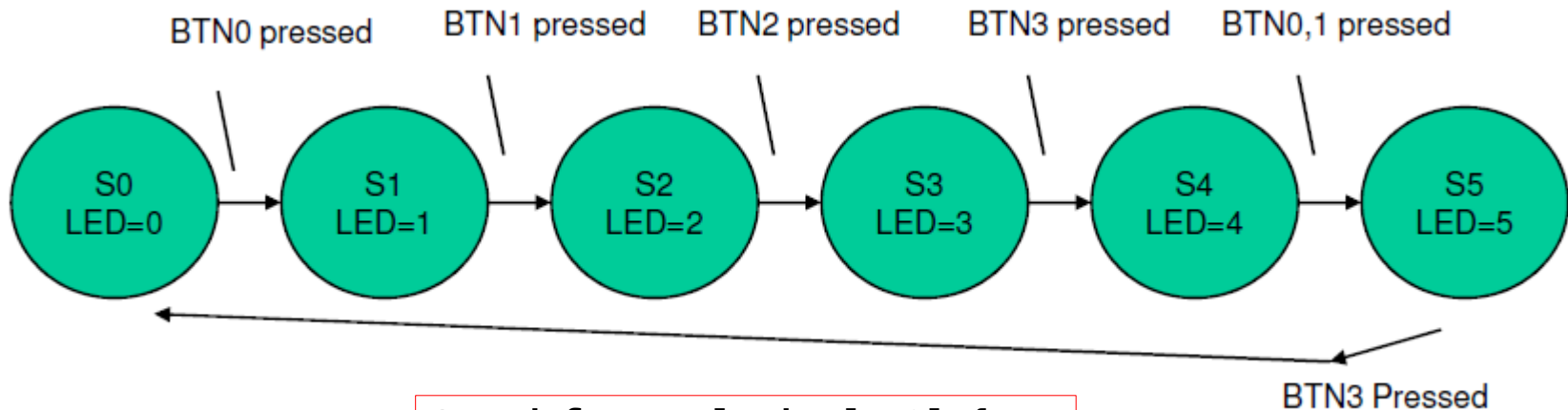- Suppose we use one-hot encoding for the following:




```
typedef enum logic [5:0] {  
    s0=6'b100000,  
    s1=6'b010000,  
    s2=6'b001000,  
    s3=6'b000100,  
    s4=6'b000010,  
    s5=6'b000001} statetype;
```

FSM Implementation: One-Hot


Imagine:

 - Current_State = “100000”
- Button pressed near clock edge
- Line A to go from 1 – 0
- Line B to go from 0 – 1
- Possible outcome:
 - $S0 \rightarrow 0$
 - S1 stays 0
- What now???



Dealing with Illegal States

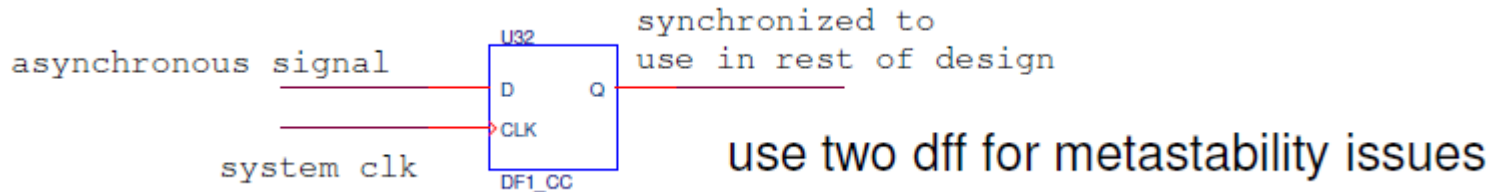- Problems not specific to one-hot encoding – they are simply magnified by the scheme as there are more illegal states
- Solutions:
 - Always have a reset state – somewhat obvious
 - Carefully synchronize all inputs



- If design in inaccessible place and cannot be restarted, etc.
 - Make a “safe” state machine...

Safe State Machines

- The “others” clause is typically not implemented by FSM extractor
 - There are no others, everything in enumerated type is covered
 - Might call this the result of “reachability” analysis
 - Likely up to you to generate reset logic which places machine in a known state
- Some synthesis tools provide attributes for encoding machine that include: safe, onehot; safe, grey ... etc.

Summary

- More issues in FSM design and implementation
 - Combining processes in FSM design
 - FSM implementation
- State encoding
 - One-hot encoding
 - Compact encoding
 - Gray encoding
- Dealing with illegal states
 - Safe state machines