

Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

# Digital Signal Processing

## Lecture 7 - Structures for Discrete-Time Systems

Electrical Engineering and Computer Science  
University of Tennessee, Knoxville

# Overview

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

- 1 Recap
- 2 Representations
- 3 IIR
- 4 FIR
- 5 Lattice
- 6 Finite Numerical Precision
- 7 Coefficient Q

# Discrete-time systems

Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

- Special properties: linearity, TI, stability, causality
- LTI systems: the unit sample response  $h[n]$  uniquely characterizes an LTI system

$$y[n] = \sum_{k=-\infty}^{\infty} x[k]h[n-k] = x[n] * h[n]$$

- Frequency response:  $H(e^{j\omega})$  is eigenvalues of LTI systems, complex exponentials are eigenfunctions of LTI systems, i.e., if  $x[n] = e^{j\omega n}$ ,

$$y[n] = H(e^{j\omega})x[n] = (\sum_{k=-\infty}^{\infty} h[k]e^{-j\omega k})e^{j\omega n}$$

- Fourier transform: Generalization of frequency response (a periodic continuous function of  $\omega$ )

$$X(e^{j\omega}) = \sum_{n=-\infty}^{\infty} x[n]e^{-j\omega n}, x[n] = \frac{1}{2\pi} \int_{-\pi}^{\pi} X(e^{j\omega})e^{j\omega n}d\omega$$

- The z-transform as a generalization to the Fourier transform,  $X(z) = \sum_{n=-\infty}^{\infty} x[n]z^{-n}$ , and the system function  $H(z)$
- Sampling, Aliasing, Reconstruction

# Transform-domain Analysis

## Lecture 7

### Recap

#### Representations

#### IIR

#### FIR

#### Lattice

#### Finite Numerical Precision

#### Coefficient Q

- FIR vs. IIR
- FIR filters with generalized linear phase (special pattern for zeros)
- Minimum phase systems (special pole-zero properties)
- All-pass systems (special pole/zero properties)
- $H = H_{min}H_{ap}$
- Geometric interpretation of the pole-zero plot

# Different system representations

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

- Using LCDE with initial rest condition

$$y[n] = \sum_{k=0}^M b_k x[n-k] + \sum_{k=1}^N a_k y[n-k]$$


- Using system function with ROC  $|z| > R_+$

$$H(z) = \frac{\sum_{k=0}^M b_k z^{-k}}{1 - \sum_{k=1}^N a_k z^{-k}}$$


# Block diagram vs. Signal flow graph
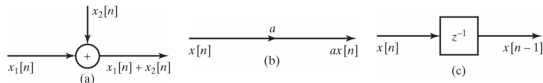
## Lecture 7


- Block diagram symbols: adder, multiplier, unit delay (memory)



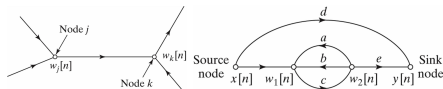- Signal flow graph: directed branches (branch gain, delay branch), nodes (source node, sink node)



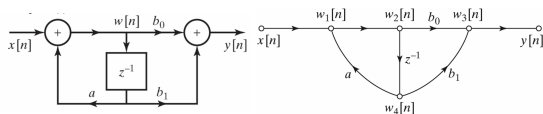- A comparison: nodes in the flow graph represent both branching points and adders, whereas in the block diagram a special symbol is used for adders



# Determination of the system function from a flow graph

## Lecture 7

Recap

Representations

IIR


FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

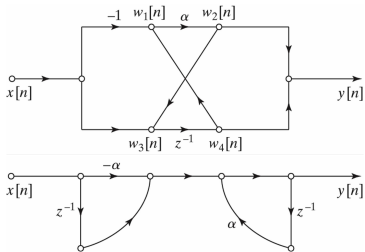- Different flow graph representations require different amounts of computational resources



# Direct form I and II

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

$$H(z) = \frac{\sum_{k=0}^M b_k z^{-k}}{1 - \sum_{k=1}^N a_k z^{-k}}$$

### ■ Direct form I: implementing zeros first

$$H(z) = H_2(z)H_1(z) = \left( \frac{1}{1 - \sum_{k=1}^N a_k z^{-k}} \right) \left( \sum_{k=0}^M b_k z^{-k} \right) \quad (1)$$

$$V(z) = H_1(z)X(z) = \left( \sum_{k=0}^M b_k z^{-k} \right) X(z) \quad (2)$$

$$Y(z) = H_2(z)V(z) = \left( \frac{1}{1 - \sum_{k=1}^N a_k z^{-k}} \right) V(z) \quad (3)$$

$$y[n] = \sum_{k=0}^M b_k x[n-k] + \sum_{k=1}^N a_k y[n-k] \quad (4)$$

### ■ Direct form II: implementing poles first

$$H(z) = H_1(z)H_2(z) = \left( \sum_{k=0}^M b_k z^{-k} \right) \left( \frac{1}{1 - \sum_{k=1}^N a_k z^{-k}} \right) \quad (5)$$

$$W(z) = H_2(z)X(z) = \left( \frac{1}{1 - \sum_{k=1}^N a_k z^{-k}} \right) X(z) \quad (6)$$

$$Y(z) = H_1(z)W(z) = \left( \sum_{k=0}^M b_k z^{-k} \right) W(z) \quad (7)$$

$$y[n] = \sum_{k=1}^N a_k y[n-k] + \sum_{k=0}^M b_k x[n-k] \quad (8)$$



# Comparison

## Lecture 7

Recap

Representations


IIR

FIR

Lattice

Finite  
Numerical  
Precision



Coefficient Q

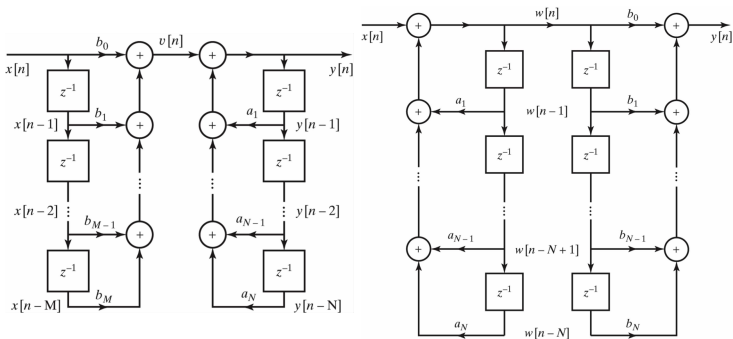

# Comparison (cont')
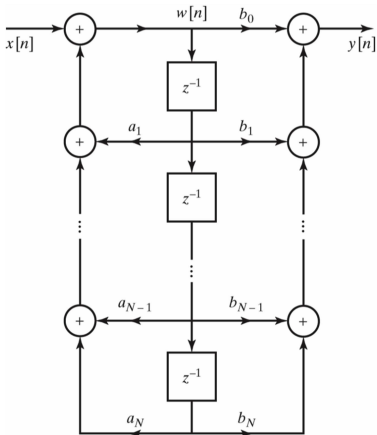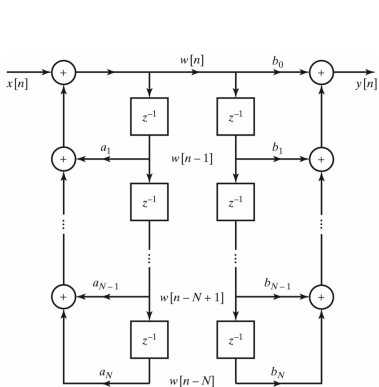
## Lecture 7

- Recap
- Representations
- IIR
- FIR
- Lattice
- Finite Numerical Precision
- Coefficient Q



# Comparison (cont')

## Lecture 7

Recap

Representations



IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

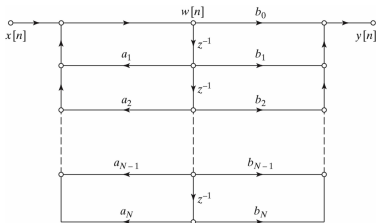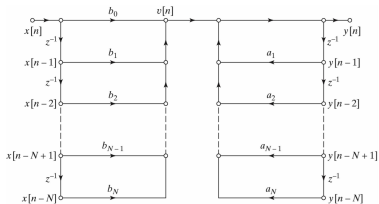

# Exercises

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

- Ex1:  $H(z) = \frac{1+2z^{-1}}{1-1.5z^{-1}+0.9z^{-2}}$
- Ex2:  $H(z) = \frac{1+2z^{-1}+z^{-2}}{1-0.75z^{-1}+0.125z^{-2}}$

# Solution

## Lecture 7

Recap

Representations


IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

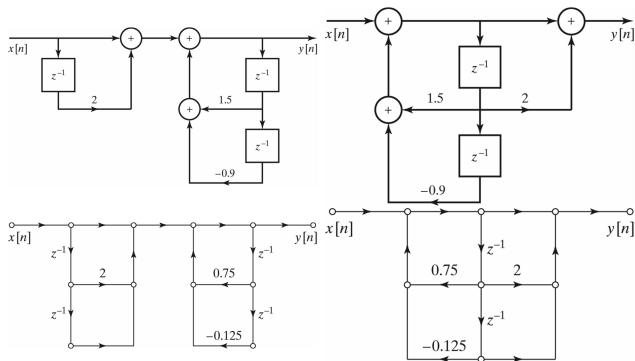

# Canonical vs. Noncanonical structures

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

- A digital filter structure is said to be *canonical* if the number of delays is equal to the order of the difference equation. Otherwise, it is a *noncanonical* structure. That is, minimum number of delays required is  $\max(N, M)$ .

# Transposed form

## Lecture 7

Recap

Representations

IIR



FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

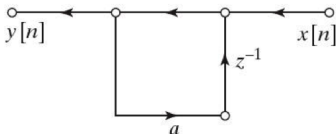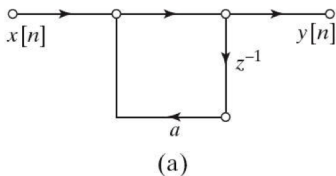- The transposition theorem: For single-input, single-output systems, the resulting flow graph has the same system function as the original graph if the input and output nodes are interchanged.
  - reverse direction of all branches
  - interchange input and output
- Implement zeros first, then poles as compared to the direct II form



# Example

## Lecture 7

Recap

Representations


IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

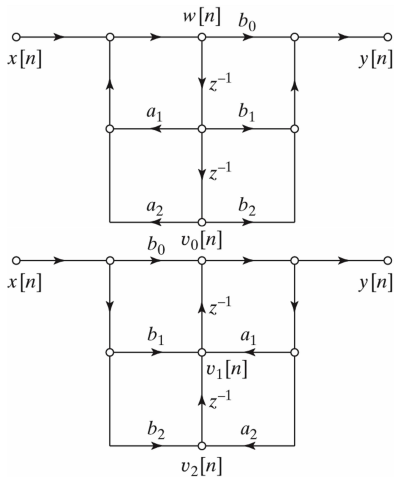



# Comparison - Direct form II vs. Transposed direct form II

## Lecture 7

Recap

Representations


IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

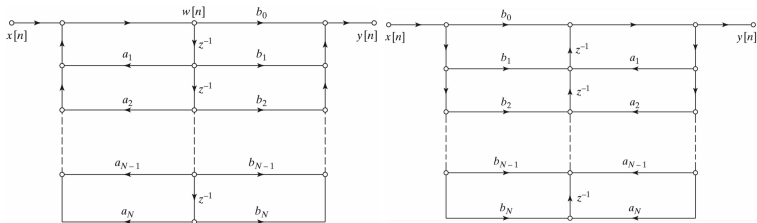

# Cascade form

## Lecture 7

Recap

Representations

IIR

FIR

Lattice


Finite  
Numerical  
Precision

Coefficient Q

$$H(z) = \frac{\sum_{k=0}^M b_k z^{-k}}{1 - \sum_{k=1}^N a_k z^{-k}}$$

$$H(z) = \prod_{k=1}^{N_s} \frac{b_{0k} + b_{1k}z^{-1} + b_{2k}z^{-2}}{1 - a_{1k}z^{-1} - a_{2k}z^{-2}}$$

$$N_s = \lfloor (N + 1)/2 \rfloor$$

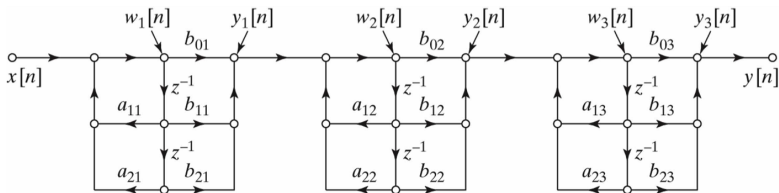

# Exercises

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision


Coefficient Q

$$\blacksquare \text{ Ex: } H(z) = \frac{1+2z^{-1}+z^{-2}}{1-0.75z^{-1}+0.125z^{-2}} = \frac{(1+z^{-1})(1+z^{-1})}{(1-0.5z^{-1})(1-0.25z^{-1})}$$


# Solution
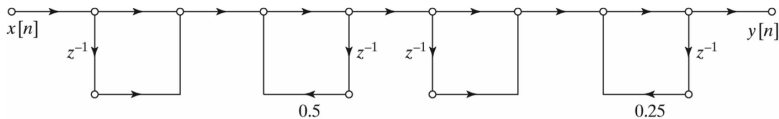
## Lecture 7

- Recap
- Representations
- IIR
- FIR
- Lattice
- Finite Numerical Precision
- Coefficient Q



(a)

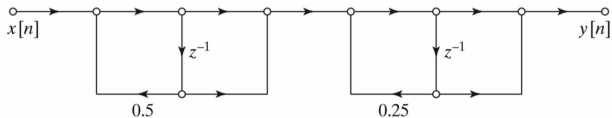

(b)

# Why cascading?

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

- Use of computation resource
  - Direct form II structure:  $2N + 1$  constant multipliers

$$H(z) = \frac{\sum_{k=0}^M b_k z^{-k}}{1 - \sum_{k=1}^N a_k z^{-k}}$$

- Cascade form structure:  $5N/2$  constant multipliers  
(assume  $M = N$  and  $N$  is even)

$$H(z) = \prod_{k=1}^{N_s} \frac{b_{0k} + b_{1k}z^{-1} + b_{2k}z^{-2}}{1 - a_{1k}z^{-1} - a_{2k}z^{-2}}$$

- Precision

# Parallel form

## Lecture 7

Recap

Representations


IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

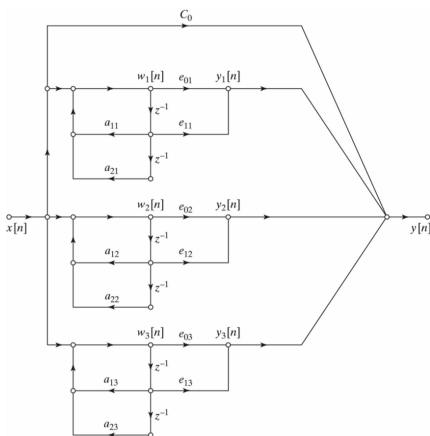

$$H(z) = \sum_{k=0}^{N_p} C_k z^{-k} + \sum_{k=1}^{N_s} \frac{e_{0k} + e_{1k} z^{-1}}{1 - a_{1k} z^{-1} - a_{2k} z^{-2}}$$

# Exercises

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

$$\blacksquare \text{ Ex: } H(z) = \frac{1+2z^{-1}+z^{-2}}{1-0.75z^{-1}+0.125z^{-2}} = 8 + \frac{-7+8z^{-1}}{1-0.75z^{-1}+0.125z^{-2}}$$

# Solution

## Lecture 7

Recap

Representations



IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

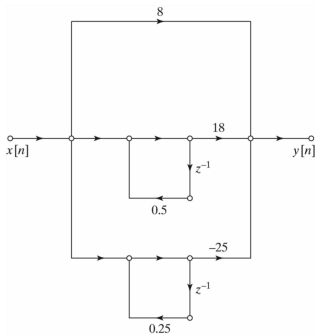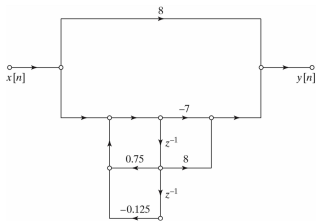





# Feedback in IIR systems
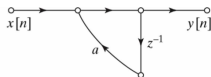
## Lecture 7

- Closed path: **necessary** to generate infinite long impulse responses (not sufficient)
- The computability of a flow graph is that all loops must contain at least one unit delay element



(a)

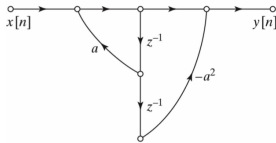


(b)



(c)

# FIR - Direct and transposed direct form

## Lecture 7

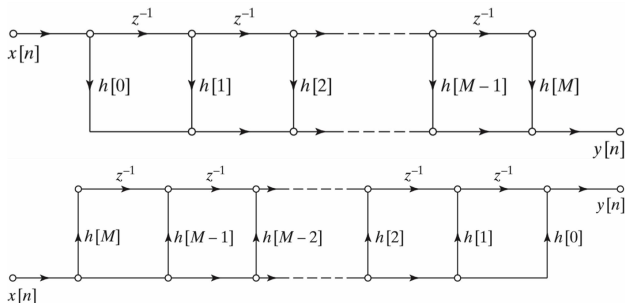

- tapped delay line structure (transversal filter structure)
- discrete convolution

$$y[n] = \sum_{k=0}^M h[k]x[n-k]$$

# Cascade form

## Lecture 7

Recap

Representations


IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

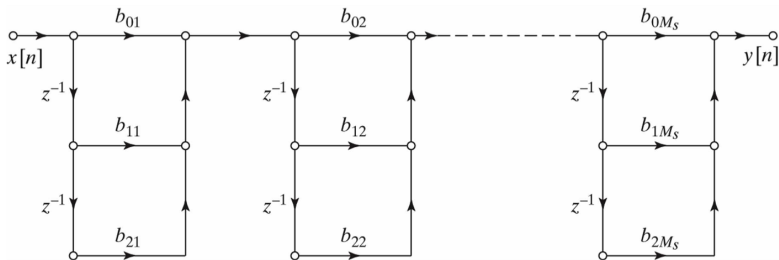

$$H(z) = \sum_{n=0}^M h[n]z^{-n} = \prod_{k=1}^{M_s} (b_{0k} + b_{1k}z^{-1} + b_{2k}z^{-2})$$

$$M_s = \lfloor (M + 1)/2 \rfloor$$

# Linear phase FIR systems

## Lecture 7

Recap

Representations

IIR


FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

$$h[M - n] = h[n], n = 0, 1, \dots, M$$

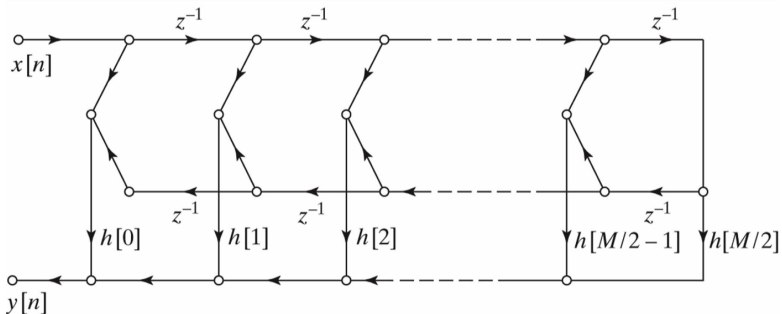


When  $M$  is even

# Linear phase FIR systems (cont')

## Lecture 7

- Recap
- Representations
- IIR
- FIR**
- Lattice
- Finite Numerical Precision
- Coefficient Q

$$h[M - n] = h[n], n = 0, 1, \dots, M$$

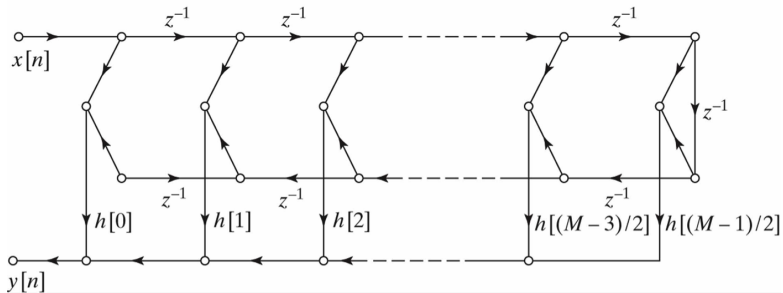

When  $M$  is odd

# Sources of errors

## Lecture 7

Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

$$y[n] = ay[n - 1] + x[n]$$

- Coefficient quantization problem:  $a \rightarrow \hat{a}$
- Input quantization error:  $x[n] \rightarrow \hat{x}[n] = x[n] + e[n]$
- Product quantization error:  
 $v[n] = ay[n - 1] \rightarrow \hat{v}[n] = v[n] + e_a[n]$
- Limit cycles: caused by the nonlinearity by the quantization of arithmetic operations. When the input is absent or constant input or sinusoidal input signals are present, the output is in the form of oscillation

# Quantization problem in Implementation

## Lecture 7

Recap

Representations




IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

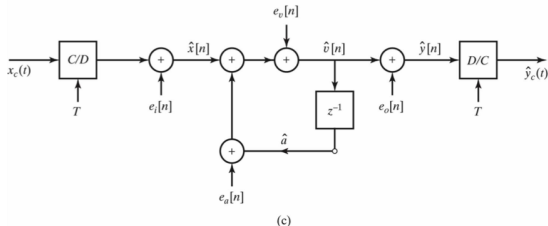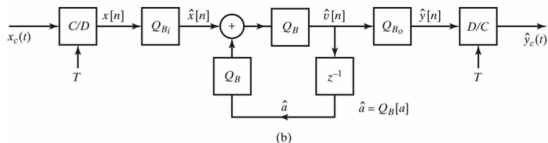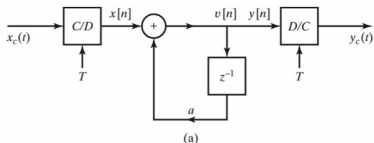

# Number representations

## Lecture 7

- The two's complement format

$$x = X_m(-b_0 + \sum_{i=1}^{\infty} b_i 2^{-i})$$

- $X_m$ : an arbitrary scale factor
- $b_0$ : the sign bit.  $0 \leq x \leq X_m$  if  $b_0 = 0$ ;  $-X_m \leq x < 0$  if  $b_0 = 1$

- Fix-point binary numbers

$$\hat{x} = Q_B[x] = X_m(-b_0 + \sum_{i=1}^B b_i 2^{-i}) = X_m \hat{x}_B$$

- Quantizing a number to  $B + 1$  bits. Quantization error:  
 $e = Q_b[x] - x$





# Quantization error
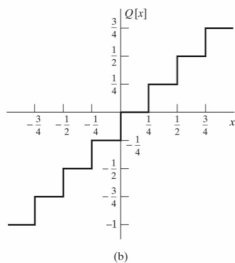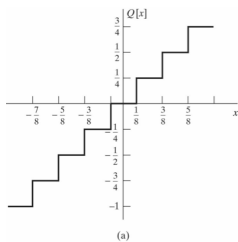
## Lecture 7

Recap  
Representations  
IIR  
FIR  
Lattice  
Finite  
Numerical  
Precision  
Coefficient Q

- Rounding:  $-\Delta/2 < e \leq \Delta/2$
- Truncating:  $-\Delta < e \leq 0$



# Quantization error (cont')

## Lecture 7

Recap

Representations


IIR

FIR

Lattice

Finite  
Numerical  
Precision


Coefficient Q

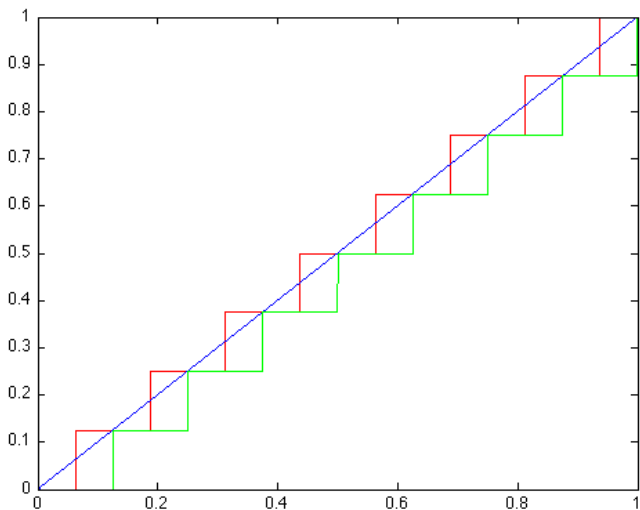


# Overflow
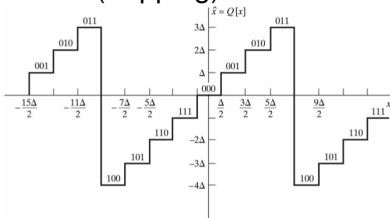
## Lecture 7

- When  $x > X_m$
- Saturation overflow (Clipping)



(a)

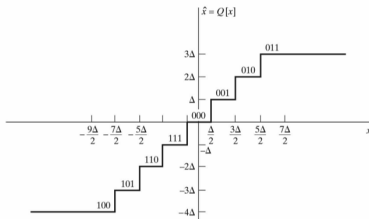



(b)

# Coefficient quantization - IIR
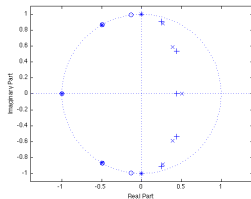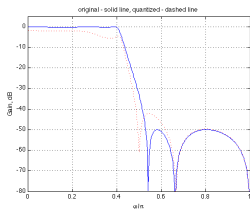
## Lecture 7

Recap  
Representations  
IIR  
FIR  
Lattice  
Finite  
Numerical  
Precision  
Coefficient Q


- Effect of coefficient quantization of an IIR digital filter implemented in direct form (5th-order IIR elliptic lowpass filter)



# Coefficient quantization - IIR (cont')
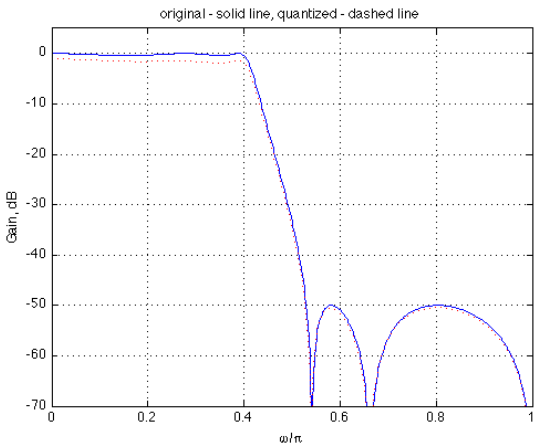
## Lecture 7

- Effect of coefficient quantization of an IIR digital filter implemented in cascade form (5th-order IIR elliptic lowpass filter)



Recap

Representations

IIR

FIR

Lattice


Finite  
Numerical  
Precision

Coefficient Q

# Coefficient quantization - FIR
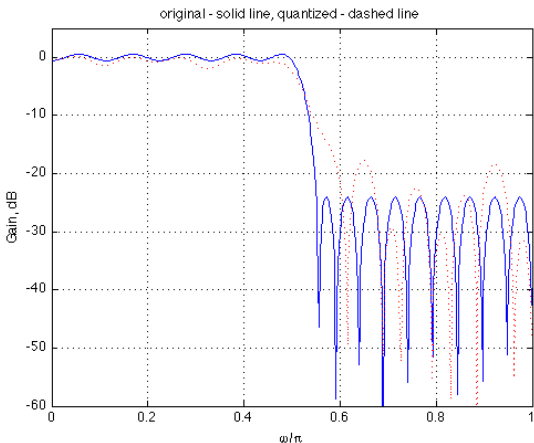
## Lecture 7

- Effect of coefficient quantization of an FIR digital filter implemented in direct form (39th-order FIR equiripple lowpass filter)



Recap

Representations

IIR

FIR

Lattice




Finite  
Numerical  
Precision

Coefficient Q

# Pole sensitivity of second-order structures (Product quantization)
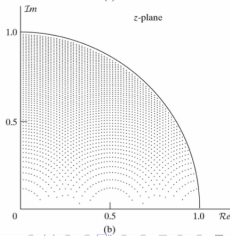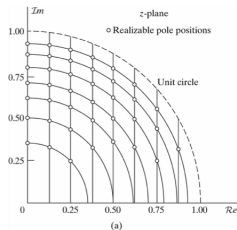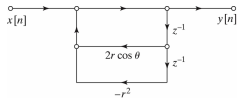
## Lecture 7

- The direct form structure exhibits high pole sensitivity with poles closer to the real axis and low pole sensitivity with poles closer to  $z = \pm j$



Recap

Representations

IIR

FIR

Lattice

Finite  
Numerical  
Precision

Coefficient Q

# Pole sensitivity of second-order structures (cont')

## Lecture 7

- The coupled form structure is more suitable for implementing any type of second-order transfer function.

